

UNIT-5

RECTIFIERS AND FILTERS


Rectifier:-

It is a device which can convert an ac input into (pulsating) dc output. The o/p will have always some ac components. filtering will be used to obtain a more accurate dc o/p.

Rectifier (or) large signal diodes have larger junction area $\Rightarrow G$ is high & power rating high


Half wave Rectifier:-

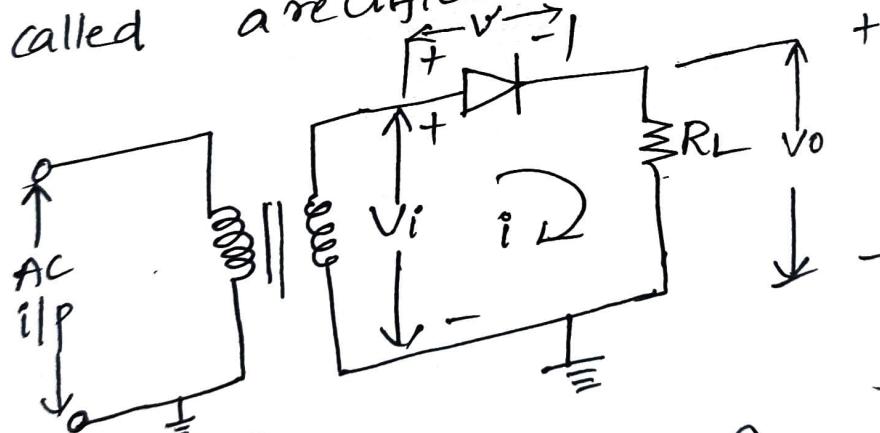Any electrical device which offers a low resistance to the current for one direction but a high resistance to I in opposite direction is called a rectifier.



$$V_i = V_m \sin \omega t$$

$$V_m \gg V_r$$

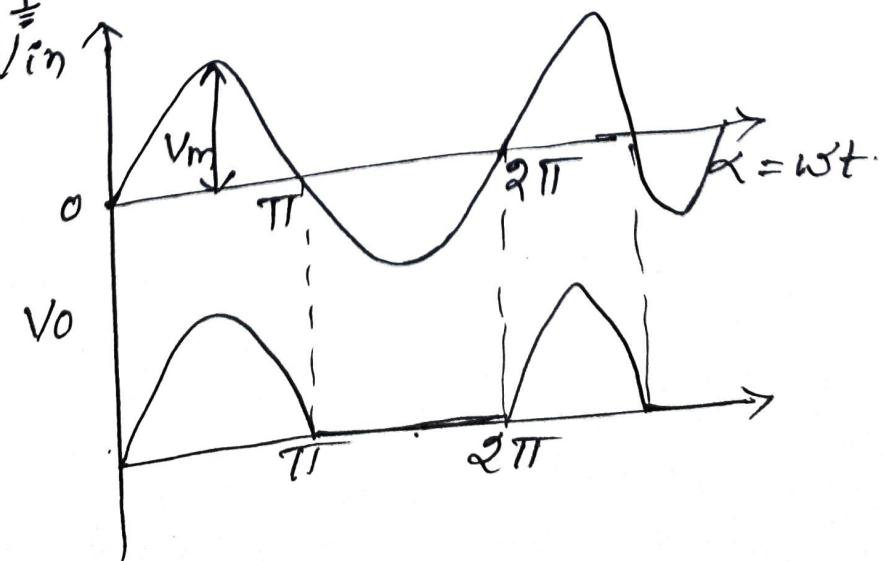


During +ve half cycle \rightarrow diode conducts (FB) (short cut)
 $V_i = V_r \rightarrow$ " RB (open) $\Rightarrow I_f = 0$


So a.c. will be connected to pulsating DC.



$0 \rightarrow T/2$:

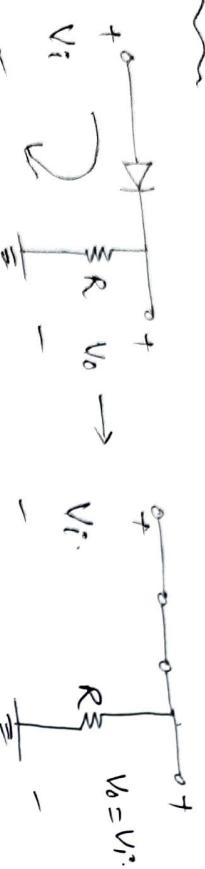

$T/2$ to T :

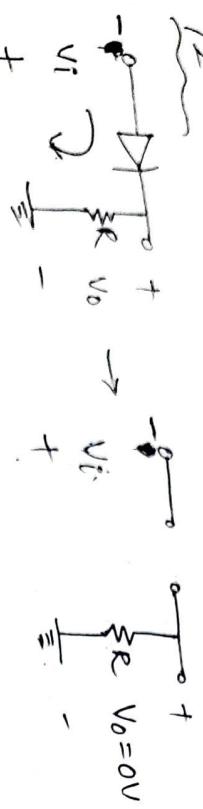

for V_{in} , $V_{dc} = 0 \Rightarrow$ avg. value = 0.
 for V_{in} , $V_{dc} = 0.318 V_m$ [half-wave (net +ve a.c. axis),
 the process of removing one half the AC signal to
 establish a dc level is called half wave rectification]

practical case: $V_i = V_r$
 $V_r = 0.7V$ $V_i = V_r$ $R \approx \frac{V_o}{I_f}$

V_o $V_m - V_r$

V_o $V_m - V_r$

The applied signal must now at least $0.7V$ positive for the diode to turn out. $V_i < 0.7V \rightarrow$ diode off $\Rightarrow V_o = 0V$


$V_i > 0.7V \Rightarrow V_o = V_i - V_r$

$V_{dc} \approx 0.318 (V_m - V_r)$

PTV (PRV)

Peak inverse voltage (or) peak reverse voltage. It decides the max. reverse vol. that can be applied to the diode so that it can't enter zener avalanche / breakdown region. It is generally peak of -ve half cycle.

PTV rating $\geq V_m$ | half wave (V_m)

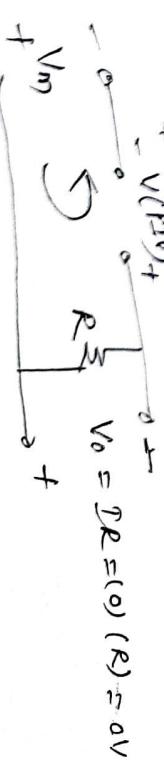

Ripple factor :-

A rectifier converts alternating current into unidirectional current but the dc still has periodically varying components & measure of fluctuating components is given by ripple factor η_1 ,

$$\eta_1 = \frac{\text{rms value of alternating components of a wave}}{\text{average value of wave}}$$

$$\eta_1 = \frac{\text{rms value of ac component}}{\text{dc value of component}}$$

$$\eta_1 = \frac{V_{\eta_1, \text{rms}}}{V_{\text{dc}}} = \frac{I_{\eta_1, \text{rms}}}{I_{\text{dc}}}$$

$$\text{where } V_{\eta_1, \text{rms}} = \sqrt{V_{\text{rms}}^2 - V_{\text{dc}}^2}$$
$$\eta_1 = \sqrt{\left(\frac{V_{\text{rms}}}{V_{\text{dc}}}\right)^2 - 1}$$

Now -

V_{av} (or) V_{dc} content of voltage across load

$$V_{\text{av}} = V_{\text{dc}} = \frac{1}{2\pi} \left[\int_0^\pi V_m \sin \omega t \, d(\omega t) + \int_0^\pi 0 \cdot d(\omega t) \right]$$

$$\Rightarrow V_{\text{dc}} = \frac{V_m}{2\pi} \left[-\cos \omega t \right]_0^\pi = \frac{V_m}{\pi}$$

$$\Rightarrow I_{\text{dc}} = \frac{V_{\text{dc}}}{R_L} = \frac{V_m}{\pi R_L} = \frac{I_m}{\pi}$$

If diode forward resistance (r_f) and secondary winding resistance (r_s) are considered

$$V_{\text{dc}} = \frac{V_m}{\pi} - I_{\text{dc}} (r_s + r_f)$$

$$I_{\text{dc}} = \frac{V_{\text{dc}}}{(r_s + r_f) + R_L} = \frac{V_m}{\pi(r_s + r_f + R_L)}$$

Now -

$$\begin{aligned} V_{\text{rms}} &= \sqrt{\frac{1}{2\pi} \int_0^\pi V_m^2 \sin^2 \omega t \, d(\omega t)} \\ &= V_m \sqrt{\frac{1}{2\pi} \int_0^\pi \left[\frac{1}{2} (1 - \cos 2\omega t) \right] d(\omega t)} \\ &= V_m \sqrt{\frac{1}{4\pi} \int_0^\pi (1 - \cos 2\omega t) d(\omega t)} \\ &= V_m \sqrt{\frac{1}{4\pi} [\pi]} = \frac{V_m}{2} \\ \eta_1 &= \sqrt{\left(\frac{V_m/2}{V_m/\pi}\right)^2 - 1} = \sqrt{\left(\frac{\pi}{2}\right)^2 - 1} = 1.21 \end{aligned}$$


Efficiency :-

$$\begin{aligned} \eta &= \frac{\text{dc o/p power}}{\text{ac i/p power}} = \frac{I_{\text{dc}}}{I_{\text{ac}}} = \frac{I_{\text{dc}}}{I_{\text{av}}} \\ &= \frac{(V_{\text{dc}})^2 / R_L}{(V_{\text{rms}})^2 / R_L} = \frac{\left(\frac{V_m}{\pi}\right)^2}{\left(\frac{V_m}{2}\right)^2} = 0.406 = 40.6\% \end{aligned}$$

max. efficiency of half wave rectifier = 40.6%

Transformer utilisation factor :- (TUF)

In the design of any power supply, the rating of transformer should be determined.

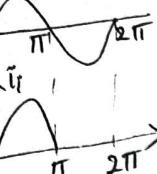Transformer secondary
V_s :

TUF = dc power delivered to the load
ac rating of the transformer

$$= \frac{P_{dc}}{P_{ac\text{ rated}}}$$

In half-wave rectifier, the rated voltage of the transformer secondary is $V_m/\sqrt{2}$ but actual rms current flowing through winding is only $\frac{I_m}{2}$ but not $I_m/\sqrt{2}$

$$\text{TUF} = \frac{\frac{I_m^2}{\pi^2} R_L}{\frac{V_m}{\sqrt{2}} \times \frac{I_m}{2}} = \frac{\left(\frac{V_m}{\pi}\right)^2 \frac{1}{R_L}}{\left(\frac{V_m}{\sqrt{2}}\right) \left(\frac{V_m}{2R_L}\right)} = \frac{2\sqrt{2}}{\pi^2} = 0.287$$


Form factor :-

$$\text{Form factor} = \frac{\text{gms value}}{\text{avg value}} = \frac{V_{rms}}{V_{dc}} = \frac{V_m/2}{V_m/\pi} = \frac{\pi}{2} = 1.57$$

Peak factor

$$\text{Peak factor} = \frac{\text{Peak value}}{\text{rms value}} = \frac{V_m}{V_m/2} = 2$$

Full wave rectifier :-

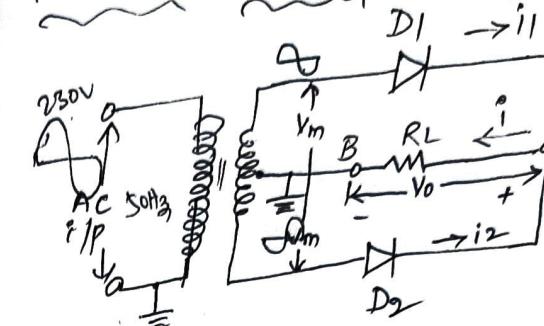

* Converts ac voltage into a pulsating dc voltage using both half cycles of applied ac voltage


* During +ve half, D1 is FB (Anode of D1 is +ve) and D2 is RB (Anode of D2 is -ve). hence D1 conducts and D2 doesn't conduct. The load current flows through D₁ and

Voltage drop occurs at R_L

* During -ve half, D1 → RB, D2 → FB. Voltage drop across R_L because of current through D₂.

Ripple factor :-
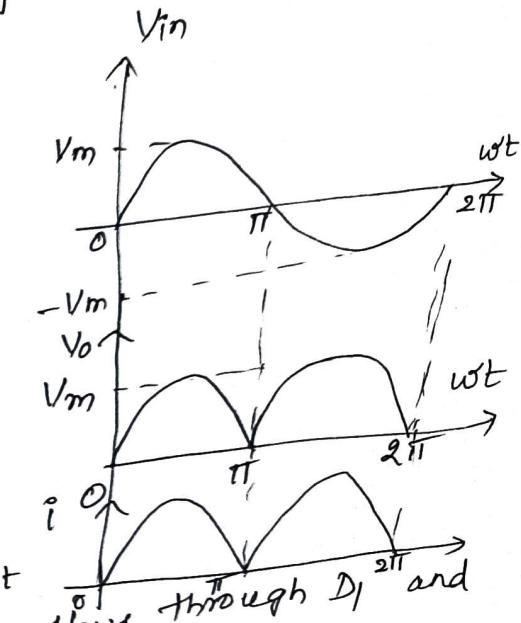
$$\eta_1 = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$



$$\text{i) } V_{dc} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{\pi} [-\cos \omega t]_0^{\pi} = \frac{2V_m}{\pi}$$

since avg. value of periodic fn is given by
 avg. value = $\frac{\text{area of one cycle of curve}}{\text{base}}$

$$I_{dc} = \frac{V_{dc}}{R_L} = \frac{2V_m}{\pi R_L} = \frac{2V_m}{\pi} \quad I_{rms} = \frac{V_m}{\sqrt{2}}$$

If diode resistance (r_f) and transformer secondary winding resistance (r_s) are included

$$V_{dc} = \frac{2V_m}{\pi} - I_{dc} (r_s + r_f)$$

$$I_{dc} = \frac{V_{dc}}{(r_s + r_f) + R_L} = \frac{2V_m}{\pi(r_s + r_f + R_L)}$$

Now

$$V_{rms} = \sqrt{\left[\frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right]} = \frac{V_m}{\sqrt{2}}$$

$$g_f = \sqrt{\left(\frac{V_m}{\sqrt{2}} \right)^2 - 1} = \sqrt{\frac{\pi^2}{8} - 1} = 0.482$$

TUF is separate for primary & secondary

$$\text{TUF} = \frac{(V_{dc})^2 / R_L}{V_{rms} \cdot I_{rms}} = \frac{\frac{4V_m^2}{\pi^2} \cdot \frac{1}{R_L}}{\frac{V_m}{\sqrt{2}} \cdot \frac{V_m}{\sqrt{2} R_L}} = \frac{8}{\pi^2} = 0.812$$

Primary is serving two HWR independently
 Primary TUF = 2×0.287
 $Avg = \frac{0.574 + 0.812}{2} = 0.693$

efficiency :-

$$\eta = \frac{dc \text{ o/p power}}{ac \text{ i/p power}} = \frac{P_{dc}}{P_{ac}}$$

$$= \frac{(V_{dc})^2 / R_L}{(V_{rms})^2 / R_L} = \frac{\left(\frac{2V_m}{\pi}\right)^2}{\left(\frac{V_m}{\sqrt{2}}\right)^2} = \frac{8}{\pi^2} = 81.2\%$$

$$TUF := 0.693$$

form factor :-

$$FF = \frac{V_m / \sqrt{2}}{2V_m / \pi} = \frac{\pi}{2\sqrt{2}} = 1.11$$

Peak factor :-

$$PF = \frac{\text{Peak Value of o/p voltage}}{\text{rms " " "}} = \frac{V_m}{V_m / \sqrt{2}} = \sqrt{2}$$

PIV = $2V_m$ because entire secondary voltage appears across the non-conducting diode while $D_1 \rightarrow$ conducting, apply KVL at outer loop, total $2V_m$ at transformer secondary drops at D_2 .

Regulation :-

Variation of dc o/p voltage as a fn of dc load current is called regulation

$$\% \text{ regulation} =$$

Half
 $V_{no load} = \frac{V_m}{\pi}$

$$V_{full load} = \frac{V_m}{\pi} - I_{dc} R_f$$

$$\% \text{ reg} = \frac{\frac{V_m}{\pi} - \left(\frac{V_m}{\pi} - I_{dc} R_f \right)}{\frac{V_m}{\pi}} \times 100.$$

$$\% \text{ reg.} = \frac{I_{dc} R_f}{R_L} \times 100.$$

$$\frac{V_{no load} - V_{full load}}{V_{full load}} \times 100\%$$

full
 $V_{no load} = \frac{2V_m}{\pi}$



$$V_{full load} = \frac{2V_m}{\pi} - I_{dc} R_f$$

$$\% \text{ reg} = \frac{\frac{2V_m}{\pi} - \left(\frac{2V_m}{\pi} - I_{dc} R_f \right)}{\frac{2V_m}{\pi}} \times 100.$$


$$\% \text{ reg.} = \frac{I_{dc} R_f}{R_L} \times 100$$

Bridge Rectifiers


CKT:

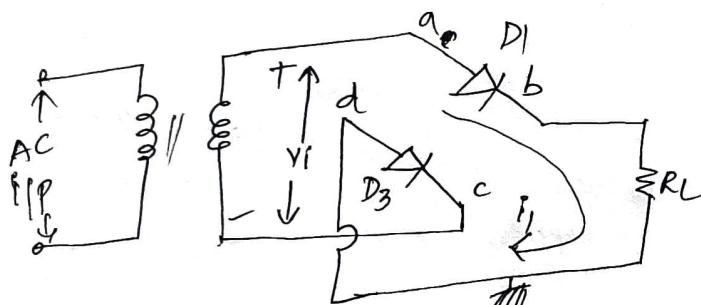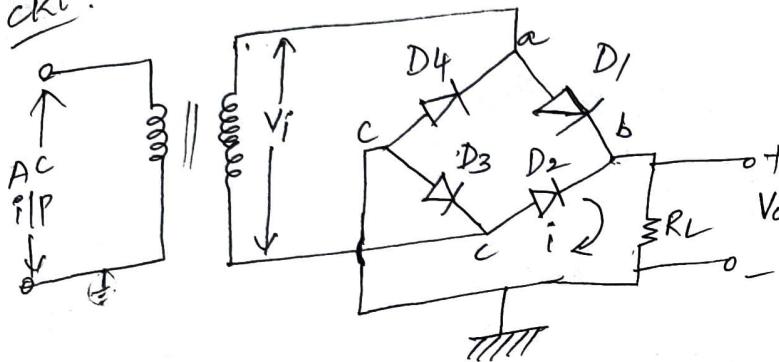

(b) ex. CKT for the half-cycle.

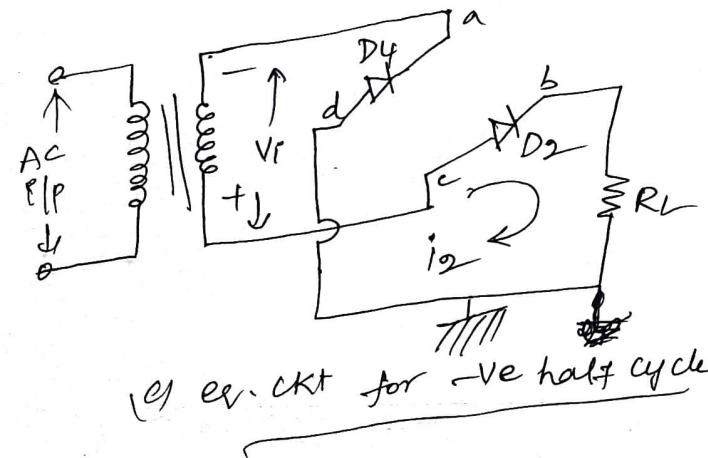

(c) ex. CKT for -ve half cycle

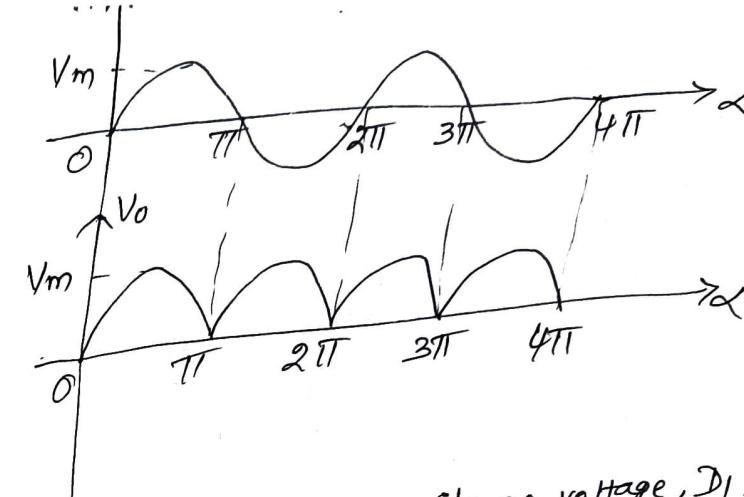

- * For +ve half-cycle of i/p ac voltage, $D_1, D_3 \rightarrow FB$
 $D_2, D_4 \rightarrow RB$
- * For -ve, $D_1, D_3 \rightarrow RB, D_2, D_4 \rightarrow FB$. hence current flows in same direction in both half cycles.
- * PIV = V_m since each diode has only transformer voltage across it on the inverse cycle.

Advantages:-

- ① PIV is less (Half of centre tapped)
- ② bulky center tapped transformer not required
- ③ TUF is high
- ④ No need to ground o/p

INDUCTOR FILTER


INDUCTOR FILTER

- * Fourier series representation of o/p wave in a halfwave rectifier contains "harmonics" (multiples of fundamental angular freq. ω i.e. $\omega, 2\omega, 3\omega, \dots$). These are undesirable. ' ω ' is eliminated in full wave o/p i.e. eliminated ~~at~~ first harmonic. So filtering the o/p of rectifying is advantageous in removing harmonics since full wave is more sinusoidal than half wave rectifier.

Inductor filter :-

- * Inductor opposes sudden change in "current". So any sudden changes that might occur in a.c.t without an inductor are smoothed out by the presence of it.

Half wave Rectification

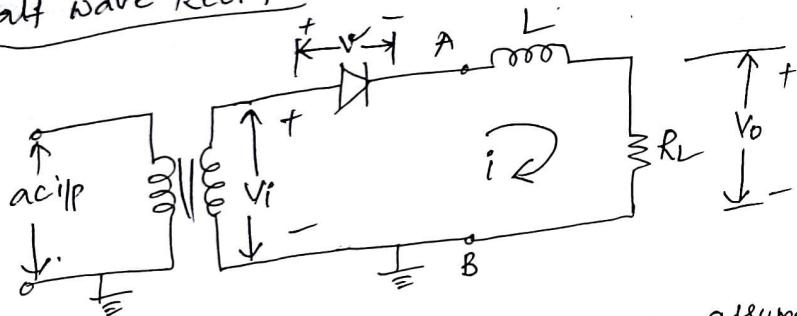

- * Inductor (or choke filter) is placed. Assume diode & choke resistances are negligible.



$$V_i = V_m \sin \omega t = L \frac{dI}{dt} + R_L I$$

The time at which I falls to zero is called cut-off point.

from graph :- at constant R_L .

$L \uparrow \rightarrow$ fluctuation \downarrow .
(\downarrow of a.c) more dc

Full Wave :-

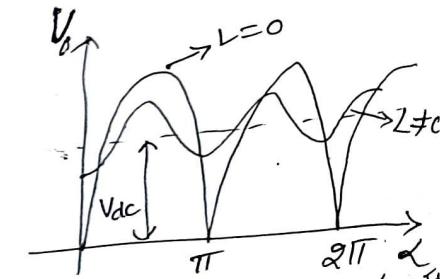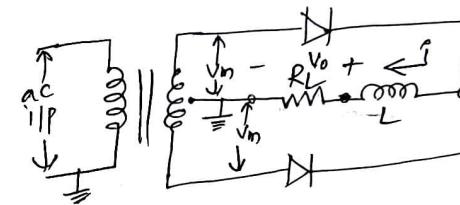

- * Because of 'L', a dc level is established. Since the impedance of 'L' ($X_L = \omega L$) \uparrow with \uparrow in freq., better filtering can be done for higher harmonics. o/p voltage also \downarrow since inductor has high ~~dc~~ resistance voltage drop -

$$V_o = \frac{2V_m}{\pi} - \frac{4V_m}{\pi} \left[\frac{1}{3} \cos 2\omega t + \frac{1}{15} \cos 4\omega t + \frac{1}{35} \cos 6\omega t + \dots \right]$$

dc

neglecting higher terms and third

$$V_o = \frac{2V_m}{\pi} - \frac{4V_m}{3\pi} \cos 2\omega t$$

a.c.

The total impedance is series of L and R_L at 2ω

$$Z = \sqrt{R_L^2 + (2\omega L)^2} = \sqrt{R_L^2 + \omega^2 L^2}$$

$$I_m = \frac{V_m}{R_L}$$

$$= \frac{V_m}{\sqrt{R_L^2 + 4\omega^2 L^2}}$$

The resulting current 'i'

$$i = \frac{2V_m}{\pi R_L} - \frac{4V_m}{3\pi} \frac{\cos(2wt - \phi)}{\sqrt{R_L^2 + 4\omega^2 L^2}}$$

$$\phi = \tan^{-1}\left(\frac{2\omega L}{R_L}\right)$$

(current lags voltage by inductor)

ripple factor :-

$$g_1 = \frac{\text{rms value of ac}}{\text{dc value}}$$

$$= \frac{4V_m}{\left(3\pi\sqrt{R_L^2 + 4\omega^2 L^2}\right)\sqrt{2}} \left(\frac{2V_m}{\pi R_L}\right)$$

$$= \frac{2}{3\sqrt{2}} \times \frac{1}{\sqrt{1 + \frac{4\omega^2 L^2}{R_L^2}}}$$

$$\text{if } \frac{4\omega^2 L^2}{R_L^2} \gg 1, \quad g_1 = \frac{R_L}{3\sqrt{2} \omega L} \quad \text{--- (1)}$$

* if $R = \infty$ (no load) (or open circuit)


$$g_1 = \frac{2}{3\sqrt{2}} = 0.471 \quad (< 0.482 \text{ nominal full wave})$$

From (1) $\rightarrow g_1 \downarrow$ when $L \uparrow$ and R_L should be small and constant to use inductor filter. The \downarrow in 'g1' is because of elimination of higher harmonics.

$$i = \frac{V_m}{\sqrt{R_L^2 + \omega^2 L^2}} \left[\sin(\omega t - \phi) + e^{-R_L t / L} \sin \phi \right]$$

where $\tan \phi = \frac{\omega L}{R_L}$

Capacitor filter:-

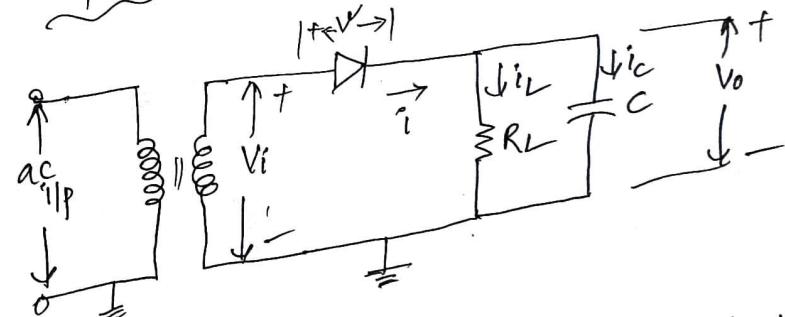

* Capacitor stores energy during the conduction period and delivers this energy to the load during non-conducting period. In this way, the time during which the current passes through load is prolonged, and the ripple is considerably decreased.


* If $R_L = \infty$, capacitor will charge to the potential V_m the transformer max. value. The capacitor will maintain this potential for no path exists by which this charge is permitted to leak off, since diode ~~will not~~ ~~not~~ pass -ve current. hence filtering is perfect, the capacitor voltage V_o remains constant at its peak value $= V_m$.

$$\text{Diode voltage, } V = V_i - V_o.$$

From above, V is always -ve and $\text{PIV} = 2V_m$. hence ($V = V_m - V_m = -2V_m$)

the presence of capacitor causes PIV ~~to increase~~ to increase from V_m to $2V_m$.

* R_L = finite. without 'C', the load I and V during the conduction period are sinusoidal. when 'C' is present, capacitor charges in step with the applied voltage. Also it must discharge through R_L only since diode doesn't allow. The diode acts as a switch which permits charge to flow into the capacitor when transformer voltage exceeds the capacitor vol. and then off when the transformer vol. falls below that of capacitor (disconnects)

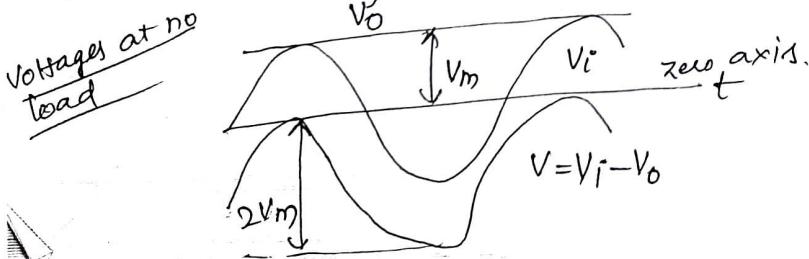

(a) Diode conducting:

Consider diode drop is negligible. V_i directly applies across R_L . The point at which diode starts to conduct is called the cut-in point and that at which it stops conducting is called cut-out point.

since V_i is sine and is impressed across \parallel R_L and C' , the diode current (an phasor current)

$$I = \left(\frac{1}{R_L} + j\omega C \right) V$$

admittance

$$= \left[\left(\frac{1}{R_L} \right)^2 + \omega^2 C^2 \tan^{-1} \omega C R_L \right] V.$$

since 'V' has a peak value V_m , then instantaneous current

$$I = V_m \sqrt{\omega^2 C^2 + \frac{1}{R_L^2}} \sin(\omega t + \phi)$$

when $C \uparrow$, peak diode $I \uparrow$. The conduction period will \downarrow as the capacitance is made larger. The cut out time t_1 is found by equating diode current to zero

$$\sin(\omega t_1 + \phi) = 0.$$

$$\omega t_1 + \phi = n\pi$$

$$n=1 \quad \omega t_1 = \pi - \tan^{-1}(\omega C R_L)$$

$$\phi = \tan^{-1}(\omega C R_L)$$

~~(I leads V in 'C')~~

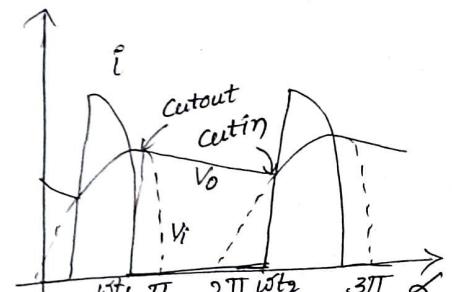


fig: diode current i and o/p voltage V_o in a half wave capacitor filtered rectifier

Diode Non-conducting

B/w cutout time t_1 and cutin time t_2 , the diode is effectively out of the ckt and 'C' discharges through the load R_L with time const = $R_L C$

Capacitor Voltage :-

$$V_o = A \exp(-t/R_L C)$$

at $t=t_1$, the cutout time from fig :-

$$V_o = V_i = V_m \sin \omega t$$

when $A = (V_m \sin \omega t_1) \exp(t_1/R_L C)$

$$\Rightarrow V_o = (V_m \sin \omega t_1) \exp(-(t-t_1)/R_L C)$$

The exponential curve in the graph intersects line $V_o = V_m \sin \omega t$ at the cutin point t_2 . When time $>t_2$, the transformer vol. $V_i >$ cap. vol. V_o . Since the diode Vol. is $V = V_i = V_o$, then 'V' will be +ve beyond t_2 and diode will be conducting. Thus t_2 is cutin point.


* For full wave cut-in point lies b/w π and 2π . where exponential curve of V_o intersects this line. The cutout point is same as like half wave

Approximate Analysis:-

* V_o of full wave is indicated in graph of capacitor discharge

Vol. is V_R
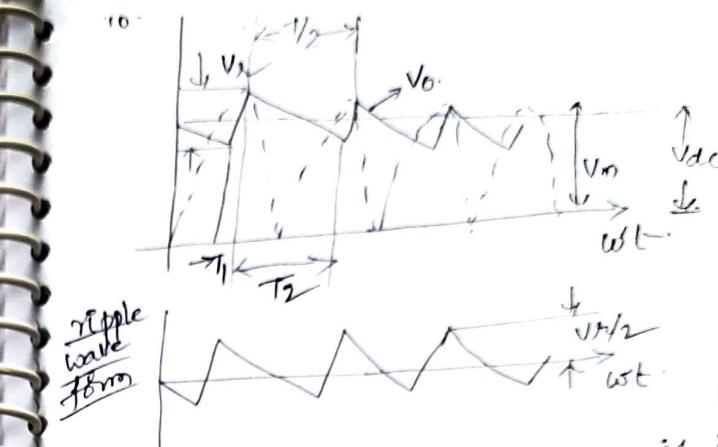
$$V_{dc} = V_m - \frac{V_R}{2} \quad (\text{from diag.})$$



V_{rms} value of triangular wave is independent of slope fm lengths of st. lines and depends on only peak value.

$$V_{rms}^1 = \frac{V_m}{2\sqrt{3}}$$

* If T_2 is non-conducting time, the capacitor, when discharging at const. rate I_{dc} , will lose charge = $I_{dc} T_2$ hence Capacitor vol.

$$V_R = \frac{I_{dc} T_2}{C}$$

for better filtering :-

$$T_2 = \frac{T}{2} = \frac{1}{2f}$$

$$V_R = \frac{I_{dc}}{2f C}$$

$$\eta_1 \equiv \frac{V_{rms}}{V_{dc}} = \frac{I_{dc}}{4\sqrt{3} f C V_{dc}} = \frac{1}{4\sqrt{3} f C R_L}$$

$$V_{dc} = V_m - \frac{I_{dc}}{4f C}$$

↳ fundamental power line free.


$$g_1 \propto \frac{1}{\sqrt{C}}$$

'g' for half wave approx. double of full wave. we need high

'C' for better regulation. it has disadvantages of poor regulation and high ripple at large loads. (it means drawing large currents - value of R_L is small)

L-Section filter:-

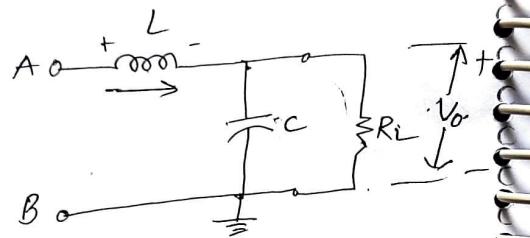* this filter combines the ripple with ↑ load of series inductor with the ↑ ripple with ↑ load of shunt capacitor.



* The inductor offers a high series impedance to the harmonic terms, and the capacitor offers a low shunt impedance to them. The resulting current through R_L is smoothed out much more effectively than single 'L' or 'C' ckt.

Regulation:-

Fourier series representation of o/p of Voltage of the rectifier

$$V = \frac{2V_m}{\pi} - \frac{4V_m}{3\pi} \cos 2\omega t \quad \text{--- (1)}$$

If the sum of the diode, transformer and choke resistances is 'R', then

too diodes replaced by battery in series with ac source having twice

$$V_{dc} = \frac{2V_m}{\pi} - I_{dc} R. \quad \text{--- (2)}$$

Ripple factor:-

* filter is to suppress harmonics. so the reactance of choke must be large compared to net impedance of capacitor & resistor. The latter combination is made small by making the reactance of 'C' small when compared to R_L .

* Assume entire ac (alternating current) passes through 'C' and none through R_L under these conditions, the net impedance across AB is approx.

$$\Rightarrow X_L = 2\omega L, \quad (\text{reactance of } L \text{ at second harmonic free.})$$

The alternating I through ckt -

$$I_{rms} = \frac{4V_m}{3\sqrt{2}\pi} \cdot \frac{1}{X_L}$$

$$= \frac{\sqrt{2}}{3} V_{dc} \cdot \frac{1}{X_L}$$

when 'R' is neglected in eqn (2). The ac voltage across the load is the voltage across capacitor.

$$V'_{rms} = I_{rms} X_C = \frac{\sqrt{2}}{3} V_{dc} \frac{X_C}{X_L}$$

Ripple factor

$$\alpha = \frac{V'_{rms}}{V_{dc}} = \frac{\sqrt{2}}{3} \frac{X_C}{X_L}$$

$$\alpha = \frac{\sqrt{2}}{3} \cdot \frac{1}{2\omega C} \cdot \frac{1}{2\omega L}$$

$$\text{where } X_C = \frac{1}{2\omega C}$$

(reactance of capacitor at second harmonic)

~~there~~ the effect of combining the \downarrow ripple because of

simple L-filter and the \uparrow ripple because of simple C-filter for \uparrow loads is a constant ripple independent of load

Critical Inductance:

- * Assume current flows through ckt at all times.
- * If cutout point exist this analysis is invalid.
- * When L is not present, capacitor charges to V_m in each cycle. Now 'L' is made to prevent in ckt. Although the time over which the diode I will exist is more what lengthened, cut-out may still occur. As 'L' it's value of 'I' the diode continuously supplies to R_L and no cutout occurs. This value is called

Critical Inductance L_c

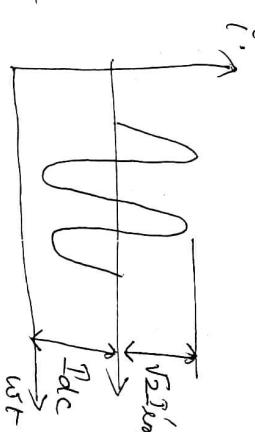



Fig: Diode current in a full wave ckt with L-section

$$\frac{V_{dc}}{R_L} \geq \sqrt{2} I_{lens} = \frac{2V_{dc}}{3} \cdot \frac{1}{X_L}$$

$$X_L \geq \frac{2R_L}{3}$$

From graph of regulation for constant 'L' and a varying load I . When $I=0$ ($R_L=\infty$), the filter is of capacitor type and off vol. V_m . with \uparrow load I the voltage falls, until at $I=I_c$ (current at $L=L_c$) the off potential is that corresponding to simple L-filter with no cutout $I \rightarrow I_c$, the change in potential result from effect of resistance of elements in ckt.

multiple L-section:

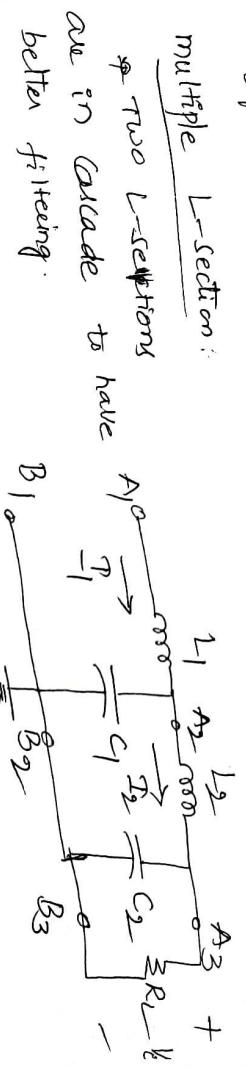

* Assume that reactances of all chokes \rightarrow reactances of the capacitors and reactance of last capacitor is small compared with the resistance of load.

* To have current through entire cycle, peak $\sqrt{2} I_{lens}$ of ac of current must not exceed direct current

$$\frac{V_{dc}}{R_L} \geq \sqrt{2} I_{lens} = \frac{2V_{dc}}{3} \cdot \frac{1}{X_L}$$

$$\frac{V_{dc}}{R_L} \geq \frac{\sqrt{2} I_{lens}}{3} \cdot \frac{1}{X_L}$$

* The ac current $I_1 \approx \frac{\sqrt{2} V_{dc}}{3} \cdot \frac{1}{X_L}$

$$A_2 \text{ and } B_2 \text{ in } X_C 1$$

$$A_1 \text{ and } B_1 \text{ in } X_L$$

ac voltage across C_1

$$\left. \begin{aligned} V_{A2B2} &= I_1 X_{C1} \\ I_{2m}' &= \frac{\sqrt{2} V_{dc}}{3} \frac{X_{C1}}{X_L} \end{aligned} \right\} \text{from L-section}$$

for I_1 in
previous page

$$(ii) \quad T_2 = \frac{V_{A2B2}}{X_{L2}}$$

ac voltage across C_2 and hence across R_L is approx

$$I_2 X_{C2} = I_1 \frac{X_{C2} X_{C1}}{X_{L2}} = \frac{\sqrt{2} V_{dc}}{3} \frac{X_{C2}}{X_{L2}} \frac{X_{C1}}{X_{L1}}$$

ripple factor

$$\eta = \frac{\sqrt{2}}{3} \frac{X_{C1}}{X_{L1}} \cdot \frac{X_{C2}}{X_{L2}} \quad \left(\text{- divide above with } V_{dc} \right)$$

for 'n' similar section of multiple 'L' filter

$$\eta = \frac{\sqrt{2}}{3} \left(\frac{X_C}{X_L} \right)^n = \frac{\sqrt{2}}{3} \cdot \frac{1}{(16\pi^2 f^2 n C)^n}$$

At 60 Hz \rightarrow from above \rightarrow

$$LC = 1.76 \left(\frac{0.471}{n} \right)^{1/n}$$

\therefore Assume imp. b/w A_1 and B_1 is X_{L1} , L_C is same for single section and first inductor of multiple L-section