


For the circuit shown in figure, calculate reactance of capacitor x_c when the circuit is in resonance &

A

$$R = 50\Omega$$

$$x_L = 25\Omega$$

$$x_C = \text{unknown}$$

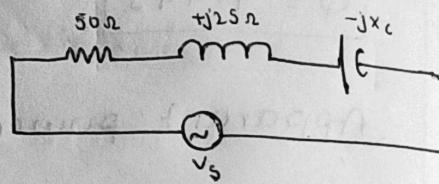


Impedance at Resonance is

$$Z = R = 50\Omega$$

$$\text{At resonance } x_L = x_C = 25\Omega$$

Q Determine resonant frequency of circuit shown in figure

A

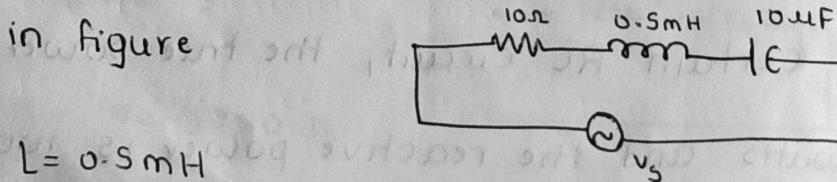

$$C = 10\mu F$$


$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.5 \times 10^{-3} \times 10 \times 10^{-6}}} \text{ Hz}$$

$$f_r = 2.250 \text{ kHz}$$

Q

From the circuit shown in figure, determine the impedance & resonant frequency, resonant frequency above 10Hz and below 10Hz, when the circuit is in

Resonance.

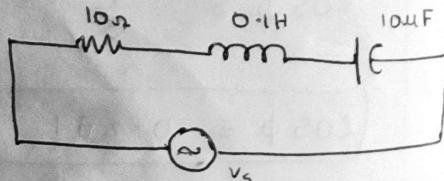

A) At resonance frequency, $Z = R = 10 \Omega$

$$2) f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 10 \times 10^{-6}}} \text{ Hz}$$

$$f_r = 159.15 \text{ Hz}$$

3) 10 Hz above resonant frequency = 169.15 Hz

4) 10 Hz below resonant frequency = 149.15 Hz

Q Determine the quality factor of a coil for a series circuit, consisting of $R = 10 \Omega$,

$$L = 0.1 \text{ H}, C = 10 \mu\text{F}$$

A) $R = 10 \Omega$

$$L = 0.1 \text{ H}$$

$$C = 10 \mu\text{F}$$

Quality factor = $\frac{f_r}{B.W} = \frac{\text{Resonant frequency}}{\text{Band width}}$

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 10 \times 10^{-6}}} = 159.15 \text{ Hz}$$

$$B.W = \frac{R}{2\pi L} = \frac{10}{2\pi(0.1)} = 15.9 \text{ Hz}$$

$$\text{Quality factor} = \frac{159.15 \text{ Hz}}{15.9 \text{ Hz}} = \boxed{10}$$

Q For the circuit, shown in figure, Determine

Q at resonance and determine Band width


of the circuit. { Q is quality factor }

$$Q = \frac{f_r}{Bw}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{5 \times (100 \times 10^{-6})}}$$

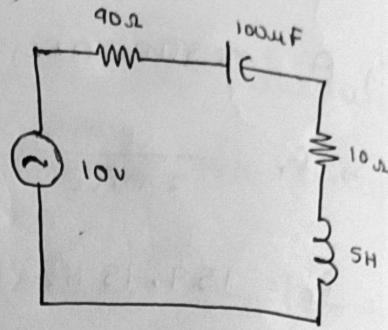
$$= 318.3 \text{ Hz} \quad \{ f_r = 7.117 \text{ Hz} \}$$



$$Q = \frac{x_L}{R} = \frac{2\pi f L}{R} = \frac{2\pi (7.117)(5)}{100}$$

$$Q = 2.23 \rightarrow B.W = \frac{f_r}{Q} = \frac{7.117}{2.23} = 3.18 \text{ Hz}$$

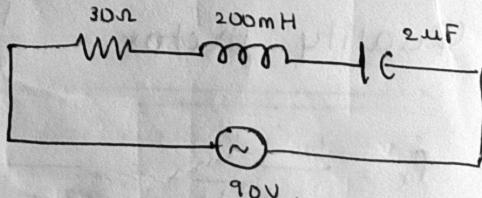Q) For the 's' circuit shown in figure, determine resonant frequency, Band width, quality factor, impedance at resonance, maximum current in the circuit



A) 1) Resonant frequency

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{20 \times 10^{-3} \times 2 \times 10^{-6}}} = 796.17 \text{ Hz}$$

2) Band width

$$\text{Band width} = \frac{R}{2\pi L} = \frac{30}{2\pi(20 \times 10^{-3})} = 238.85$$

3) Quality.


$$Q = \frac{f_r}{B.W} = \frac{796.17}{238.85} = 3.33$$

4) Impedance at resonance

$$z = 30\Omega$$

s) Current in the circuit $I = 90 / 30 = 3A$

Three phase circuits

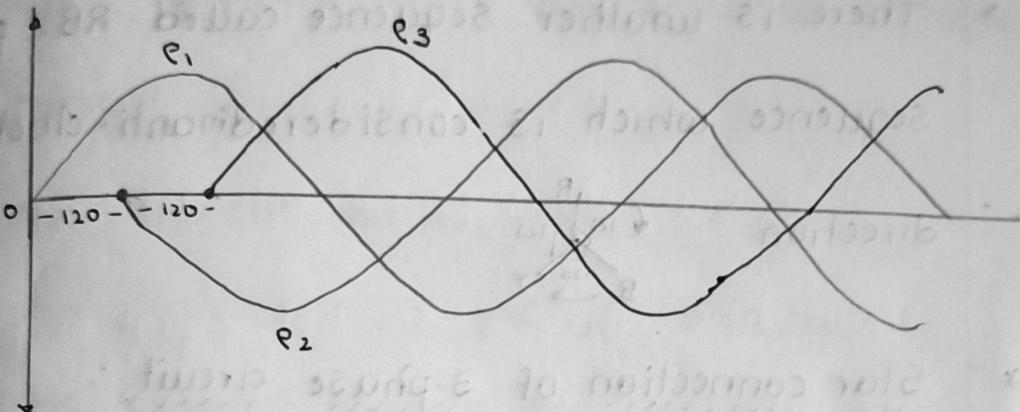

$$\text{we have } e_1 = e_m \sin \omega t$$

$$e_2 = e_m \sin(\omega t - 120)$$

$$e_3 = e_m \sin(\omega t - 240)$$

The difference (ϕ difference) between each wave (here) is 120 "electrical degrees".

{These waves can be currents wave}


$$\text{i.e. } i_1 = i_m \sin \omega t$$

$$i_2 = i_m \sin(\omega t - 120)$$


$$i_3 = i_m \sin(\omega t - 240)$$

* Generally in three phase circuits, we use a sequence called RYB phase sequence which is used to calculate the different parameters of

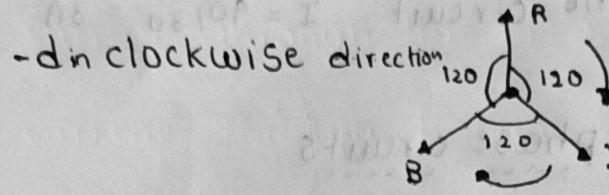
Three phase circuits. RYB sequence is considered



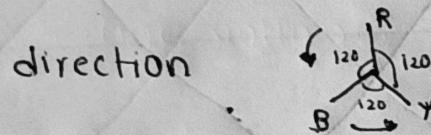- * There is another sequence called RBY phase sequence which is considered in anti-clockwise direction.



- * Star connection of 3-phase circuit.

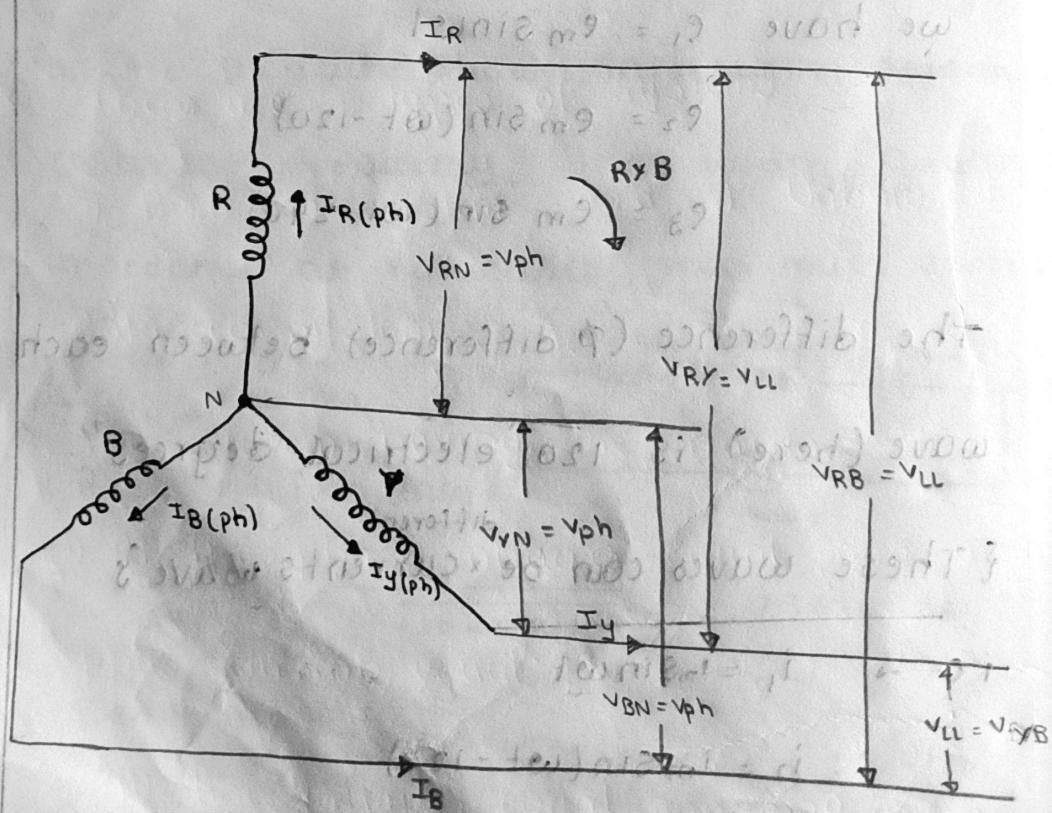


Neutral point (N): A point is said to be neutral when its electrical potential is zero. and also

it is a point which joins all 3 conductors in a star.

Line voltage (V_{LL}): The voltage between two conductors is known as line current (I_{LL})

Phase voltage (V_{ph}): The voltage between the main conductor and neutral is called phase current (V_{ph}).

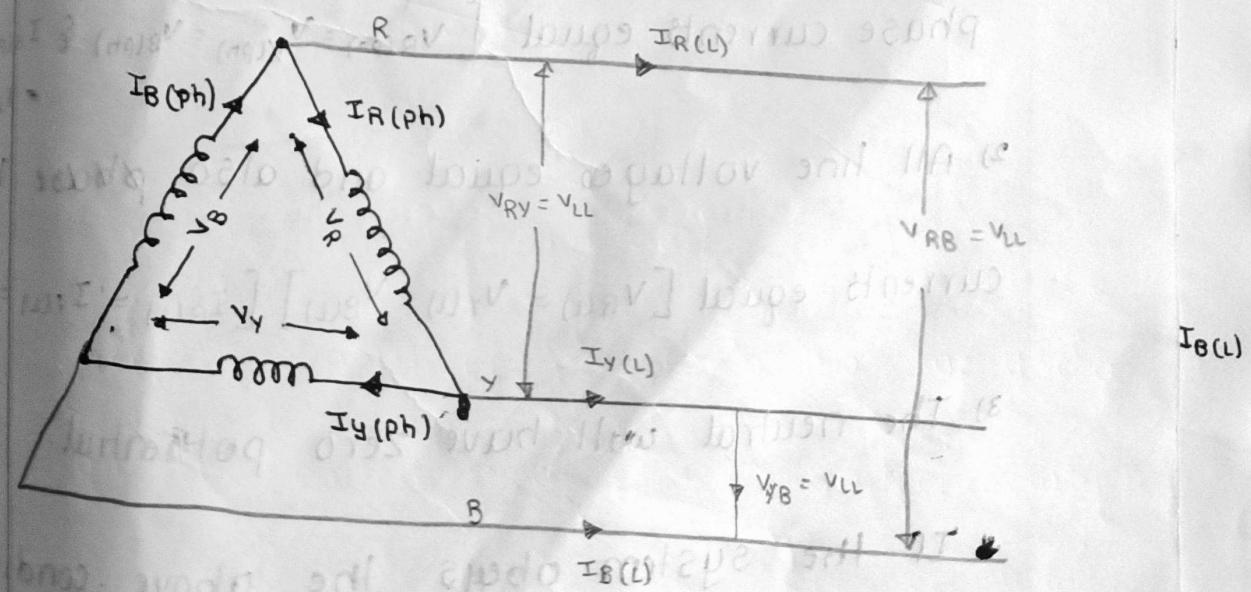- * The current in R-phase is $I_R(ph)$
- * The current in Y-phase is $I_Y(ph)$
- * The current in B-phase is $I_B(ph)$
- * In star connection of 3-phase circuit, we have
 - Line currents = phase currents {only for balanced systems}
 - i.e. $I_L = I_{ph}$
 - But phase voltages are not equal to line voltages.
- * Delta connection of 3-phase circuit:



- * Current through line of R phase is $I_{R(L)}$
- * Current through line of Y phase is $I_{Y(L)}$
- * Current through line of B phase is $I_{B(L)}$
- * In delta connection of 3-phase connection is,
we have {only for balanced system}

→ Line voltages = phase voltages $\{V_L = V_{ph}\}$
 → But line currents are not equal to phase currents.

- * There are 2 types of systems
 - Balanced system and 2) Unbalanced system.

→ Balanced system:

The system having the conditions.

1) All the phase voltages equal and also

phase currents equal $[V_{R(ph)} = V_{Y(ph)} = V_{B(ph)} \text{ & } I_{R(ph)} = I_{Y(ph)} = I_{B(ph)}]$

2) All line voltages equal and also phase line

currents equal $[V_{R(L)} = V_{Y(L)} = V_{B(L)}] [I_{R(L)} = I_{Y(L)} = I_{B(L)}]$


3) The neutral will have zero potential.

• If the system obeys the above conditions

then the system is known as Balanced system.

- * Note: The balanced system should also have equal amount of loads on each phase.

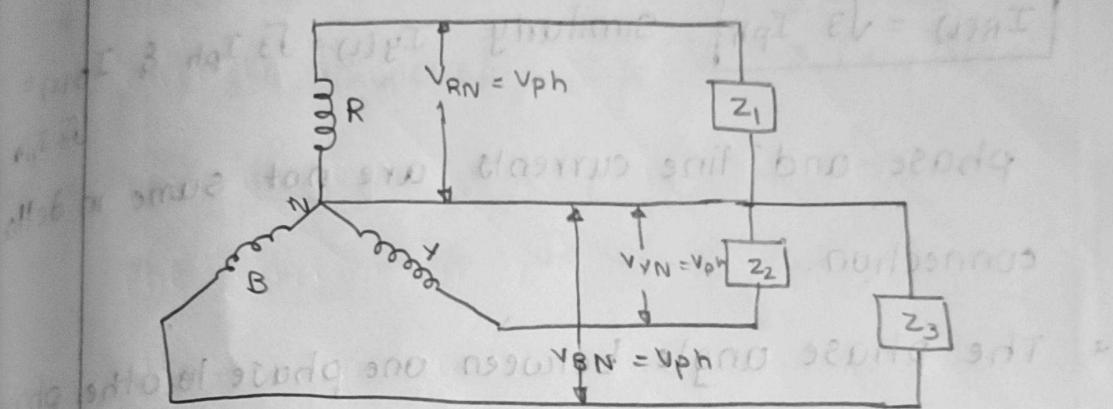i.e. $z_1 = z_2 = z_3$ otherwise it is unbalanced



Each phase gives same magnitude of voltage

Unbalanced System:

The loads of each phase are not equal

$z_1 \neq z_2 \neq z_3$, then it is unbalanced.

→ In delta connection, line voltages are equal


to individual phase voltages { $V_L = V_{ph}$ }

* In delta connection.

$$I_{R(L)} = I_{B(ph)} - I_{R(ph)}$$

$$I_{Y(L)} = I_{R(ph)} - I_{Y(ph)}$$

$$I_{B(L)} = I_{Y(ph)} - I_{B(ph)}$$

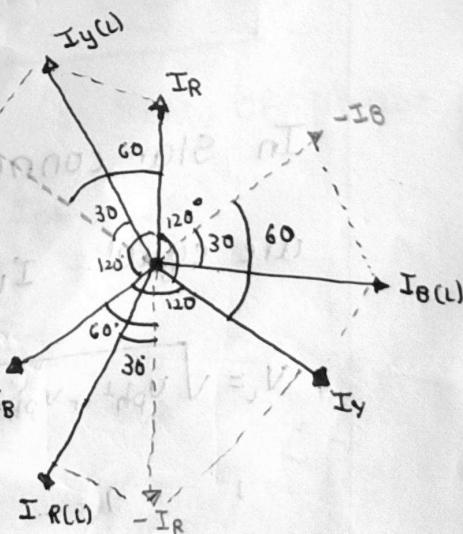

$$I_{R(L)} = \sqrt{I_{R(ph)}^2 + I_{B(ph)}^2 + 2I_{R(ph)}I_{B(ph)} \cos 60^\circ}$$

For a balanced supply $I_{R(ph)} = I_y(ph) = I_B(ph) = I_{ph}$


$$I_{R(L)} = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph}^2 \cos 60^\circ}$$

$$I_{R(L)} = \sqrt{3} I_{ph}$$

Similarly $I_y(L) = \sqrt{3} I_{ph}$ & $I_{B(L)} = \sqrt{3} I_{ph}$

phase and line currents are not same in delta connection.

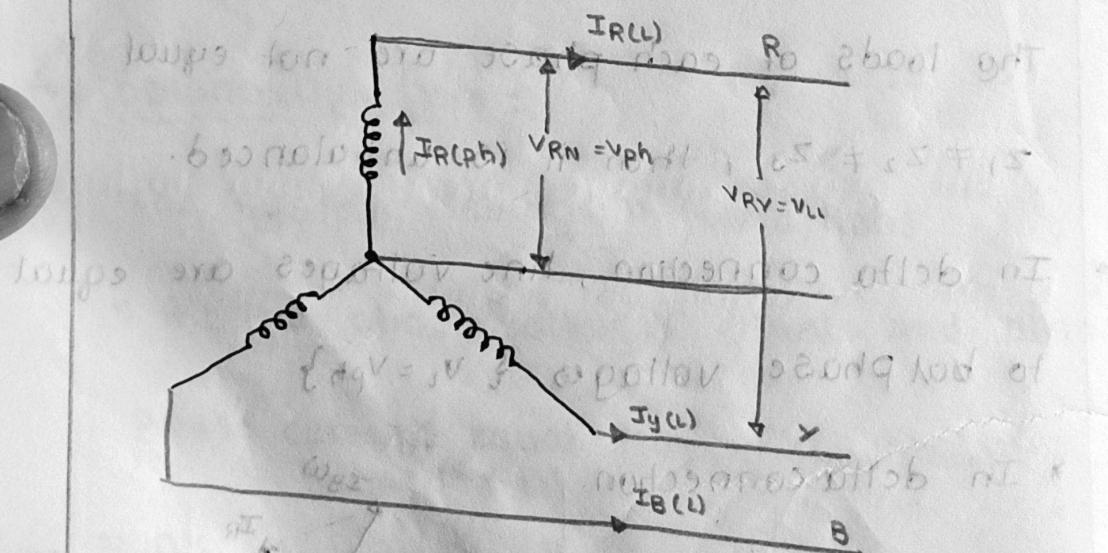- * The phase angle between one phase to other phase is 120° and the phase angle between a phase and its line called 30°



In Star connection line currents and phase currents are equal. $I_L = I_{ph}$

$$V_L = \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph}^2 \cos 60^\circ}$$

$$V_L = \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph}V_{ph} \cos\phi}$$

$$V_L = \sqrt{3} V_{ph}$$

$$P = 3 V_{ph} I_{ph} \cos\phi$$

* Power for 3-phase

$$P = 3 V_{ph} I_{ph} \cos\phi$$

* Power for line

$$P = 3 V_L \frac{I_L}{\sqrt{3}} \cos\phi = \sqrt{3} V_L I_L \cos\phi$$

Note-1 :

In 3-phase star connected system, line currents are equal to phase currents i.e $I_L = I_{ph}$

whereas the line voltages are $\sqrt{3}$ times of

phase voltages ($V_L = \sqrt{3} V_{ph}$ or $V_{ph} = \frac{V_L}{\sqrt{3}}$)

Note-2 :

In 3-phase delta connected System line voltages are equal to phase voltages ($V_L = V_{ph}$)

whereas line currents are $\sqrt{3}$ times of phase currents (i.e $I_L = \sqrt{3} I_{ph}$ or $I_{ph} = \frac{I_L}{\sqrt{3}}$)

Real power

for phase : $P_{3-\phi} = 3 V_{ph} I_{ph} \cos\phi$

for line : $P_{3-\phi} = \sqrt{3} V_L I_L \cos\phi$

Apparent power:

$$\text{for phase: } S = 3V_{ph} I_{ph}$$

$$\text{for line: } S = \sqrt{3} V_L I_L$$

Reactive power:

$$\text{for phase: } P_{3-\phi} = 3V_{ph} I_{ph} \sin \phi$$

$$\text{for line: } P_{3-\phi} = \sqrt{3} V_L I_L \sin \phi$$

$$(\frac{\sqrt{3}}{2} V_E I_L) \sin \phi = (\frac{\sqrt{3}}{2} \times 100 \times \frac{1}{\sqrt{3}}) \sin 30^\circ = 50$$

to comf. the no. of turns on the primary side

$$(\frac{N_1}{N_2} = \text{adj ratio} = \frac{V_1}{V_2}) \text{ adj ratio}$$

to comf. the no. of turns on the secondary side

$$(N_2 = \text{adj ratio} \times N_1 = 10 \times 50 = 500)$$

scoring to omit the no. of turns on the primary side

$$(\frac{N_2}{N_1} = \text{adj ratio} = \frac{V_2}{V_1}) \text{ adj ratio}$$

ratio 100:8

$$(\cos 30^\circ) \times 100 = 86.6$$

$$(\cos 30^\circ) \times 100 = 86.6$$