



## Encoder

- An encoder is a combinational logic circuit that essentially performs a “reverse” of decoder functions.
- An encoder accepts an active level on one of its inputs, representing digit, such as a decimal or octal digits, and converts it to a coded output such as BCD or binary.
- Encoders can also be devised to encode various symbols and alphabetic characters.
- The process of converting from familiar symbols or numbers to a coded format is called encoding.




IIT KHARAGPUR




NPTEL ONLINE  
CERTIFICATION COURSES



- 
- Most decoders accept an input code and produce a HIGH (or a LOW) at one and only one output line.
  - In other words, a decoder identifies, recognizes, or detects a particular code. The opposite of this decoding process is called encoding and is performed by a logic circuit called an encoder.
  - An encoder has a number of input lines, only one of which input is activated at a given time and produces an N-bit output code, depending on which input is activated.



## General encoder diagram

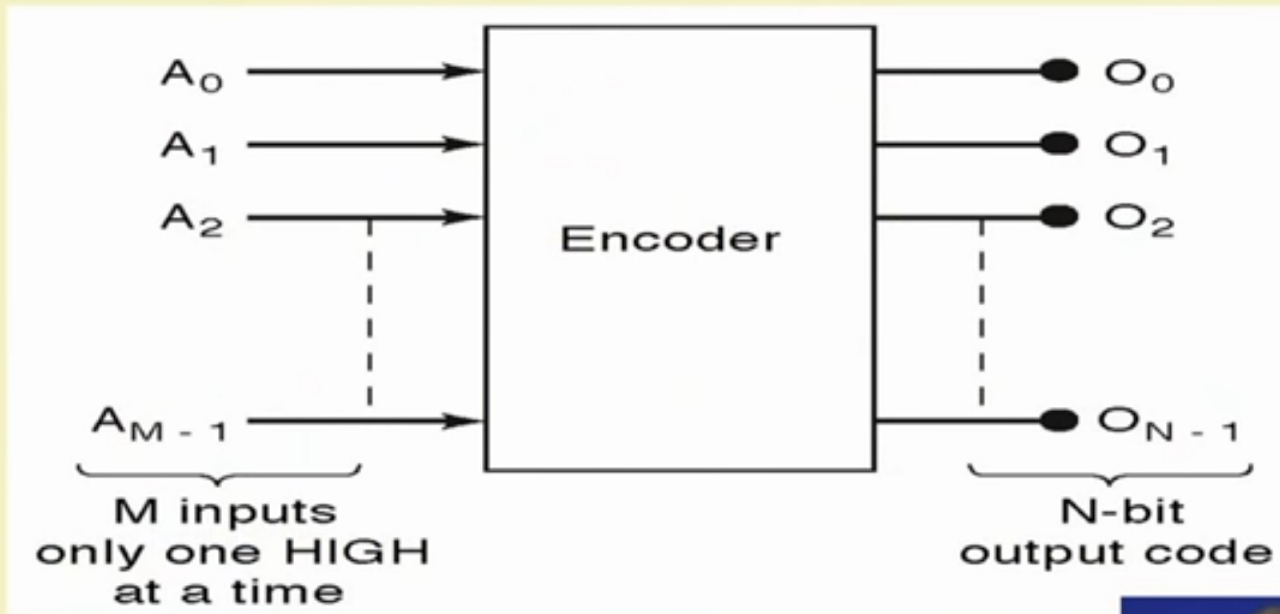


IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES


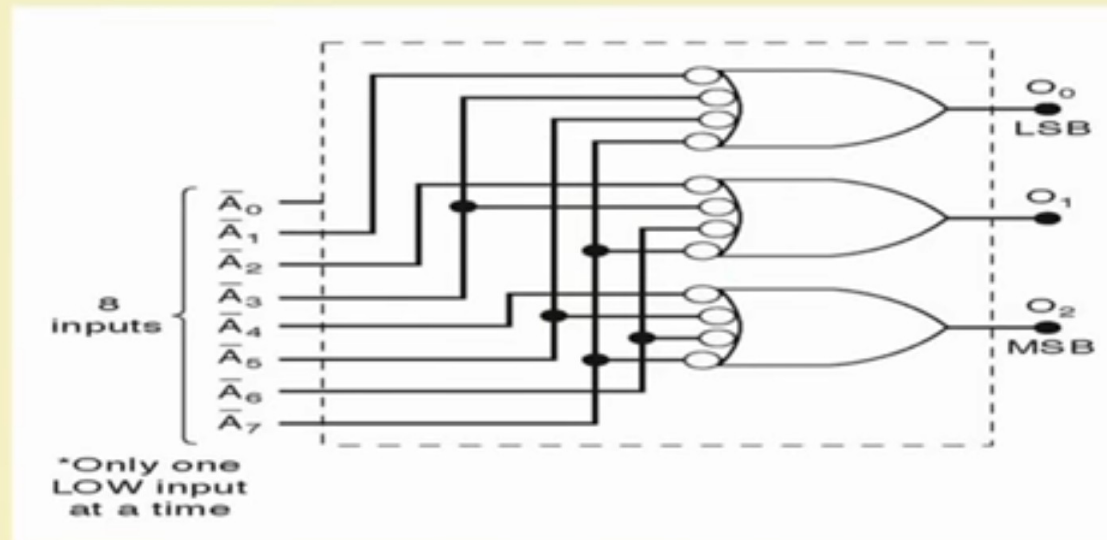
## Logic circuit for octal-to binary encoder [8-line- 3-line ]



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



## Truth table for octal-to binary encoder [8-line- 3-line ]

Inputs								Outputs		
$\bar{A}_0$	$\bar{A}_1$	$\bar{A}_2$	$\bar{A}_3$	$\bar{A}_4$	$\bar{A}_5$	$\bar{A}_6$	$\bar{A}_7$	$O_2$	$O_1$	$O_0$
X	1	1	1	1	1	1	1	0	0	0
X	0	1	1	1	1	1	1	0	0	1
X	1	0	1	1	1	1	1	0	1	0
X	1	1	0	1	1	1	1	0	1	1
X	1	1	1	0	1	1	1	1	0	0
X	1	1	1	1	0	1	1	1	0	1
X	1	1	1	1	1	0	1	1	1	0
X	1	1	1	1	1	1	0	1	1	1

A low at any single input will produce the output binary code corresponding to that input. For instance , a low at  $A_3'$  will produce  $O_2 = 0$ ,  $O_1 = 1$  and  $O_0 = 1$ , which is binary code for 3.  $A_0'$  is not connected to the logic gates because the encoder outputs always be normally at 000 when none of the inputs is LOW






### Design of 4-input Priority Encoder ( 4-line-to 2 line priority encoder) (1)...

- A priority encoder is an encoder that includes the **priority function**
- If two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence.
- **Truth Table of a 4-input Priority Encoder:**

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1





## Design of 4-input Priority Encoder ( 4-line-to 2 line priority encoder) (2)...

- In addition to two outputs  $x$ , and  $y$ , the truth table has a third output designated by  $V$ , which is a valid bit indicator that is set 1 when one or more inputs are equal to 1. If all inputs are 0, there is no valid input and  $V$  is equal to 0.
- X's in the output column indicate don't care conditions, the X's in the input columns are useful for representing a truth table in condensed form.
- The higher the subscript number, the higher the priority of the input. Input  $D_3$  has the highest priority, so regardless of the values of the other inputs, when this input is 1, the output for  $xy$  is 11 (binary 3)



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



## Design of 4-input Priority Encoder ( 4-line-to 2 line priority encoder) (3)...

		$D_2$				
		00	01	11	10	
$D_0$	00	X	1	1	1	$D_1$
	01		1	1	1	
	11		1	1	1	
	10		1	1	1	
		$D_3$				
		$x = D_2 + D_3$				

		$D_2$				
		00	01	11	10	
$D_0$	00	X	1	1		$D_1$
	01	1	1	1		
	11	1	1	1		
	10		1	1		
		$D_3$				
		$y = D_3 + D_1 D'_2$				


$$V = D_0 + D_1 + D_2 + D_3$$

K-Maps for 4-input Priority Encoder




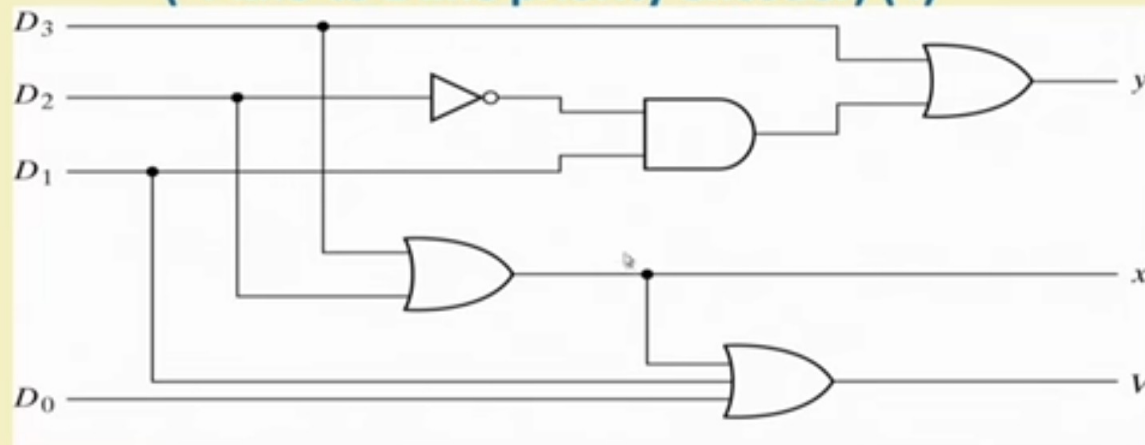
## Design of 4-input Priority Encoder ( 4-line-to 2 line priority encoder) (4)



Logic Diagram for 4-input priority encoder

