

## Electrical Technology Terminology :-

- i) charge:- Basic property of any matter which made with elementary particles which governs the forces when it is placed in electrical or magnetical field.

Generally, charge is of two types (electrically)

\* Electrically positive (protons have it)

\* Electrically negative (electrons have it)

$$\rightarrow 1p^+ = +1.62 \times 10^{-19} \text{ Coulomb}$$

$$\rightarrow 1e^- = -1.62 \times 10^{-19} \text{ Coulomb}$$

\* Unit of charge = Coulomb

$$\rightarrow 1e^- = -1.62 \times 10^{-19} \text{ Coulomb}$$

$$\rightarrow \text{Coulomb} = \frac{1}{+1.62 \times 10^{-19}} e^- \quad \{-ve\ \text{neglected}\}$$

$$\rightarrow 1 \text{ Coulomb} = 6.24 \times 10^{18} e^-$$

i.e.  $6.24 \times 10^{18}$  number of electrons constitute

the exact value of 1 coulomb

\* Charge is denoted by letter "Q" (or q)



{ matter  $\rightarrow$  atom  $\rightarrow$  sub atomic particles — Electrically charged  
+ or - }  $\rightarrow$  Electrically neutral

## Properties of charge:

- \* Consider the charge in a circuit, then the algebraic sum of charge in a circuit is always equal to zero.


A → B → C {net charge on B = 0}

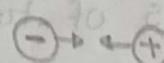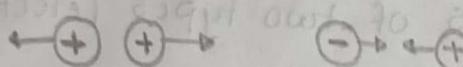- \* Like charges repel each other, unlike charges attract each other like magnets



## 2) Electric Current (I) :-

Generally Electric current is defined as flow of charges or flow of electrons.

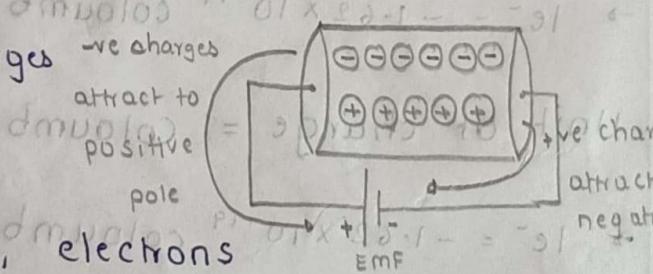- \* Here -ve charges are electrons. 
- \* By observing, electrons are travelling from negative pole to positive pole

But current flows from positive to negative pole

{current is flow of electrons}

- Actually current flows -ve to +ve pole only.

But according to certification by International Organisation of EEE, current is flowed from positive (+) to negative (-) pole.

This is known as "conventional current direction."

- \* Mass of electron =  $\frac{\text{mass of proton}}{1837}$
- \* As electron is lighter, current flow involves in flow of electrons only

### Formula & Unit

$$\text{current } (I) = \frac{Q}{t}$$

$$i = \frac{q}{t} = \frac{\text{Coulomb}}{\text{time}} \text{ or Ampere.} = \frac{6.24 \times 10^{18} e^-}{1 \text{ sec}}$$

i.e To produce 1 ampere of current,  $6.24 \times 10^{18}$  electrons should move in one second.

Ex:- Fan consumes 80 watt Power, and we get 230 volts of voltage

$$I = \frac{P}{V} = \frac{80}{230} = 0.35 \text{ A}$$

\* 0.35 amp is cause of speed of fan.


### 3) Voltage or Electric Potential

In absence of current charges bound together

& flows in different direction.

- \* When current is applied to circuit, charges separate and gain potential energy.

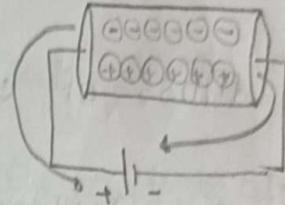- \* The potential difference b/w two charged bodies is called Electric voltage.
- \* In other words, "the amount of work done for a unit charge to create the movement"



$$V = \frac{\text{Energy}}{\text{charge}} = \boxed{\frac{J}{C} = \text{Volts}}$$

4) Electrical Energy (W):- The capacity to do some work, is known as Energy.

We know  $V = \frac{W}{Q}$

$\rightarrow W = VQ$

$\rightarrow W = V \cdot I \cdot t$

$\rightarrow W = P \cdot t$  {watt · second or Joule}

kilowatt-hour = 1 unit

calculated by Energy meter

- \* Product of electrical power and time is known as Electrical energy.

Ex:- 6 fans, each consuming 80 w power &

for 2pm to 5pm

$$6 \times 80 \text{ w} = 480 \text{ watt} = 0.48 \text{ kw/hour}$$

$$= 0.48 \text{ kW} \times 3 \text{ hours}$$

$$= 1.44 \text{ kilowatt hour (or) unit}$$

\* My Household unit consumption:-

$$6 \text{ lights for } 8 \text{ hours } \{ 10 \text{ watt/hour} \} = 0.48 \text{ kWh}$$

$$2 \text{ fans for } 10 \text{ hours } \{ 8 \text{ watt/hour} \} = 0.16 \text{ kWh}$$

$$1 \text{ fridge for } 24 \text{ hours } \{ 150 \text{ watt/hour} \} = 3.60 \text{ kWh}$$

$$1 \text{ motor pump for } \frac{1}{2} \text{ hour } \{ 1 \text{ unit/hour} \} = 0.50 \text{ kWh}$$

$$1 \text{ TV for } 4 \text{ hours } \{ 100 \text{ watt/hour} \} = 0.40 \text{ kWh}$$

\* Total kilowatt hours (units)

$$= 0.48 + 0.60 + 3.60 + 0.50 + 0.40$$

$$= 5.14 \text{ units per day } \{ \times 30 \text{ for monthly} \}$$

$$= 154.2 \text{ units per month } \{ \text{Actual units} = 179 \text{ units} \}$$

5) Power (P) :- The ability to do some work per unit

time is known as power.

\* Unit of power = watt

$$* P = \frac{W}{t} \quad \{ W = \text{energy or work done} \}$$

$$* P = \frac{W}{t} = \frac{W}{Q} \times \frac{Q}{t}$$


$$P = V \cdot I \quad \{ \text{watts} \}$$

$$\boxed{\text{volt} \cdot \text{Amp} = \text{watt}}$$

# Basic definitions of electric circuit:-


Circuit:- A simple closed path with source and load or with active & passive sources / load.

is known as circuit.

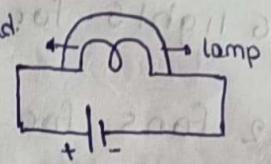
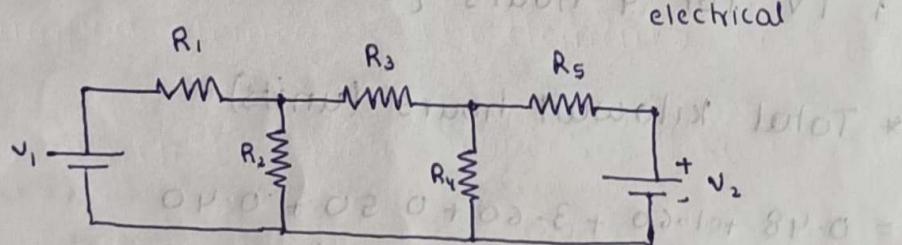
## \* Electric Network:


Interconnection of different electrical elements or interconnection of different sub-circuits.



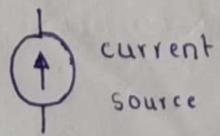
i) \* Active elements:- The elements which supplies or generates electrical energy to rest part of

the circuit are known as Active elements.

Ex:- Battery, Voltage Source, generator etc.



current source

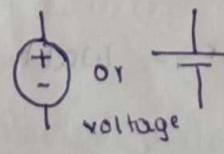

voltage source

ii) \* Passive elements:- The elements which consumes / receives or take the electrical energy from Active elements are known as Passive elements.


Ex: Resistors, Inductors, capacitors

- \* Active elements & passive elements are known as Network elements.

3) Linear elements:- The elements which always obey linearity principle are known as linear elements.

\* Principle of linearity:- If the graphical relation or representation b/w Voltage and current is a straight line.

Ex: Resistor, inductor, capacitor

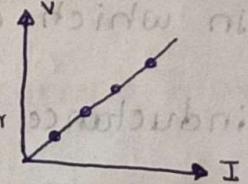


4) Non-linear elements:- The elements which does not obey principle of linearity are known as non-linear elements.

Ex: Diode.

5) Bi-lateral elements:- The elements which holds the relationship between voltage & current is same in either direction of current flow

through it

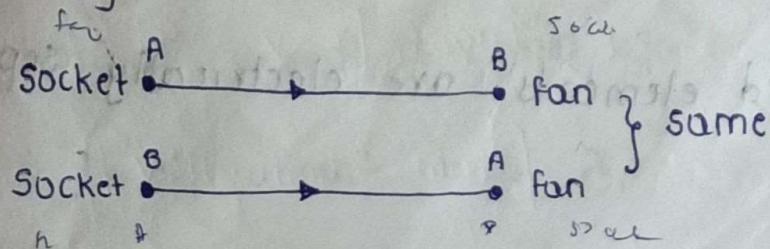

Ex: resistors, inductor, capacitor etc.

- ⑥ Symmetrical elements :- Elements which does not hold the relationship b/w Voltage and current as same in either direction of current flow through it.

Ex: Diode , semi-conducting devices { allows current in only one direction}

- ⑦ Lumped elements:- The elements or systems in which electrical properties like resistance, inductance & capacitance etc. are assumed to be located on a small space of circuit.

- \* Lumped elements are not electrically separable

Ex: Resistor, inductor & capacitor in labs.

- ⑧ Distributed elements:- The elements or systems in which electrical properties like resistance, inductance & capacitance etc. are assumed to be distributed across the entire circuit.

- \* Distributed elements are electrically separable


- \* Resistance in lumped element = concentrated resistance
- \* Resistance in distributed element = distributive
- \* Circuit parameters :- Ex: Transmission distribution lines, resistance

i) Resistor ( $R$ )

ii) Inductor ( $L$ )


iii) Capacitor ( $C$ )

iv) Resistor ( $R$ ) :- The element which opposes the flow of the current through it is known as

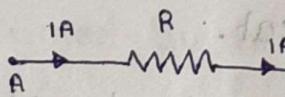Resistor.  unit = ohm ( $\Omega$ )

\* Resistor should oppose the current flow, but the current at point A & point B are same (no loss of current). because ...

consider a resistor of  $2\Omega$  connected to

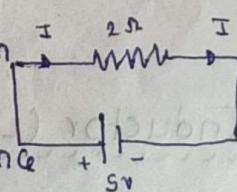
5 Volt source. After connection 

is made, the total resistance


$$\text{Current in the circuit} = I = \frac{V}{R} = \frac{5}{2} = 2.5 \text{ amp}$$

\* 2.5 amp is current produced after the opposition of current is done. So there is no change in the current b/w A & B points.


## Representation of resistor (R):

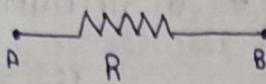

{Resistance = R}

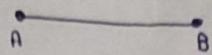

{Resistance = 0}

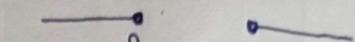

{Resistance = ∞}

## Formula:

$$V = IR$$

Volts

$$R = \frac{V}{I}$$

Ω

$$I = \frac{V}{R}$$

amp

Power dissipated =  $P = \frac{V^2}{R}$  or  $P = I^2 R$

- \* Resistor dissipates the electrical energy in the form of heat.
- \* Opposition is required should be in limit only i.e. Resistance should be not so high or not so low.
- Energy dissipated by resistor  $(W) = P \cdot t$

$$= V \cdot I \cdot t \text{ or } I^2 R t \text{ or } \frac{V^2}{R} t$$

- 2) Inductor (L): The element which opposes the sudden change of current in the circuit is known as Inductor (L).

Unit = Henry (H)

$$L = R + jx \quad \{jx = \text{reactance}\}$$

- \* Inductance (L) is combination of Resistance and Reactance.

\* voltage across the inductor  $(V) = L \cdot \frac{di}{dt}$

\* current through the inductor

$$\rightarrow V = L \cdot \frac{di}{dt}$$

$$\rightarrow di = \frac{1}{L} \cdot V \cdot dt$$

Integrating on both sides from 0 to t

$$\int_0^t di = \frac{1}{L} \int_0^t V \cdot dt$$

$$i(t) = \frac{1}{L} \int_0^t V \cdot dt \quad \text{amperes.}$$

\* Power consumed by inductor

$$P = V \cdot I$$

$$P = L \cdot \frac{di}{dt} \cdot I$$

$$P = L \cdot I \cdot \frac{di}{dt} \quad \text{watts}$$

\*\* Inductor stores the energy in electromagnetic

form. we know  $\text{energy } (W) = \frac{1}{2} L I^2$

$$\rightarrow \int_0^t W = \int_0^t P \cdot t \cdot dt$$

$$\int_0^t L I \cdot \frac{di}{dt} \cdot dt$$

$$= L \int_0^t i \cdot di$$

$$\boxed{\text{Energy}(W) = \frac{1}{2} L i^2} \quad \text{Joules}$$

$L$  = inductance of inductor in Henry

$i$  = current through inductor (Amp)

3) Capacitor ( $C$ ):

Any 2 conducting plates which are separated by an insulating medium, then it exhibits the property of a capacitor in presence of current flow. Representation  $\begin{array}{c} i \\ | \\ \text{---} \end{array}$  or  $\begin{array}{c} C \\ | \\ \text{---} \end{array}$

- \* The insulating medium is also called dielectric medium.
- \* The element which opposes the sudden change of voltage across the circuit is known as capacitor ( $C$ ).
- \* The value of capacitance is high for a particular capacitor if the capacity to store the charge is high for unit voltage.

Similarly, low capacitance if the capacity to store the charge is low for unit charge.

\* Current through capacitor  $\rightarrow i = C \frac{dv}{dt}$  amp.

\* Voltage across capacitor:  $dv = \frac{1}{C} \cdot i \cdot dt$

$$\int_0^t dv = \frac{1}{C} \int_0^t i \cdot dt \rightarrow V(t) = \frac{1}{C} \int_0^t i \cdot dt \text{ volts.}$$

\*\* Capacitor stores energy in electrostatic form

① Energy ( $w$ ) = P.  $\times$  capacity to do work.

$\{ w = V \cdot C \cdot \frac{dV}{dt} \}$  Power consumed by inductor

$$\int_0^t w dt = \int_0^t V \cdot C \cdot \frac{dV}{dt} dt$$

$$w(t) = \frac{1}{2} CV^2 \text{ Joules } \{ \text{Energy} \}$$

\* Power consumed by the capacitor.

$$\rightarrow P = V \cdot I$$

$$\{ i = C \frac{dV}{dt} \}$$

$$\rightarrow P = V \cdot C \cdot \frac{dV}{dt} \text{ Volts.watts.}$$

\*  $C$  = capacitance of capacitor in "Farad"

$V$  = voltage across capacitor in "Volts"

Energy sources:

\* Independent sources:

ii) Ideal Voltage source:


The source which supplies constant magnitude

of source voltage, independent of source current.


is known as Ideal Voltage Source.

$I_s$  = source current

$V_s$  = source voltage

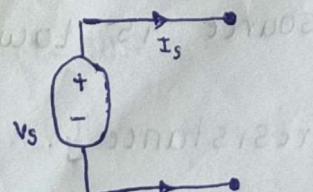


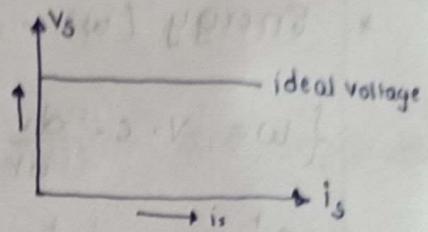- \* It is a 2 terminal element
- \* It is an active element.
- \* Voltage = constant.


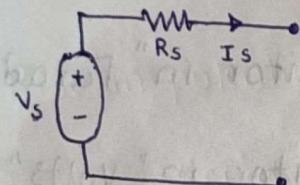
## 2) Practical Voltage Source:

- \* It is a 2 terminal active element.
- \* The source which produces the source voltage which slightly decreases with increase in source current is called Practical voltage source.




$V_s$  = SOURCE VOLTAGE

$R_s$  = SOURCE RESISTANCE (LOW)

$i_s$  = SOURCE CURRENT.

Graph

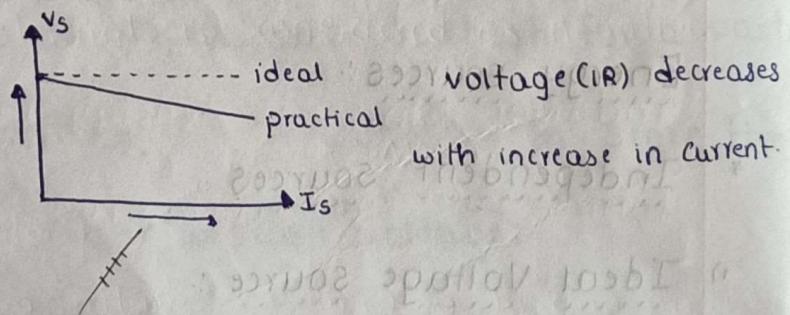


NOTE

- \* The internal resistance for Ideal voltage source is always zero.


$\{ n=0 \}$

- \* The internal resistance for practical voltage source is low { contains some internal resistance }.

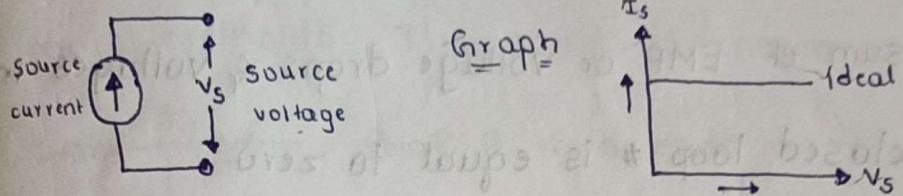- 3) Ideal Current Source:
- The current source which supplies the constant current, independent of source voltage is called Ideal Current source.




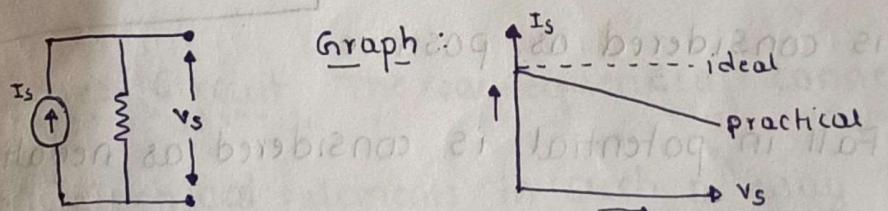- 4) Practical Current Source: The current source which supplies current which decreases with increase in voltage is called Practical Current Source.



NOTE:

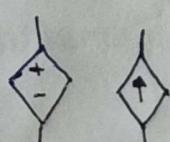- \* The internal resistance of Ideal Current Source is infinite {  $\boxed{R=\infty}$  }
- \* The practical current source have internal resistance, which is very high.
- \* Dependent Sources representation.



$$\boxed{eV \text{ for } +, eV - eV}$$

\* Kirchoff's Laws:

1) Kirchoff voltage law

2) Kirchoff current law.


3) Kirchoff Voltage law:- It states that the algebraic sum of EMF or voltage drops & voltages in a closed loop is equal to zero.

\* Voltage across source is known as EMF

\* Voltage across resistors is known as Voltage drop.



→ Sign convention

\* Rise in potential

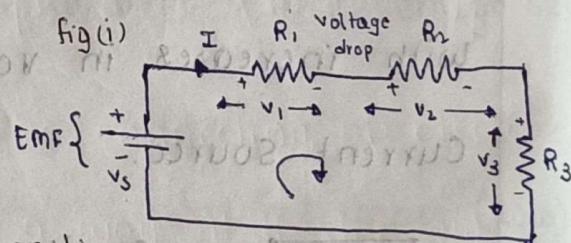

is considered as positive

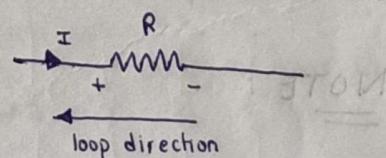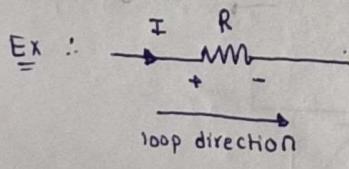\* Fall in potential is considered as negative.



(+ to -) so fall in (- to +) so Rise in potential  
potential =  $-IR$  =  $+IR$

\* for fig(i)


$$-IR_1 - IR_2 - IR_3 + Vs = 0$$

$$Vs - V_1 - V_2 - V_3 = 0$$

→  $V_s = V_1 + V_2 + V_3 //$

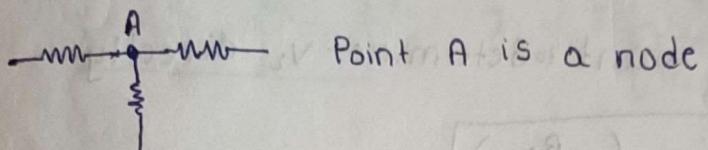- 2) Kirchoff current law: This law states that the algebraic sum of currents at a point or node or junction is equal to zero.

Node: It is a point, which connects two or more elements. The point is known as node.




Point A is a node

- \* From Kirchoff current law,

$$\text{we get } I_1 + I_3 + I_2 + I_8 - I_4$$


$$- I_5 - I_6 - I_7 = 0$$

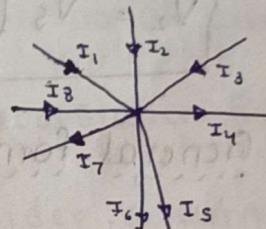

$$\text{i.e. } I_1 + I_2 + I_3 + I_8 = I_4 + I_5 + I_6 + I_7$$

- \* Series Circuit: The sequential connection

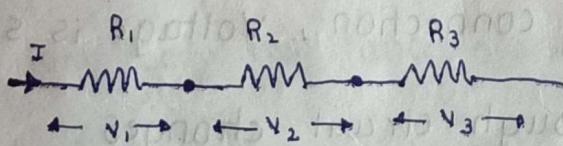
of electrical elements in such a way that end point of one element is connected to starting point the next element.



- \* In Series connection, current is always same and voltage across circuit changes.

$$\text{Resistance (Total)} = R_1 + R_2 + R_3 + \dots + R_n$$

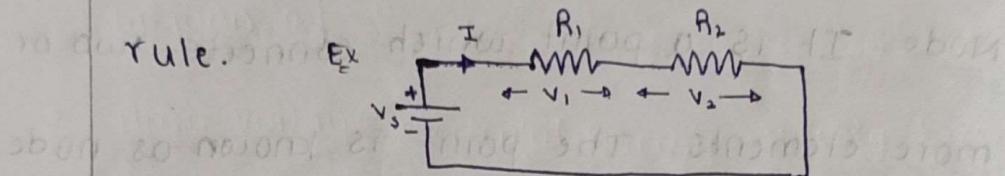- \* Voltage division Rule: only applicable for series connection. If we want to determine a particular voltage in the circuit, we use this rule.




If we want to determine  $V_2$  directly -

$$V_2 = V_s \left( \frac{R_2}{R_1 + R_2} \right)$$


- \* General formula:  $V_n = V_{\text{Total}} \left( \frac{R_n}{R_1 + R_2 + \dots + R_n} \right)$

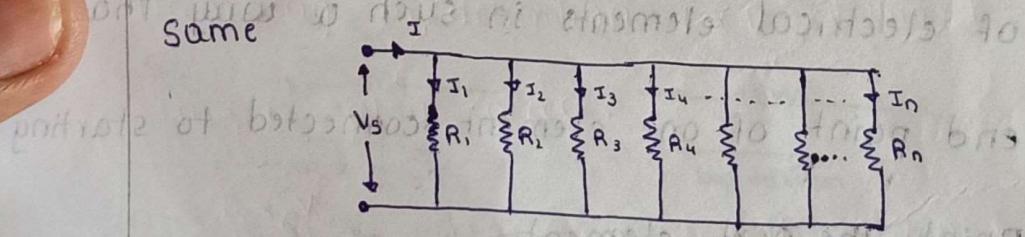- \* \* 2) Parallel circuit: The connection of electrical elements in such a way that the starting and ending points of all the elements are same




- \* In parallel connection, Voltage is same and current through circuit changes
- \* Resistance (Total):  $\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$
- \* Current division rule: only applicable for series parallel connection. If we want to

determine a particular current in circuit, we use this rule.

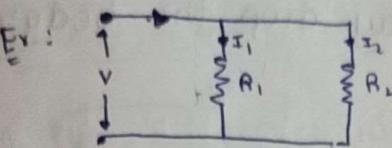Ex: 

$$I_1 = I \left( \frac{R_2}{R_1 + R_2} \right) \text{ opposite resistance}$$

$$I_2 = I \left( \frac{R_1}{R_1 + R_2} \right) \text{ opposite resistance}$$

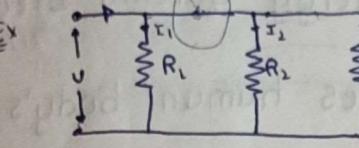Ex: 

$$I_1 = I \left[ \frac{\frac{1}{R_2} + \frac{1}{R_3}}{R_1 + \left( \frac{1}{R_2} + \frac{1}{R_3} \right)} \right]$$

\* General formula: Let there  $n$  no. of currents with  $n$  no. of resistors of resistance  $R_1, R_2, R_3, \dots, R_n$  respectively. Consider a current  $I_a$  & resistor of resistance  $R_a$  & current through it is  $I_a$

Now  $I_a = \frac{V}{R_a}$   $\left[ \frac{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_{a-1}} + \frac{1}{R_{a+1}} + \dots + \frac{1}{R_n}}{R_a + \left[ \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_{a-1}} + \frac{1}{R_{a+1}} + \dots + \frac{1}{R_n} \right]} \right]$

H.W \* Range of resistance in human body

\* The total body resistance of the person is composed of the very internal body resistance {approx 300 $\Omega$ } But skin has higher resistance.

The skin contact resistance will usually be between 1000 and 100,000 $\Omega$  of resistance.

- \* Under dry conditions, the resistance offered by the human body may be as high  $100,000 \Omega$
- \* Wet or broken skin may drop the body's resistance to  $1000 \Omega$
- \* High voltage electrical energy quickly breaks down human skin which reduces human body's resistance to  $500 \Omega$

→ Ohm's law: Ohm's law states that the current through a conductor is directly proportional to the voltage across it.

$$I \propto V \quad \{ \text{But } V = IR \}$$

If we consider  $V \propto I$ , then  $V = IR$

\* According to definition  $I \propto V \quad \{ \text{then } I = kV \}$

This is also correct.

$$I \propto V \quad \{ G = \text{proportional constant} \}$$

$$I = GV$$

Here  $G$  is known as conductance

"Conductance" is an expression of the ease with which electric current flows through materials like metals.

- \* In electrical purposes, conductance is very rarely considered. So we don't use the expression  $I = G \cdot V$ . But resistance (R) is used regularly.
- So,  $V = IR$  expression is used to determine Ohm's law.

Problems:

- 1) If a 70 Joules energy is available for every 30 coulomb charge. What is voltage.

A Given Energy ( $w$ ) = 70 J

charge ( $Q$ ) = 30 C

$$V = \frac{w}{Q} = \frac{70}{30} = 2.33 \text{ Volts}$$

- 2) What is the power in watts if energy = 50 J is used in 2.5 seconds


A Given Energy ( $w$ ) = 50 J

time ( $t$ ) = 2.5 sec

$$P = \frac{w}{t} = \frac{50}{2.5} = 20 \text{ watts}$$

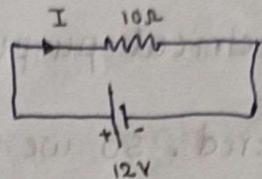- 3) A 10 ohms resistor is connected across 12 V battery. How much current flows through the resistor.

$$A \quad I = \frac{12}{10} = 1.2 \text{ Amp}$$



- 4) Current in a 2 Henry inductor varies at the rate of 2 amp per second. Find the voltage across inductor and energy stored in inductor in magnetic field after 2 seconds.

$$A \quad L = 2 \text{ H}$$

$$\text{Energy } (w) = \frac{1}{2} L I^2$$

$$\frac{di}{dt} = 2 \text{ Amp/s}$$

$$w = \frac{1}{2} (2)(4)^2 \quad \{ \text{current for 2 sec} = 4 \text{ amp} \}$$

$$V = L \cdot \frac{di}{dt} = 2 \times 2 = 4 \text{ Volts}$$

$$w = 16 \text{ J}$$

- 5) Capacitor having capacitance of 2 μF is charged to a voltage of 1000 V. Calculate the stored energy in Joules.


$$A \quad C = 2 \mu\text{F} = 2 \times 10^{-6} \text{ F}$$

$$V = 1000 \text{ V}$$

$$\text{Energy } (w) = \frac{1}{2} CV^2 = \frac{1}{2} (2 \times 10^{-6}) (1000)^2$$

$$= 1 \text{ J} = \frac{w}{e \cdot c} = \frac{w}{q} = q$$

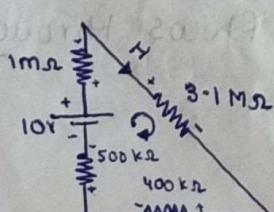- 6) For the circuit shown below, determine the voltage across each resistor.



\* Apply KVL to the above circuit

$$* 3.1 \text{ m}\Omega = 3.1 \times 10^6 \Omega$$

$$* 400 \text{ k}\Omega = 400 \times 10^3 \Omega = 4 \times 10^5 \Omega = 0.4 \text{ m}\Omega$$

$$\rightarrow +10 - I(1 \text{ m}\Omega) - I(3.1 \text{ m}\Omega) - I(0.4 \text{ m}\Omega) - I(0.5 \text{ m}\Omega) = 0$$

$$\rightarrow 10 - I - 3.1I - 0.4I - 0.5I = 0 \quad \{ \text{in mega ohm} \}$$

$$\rightarrow 10 + (-I - 3.1I - 0.4I - 0.5I) \text{ M}\Omega = 0$$

$$\rightarrow 10 - (5I) \times 10^6 \Omega = 0$$

$$\rightarrow 10 = 5I \times 10^6 \Omega = (0.6) AB \cdot I = 300V$$

$$\rightarrow I = 2 \times 10^{-6} A$$

$$\rightarrow I = 2 \mu A$$

$$* V_{1\text{m}\Omega} = (2 \times 10^{-6} A) (1 \times 10^6 \Omega) = 2V$$


$$* V_{3.1\text{m}\Omega} = (2 \times 10^{-6} A) (3.1 \times 10^6 \Omega) = 6.2V$$

$$* V_{400\text{k}\Omega} = (2 \times 10^{-6} A) (0.4 \times 10^6 \Omega) = 0.8V$$

$$* V_{500\text{k}\Omega} = (2 \times 10^{-6} A) (0.5 \times 10^6 \Omega) = 1V$$

(i) In the circuit shown in figure, Find


i) Current ( $I$ )

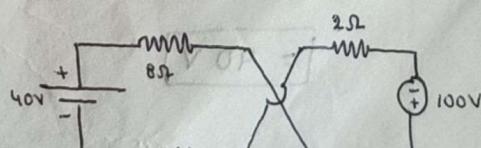

ii) Voltage ( $V$ ) across  $30\Omega$

{ not connected

A Redraw above circuit

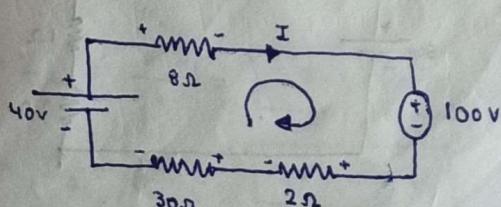

Apply KVL to above circuit...

$$+40 - I(8) - 100 - 2I - 30I = 0$$

$$-60 - 40I = 0$$

$$I = \frac{-60}{40} = -1.5 A$$

$I = -1.5 A$  current in circuit is  $1.5 A$  which


is in opposite direction of assumed loop direction.

$$V_{30\Omega} = 1.5 A (30) = 45 \text{ Volts}$$

- 7) What is the voltage across  $10\Omega$  resistor in given circuit.

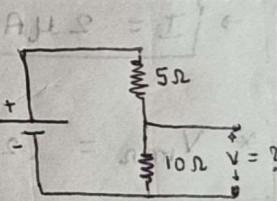A) Apply voltage division rule.

$$V_{10\Omega} = 50 \left( \frac{10}{10+5} \right) = 33.33 V$$




- 8) Find the voltage b/w A & B in given circuit.

A) Apply voltage division rule


$$V_{AB} = 100 \left( \frac{(5+4)k\Omega}{(1+5+4)k\Omega} \right)$$

$$= 90 V$$

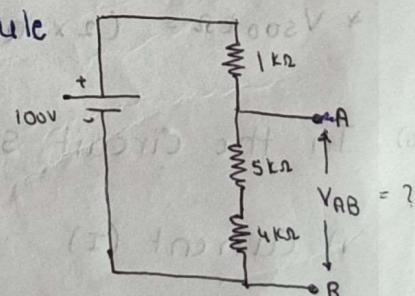

- 9) Determine the total amount of power in given circuit

A) Power ( $P$ ) =  $\frac{V^2}{R}$

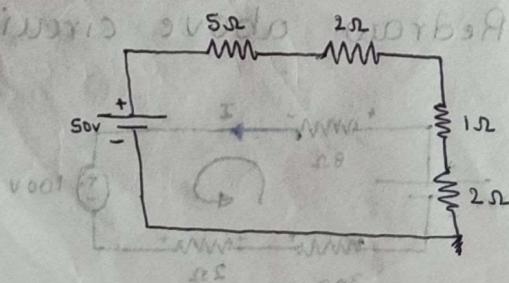

$$P_T = (50)^2 / (5 + 2 + 2) = 250 \text{ watt}$$

$$P_T = 250 \text{ watt}$$

(or)

$$\{ R_{\text{Total}} = R_1 + R_2 + R_3 + R_4 \text{ (series)} \}$$

$$I = \frac{V}{R_T} = \frac{50}{10} = 5 \text{ A}$$

$$P_{5\Omega} = I^2 R = 5^2 \times 5 = 125 \text{ W}$$


$$P_{2\Omega} = 5^2 \times 2 = 50 \text{ W}$$

$$P_{1\Omega} = 5^2 \times 1 = 25 \text{ W}$$

$$\begin{aligned} \text{Total power consumed} &= 125 + 25 + 50 + 50 \\ &= 250 \text{ watt} \end{aligned}$$

- 10) Determine the current in all resistors in given circuit.

\* Apply KCL to circuit  $SOA$

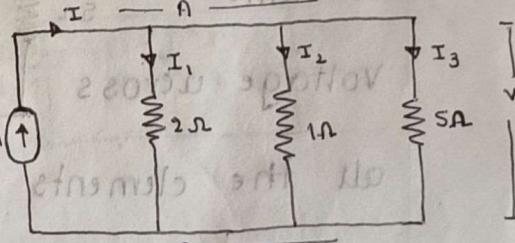

\* Apply KCL to node A

$$I = I_1 + I_2 + I_3 \quad \{ I = 50 \text{ A} \}$$

$$= 50 = \frac{V}{2\Omega} + \frac{V}{1\Omega} + \frac{V}{5\Omega}$$

$$= 50 = V \left( \frac{1}{2} + \frac{1}{1} + 1 \right)$$

$$= V = \frac{50}{1.7} = 29.4 \text{ Volts}$$

$$* I_1 = \frac{V}{2\Omega} = \frac{29.4}{2\Omega} = 14.7 \text{ Amp}$$

$$* I_2 = \frac{V}{1} = 29.4 \text{ Amp}$$

$$* I_3 = \frac{V}{5} = 5.8 \text{ Amp}$$

(Or) Apply current division rule

$$I_1 = 50 \left[ \frac{\frac{1}{1} + \frac{1}{6}}{2 + \frac{1}{1} + \frac{1}{6}} \right]$$

$$I_1 = 50 \left[ \frac{\frac{5}{6}}{2 + \frac{5}{6}} \right]$$

$$I_1 = 50 \left[ \frac{5}{17} \right]$$

$$I_1 = 14.7 \text{ Amp}$$

similarly we can find  $I_2$  &  $I_3$


$$I_2 = 7.2 \text{ Amp}$$

- ii) For the circuit shown in figure, Find the  
Voltage across  $10\Omega$  resistor & current passing  
through it.

\* Assume

Voltage across

all the elements is 'V' Volts.

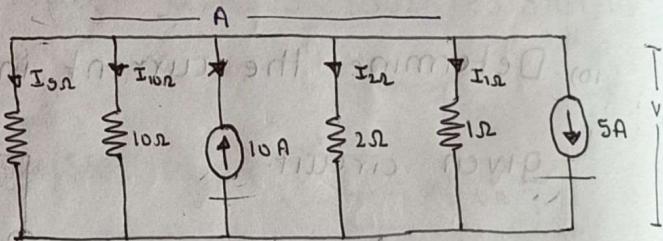

Apply KCL to above circuit

\* Apply KCL to node A

$$10 = I_{5\Omega} + I_{10\Omega} + I_{2\Omega} + I_{1\Omega} + 5$$

$$5 = I_{5\Omega} + I_{10\Omega} + I_{2\Omega} + \frac{1}{2} I_{1\Omega} + 0$$

$$5 = \frac{V}{5} + \frac{V}{10} + \frac{V}{2} + \frac{V}{1}$$

$$5 = V \left( \frac{1}{5} + 0.2 + 0.1 + 0.5 + 1 \right) = \frac{V}{25} = 1.8 \times$$

$$5 = 1.8$$

$$\frac{V}{25} = 1.8 \times$$

$$\frac{V}{25} = 1.8 \times$$

$$V = 2.77 \text{ Volts}$$

$$V \text{ across } 10\Omega \text{ resistor} = 2.77 \text{ Volts}$$

$$I \text{ through } 10\Omega \text{ resistor} = \frac{V}{10} = \frac{2.77}{10}$$

$$= 0.277 \text{ Amp}$$

- (2) Determine the parallel resistance between A & B of given circuit.


A

$$\frac{1}{R_{AB}} = \frac{1}{10} + \frac{1}{20} + \frac{1}{30} + \frac{1}{40}$$

$$R_{AB} = 4.8 \Omega$$

- (3) Determine the current through each resistor in the circuit shown in figure.

A Apply current division rule.

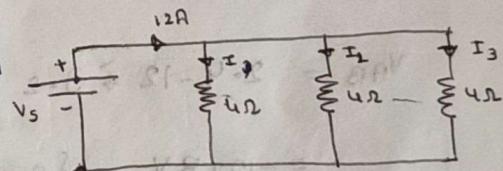

$$I_1 = 12 \left[ \frac{\frac{4 \times 4}{4+4}}{4 + \frac{4 \times 4}{4+4}} \right]$$

$$I_1 = 12 \left[ \frac{16/8}{4 + 16/8} \right]$$

$$I_1 = 4 \text{ Amp}$$


similarly


$$I_2 = I_3 = 4 \text{ Amp}$$

$$\text{Bcoz } R_1 = R_2 = R_3 = 4 \Omega$$

- (4) What is the voltage across A & B in the circuit shown in figure.

Diagram in next page

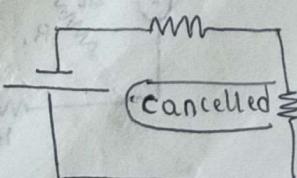

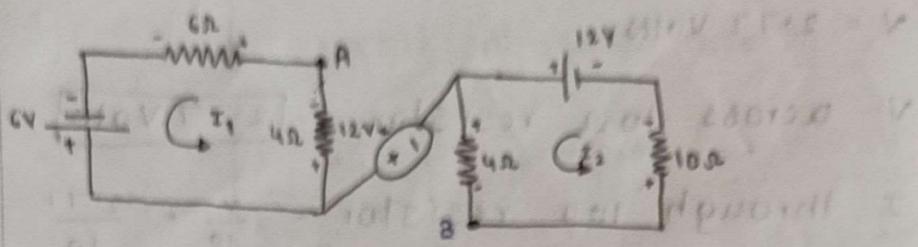


A Total resistance for  $I_1 = 6 + 4 = 10\Omega$

Total voltage for  $I_1 = 6V$

$$I_1 = \frac{6}{10} = 0.6 \text{ Amp}$$
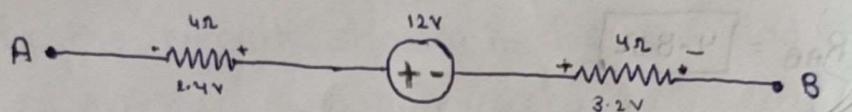
$$\text{similarly } I_2 = \frac{12}{14} = 0.8 \text{ Amp}$$



$$V_{un} (\text{left}) = 0.6 \times 4 = 2.4V$$


$$V_{un} (\text{Right}) = 0.8 \times 4 = 3.2V$$

$$V_{AB} = 2.4 - 12 + 3.2$$

$= -12.8V$  {opposite to assumed direction}

Voltage across AB = 12.8V

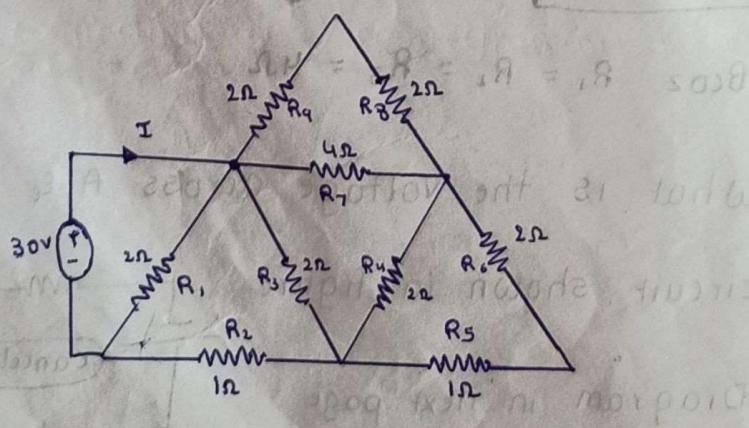- is) Determine the current delivered by the source in the circuit shown in figure.




A In above circuit

$(R_9 \& R_8)$  and  $(R_5 \& R_6)$  are in series

$$R_{10} = R_9 + R_8 = 2 + 2 = 4\Omega$$

$$R_{11} = R_5 + R_6 = 2 + 1 = 3\Omega$$


Now Redraw the circuit.

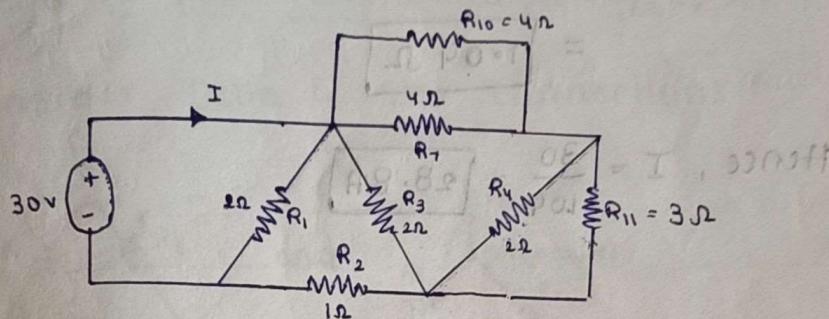

$$\text{Now } R_{10} \parallel R_7 = \frac{4 \times 4}{4+4} = 2\Omega \rightarrow R_{12}$$

$$\text{Also } R_4 \parallel R_{11} = \frac{2 \times 3}{2+3} = 1.2\Omega \rightarrow R_{13}$$


Redraw the circuit

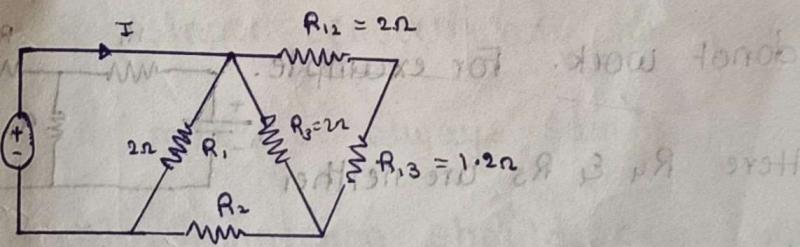

Now,  $R_{12}$  is in series with  $R_{13}$


$$= R_{12} + R_{13} = 2 + 1.2 = 3.2\Omega \rightarrow R_{14}$$

Now Redraw the the circuit

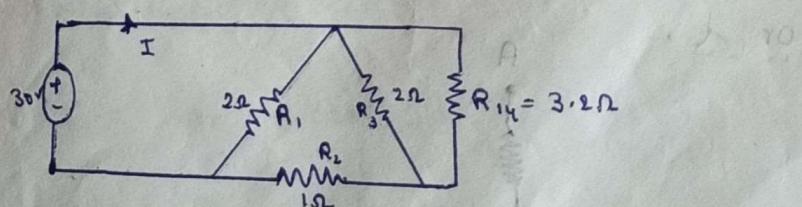

$$R_3 \parallel R_{14} = \frac{2 \times 3.2}{2+3.2} = 1.2\Omega \rightarrow R_{15}$$


Now circuit is

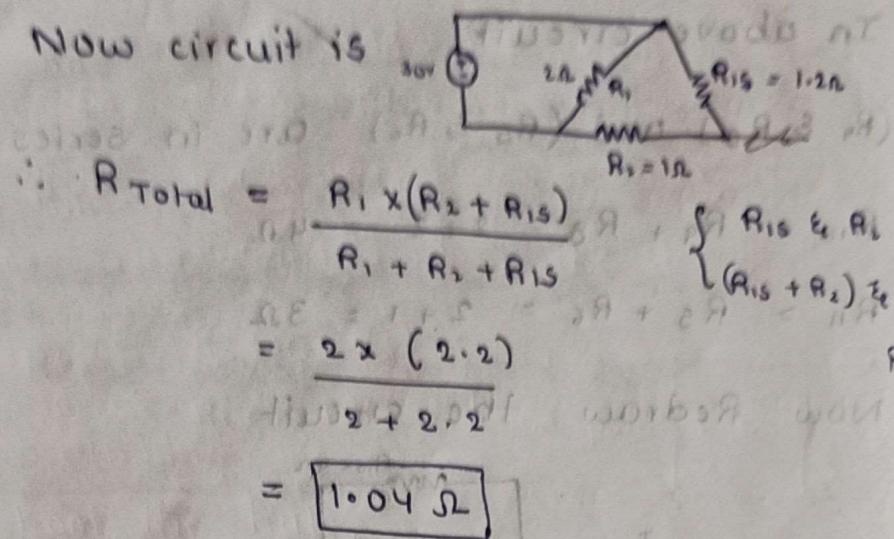

Hence,  $I = \frac{30}{1.04} = 28.8 \text{ A}$


Star to delta & Delta to star transformation.

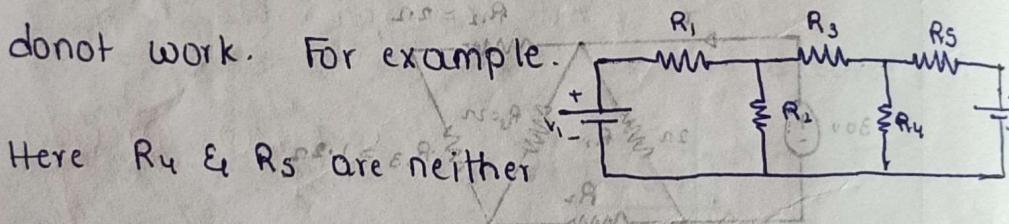This process is used when the formula of total resistance in series & parallel connection donot work. For example.




- \* Here  $R_4$  &  $R_5$  are neither in parallel or series. we can't determine the total resistance for it. Then we use this process
- "Star connection"  $\leftrightarrow$  "Y connection"  $\leftrightarrow$  "T connection"

or


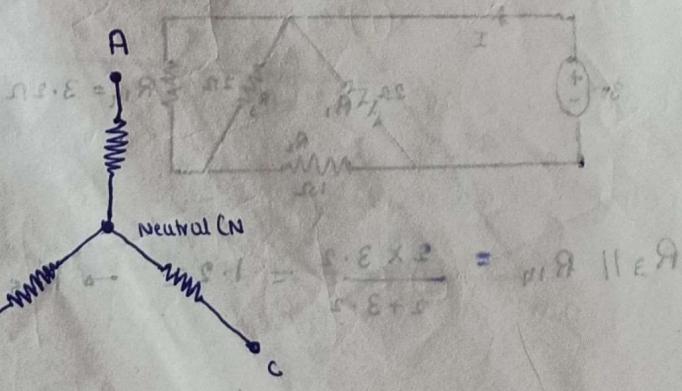


## Delta connection / $\pi$ connection

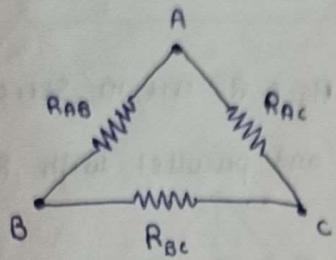

① Delta to star transformation:  $\Delta \rightarrow \lambda$

consider Delta & star connections

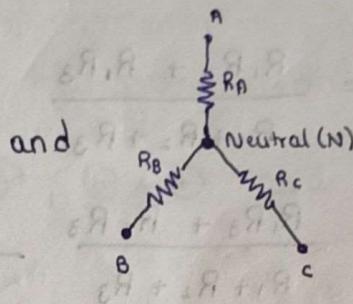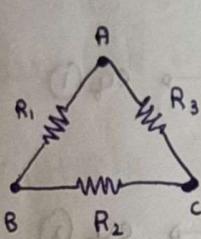

\* To make delta to star transformation possible,

there is one important rule.

\* Rule: Resistance between any two points or terminals must be always same.

$\rightarrow R_{AB}$  in star connection should be equal to

$R_{AB}$  in delta connection

\* Now, in star connection

$$R_A + R_B = R_{AB} \quad \{ \text{series} \}$$

$$R_B + R_C = R_{BC} \quad \{ \text{series} \}$$

$$R_A + R_C = R_{AC} \quad \{ \text{series} \}$$

\* Now, from delta connection

$$R_{AB} = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3} \quad \left\{ \begin{array}{l} R_2 \text{ & } R_3 \text{ in series} \\ \text{parallel with } R_1 \end{array} \right.$$

$$R_{AC} = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3} \quad \left\{ \begin{array}{l} R_1 \text{ & } R_2 \text{ are in series themselves} \\ \text{and parallel with } R_3 \end{array} \right.$$

$$R_{BC} = \frac{R_2(R_1 + R_3)}{R_1 + R_2 + R_3} \quad \left\{ \begin{array}{l} R_1 \text{ & } R_3 \text{ are in series themselves} \\ \text{and parallel with } R_2 \end{array} \right.$$

\* from the Rule,

$$R_A + R_B = \frac{R_1R_2 + R_1R_3}{R_1 + R_2 + R_3} \quad \xrightarrow{\text{eq 1}}$$

$$R_A + R_C = \frac{R_1R_3 + R_2R_3}{R_1 + R_2 + R_3} \quad \xrightarrow{\text{eq 2}}$$

$$R_B + R_C = \frac{R_1R_2 + R_2R_3}{R_1 + R_2 + R_3} \quad \xrightarrow{\text{eq 3}}$$

{  $R_{AB}$  of star connection =  $R_{AB}$  of delta connection }

Now (1) - (2) + 3

$$\underline{R_A + R_B} - \underline{R_A + R_C} + \underline{R_B + R_C} = \frac{R_1R_2 + R_1R_3 - R_1R_3 - R_2R_3 + R_1R_2}{R_1 + R_2 + R_3} + R_B$$

$$= 2R_B = \frac{2R_1R_2}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_1R_2}{R_1 + R_2 + R_3} \quad \xrightarrow{\text{eq 4}}$$


Substitute in 1 & 3

we get

$$R_A = \frac{R_1R_3}{R_1 + R_2 + R_3} \quad \xrightarrow{\text{eq 5}}$$

and  $R_C = \frac{R_1 R_3}{R_1 + R_2 + R_3} \rightarrow \text{Q6}$

The resultant diagram is

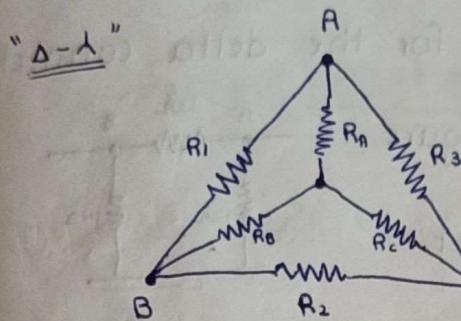

- ② Start to Delta transformation:  
multiply ④ × ⑤, ⑤ × ⑥ and ⑥ × ④ and all  
of them

$$R_A R_B + R_B R_C + R_C R_A = \frac{R_1^2 R_2 R_3 + R_2^2 R_1 R_3 + R_3^2 R_1 R_2}{(R_1 + R_2 + R_3)^2}$$

$$= R_1 R_2 R_3 (R_1 + R_2 + R_3)$$

$$R_A R_B + R_B R_C + R_C R_A = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_A R_B + R_B R_C + R_C R_A = \frac{R_1 R_3}{R_1 + R_2 + R_3} (R_2) \text{ from } ⑤$$

$$R_2 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

Similarly


$$R_1 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

$$R_3 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$


## Resultant diagram

- 19 Obtain the star connected equivalent for the delta connected circuit shown in figure

A Redrawing the circuit

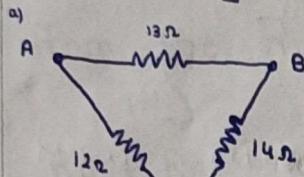

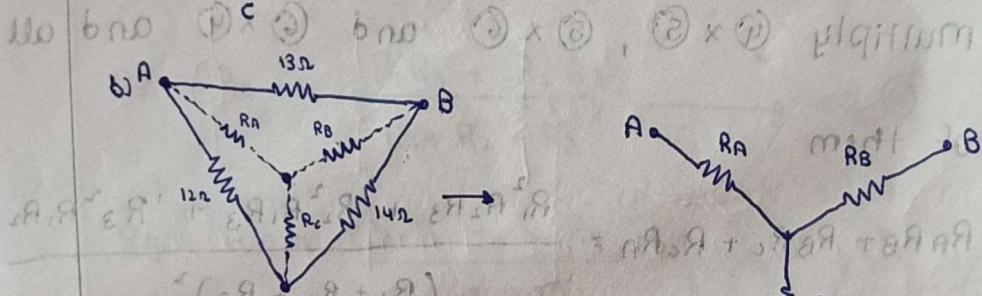Now convert the delta connection to star connection.



$$\text{Now } R_A = \frac{12 \times 13}{12 + 13 + 14} = 4\Omega$$



$$\& R_B = \frac{13 \times 14}{12 + 13 + 14} = 4.6\Omega$$

$$\& R_C = \frac{12 \times 14}{12 + 13 + 14} = 4.3\Omega$$

- 20 Obtain the delta connected equivalent for the

star connected circuit shown in figure.

A Convert into delta connection

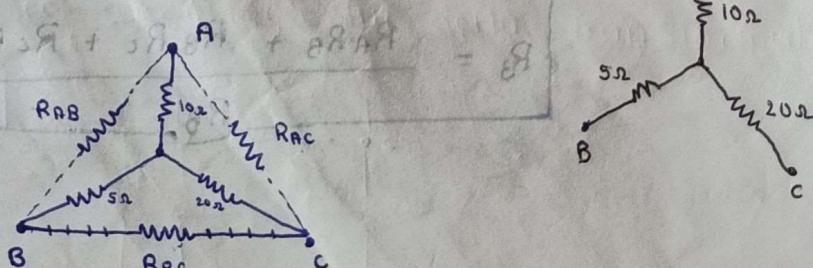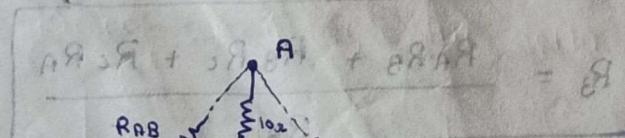


$$\text{Now } R_{AB} = \frac{(10 \times 5) + (5 \times 20) + (20 \times 10)}{20} = 17.5 \Omega$$

$$R_{BC} = \frac{(10 \times 5) + (5 \times 20) + (20 \times 10)}{10} = 35 \Omega$$

$$R_{AC} = \frac{(10 \times 5) * (5 \times 20) + (20 \times 10)}{5} = 70 \Omega$$

30 Determine the current drawn by circuit

shown in figure.

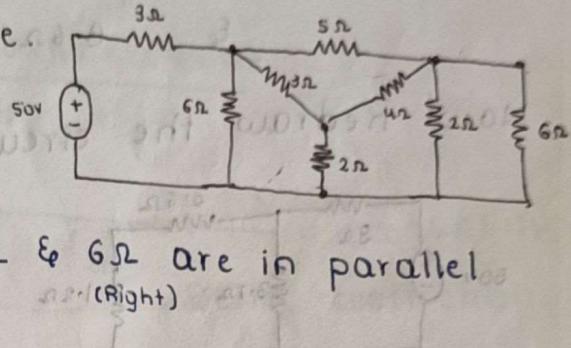


A In above circuit

$I = \frac{V}{R_T}$ , & 2Ω & 6Ω are in parallel


$$2\Omega // 6\Omega = \frac{6 \times 2}{6 + 2} = 1.5 \Omega$$

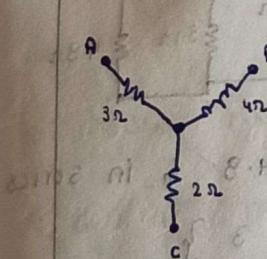Further, 3Ω, 4Ω & 2Ω are in Star connection



Now convert it

into delta connection

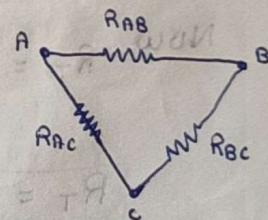

$$\text{Now } R_{AB} = \frac{(3 \times 4) + (4 \times 2) + (2 \times 3)}{2} = 13 \Omega$$

$$R_{BC} = \frac{(3 \times 4) + (4 \times 2) + (2 \times 3)}{3} = 8.6 \Omega$$


$$R_{AC} = \frac{(3 \times 4) + (4 \times 2) + (2 \times 3)}{4} = 6.5 \Omega$$

\* Redraw the circuit with these new values

$$R_{AB} = 13 \Omega$$

$$R_{AC} = 6.5 \Omega$$

$$R_{BC} = 8.6 \Omega$$

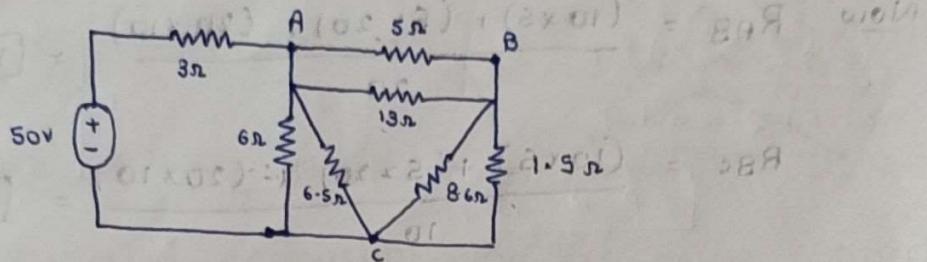


\* In above circuit (B)  $\frac{6 \times 6.5}{6 + 6.5} = \frac{6 \times 6.5}{12.5} = 3.1\Omega$

also  $5\Omega \parallel 13\Omega = \frac{5 \times 13}{5 + 13} = 3.6\Omega$

&  $8.6\Omega \parallel 1.5\Omega = \frac{8.6 \times 1.5}{8.6 + 1.5} = 1.27\Omega$

Now Redraw the circuit.

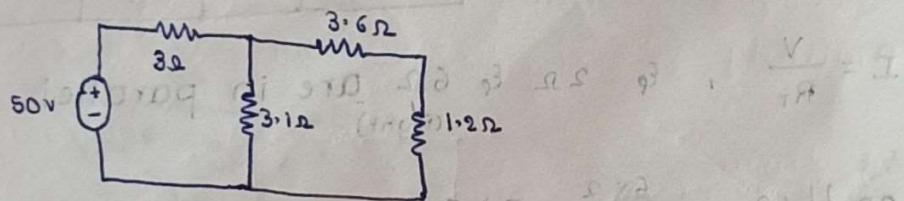

In above circuit  $3.6\Omega$  is in series with  $1.2\Omega$

$= 1.2 + 3.6 = 4.8\Omega$ , then


Now  $R_T = 3 + \frac{4.8 \times 3.1}{4.8 + 3.1}$  {  $3.1 \parallel 4.8$  & in series with 3 }

$$R_T = 4.88\Omega$$

Now,  $I = \frac{V}{R_T} = \frac{50}{4.88} = 10.4\text{Amp}$

$$I = 10.4 \text{ Amp}$$

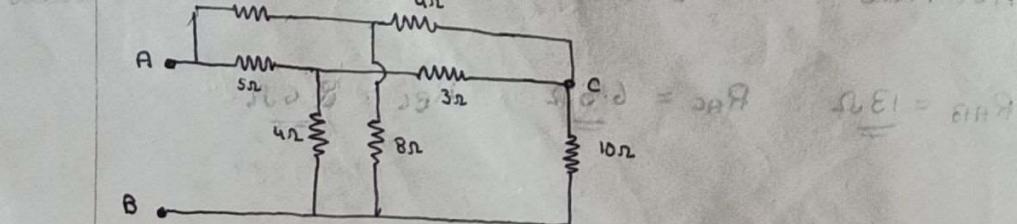In the figure, Determine the equivalent resistance by using star delta transformation.



A In above circuit. convert it into star connection


Delta connection

$$R_{AB} = \frac{(5 \times 3) + (3 \times 4) + (4 \times 5)}{3} = 15.6 \Omega$$

$$R_{BC} = \frac{(5 \times 3) + (3 \times 4) + (4 \times 5)}{5} = 9.4 \Omega$$

$$R_{CA} = \frac{(5 \times 3) + (3 \times 4) + (4 \times 5)}{4} = 11.7 \Omega$$

Also, convert it into Delta connection.

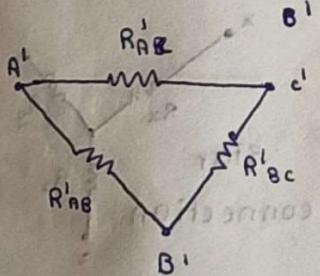


$$R'_{AB} = 2.6 \Omega$$

$$R'_{BC} = 17.3 \Omega$$

$$R'_{AC} = 13 \Omega$$

Now Redraw the circuit.

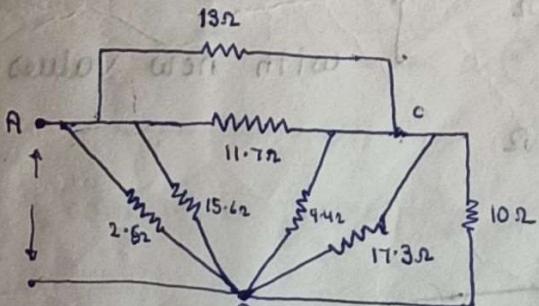


9.4 ohms, 17.3 ohms and 10 ohms are in parallel

$$\text{Effective resistance} = \frac{1}{\frac{1}{9.4} + \frac{1}{17.3} + \frac{1}{10}} = 3.78 \Omega$$

$$\text{In above circuit, } 13 \Omega \parallel 11.7 \Omega = \frac{13 \times 11.7}{13 + 11.7} = 6.15 \Omega$$
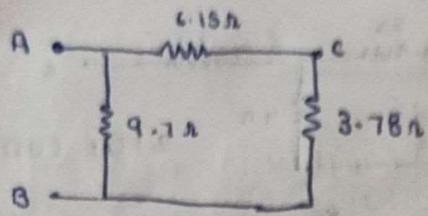
$$\text{Also, } 2.6 \text{ & } 15.6 \text{ in parallel} = \frac{2.6 \times 15.6}{2.6 + 15.6} = 9.7 \Omega$$



$$R_T = \frac{9.7(6.15 + 3.78)}{9.7 + 6.15 + 3.78}$$

$$R_T = 4.9 \Omega$$


Q Find the equivalent resistance b/w A & B.

A Here  $8\Omega$  &  $4\Omega$  (down)

are in parallel { because B terminal

is present } If it is absent,



they both will be in

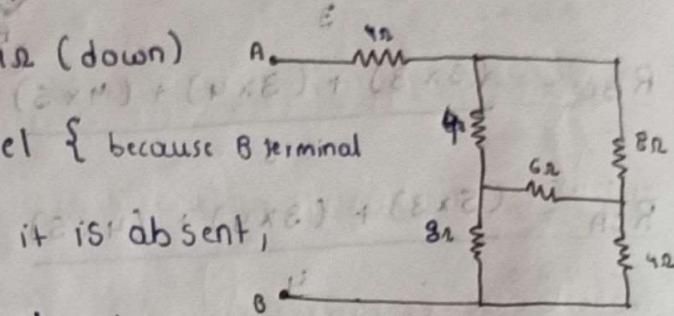

Series:

Consider

Delta conn  
ection

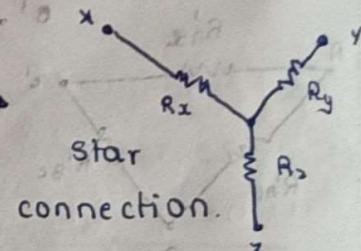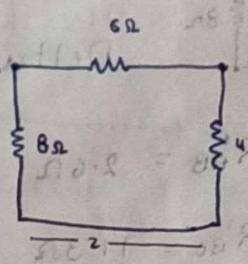


$$R_x = \frac{6 \times 8}{6+8+4} = 2.6 \Omega$$

$$R_y = \frac{6 \times 4}{6+8+4} = 1.3 \Omega$$

$$R_z = \frac{8 \times 4}{6+8+4} = 1.7 \Omega$$

Redraw the circuit  
with new values

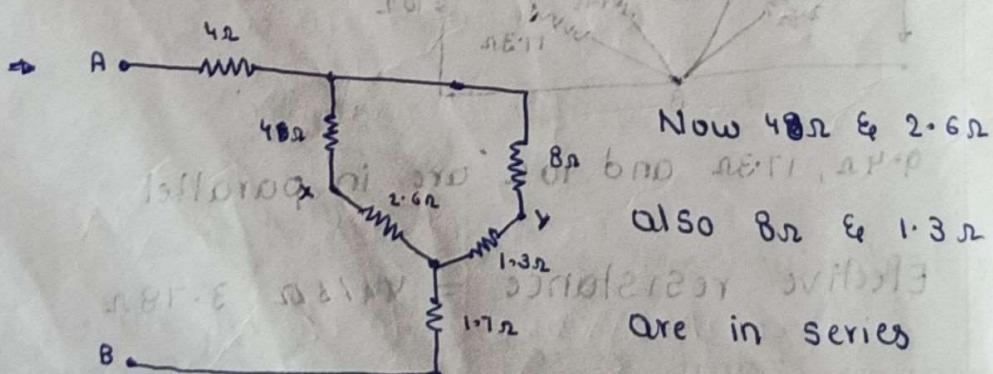


Now  $4\Omega$  &  $2.6\Omega$   
are in series

Also  $8\Omega$  &  $1.3\Omega$

are in series

$$= 4\Omega + 2.6\Omega = 6.6\Omega$$

$$= 8\Omega + 1.3\Omega = 9.3\Omega$$

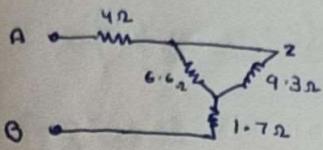

In above circuit,  $6\Omega \parallel 9.3\Omega$


$$= \frac{6 \cdot 9.3}{6 + 9.3} = 3.86\Omega$$

Total resistance  $= 3.86 + 4 + 1.7 = 9.56\Omega$


{ 4Ω & 3.86Ω & 1.7 are in series }
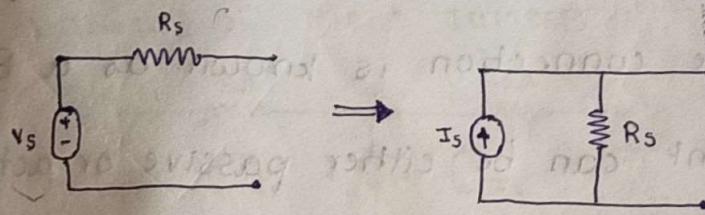
### ④ \* Source Transformation:

It is process which gives the idea of transformation of voltage source to current source & current source to voltage source.




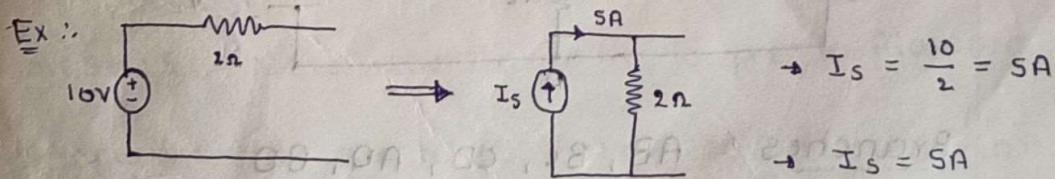For conversion,  $I_s = \frac{V_s}{R_s}$  { voltage to current }




{ voltage to current }

### → Current to voltage conversion:

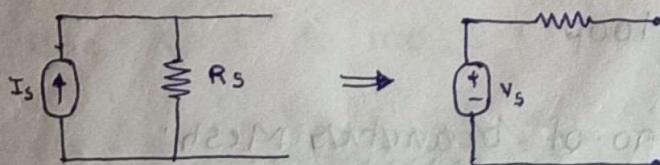


For conversion,  $V_s = I_s R_s$

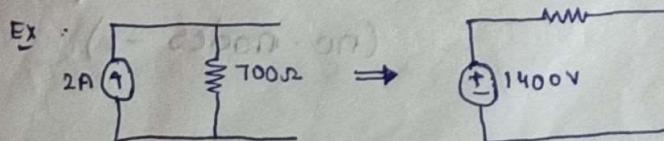

$$N_s = 2 \times 700 = 1400 \Omega$$
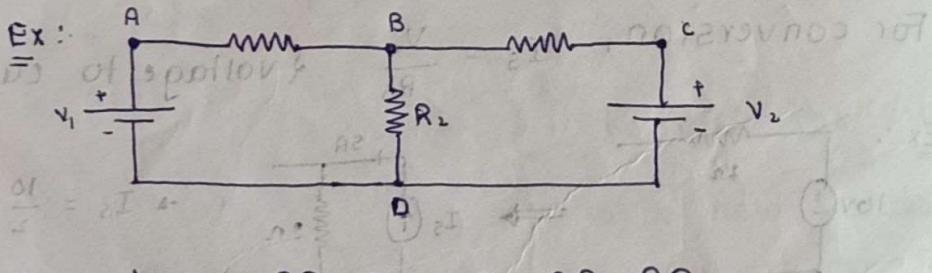
## ① Mesh Analysis:-

- \* Mesh is a simple closed loop, or simple closed path. Mesh don't contain any other mesh or loop inside it {no internal loops are there}
- \* Loop is a closed path, It can contain another loops inside it {internal loops are present}
- \* The element which is connected to any two points, the connection is known as a Branch {The element can be either passive or active}.



Branches :- AB, BC, CD, AD, BD

ABDA is a mesh and loop

BCDB is a mesh and loop

ABCDA is a loop


Formula for no. of branches Mesh:-

No. of Mesh equations = (no. of branches) - (no. nodes - 1)

$$\text{No. of mesh} = B - (n - 1)$$

Procedure:

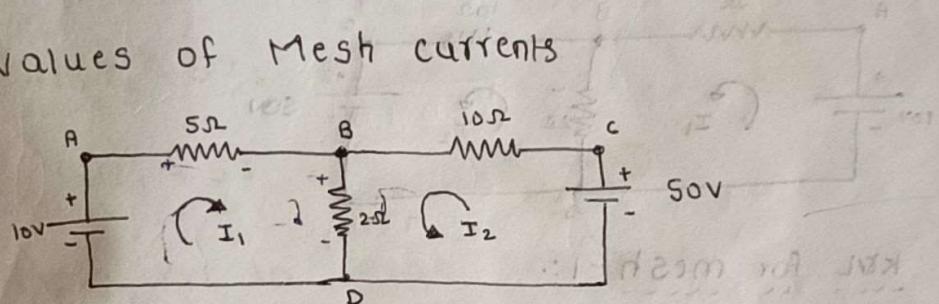- 1) Identify the number of meshes
  - 2) Assume currents in each mesh
  - 3) Write the current equations.
  - 4) Solve the equations to find the current.
- Q Write the mesh current equations in the circuit shown in figure also determine the values of Mesh currents



In the above circuit, ABDA & BCDB are two meshes. Now consider  $I_1$  current flowing clockwise in mesh-1. And consider current  $I_2$  flowing anti-clockwise in mesh-2.

Apply Mesh analysis:

Use K.V.L to mesh-1: ABDA {loop direction - ↗}

$$+10 - 5I_1 - 2(I_1 + I_2) = 0 \quad \text{①}$$

$$+10 - 7I_1 - 2I_2 = 0$$

$$7I_1 + 2I_2 = 10 \rightarrow \text{②}$$

Use KVL to mesh-2 : BCDB {loop direction  $\curvearrowleft$ }

$$10I_2 - 50 + 2(I_2 + I_1) = 0$$

$$= 2I_1 + 12I_2 = 50 \rightarrow ②$$


By solving ① & ② equations

$$I_1 = 0.25 \text{ A}$$

$$I_2 = 4.125 \text{ A}$$

{ Assumed current directions are true }

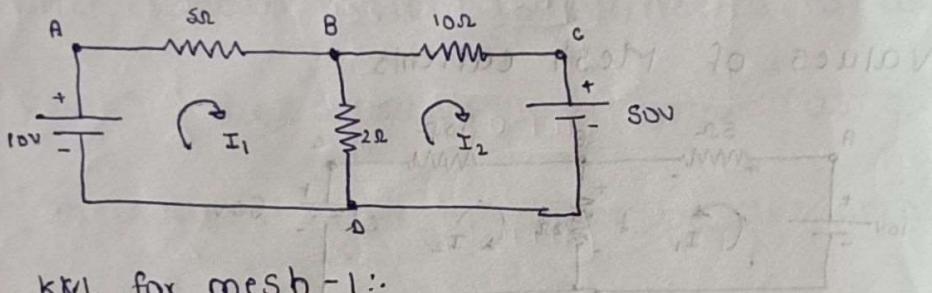\* Let us consider different current directions.



KVL for mesh-1 :

$$\rightarrow 10 - 5I_1 - 2(I_1 - I_2) = 0$$

$$\rightarrow 7I_1 - 2I_2 = 10 \rightarrow ①$$

KVL for mesh-2 :

$$\rightarrow +10I_2 - 50 + 2(I_2 - I_1) = 0$$

$$= 10I_2 + 2I_2 - 2I_1 = 50$$

$$\rightarrow 12I_2 - 2I_1 = 50 \rightarrow ②$$

By solving ① & ②, we get

$$I_1 = 0.25 \text{ A}$$

$$I_2 = -4.125 \text{ A}$$

{ flowing reverse to the assumed direction }

Q Determine the mesh currents in given circuit


A Assume current in 1st

mesh as  $I_1$ , in clockwise,

& current in 2nd mesh as  $I_2$

in anticlockwise & current in 3rd mesh as  $I_3$

in anti-clockwise directions.

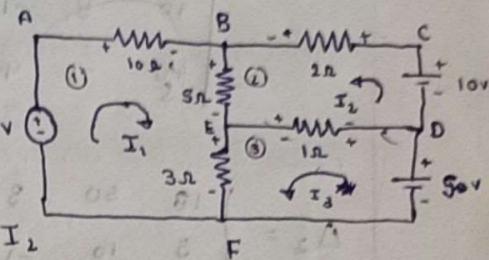

Apply KVL to Mesh ABEFA

$$-10I_1 - 5(I_1 + I_2) - 3(I_1 + I_3) + 50 = 0$$

$$-18I_1 - 5I_2 - 3I_3 = -50$$

$$18I_1 + 5I_2 + 3I_3 = 50 \rightarrow ①$$

Apply KVL to Mesh BCDEB

$$-2I_2 - 5(I_2 + I_1) - 1(I_2 - I_3) + 10 = 0$$

$$-8I_2 - 5I_1 + I_3 = -10$$

$$8I_1 + 8I_2 - I_3 = 10 \rightarrow ②$$

Apply KVL to mesh EDFE

$$+3(I_3 + I_1) + 1(I_3 - I_2) - 50 = 0$$

$$3I_1 - I_2 + 4I_3 = 50 \rightarrow ③$$

$$\Delta = \begin{vmatrix} 18 & 5 & 3 \\ 5 & 8 & -1 \\ 3 & -1 & 4 \end{vmatrix} = 18(8(4) - (-1)(-1)) - 5(5 \times 4 - 3(-1)) + 3(5(-1) - 8(3)) = 356$$

$$\Delta_1 = \begin{vmatrix} 80 & 5 & 3 \\ 10 & 8 & -1 \\ 5 & -1 & 4 \end{vmatrix} = 80(8 \times 4 - (-1)(-1)) - 5(10(4) - (5)(-1)) + 3(10(-1) - 8(5)) = 1175$$

$$\Delta_2 = \begin{vmatrix} 18 & 50 & 3 \\ 5 & 10 & -1 \\ 3 & 5 & 4 \end{vmatrix} = 18(10(4) - (5)(-1)) - 50(5(4) - 3(-1)) + 3(5(5) - 3(10)) = -355$$

$$\Delta_3 = \begin{vmatrix} 18 & 5 & 50 \\ 5 & 8 & 10 \\ 3 & -1 & 5 \end{vmatrix} = 18(40 + 10) - 5(25 - 30) + 50(-5 - 24) = -525$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{1175 + 175}{356} = 3.3A$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-355}{356} = -0.9A$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-525}{356} = -1.47A$$

2) Determine the values of mesh current in given circuit.

A) Assume current in mesh 1

as  $I_1$  in clockwise & in mesh

2 as  $I_2$  in clockwise & in mesh


3 as  $I_3$  in anticlockwise directions.

Apply KVL to mesh-1

$$+20V - 10(I_1 - I_2) - 6(I_1 + I_3) = 0$$

$$-16I_1 + 10I_2 - 6I_3 = -20$$

$$-16I_1 + 10I_2 - 6I_3 = -20$$

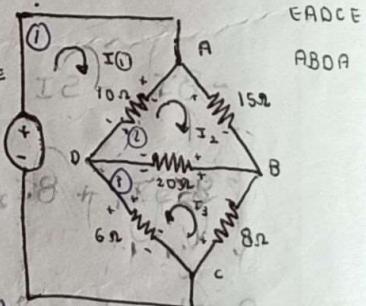

$$16I_1 - 10I_2 + 6I_3 = 20 \rightarrow ①$$

Apply KVL to mesh ② ABDA

$$-10(I_2 - I_1) = 15I_2 - 20(I_2 + I_3) = 0$$

$$-45I_2 + 10I_1 - 20I_3 = 0$$

$$10I_1 - 45I_2 - 20I_3 = 0 \rightarrow ②$$

Apply KVL to mesh ③ DBCD

$$6(I_3 + I_1) + 20(I_3 + I_2) + 8I_3 = 0$$

$$6I_1 + 20I_2 + 34I_3 = 0 \rightarrow ③$$

By Cramers rule

$$\Delta = \begin{vmatrix} 16 & -10 & 6 \\ 10 & -45 & -20 \\ 6 & 20 & 34 \end{vmatrix} = 16(-1530 + 400) + 10(340 + 120) + 6(200 + 270) = -10,660$$

$$\Delta_1 = \begin{vmatrix} 20 & -10 & 6 \\ 0 & -45 & -20 \\ 0 & 20 & 34 \end{vmatrix} = 20(-1530 + 400) + 10(340 + 120) - 22,600$$

$$\Delta_2 = \begin{vmatrix} 16 & 20 & 6 \\ 10 & 0 & -20 \\ 6 & 6 & 34 \end{vmatrix} = 20(340 + 120) = -9200$$

$$\Delta_3 = \begin{vmatrix} 16 & -10 & 20 \\ 10 & -45 & 0 \\ 6 & 20 & 0 \end{vmatrix} = 20(200 + 270) = 9400$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-22600}{-10660} = 2.12 \text{ Amp}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-9200}{-10660} = 0.86 \text{ Amp}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{9400}{-10660} = -0.88 \text{ Amp}$$


→ Super mesh: A branch which is having a current source which is common

$$0 = \epsilon I_0 S - BC \text{ is supermesh.}$$

for 2 or more meshes

$$0 = \epsilon I_0 S - c I_2 P - r I_0$$

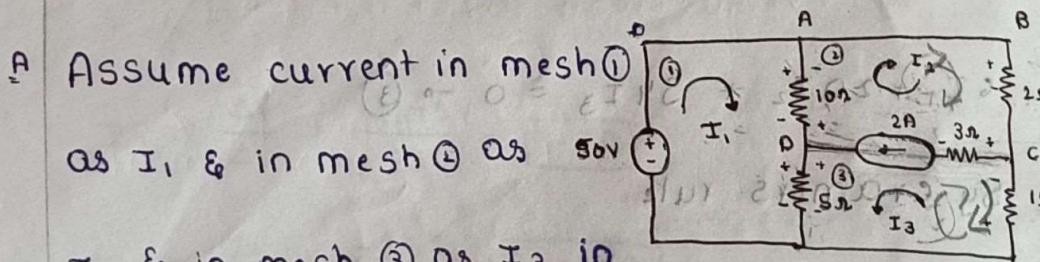34 Determine the current in the  $S_{22}$  resistor for the network shown in figure.



$I_2$  & in mesh ③ as  $I_3$  in

clock wise, anti-clockwise, anti-clockwise direction respectively

Apply KVL to ADEA

$$-10(I_1 - I_2) - 5(I_1 + I_3) + 50 = 0$$

$$3I_1 - 2I_2 + I_3 = 10 \rightarrow ①$$

Apply KVL to super mesh → 'ABCDEA'

$$0.05P = (0.5 + 0.05) 0.5 = 0.25$$

$$-2I_2 + 2I_3 (1) + 5(I_1 + I_3) - 10(I_2 - I_1) = 0$$

$$15I_1 - 12I_2 + 6I_3 = 0$$

$$5I_1 - 4I_2 + 2I_3 = 0 \rightarrow ②$$

From common branch with current source

$$0I_1 + I_2 + I_3 = 2 \text{ Amp} \rightarrow \text{Eqn 3}$$

By cramers rule,

$$\Delta = \begin{vmatrix} 3 & -2 & 1 \\ 5 & -4 & 2 \\ 0 & 1 & 1 \end{vmatrix} = 3(-4-2) + 2(5) + 1(5) = -3$$

$$\Delta_1 = \begin{vmatrix} 10 & -2 & 1 \\ 0 & -4 & 2 \\ 2 & 1 & 1 \end{vmatrix} = 10(-4-2) + 2(+4) + 1(+8) = -60$$

$$\Delta_2 = \begin{vmatrix} 3 & 10 & 1 \\ 5 & 0 & 2 \\ 0 & 2 & 1 \end{vmatrix} = 3(-4) - 10(+5) + 1(+10) = -52$$

$$\Delta_3 = \begin{vmatrix} 3 & -2 & 10 \\ 5 & -4 & 0 \\ 0 & 1 & 2 \end{vmatrix} = 3(+8) + 2(+10) + 10(+5) = 46$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-60}{-3} = 20 \text{ Amp}$$


$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-52}{-3} = 17.3 \text{ Amp}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{46}{-3} = -15.3 \text{ Amp}$$

Q8 Write the mesh equations for the circuit shown in figure and determine mesh currents.

A Assume Current  $I_1$  in mesh 1

Current  $I_2$  in mesh 2, current

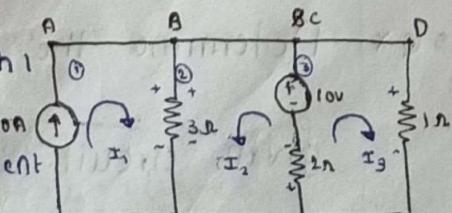

$I_1$  in mesh 1 in clockwise direction  
 $I_2$  in mesh 2 in clockwise direction  
 $I_3$  in mesh 3 in clockwise direction respectively.

Apply KVL to 'BCEB'

$$-10 + 2(I_2 + I_3) + 3(I_2 + I_1) = 0$$

$$3I_1 + 5I_2 + 2I_3 = 10 \rightarrow ①$$

Apply KVL to 'CDEC'

$$-(I_1) - 2(I_3 + I_2) + 10V = 0$$

$$-2I_2 - 3I_3 = -10$$

$$2I_2 + 3I_3 = 10 \rightarrow ②$$

From mesh 1,  $I_1 = 10A \rightarrow ③$

Substitute in ①

$$(5I_2 + 2I_3 = -20) 3$$

$$(2I_2 + 3I_3 = 10) 2$$

$$15I_2 + 6I_3 = -60$$

$$4I_2 + 6I_3 = 20$$

$$11I_2 = -80 \Rightarrow I_2 = \frac{-80}{11} = -7.2A$$

$$I_2 = -80/11 = -7.2A$$


Substitute in ②, then  $I_3 = 8.1A$

SQ\* Determine the values of mesh current in

given circuit.

A Assume currents

in each mesh as

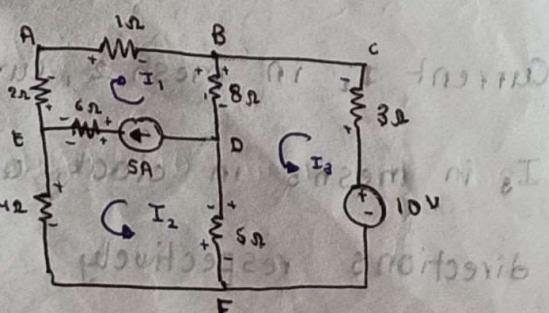

shown figure.

Apply KVL to super mesh A-B-D-F-E-A'

$$-I_1 - 8(I_1 + I_3) + 5(I_2 - I_3) + 4I_2 - 2I_1 = 0$$

$$-3I_1 - 11I_1 + 9I_2 - 13I_3 = 0$$

$$11I_1 - 9I_2 + 13I_3 = 0 \rightarrow ①$$

From common branch, with current source

$$I_1 + I_2 = 5 \text{ Amp} \rightarrow ②$$

Apply KVL to mesh-3 B-C-F-D-B

$$5I_3 + 8I_1 - 8(I_3 - I_2) + 8(I_3 + I_1) + 3I_3 - 10 = 0$$

$$8I_1 + 5I_2 + 16I_3 = 10 \rightarrow ③$$

By Cramers rule.

$$\begin{vmatrix} 11 & -9 & 13 \\ 1 & 1 & 0 \\ 8 & -5 & 16 \end{vmatrix} = \Delta = \frac{11(16-0) + 9(16-0) + 13(-5-8)}{265151}$$

$$\begin{vmatrix} 0 & -9 & 13 \\ 5 & 1 & 0 \\ 10 & -5 & 6 \end{vmatrix} = \Delta_1 = \frac{-9(30-0) + 13(-25-10)}{265} = 265$$

$$\begin{vmatrix} 11 & 0 & 13 \\ 1 & 5 & 0 \\ 8 & 10 & 6 \end{vmatrix} = \Delta_2 = \frac{11(30-0) + 13(10-40)}{490}$$

$$\begin{vmatrix} 11 & -9 & 0 \\ 1 & 1 & 5 \\ 8 & -5 & 10 \end{vmatrix} = \Delta_3 = \frac{11(10+25) + 9(10-40)}{150}$$


$$I_1 = \frac{\Delta_1}{\Delta} = \frac{265}{151} = 1.75 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{490}{151} = 3.24 \text{ A}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{1150}{151} = 7.6 \text{ A}$$
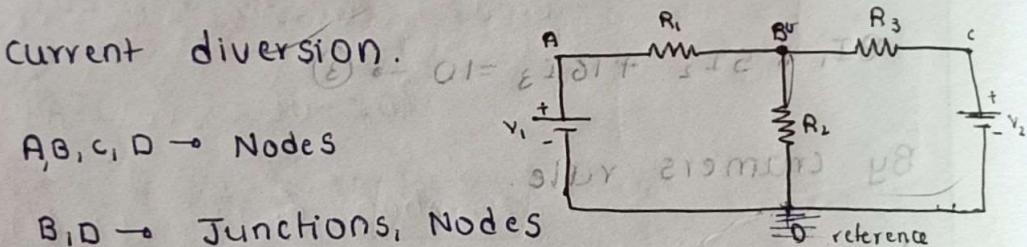
## \* Nodal Analysis:

- \* Node: Node is a common point which connects 2 or more elements {synonym - Junction}
- \* At every junction, current diversion takes place
- \* But at node, it is not compulsory to have a current diversion.




## \* Solving by nodal Analysis

- 1) First identify the nodes where current diversion takes place (i.e. Junctions) in the circuit.
- 2) No. of nodal equations = no. of main nodes.
- 3) Assume voltage at each node and write nodal equations
- 4) Solve the equations to find out the assumed voltage

Write the nodal equations and determine the node voltage values.

Here 1, 2, 3 are nodes

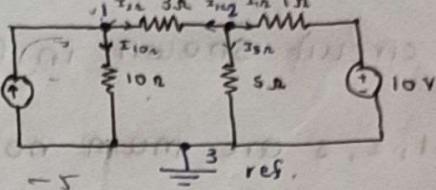

& 1, 2 are main nodes.

Assume the voltage at each node as  $V_1, V_2$

at 1 & 2 respectively

Apply KCL at node-1,

\* Take unknown currents as outgoing currents

\* Take currents (outgoing) as positive and incoming currents as negative.

$$S = I_{10\Omega} + I_{3\Omega}$$

$$S = \frac{V_1 - V_2}{3} + \frac{V_1 - 0}{10} \quad \left\{ \text{resistance b/w } V_1 \text{ & } V_2 \text{ is } 3\Omega \right\}$$

$$13V_1 - 10V_2 = 150 + 0$$

Apply KCL to node-2,

$$I_{3\Omega} + I_{5\Omega} + I_{1\Omega} = 0$$

$$\frac{V_2 - V_1}{3} + \frac{V_2 - 0}{5} + \frac{V_2 - 10}{1} = 0$$

$$5V_2 - 5V_1 + 3V_2 + 15V_2 - 150 = 0$$

$$-5V_1 + 23V_2 = 150 \rightarrow ②$$


By solving ① & ②, we get

$$V_1 = 19.87 \text{ V}$$

$$V_2 = 10.84$$

Q Determine the voltage at each node for the circuit shown in figure.

A 1, 2, 3 are main nodes.

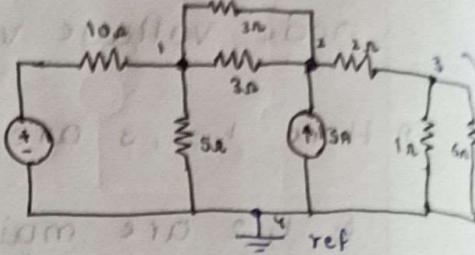


In the above circuit,  $3\Omega$  &  $3\Omega$

are in parallel, effective resistance =  $1.5\Omega$

Apply KCL to node-1
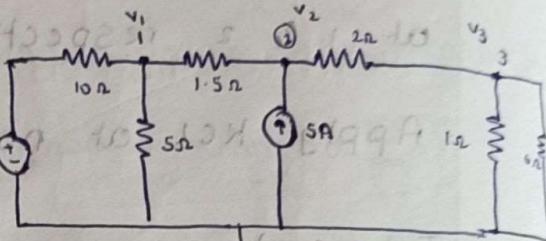
$$I_{10\Omega} + I_{1.5\Omega} + I_{5\Omega} = 0$$



$$\frac{V_1 - 10}{10} + \frac{V_1 - V_2}{1.5} + \frac{V_1}{5} = 0 \quad \left\{ \begin{array}{l} V \text{ at node-1} = V_1 \\ V \text{ at node-2} = V_2 \end{array} \right.$$

$$3V_1 - 30 + 20V_1 - 20V_2 + 6V_1 = 0 \quad \left\{ \begin{array}{l} V \text{ at node-3} = V_3 \\ V \text{ at node-2} = V_2 \end{array} \right.$$

$$29V_1 - 20V_2 = 30 \rightarrow ①$$

$$net I + out I = 0$$

Apply KCL to node-2

$$-5 + I_{2n} + I_{1.5} = 0$$

$$\frac{0 - V_2}{5} + \frac{2V_2 - V_1}{1.5} = 0$$

$$5 = I_{1.5\Omega} + I_{2\Omega}$$

$$0 + 0.2I = 5V_1 - 1.5V_2$$

$$5 = \frac{V_2 - V_1}{1.5} + \frac{V_2 - V_3}{2}$$

$$0 = 5I + 2I + 1.5I$$

$$30 = 4V_2 - 4V_1 + 3V_2 - 3V_3 \quad 0 = 0.2I + \frac{1V - 5V}{1.5}$$

$$-4V_1 + 7V_2 - 3V_3 = 30 \rightarrow ②$$


Apply KCL to node-3

$$I_{2\Omega} + I_{1\Omega} + I_{6\Omega} = 0$$


$$[V_{18-12} = 12] \text{ top sw, } ③ \text{ } ① \text{ enivole 18}$$

$$\frac{V_3 - V_2}{2} + \frac{V_3}{1} + \frac{V_3}{6} = 0$$

de for the

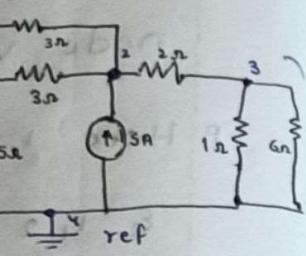

$$= 1.5 \Omega$$

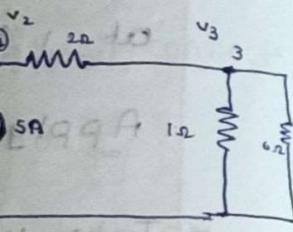

$$V_1$$

$$V_2$$

$$-3, V_3$$

$$I = 2$$

$$= 2$$

$$-1.5V_1$$

$$1.5V_2$$

$$1.5V_3$$

$$V_2$$

$$V_3$$

$$V_2$$

$$V_3$$

$$V_2$$

$$3V_3 - 3V_2 + 6V_3 + V_3 = 0$$

$$-3V_2 + 10V_3 = 0$$

$$= 3V_2 - 10V_3 = 0 \rightarrow ③$$

By cramer's method.

$$\begin{vmatrix} 29 & -20 & 0 \\ -4 & 7 & -3 \\ 0 & 3 & -10 \end{vmatrix} = \Delta = 29(-70+9) + 20(40) - 969$$

$$\begin{vmatrix} 30 & -20 & 0 \\ 30 & 7 & -3 \\ 0 & 3 & -10 \end{vmatrix} = \Delta_1 = 30(-70+9) + 20(-300) - 7769$$

$$\begin{vmatrix} 29 & 30 & 0 \\ -4 & 30 & -3 \\ 0 & 0 & -10 \end{vmatrix} = \Delta_2 = 29(-300) - 30(40) - 9900$$

$$\begin{vmatrix} 29 & -20 & 30 \\ -4 & 7 & 30 \\ 0 & 3 & 0 \end{vmatrix} = \Delta_3 = 29(-90) + 20 + 30(-12) - 2970$$

$$V_1 I_A = \frac{\Delta_1}{\Delta} = \frac{-7769}{-969} = 8.01 A$$


$$V_2 I_B = \frac{\Delta_2}{\Delta} = \frac{-9900}{-969} = 10.2 A$$

$$V_3 I_B = \frac{\Delta_3}{\Delta} = \frac{-2970}{-969} = 3.01 A$$

Q Use the nodal analysis to find power dissipated

in 6Ω resistor for the circuit shown in figure.

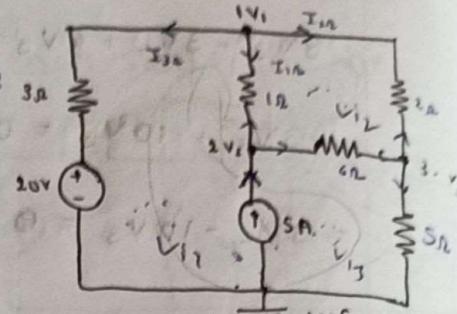A In circuit 3 main nodes are present. voltage in them is  $V_1, V_2 \& V_3$



Apply KCL to node-1

$$I_{32} + I_{21} + I_{12} = 0 \quad (P.P)$$

$$\frac{V_1 - 20}{3} + \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{1} = 0$$

$$(00E - )O\Delta + (P + O\Gamma - )O\Delta$$

$$2V_1 - 40 + 3V_1 - 3V_3 + 6V_1 - 6V_2 = 0 \quad (P\Gamma\Gamma - )$$

$$11V_1 - 6V_2 - 3V_3 = 40 \rightarrow ①$$

$$(0P)OE - (00E)PE = 4 \quad (OOPP - )$$

Apply KCL to node-2:

$$-5 + \frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{2} = 0$$

$$(5\Gamma - )O\Delta + (0P - )P\Delta = 4 \quad (O\Delta = )$$

$$-30 + 6V_2 - 6V_1 + V_2 - V_3 = 0$$

$$-6V_1 + 7V_2 - V_3 = 30 \rightarrow ②$$

$$\frac{P\Gamma\Gamma - }{P\Delta P - } = \frac{1\Delta}{\Delta} = 30V$$

Apply KCL to node-3:

$$A\Delta O\Gamma = \frac{OOPP - }{P\Delta P - } = \frac{1\Delta}{\Delta} = 30V$$

$$I_{21} + I_{32} + I_{62} = 0$$

$$\frac{V_3 - V_1}{2} + \frac{V_3}{5} + \frac{V_3 - V_2}{3} = 0$$

$$\frac{15V_3 - 15V_1 + 6V_3 + 5V_3 - 5V_2}{30} = 0$$

$$-15V_1 - 5V_2 + 26V_3 = 0 \rightarrow ③$$

$$15V_1 + 5V_2 - 26V_3 = 0$$


$$i_1 = 2.31$$

$$i_2 = 0.64$$

$$i_3 = 2.68$$

$$i_{62} = i_3 - i_2 = 2.64$$
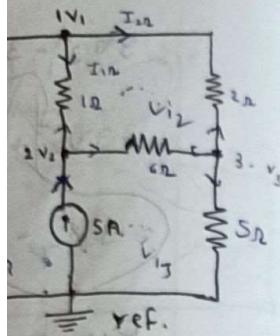
$$P = i^2 R = (2.64)^2 \times 4 \Omega = 41.3$$



By cramer's rule

$$\Delta = \begin{vmatrix} 11 & -6 & -3 \\ -6 & 7 & -1 \\ -15 & -5 & 26 \end{vmatrix} = 516$$

$$11(182-5) + 6(-156-15) - 3(30+105)$$

$$\Delta_1 = \begin{vmatrix} 40 & -6 & -3 \\ 30 & 7 & -1 \\ 0 & -5 & 26 \end{vmatrix} = 40(182-5) + 6(780) - 3(-150)$$

$$\Delta_2 = \begin{vmatrix} 11 & 40 & -3 \\ -6 & 30 & -1 \\ -15 & 0 & 26 \end{vmatrix} = 11(780) - 40(-156-15) + 3(+450)$$

$$\Delta_3 = \begin{vmatrix} 11 & -6 & 40 \\ -6 & 7 & 30 \\ -15 & -5 & 6 \end{vmatrix} =$$

$$V_1 = \frac{\Delta_1}{\Delta} = \boxed{23.6V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \boxed{27.2V}$$

$$V_3 = \frac{\Delta_3}{\Delta} = \boxed{18.8V}$$

$$I_{6\Omega} = \frac{V_2 - V_3}{6} = \frac{27.2V - 18.8V}{6} = 1.4A$$


$$P_{6\Omega} = I_{6\Omega}^2 R = (1.4)^2 \times 6 = \boxed{11.76 \text{ watts}}$$

Use the nodal analysis and determine voltages at given circuit.

A  $V_1, V_2, V_3$  are main nodes

with voltages  $V_1, V_2, V_3$

respectively.

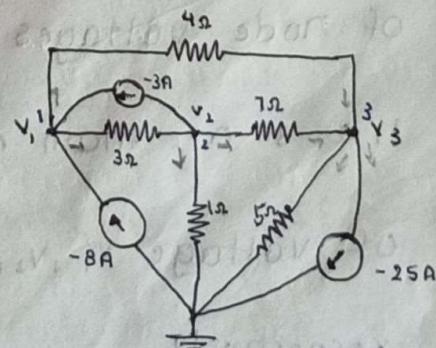

Apply KCL to node '1'.

$$-8 - 3 = I_{4n} + I_{3n}$$

$$-8 - 3 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{3}$$

$$7V_1 - 4V_2 - 3V_3 = -132 \rightarrow ①$$

Apply KCL to node-2.

$$-3 + \frac{V_2}{1} + \frac{V_2 - V_3}{7} + \frac{V_2 - V_1}{3} = 0$$

$$-7V_1 + 31V_2 - 3V_3 = 63 \rightarrow ②$$

Apply KCL to node-3.

$$I_{4n} + I_{5n} + I_{7n}$$

$$\boxed{V_{S \cdot ES}} = \frac{\Delta}{\Delta_0} = 1V$$

$$-25 + \frac{V_3 - V_1}{4} + \frac{V_3}{5} + \frac{V_3 - V_2}{7} = 0 \quad ③$$

$$-35V_1 - 20V_2 + 83V_3 = 3500 \rightarrow ④$$

By solving we get


$$V_1 = \frac{\Delta_1}{\Delta_0} = -34.5V, V_2 = \frac{\Delta_2}{\Delta} = -18.12V, V_3 = \frac{\Delta_3}{\Delta} = -145.6V$$

Q Use the nodal analysis to determine the values of node voltages in given circuit.

A 1, 2, 3 are main nodes

of voltage  $V_1, V_2, V_3$

respectively.

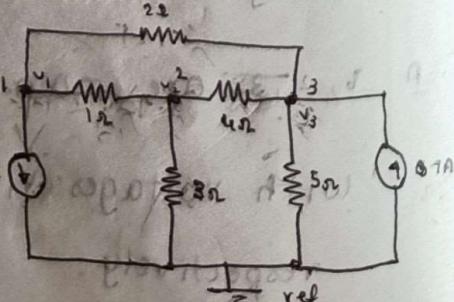

a) Apply KCL to node - 4

$$I_{2n} + I_{1n} + 3 = 0$$

$$3 + \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{1} = 0$$

$$+3V_1 - 2V_2 - V_3 = -6 \rightarrow ①$$

Apply KCL to node - 2

$$I_{1n} + I_{4n} + I_{3n} = 0$$

$$\frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{4} + \frac{V_2}{3} = 0$$

$$12V_2 - 12V_1 + 3V_2 - 3V_3 + 4V_2 = 0$$

$$-12V_1 - 3V_3 + 19V_2 = 0$$

$$-12V_1 + 19V_2 - 3V_3 = 0 \rightarrow ②$$

Apply KCL to node - 3

$$I_{4n} + I_{5n} + I_{2n} - 7 = 0$$

$$\frac{V_3 - V_2}{4} + \frac{V_3}{5} + \frac{V_3 - V_1}{2} = 7$$

$$5V_3 - 5V_2 + 4V_3 + 10V_3 - 10V_1 = 140$$

$$-10V_1 - 5V_2 + 19V_3 = 140 \rightarrow ③$$

By solving we get


$$V_1 = 5.2V$$

$$V_2 = 5.1V$$

$$V_3 = 11.4V$$

\* Super Node: In a given circuit, If a common voltage source is present in between 2 or more

nodes, then it is a super node.

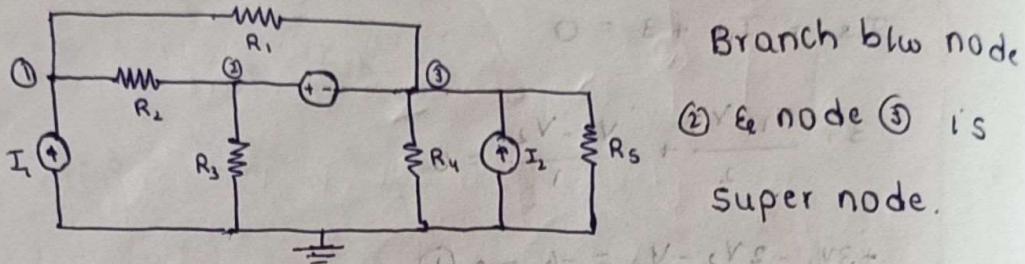

Branch b/w node 1 & 3


(2) Node 3 is super node.

Q Determine the values of node voltages in the given circuit by nodal analysis.

A 1, 2, 3 are main nodes

of voltages  $v_1, v_2$  &  $v_3$

respectively.

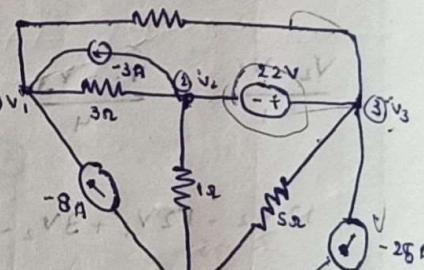

Apply KCL to node 1:

$$0 = 1V - v_1 + 8A - 3A + I_{3,0} + I_{4,0} = 0$$

$$8 + 3 + \frac{v_1 - v_2}{3} + \frac{v_1 - v_3}{4} = 0$$

$$7v_1 - 4v_2 - 3v_3 = -132 \rightarrow ①$$

$$I = \frac{1V - 6V}{3} + \frac{8V}{8} + \frac{5V - 8V}{5}$$

Apply KCL to super node (1-node<sub>2</sub> and node<sub>3</sub>)

$$\text{node-2: } -3 + \frac{v_2}{1} + \frac{v_2 - v_1 + 8V}{3} + (\text{node-3})(-25) + \frac{v_3}{5} + \frac{v_3 - v_1}{4} = 0$$

$$\rightarrow -35v_1 + 80v_2 + 27v_3 = 1680 \rightarrow ②$$

From common voltage source b/w 2 & 3

$$v_3 - v_2 = 22V \rightarrow ③$$

By solving equations, we get

$$v_1 = 1.07V$$

$$v_2 = 10.5V$$

$$v_3 = 32.5V$$


In exam, we should solve by Cramers rule only...

Compute the Voltages in given circuit by using nodal analysis.

1, 2, 3 are main

nodes with voltages

$V_1$  &  $V_2$  respectively

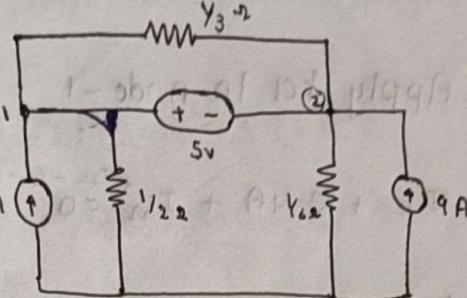

Apply KCL to supernode (i.e. node-1 & node-2)

$$-4 + \frac{V_1 - V_2}{1/V_3} + \frac{V_1}{1/V_2} + \frac{V_2}{1/V_6} + \frac{V_2 - V_1}{1/V_3} - 9 = 0$$

$$2V_1 + 6V_2 = 13 \rightarrow ①$$

$$V_1 - V_2 = 5 \rightarrow ②$$

By solving ① & ②, we get

$$V_1 = 5.37V$$

$$V_2 = 0.37V$$


Q) Determine the node voltages in the given circuit.

A) In above circuit, convert

8V source in current


source,  $I_1 = V_1 = 8A$ .

And also convert the

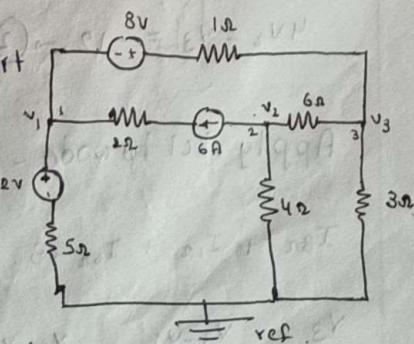

2V source to current source,  $I_2 = 2/5 = 0.4A$

A Now Redraw the circuit.

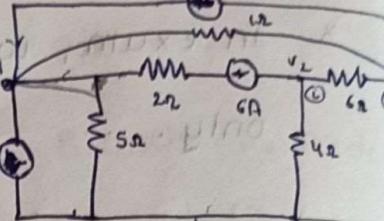

1, 2, 3 are main nodes with voltages  $V_1, V_2, V_3$  respectively.

Apply KCL to node -1

$$I_{12} + 0.4A + I_{5\Omega} = 0$$

$$\frac{V_1 - V_3}{1} + 0.4A + \frac{V_1}{5} = 0 + \frac{V_1 - V_2}{2\Omega} - 6 = 0$$

$$\frac{V_1 - V_3}{1} + 0.4A + \frac{V_1}{5} - 6 = 0$$

$$5V_1 - 5V_3 + V_1 = (6 - 0.4)5$$

$$6V_1 - 5V_3 = \frac{5}{6} \rightarrow ①$$

Apply KCL to node -2

$$6 + I_{6\Omega} + I_{4\Omega} = 0$$

$$6 + \frac{V_2 - V_3}{6} + \frac{V_2}{4} = 0$$

$$\frac{12 + V_2 - V_3 + 3V_2}{12} = 0$$

$$4V_2 - V_3 = -12 \rightarrow ②$$

Apply KCL to node -3

$$I_{5\Omega} + I_{2\Omega} + I_{4\Omega} = 0$$

$$\frac{V_3}{8} + \frac{V_3 - V_1}{1} + \frac{V_3 - V_2}{2} = 0$$

$$\frac{3V_3 + 24V_3 - 24V_1 + 4V_3 - 4V_2}{24} = 8$$

$$\rightarrow -24V_1 - 4V_2 + 31V_3 = 8 \rightarrow ③$$

By solving equations

$$\begin{vmatrix} 6 & 0 & -5 \\ 0 & 4 & -1 \\ -24 & -4 & 31 \end{vmatrix} \Delta = \frac{6(124-4) - 5(+96)}{-4 \times 24} = \frac{240}{240}$$

$$\begin{vmatrix} 68 & 0 & -5 \\ -12 & 4 & -1 \\ -8 & -4 & 31 \end{vmatrix} \Delta_1 = \frac{68(-12) - 5(-32)}{120} = \frac{832}{120} = +7760$$

$$\begin{vmatrix} 6 & 68 & -5 \\ 0 & -12 & -1 \\ -24 & -8 & 31 \end{vmatrix} \Delta_2 = \frac{6(-18) - 68(-24)}{120} = \frac{1584}{120} = 68(-24) - 5(-288) = 792$$

$$\begin{vmatrix} 6 & 0 & 68 \\ 0 & 4 & -12 \\ -24 & -4 & -8 \end{vmatrix} \Delta_3 = \frac{6(-82) + 68(48)}{6 \times 36} = \frac{6(-32 - 48) + 68(96)}{6 \times 36} = \frac{6048}{6 \times 36}$$

$$I \cdot V_1 = \frac{7760}{240} = 32.3V$$

$$V_2 = \frac{792}{240} = 3.3V$$

$$V_3 = \frac{6048}{240} = 25.2V$$

