

# 1. D.C CIRCUITS

basic concepts :-

\* Electric circuit :-

→ An 'Electric circuit' is an interconnection of 'electrical elements'.

\* charge :-

→ 'charge' is an electrical property of the atomic particles of which matter consists, measured in 'coulombs' (C).

\* Electric current :-

→ It is the time rate of change of charge.

→ measured in Amperes (A).


$$1 \text{ ampere} = 1 \text{ coulomb/second}$$

$$i = \frac{dq}{dt}$$

Direct current :-


→ D.C is a current that remains 'constant' with time.

→ Here frequency is 'zero'

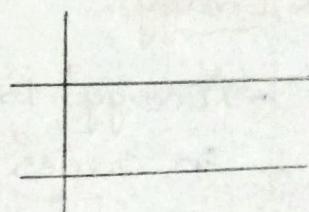

Alternating current :-

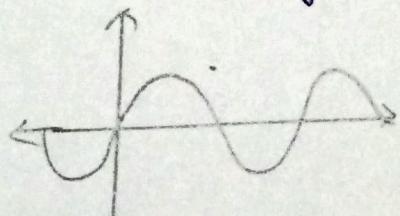→ A.C is a current that varies sinusoidally with 'time'.



### \* Voltage :-

- 'voltage' or 'potential difference' is the energy required to move a unit charge through an element.
- Measured in 'volt' (V).

$$V = \frac{dw}{dq}$$

$$1 \text{ volt} = 1 \text{ Joule/coulomb.}$$

### \* Power :-

- It is the time rate of expending or absorbing energy.
- Measured in 'watts' (W).

$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = VI$$

$$\Rightarrow P = \frac{dw}{dt}$$

$$\Rightarrow w = \int P dt = \int VI t$$

### \* Energy :-

- 'Energy' is the capacity to do work, measured in 'Joules' (J).

$$1 \text{ Wh} = 3,600 \text{ J.}$$

## \* Circuit Elements:

→ There are two types of Elements.

① Passive Elements → Requires/Takes Energy  $\rightarrow$  C, R

② Active Elements → Gives Energy  $\rightarrow$  L

Ex: 'Generator', 'Battery' [polarities].

### ① Passive Elements :-

#### i) Resistor (R) :-

→ Units 'Ω' ohms

→ opposes the flow of current

→ Made by 'carbon'.

$$\rightarrow V \propto I \Rightarrow V = IR$$

→ Resistance, ' $R \propto l$ ' & ' $R \propto \frac{1}{A}$ '

$$\Rightarrow R = \frac{\rho l}{A}$$

$$\Rightarrow \rho = \frac{RA}{l} \quad \Omega\text{-m}$$

$$\Rightarrow \rho = \frac{1}{G} \Rightarrow G = \frac{1}{\rho}$$


→ Resistivity depends on 'type of material'.

→ Resistance depends on 'material' & 'dimensions'

$$\rightarrow R = \frac{1}{G} \quad 'G' \text{ is 'conductance'}$$


'R' is 'Resistance'.

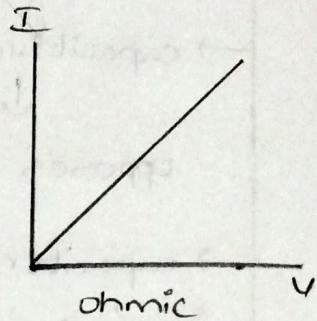
→ 'current' & 'voltage' are in same phase in Resistor.



ii) capacitor :- (C)

→ unit is 'Faraday'.

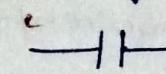→ symbol is  (or) 'F'

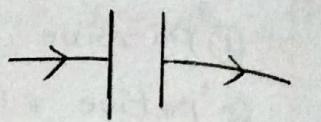

→ 'capacitor' is 'device'

current passing  
through capacitor

'capacitance' is property.

$$\rightarrow Q = CV, \quad C = \frac{\epsilon_0 A}{d} \rightarrow \text{parallel plate}$$

→ capacitive Reactance ( $X_C$ ) → units 'omega' ( $\omega$ )  
 ↓

opposes the flow of current


→ capacitor blocks 'D.C current' & allows 'A.C' [because A.C has frequency].

→ D.C acts as 'open circuit' [ $\because f=0, X_C = \frac{1}{\omega} = \infty$ ]


→ I leads v by '90°'

$$X_C = \frac{1}{2\pi f C}$$

iii) Inductor :-

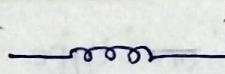→ symbol 

→ current passing through Inductor

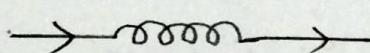

→ Inductive Reactance / Reluctance ( $X_L$ )

$$X_L = 2\pi f L$$


→ Inductor allows 'D.C' [ $\because X_L = 2\pi(0)L = 0$ ] &  
it allows some 'A.C' & resists some 'A.C'

→ I 'lags' v by '90°'

→ current is lagging.

## \* Resistor :-

Series :- [End to End]

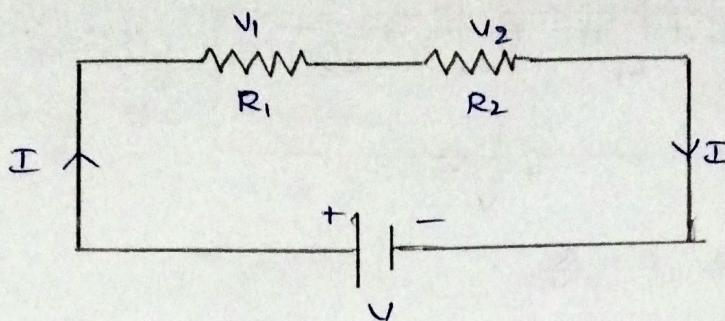

i - same  
v - dividing.

$$IR_1 + IR_2 = V \rightarrow ①$$

$$\text{we know, } v = IR' \rightarrow ②$$

$$\Rightarrow IR_1 + IR_2 = IR. \quad [\text{from } ① \text{ & } ②]$$


$$\Rightarrow I(R_1 + R_2) = IR$$

$$\therefore \boxed{R_{\text{eq}} = R_1 + R_2}$$

→ In series, current is 'same' & voltage varies.

→ 'Req' is higher than others [ $R_1, R_2$ ].

## Parallel :-

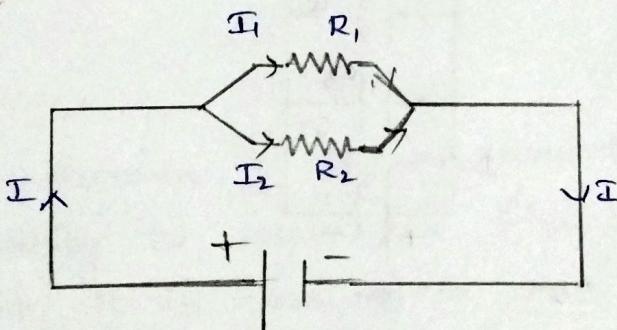

v - same  
i - dividing

$$I = I_1 + I_2$$


$$\Rightarrow \frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} \quad [\because I = \frac{V}{R}]$$

$$\Rightarrow \boxed{\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}}$$

→ 'Req' is less than any other resistances.

## \* capacitor :-

series :-

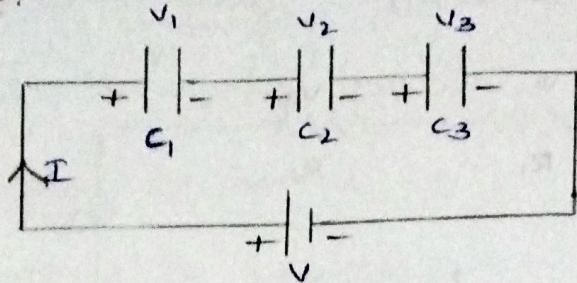

$$\text{we know, } C = \frac{Q}{V} .$$

$$\Rightarrow V_1 = \frac{Q}{C_1}, \quad V_2 = \frac{Q}{C_2}, \quad V_3 = \frac{Q}{C_3}.$$


$$\Rightarrow V = V_1 + V_2 + V_3$$

$$\Rightarrow V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} = Q \left[ \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right]$$

$$\Rightarrow \frac{V}{Q} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\Rightarrow \boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

Parallel :-

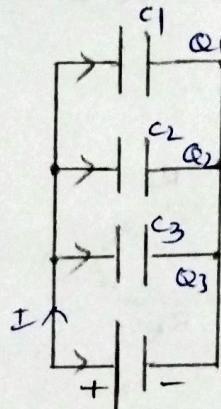

$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

$$\therefore Q = Q_1 + Q_2 + Q_3.$$

$$Q_3 = C_3 V$$

$$\Rightarrow Q = C_1 V + C_2 V + C_3 V$$

$$\Rightarrow Q = V [C_1 + C_2 + C_3]$$

$$\Rightarrow \frac{Q}{V} = C_1 + C_2 + C_3$$

$$\therefore \boxed{C_{eq} = C_1 + C_2 + C_3}$$

## BASIC LAWS

### \* Ohm's Law :-

→ It states that the 'voltage' across a resistor is directly proportional to the 'current' flowing through the resistor.

$$V \propto I$$

$$\Rightarrow V = IR$$

Here, ' $R$ ' is constant

(Or)

$$I \propto V$$

$$\Rightarrow I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

### \* Note :-

#### short circuit :-

→ A short circuit is a circuit element with 'resistance' approaching 'zero'.

#### open circuit :-

→ An open circuit is a circuit element with 'resistance' approaching 'infinity'.

#### Resistance :-

→ The Resistance ' $R$ ' of an element denotes its ability to resist the flow of electric current, it is measured in 'ohms' ( $\Omega$ ).

#### conductance :-

→ 'conductance' is the ability of an element to conduct electric current.

→ It is measured in 'mhos' ( $S$ ) or 'siemens' ( $S$ ).

## \* Nodes, Branches and Loops :-

### Branch :-

→ A Branch represents a 'single element' such as 'voltage source' or a 'resistor.'

### Node :-

→ A Node is the point of connection between 'two' or 'more branches.'

### Loop :-

→ A loop is any 'closed' path in a circuit.

## \* Kirchhoff's Laws :-

### ① Kirchhoff's current Law [KCL] :-

→ It states that 'the algebraic sum of currents entering a node (or a closed boundary) is zero.'

$$\sum_{n=1}^N i_n = 0$$

where, 'N' is no. of 'branches.'


→ It is based on 'Law of conservation of Energy'

→ It is also called as 'current Law', 'Junction Law' and 'point Law'.

→ The sum of 'the currents entering a node' is equal to the sum of 'the currents leaving the node'.

$$\Rightarrow i_1 - i_2 + i_3 - i_4 - i_5 + i_6 = 0$$
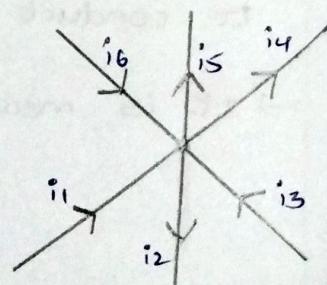
$$\Rightarrow i_1 + i_3 + i_6 = i_2 + i_4 + i_5$$




## Kirchhoff's Voltage Law [KCL]:-


→ It states that "the algebraic sum of all voltages around a closed path (or loop) is zero."


$$\boxed{\sum_{m=1}^M V_m = 0}$$

where 'M' is the 'no. of voltages' in the loop.


Rules:-

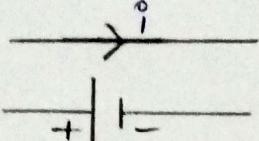①  = '-ve'

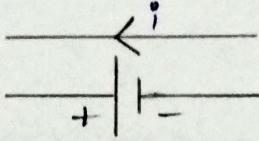②  = '+ve'

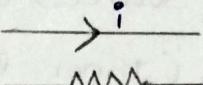③ For all resistors,  = '-ve' = '-iR'

Example :-

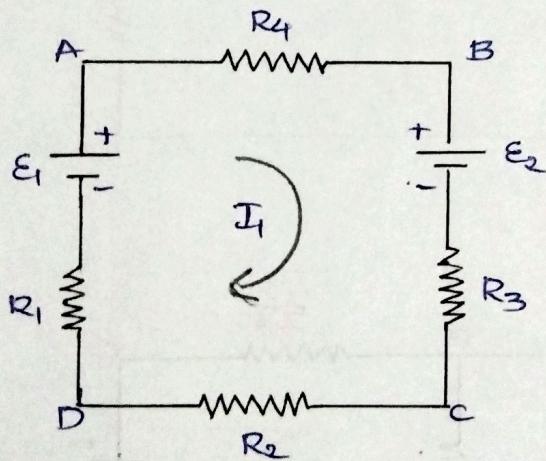

$$\boxed{\sum \mathcal{E} + \sum IR = 0.}$$

ABCDA,

$$\Rightarrow -I_1 R_4 - E_2 - I_1 R_3 - I_1 R_2 - I_1 R_1 + E_1 = 0.$$

## \* Types [in KVL] :-


### 1) Type-1 :- [General model]

→ Having only voltage sources and Resistors [E, R].

### 2) Type-2 :-

→ Having voltage sources, Resistors & current sources [outer loops].


Ex:-

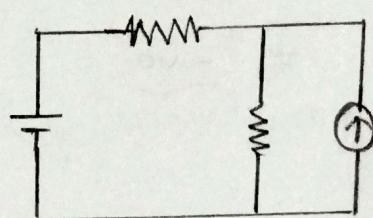


### 3) Type-3 :- [Super mesh model]

→ Having voltage sources (E), Resistors (R) and current sources (inner loops).

Ex:-

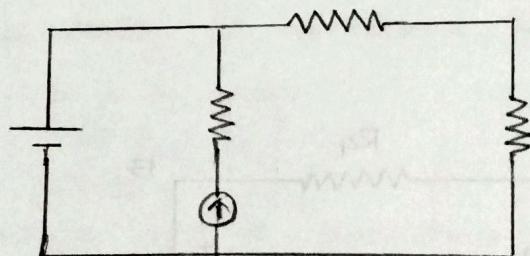

### 1) Type-1 :-

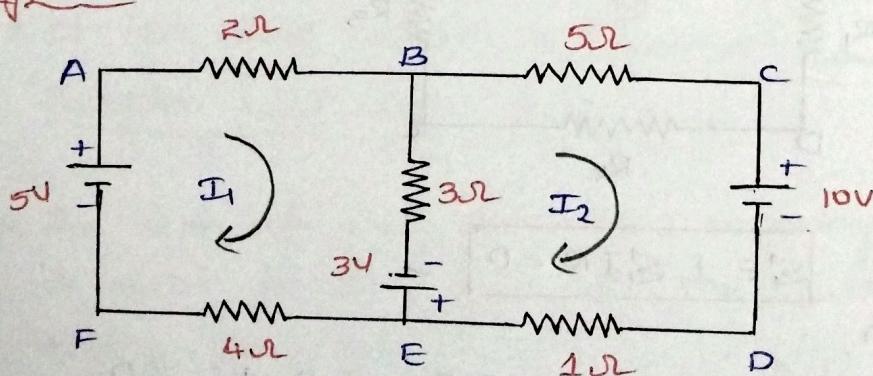

Find :-

- The current passing through 5Ω resistor.
- The voltage across 3Ω resistor.

A) Applying KVL for ABEFA loop,

$$\Rightarrow -2I_1 - 3(I_1 - I_2) + 3 - 4I_1 + 5 = 0$$

$$\Rightarrow -2I_1 - 3I_1 + 3I_2 + 3 - 4I_1 + 5 = 0$$

$$\Rightarrow -9I_1 + 3I_2 + 8 = 0$$

$$\Rightarrow -9I_1 + 3I_2 = -8 \longrightarrow \textcircled{1}$$

Applying KVL for BCDEB loop,

$$\Rightarrow -5I_2 - 10 - I_2 - 3 - 3(I_2 - I_1) = 0$$

$$\Rightarrow -5I_2 - I_2 - 13 - 3I_2 + 3I_1 = 0$$

$$\Rightarrow -9I_2 + 3I_1 - 13 = 0$$

$$\Rightarrow 3I_1 - 9I_2 = 13 \longrightarrow \textcircled{2}$$

From \textcircled{1} & \textcircled{2}

$$\Rightarrow -9I_1 + 3I_2 = -8$$

$$3I_1 - 9I_2 = 13$$

$$\therefore I_1 = \frac{11}{24} = \underline{0.46} \text{ amperes.}$$

$$\therefore I_2 = \frac{-31}{24} = \underline{-1.29} \text{ amperes.}$$

(a)  $I_{5\Omega} = I_2 = \underline{-1.29 \text{ A}}$

$$V_{5\Omega} = 1.29 \times 5 = \underline{6.45 \text{ V}} \quad [\because V = IR]$$


(b)  $I_{3\Omega} = I_1 - I_2$

$$= 0.46 - (-1.29)$$

$$= \underline{1.7 \text{ A}}$$

$$\therefore V_{3\Omega} = 1.7 \times 3 = \underline{5.1 \text{ V}} \quad [\because V = IR]$$

\* Type-1:-

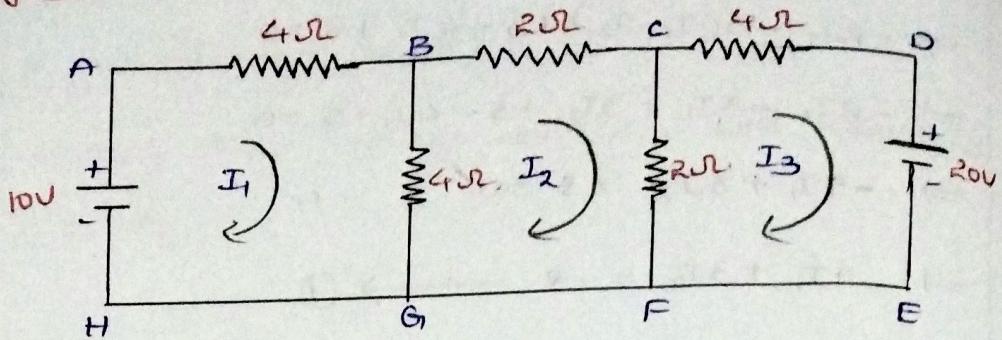

Find the current passing through  $2\Omega$  (CF) resistor

A) Applying KVL for 'ABGHA' loop

$$\Rightarrow -4I_1 - 4(I_1 - I_2) + 10 = 0$$

$$\Rightarrow -4I_1 - 4I_1 + 4I_2 = -10$$

$$\Rightarrow -8I_1 + 4I_2 = -10 \rightarrow ①$$

Applying KVL for 'BCFGIB' loop.

$$\Rightarrow -2I_2 - 2(I_2 - I_3) - 4(I_2 - I_1) = 0$$

$$\Rightarrow -8I_2 + 2I_3 - 4I_1 = 0$$

$$\Rightarrow -4I_1 + -8I_2 + 2I_3 = 0 \rightarrow ②$$

Applying KVL for 'CDEFEC' loop.

$$\Rightarrow -4I_3 - 20 - 2(I_3 - I_2) = 0$$

$$\Rightarrow -6I_3 + 2I_2 = 20$$

$$\Rightarrow 2I_2 - 6I_3 = 20 \rightarrow ③$$

$$\therefore I_1 = \frac{35}{32} = \underline{\underline{1.093 \text{ A}}}$$

$$I_2 = \frac{-5}{16} = \underline{\underline{-0.312 \text{ A}}}$$


$$I_3 = \frac{-55}{16} = \underline{\underline{-3.437 \text{ A}}}$$

$$\therefore I_{R,2} (\text{CF}) = I_3 - I_2$$

$$= -3.437 + 0.312$$

$$= \underline{\underline{-3.125 \text{ A}}}$$

2) Type - 2 :-

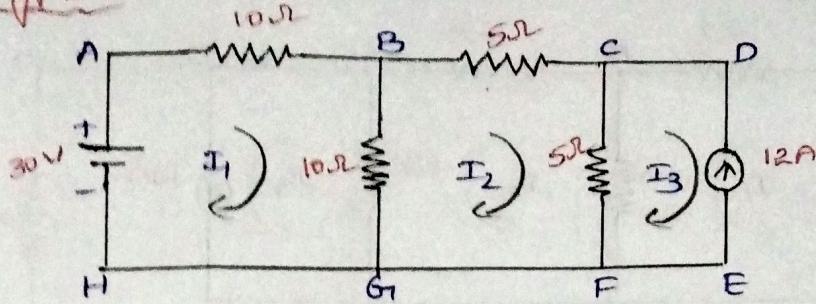

Find current passing through BC [5Ω resistor] and CF?

A) Applying 'KVL' for 'ABGHA' loop.

$$\Rightarrow -10I_1 - 10(I_1 - I_2) + 30 = 0$$

$$\Rightarrow -20I_1 + 10I_2 = -30 \rightarrow ①$$

Applying 'KVL' for 'BCFGIB' loop.

$$\Rightarrow -5I_2 - 5(I_2 - I_3) - 10(I_2 - I_1) = 0$$

$$\Rightarrow -10I_2 + 5I_3 - 10I_2 + 10I_1 = 0$$

$$\Rightarrow 10I_1 - 20I_2 + 5I_3 = 0 \rightarrow ②$$

Applying 'KVL' for 'CDEFc' loop.

$$\Rightarrow I_3 = -12 \quad [\because \text{opp direction}] \rightarrow ③$$

$$\therefore I_1 = 0 \text{ A}$$


$$I_2 = -3 \text{ A}$$

$$I_3 = -12 \text{ A}$$

$$\therefore I_{5\Omega} (\text{BC}) = I_2 \times \underline{\underline{I_3}}$$
$$= \underline{\underline{-3}} \text{ A}$$

$$\therefore I_{5\Omega} (\text{CF}) = I_2 - I_3$$
$$= -3 - (-12)$$
$$= \underline{\underline{9}} \text{ A}$$

\* Type R :-

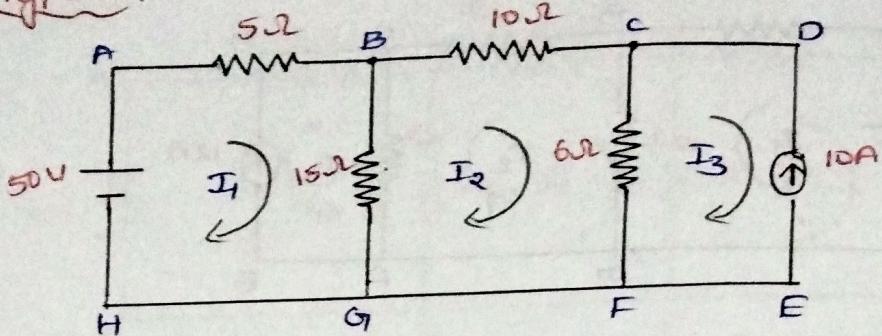

A) Applying 'KVL' to ABGHA loop.

$$\Rightarrow -5I_1 - 15(I_1 - I_2) + 50 = 0$$

$$\Rightarrow -20I_1 + 15I_2 = -50 \rightarrow ①$$

Applying 'KVL' to BCFCB loop.

$$\Rightarrow -10I_2 - 6(I_2 - I_3) - 15(I_2 - I_1) = 0$$

$$\Rightarrow -10I_2 - 6I_2 + 6I_3 - 15I_2 + 15I_1 = 0$$

$$\Rightarrow 15I_1 - 31I_2 + 6I_3 = 0 \rightarrow ②$$

Applying 'KVL' to CDEFDC loop.

$$\Rightarrow I_3 = -10 \rightarrow ③$$

$$\therefore I_1 = \underline{1.64 \text{ A}}$$

$$I_2 = \underline{1.13 \text{ A}}$$

$$\therefore I_{5\Omega} = I_1 = \underline{1.64 \text{ A}}$$


$$I_{15\Omega} = I_1 - I_2 = 1.64 + 1.13 = \underline{2.77 \text{ A}}$$

$$I_{10\Omega} = I_2 = \underline{1.13 \text{ A}}$$

$$\therefore V_{5\Omega} = 1.64 \times 5 = \underline{8.2 \text{ V}}$$

$$V_{10\Omega} = -1.13 \times 10 = \underline{-13 \text{ V}}$$

Type-3:-

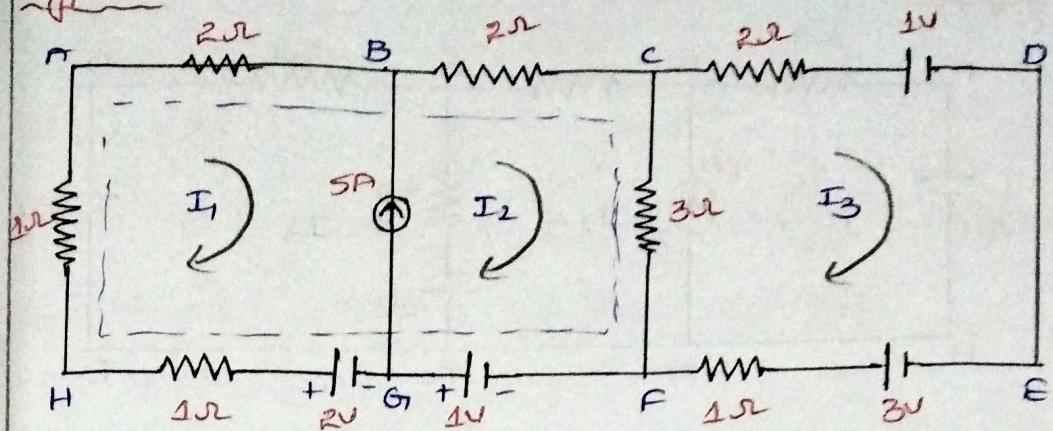

$$A) \quad I_2 - I_1 = 5$$

$$\Rightarrow -I_1 + I_2 + (0)I_3 = 5 \longrightarrow \textcircled{1}$$

Applying 'KVL' to supermesh ABCFGHIA

$$\Rightarrow -2I_1 - 2I_2 - 3(I_2 - I_3) + 1 + 2 - I_1 - I_1 = 0$$

$$\Rightarrow -4I_1 - 5I_2 + 3I_3 = -3 \longrightarrow \textcircled{2}$$

Applying 'KVL' to CDEF loop.

$$\Rightarrow -2I_3 - 1 + 3 - I_3 - 3(I_3 - I_2) = 0$$

$$\Rightarrow 3I_2 - 6I_3 = -2 \longrightarrow \textcircled{3}$$

From (1), (2) & (3)

$$\Rightarrow -I_1 + I_2 + (0)I_3 = 5$$

$$-4I_1 - 5I_2 + 3I_3 = -3$$


$$(0)I_2 + 3I_2 - 6I_3 = -2.$$

$$\therefore I_1 = \underline{-1.8 \text{ A}}$$

$$I_2 = \underline{3.2 \text{ A}}$$

$$I_3 = \underline{1.9 \text{ A}}$$

\* Type - 3 :-

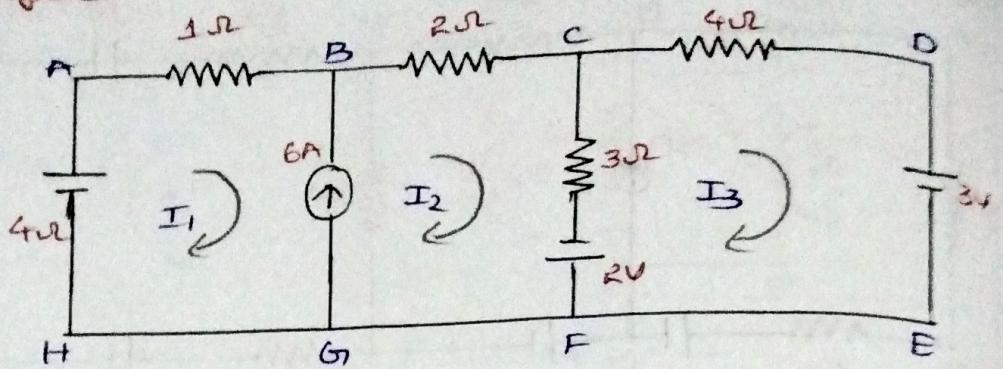

Find  $I_{2,02} = ?$

A)  $I_2 - I_1 = 6$

$$= 1 - I_1 + I_2 + (0) I_3 = 6 \rightarrow ①$$

Applying 'KVL' to supermesh ABCFGH

$$= 1 - I_1 - 2I_2 - 3(I_2 - I_3) + 2 + 4 = 0$$

$$= 1 - I_1 - 5I_2 + 3I_3 = -6 \rightarrow ②$$

Applying 'KVL' to CDEF.

$$= 1 - 4I_3 - 3 - 2 - 3(I_3 - I_2) = 0$$

$$= -4I_3 - 3I_3 + 3I_2 = 5$$

$$\Rightarrow +3I_2 - 7I_3 = 5 \rightarrow ③$$

$$\therefore I_1 = \underline{-3.90 \text{ A}}$$

$$\underline{I_2 = 2.09 \text{ A}}$$

$$\underline{I_3 = 0.18 \text{ A}}$$


$$\therefore I_{2,02} = I_2 = \underline{2.09 \text{ A}}$$

## KCL Loops

\* Steps:

- ① Identify the 'super junction'.
- ② All the currents are 'leaving' at the junction.
- ③ Assume junctions are 'high potential'.

\* Example:

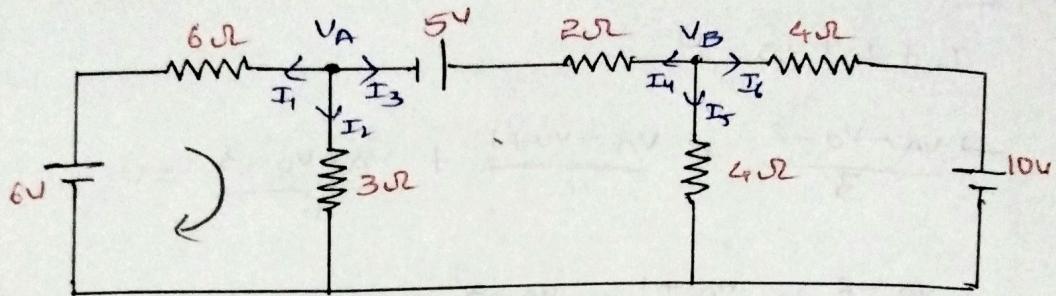

Reference junction  $V_0 = 0 \text{ V}$ .

$V_A$  &  $V_B$  are super junctions.

At Junction - A:

$$I_1 + I_2 + I_3 = 0$$

$$\Rightarrow \frac{V_A - V_0 - 6}{6} + \frac{V_A - V_0}{3} + \frac{V_A - V_B + 5}{2} = 0$$

$$\Rightarrow \frac{V_A - 6}{6} + \frac{V_A}{3} + \frac{V_A - V_B + 5}{2} = 0 \quad [ \because V_0 = 0 ]$$

$$\Rightarrow \frac{V_A - 6 + 2V_A + 3V_A - 3V_B + 15}{6} = 0$$

$$\Rightarrow 6V_A + 3V_B = -9 \rightarrow ①$$

At Junction - B:

$$I_4 + I_5 + I_6 = 0$$


$$\Rightarrow \frac{V_B - V_A - 5}{2} + \frac{V_B - V_0}{4} + \frac{V_B - V_0}{4} = 0$$

$$\Rightarrow -2V_A + 4V_B = 20 \rightarrow ②$$

$$\therefore \underline{\underline{V_A = 1.333 \text{ V}}}, \\ \underline{\underline{V_B = 5.666 \text{ V}}}.$$

\* Home Work :-

1]

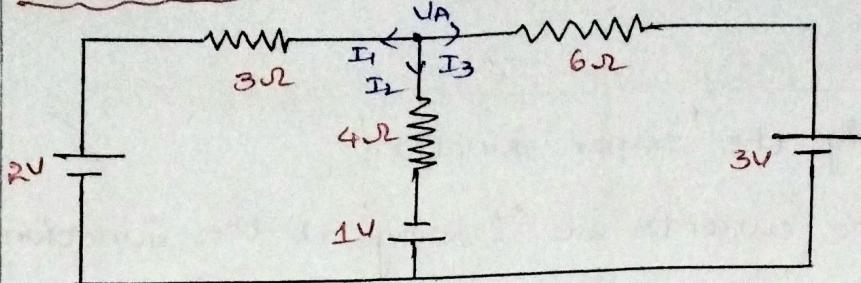

Find  $I_{4,2} = ?$  using KCL?

A) At Junction  $V_A$ :

$$I_1 + I_2 + I_3 = 0$$

$$\Rightarrow \frac{V_A - V_O - 2}{3} + \frac{V_A - V_O + 1}{4} + \frac{V_A - V_O - 3}{6} = 0$$

$$\Rightarrow \frac{V_A - 2}{3} + \frac{V_A + 1}{4} + \frac{V_A - 3}{6} = 0$$

$$\Rightarrow \frac{2(V_A - 2) + 3(V_A + 1) + 2(V_A - 3)}{12} = 0$$

$\begin{array}{r} 4,6 \\ 2 \\ 3 \\ \hline 1,1 \end{array}$

$$\Rightarrow 2V_A - 8 + 3V_A + 3 + 2V_A - 6 = 0$$

$$\Rightarrow 7V_A - 14 + 3 = 0$$

$$\Rightarrow 7V_A = 11$$

$$\Rightarrow V_A = \frac{+11}{7} = \frac{+11}{7} = +1.57 \text{ Volts}$$

$$\therefore I_{4,2} = \frac{V_A}{R}$$


$$= \frac{1.57}{4}$$

$$I_{4,2} = \underline{\underline{0.305 \text{ Amperes}}}$$

\* Super Node:

→ If the voltage source is in between two non-reference junctions, then it is called "super node".

Example:

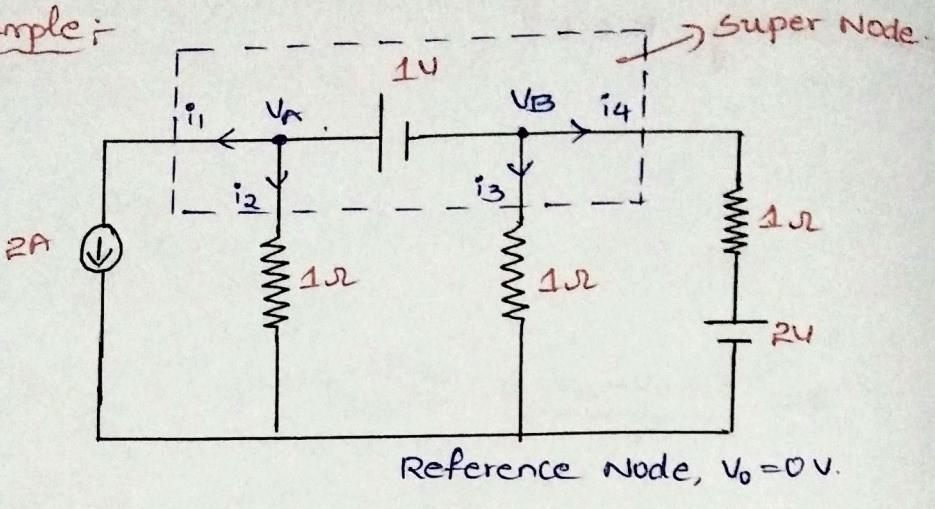

Reference Node,  $V_0 = 0V$ .

Applying 'KCL' at ' $V_A$ ' :

$$\Rightarrow \frac{2}{1} + \frac{V_A - V_0}{1} + \frac{V_B - V_0}{1} + \frac{V_B - V_0 - 2}{1} = 0$$

$$\Rightarrow 2 + V_A + V_B + V_B - 2 = 0$$

$$\Rightarrow V_A + 2V_B = 0 \quad \rightarrow \textcircled{1}$$

Applying 'KVL' at 'super node' :

$$\Rightarrow V_A - V_B = 1 \quad \rightarrow \textcircled{2}$$

$$\Rightarrow V_A = 1 + V_B$$

Substitute  $\textcircled{2}$  in eqn  $\textcircled{1}$

$$\Rightarrow 1 + V_B + 2V_B = 0$$

$$\Rightarrow 1 + 3V_B = 0$$

$$\Rightarrow 3V_B = -1$$

$$\Rightarrow V_B = -\frac{1}{3}$$


Put  $V_B = -\frac{1}{3}$  in eqn  $\textcircled{2}$

$$\Rightarrow V_A - (-\frac{1}{3}) = 1 \quad \Rightarrow V_A = 1 + \frac{1}{3} = \frac{2}{3}$$

$$\therefore I_{1\Omega} = \frac{V_1}{R}$$

$$= \frac{\frac{2}{3}}{1}$$

$$I_{1\Omega} = \frac{\frac{2}{3}}{1}$$

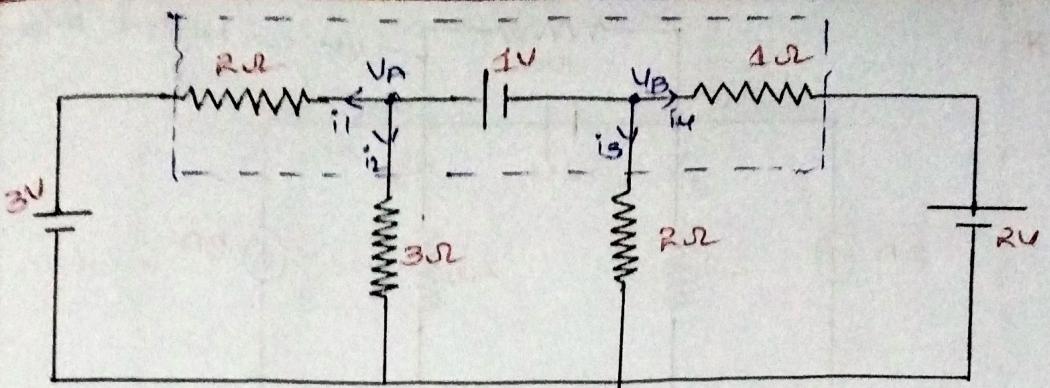

Find  $I_{3\Omega}$ ?

A) Applying 'KCL' at ' $V_A$ '.

$$\Rightarrow \frac{V_A - 3}{2} + \frac{V_A}{3} + \frac{V_B}{2} + \frac{V_B - 2}{1} = 0$$

$$\Rightarrow \frac{3V_A - 9 + 2V_A + 6V_B + 6V_B - 12}{6} = 0$$

$$\Rightarrow 5V_A + 9V_B - 21 = 0.$$

$$\Rightarrow 5V_A + 9V_B = 21 \longrightarrow \textcircled{1}$$

Applying 'KVL' at 'super Node'.

$$\Rightarrow V_A - V_B = 1 \longrightarrow \textcircled{2}$$

Substitute \textcircled{2} in \textcircled{1}.

$$\Rightarrow 5(1 + V_B) + 9V_B = 21$$

$$\Rightarrow 5 + 5V_B + 9V_B = 21$$


$$\Rightarrow 14V_B = 16 \Rightarrow V_B = \frac{16}{14} = \underline{\underline{1.14V}}$$

$$\text{Now, } V_A = 1 + V_B = 1 + 1.14 = \underline{\underline{2.14V}}.$$

$$\therefore I_{3\Omega} = \frac{V_A}{R}$$

$$= \frac{2.14}{3}$$

$$= \underline{\underline{0.71A}}.$$

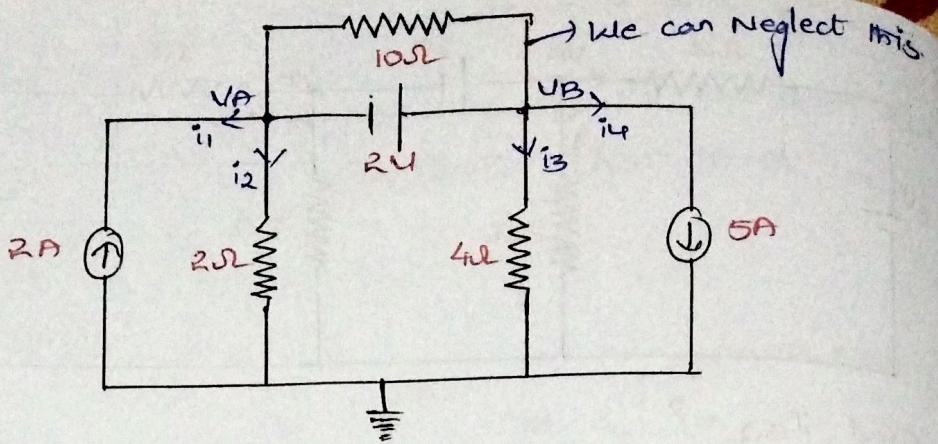

A) Applying KCL at VA:

$$\Rightarrow \frac{-2}{1} + \frac{V_A}{2} + \frac{V_B}{4} + 5 = 0$$

$$\Rightarrow \frac{-8 + 2V_A + V_B + 20}{4} = 0$$

$$\Rightarrow 2V_A + V_B = -12$$

$$\Rightarrow 2V_A + V_B = -12 \quad \rightarrow ①$$

Applying KVL at superNode:

$$\Rightarrow V_B - V_A = 2. \quad \rightarrow ②$$

$$\Rightarrow V_B = 2 + V_A$$

Substitute ② in ①

$$\Rightarrow 2V_A + 2 + V_A = -12 \qquad V_B = 2 + V_A$$

$$\Rightarrow 3V_A = -14$$


$$\Rightarrow V_B = 2 + (-4.667)$$

$$\Rightarrow V_A = \frac{-14}{3} = \underline{\underline{-4.667}} \text{ V}$$

$$\Rightarrow V_B = \underline{\underline{-2.667}} \text{ V}$$

$$I_{2\Omega} = \frac{V_A}{2} = \frac{-4.667}{2} = \underline{\underline{-2.3335}} \text{ A}$$
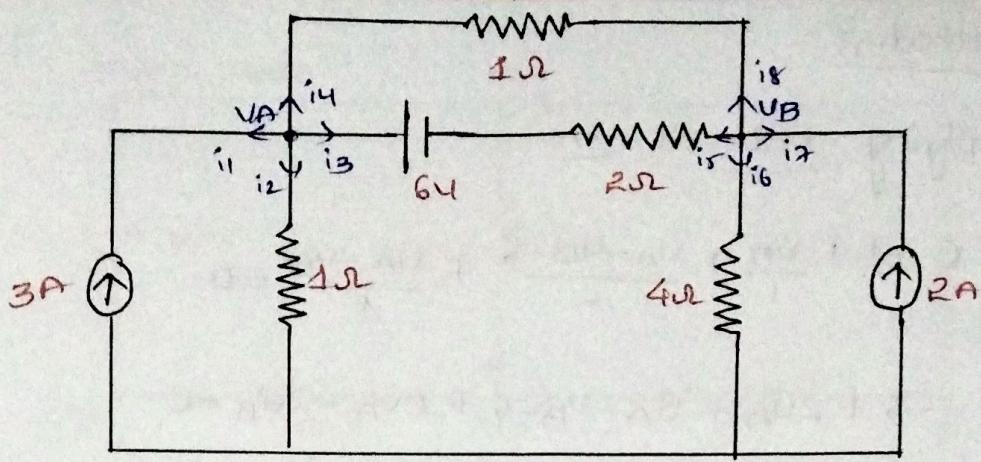
$$I_{4\Omega} = \frac{V_B}{4} = \frac{-2.667}{4} = \underline{\underline{-0.66675}} \text{ A}$$



A) Method-1 : Applying 'KCL' at 'VA'.

$$\Rightarrow -3 + \frac{VA}{1} + \frac{VA - VB - 6}{2} + \frac{VA - VB}{1} = 0$$

$$\Rightarrow -6 + 2VA + VA - VB - 6 + 2VA - 2VB = 0$$

$$\Rightarrow 5VA - 3VB = 12 \longrightarrow \textcircled{1}$$

Applying 'KCL' at 'VB'.

$$\Rightarrow \frac{VB - VA + 6}{2} + \frac{VB}{4} + \frac{VB - VA}{1} - 2 = 0$$

$$\Rightarrow 2VB - 2VA + 12 + VB + 4VB - 4VA - 8 = 0 \quad | \cdot 4$$

$$\Rightarrow -6VA + 7VB + 4 = 0$$

$$\Rightarrow -6VA + 7VB = -4 \longrightarrow \textcircled{2}$$


By solving  $\textcircled{1}$  &  $\textcircled{2}$

$$\therefore VA = \underline{\underline{4.411}} \text{ volts}$$

$$VB = \underline{\underline{3.352}} \text{ volts}$$

$$I_{1\Omega} = \frac{VA}{1} = \underline{\underline{4.411}} \text{ A}$$
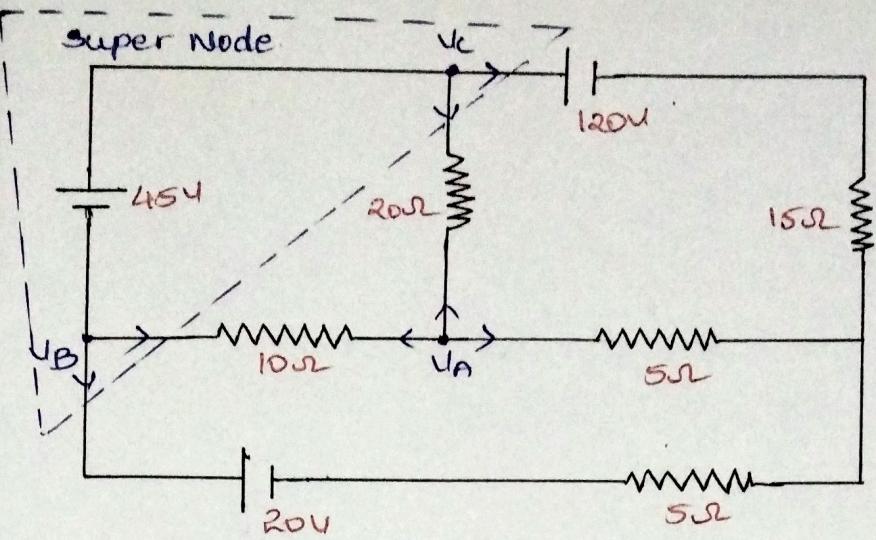
$$I_{4\Omega} = \frac{VB}{4} = \frac{3.352}{4} = \underline{\underline{0.838}} \text{ A}$$



A) Applying KCL at  $\tilde{v}_A$ :

$$\Rightarrow \frac{v_A - v_B}{10} + \frac{v_A - v_C}{20} + \frac{v_A}{5} = 0$$

$$\Rightarrow \underbrace{\frac{2v_A - 2v_B + v_A - v_C + 4v_A}{20}}_{=0} = 0$$

$$\Rightarrow 7v_A - 2v_B - v_C = 0 \rightarrow (1)$$

Applying KCL at Supernode [ $v_B$  &  $v_C$ ]:

$$\Rightarrow \frac{v_B - 20}{5} + \frac{v_B - v_A}{10} + \frac{v_C - v_A}{20} + \frac{v_C - 120}{15} = 0$$

$$\Rightarrow \underbrace{12v_B - 240 + 6v_B - 6v_A + 3v_C - 3v_A + 4v_C - 480}_{60} = 0$$

$$\Rightarrow 18v_B - 9v_A + 7v_C = 720$$

$$\Rightarrow -9v_A + 18v_B + 7v_C = 720 \rightarrow (2)$$

Applying KVL at Supernode:

$$\Rightarrow v_C - v_B = 45 \rightarrow (3)$$


$$\therefore \underline{v_A = 15.81 \text{ V}}$$

$$\underline{v_B = 21.89 \text{ V}}$$

$$\underline{v_C = 66.89 \text{ V}}$$

## star-Delta Networks :-

star  $\Rightarrow$  Delta :-

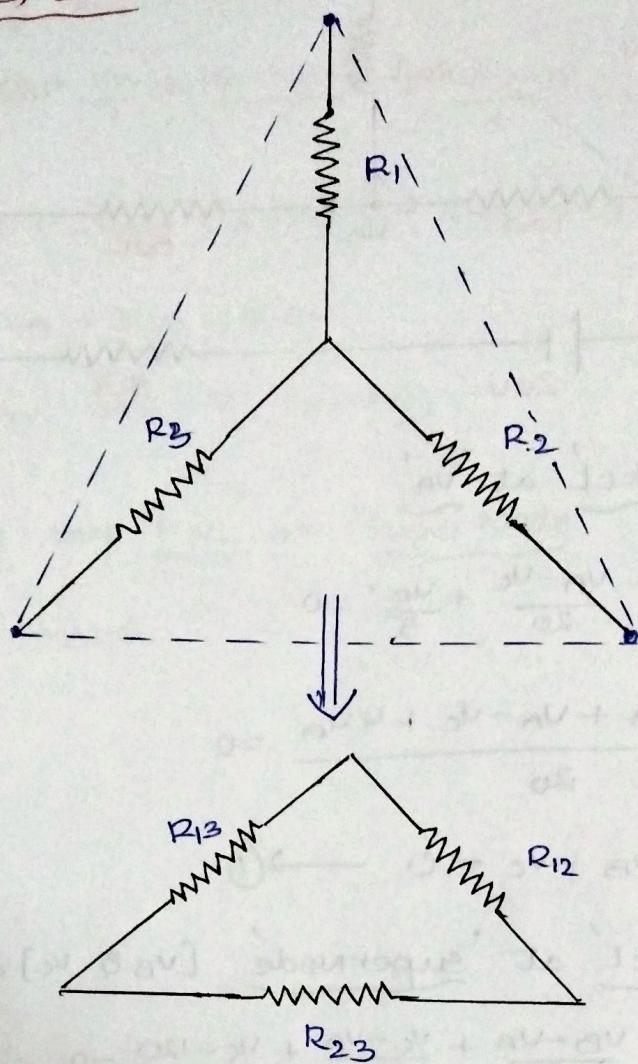


$$\rightarrow R_{1\Delta} = R_1 + R_2 + \frac{R_1 R_2}{R_3} \text{ (or) } \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_{2\Delta} = R_2 + R_3 + \frac{R_2 R_3}{R_1} \text{ (or) } \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_{1\Delta} = R_1 + R_3 + \frac{R_1 R_3}{R_2} \text{ (or) } \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

Delta  $\Rightarrow$  star :-

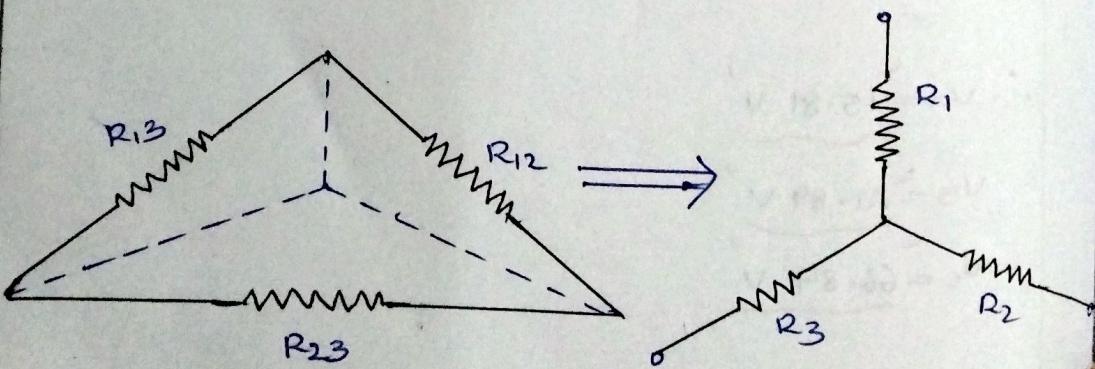

$$R_1 = \frac{R_{13} \cdot R_{12}}{R_{13} + R_{12} + R_{23}}$$


$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{13} + R_{12} + R_{23}}$$

$$R_3 = \frac{R_{13} \cdot R_{23}}{R_{13} + R_{12} + R_{23}}$$

Rules :-


- ① If there is any 'series' (or) 'parallel combination' in a given network, then reduce it.

Ex :-

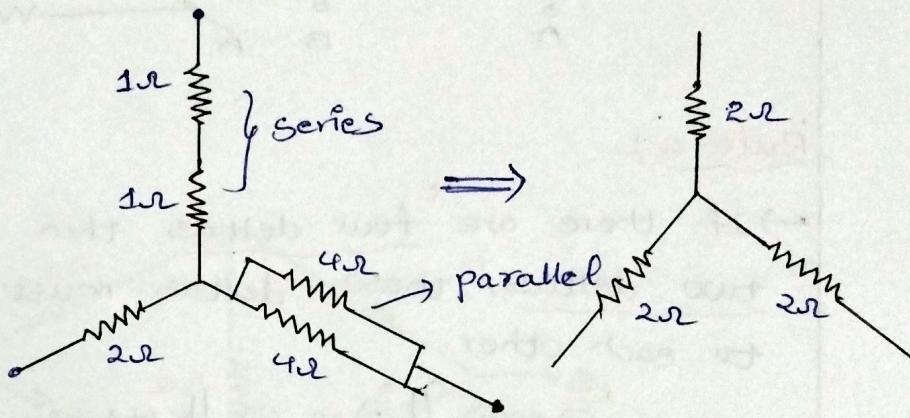

→ convert it into a single Network then apply delta to it.

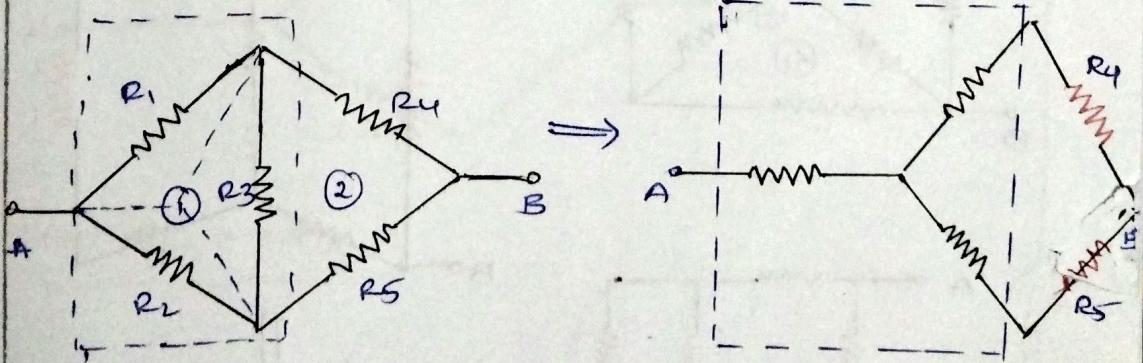- ② If there are two deltas then solve any convert one delta only.







Apply Rule-1 & solve it.

### Rule-3 :-

→ If there are '3 deltas', then convert the 'star' into 'delta'.

Ex:-

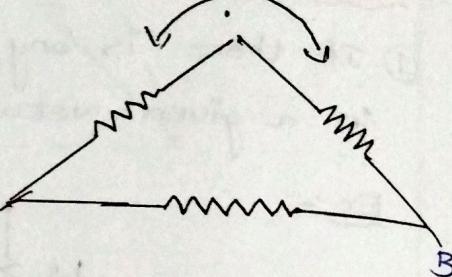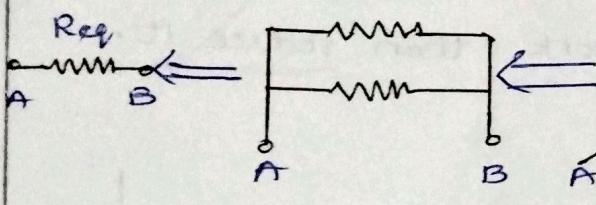
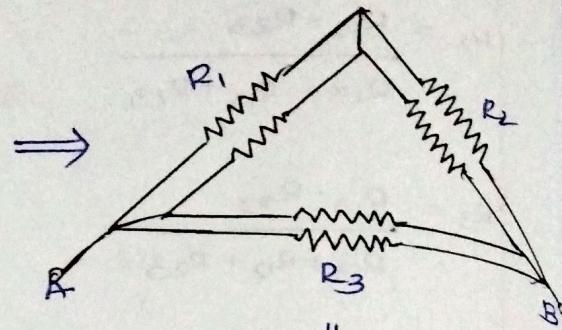
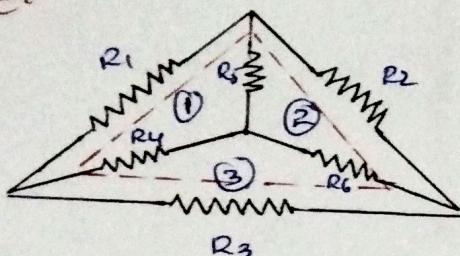


### Rule-4 :-

→ If there are 'four deltas', then convert any 'two deltas', those deltas must be 'opposite' to each other.

i.e. ① & ③ || ② & ④ (to other)


Ex:-

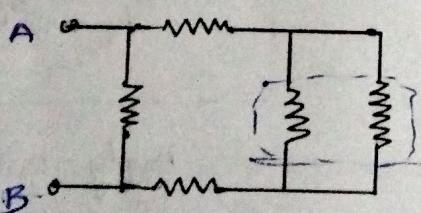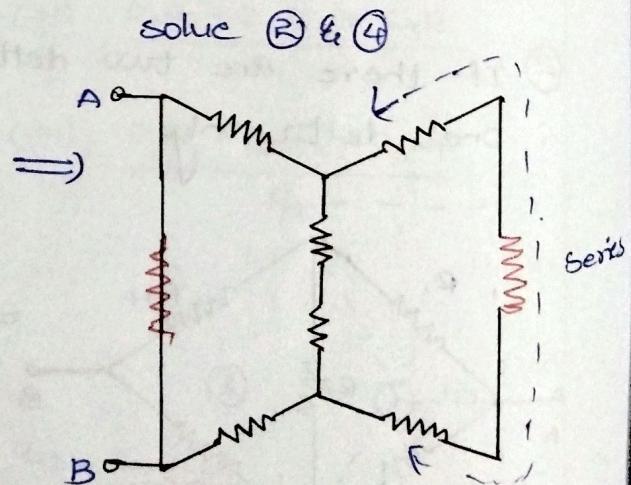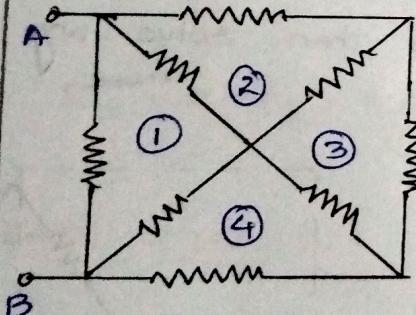

### Rule-5 :-


→ If there are 5 deltas, then convert / solve  
any three alternate deltas  
i.e., (1), (3), (5) [or] (2), (4), (6)

Ex:-

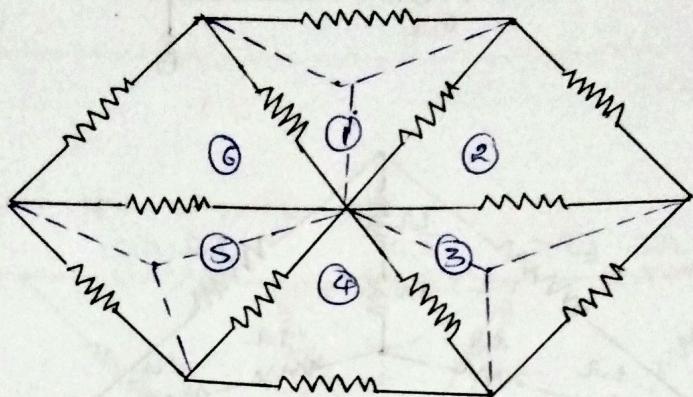


### \* Problems :-

1)

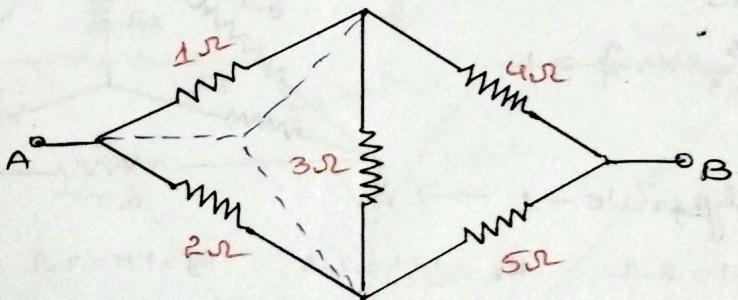


Find  $R_{AB} = ?$

A)

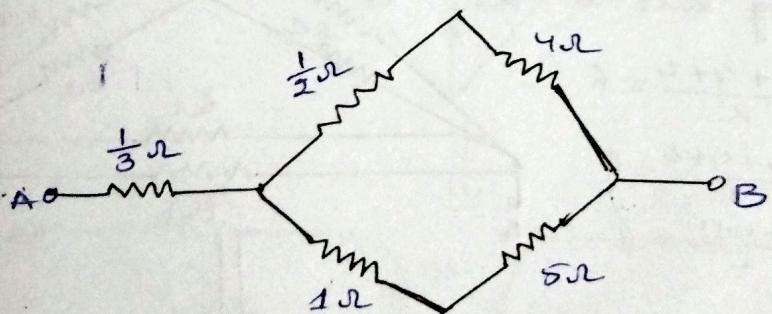


$$\Rightarrow R_{AB} = 2.9 \Omega.$$

2)

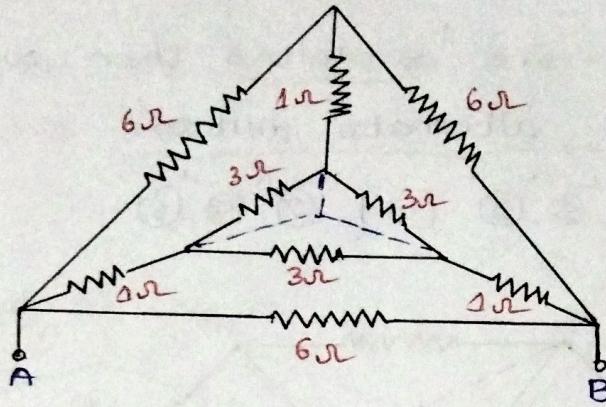

A)

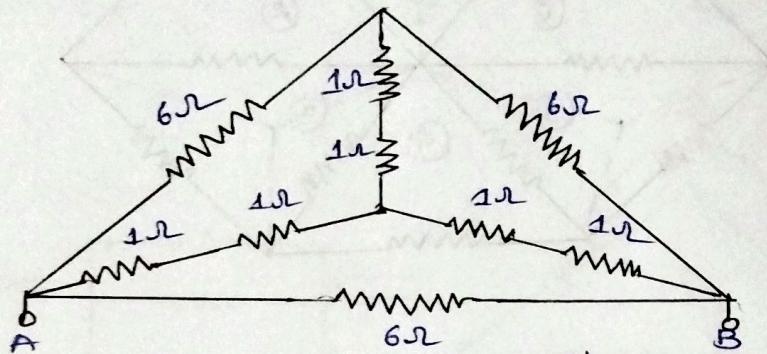


$$R_1 = \frac{3 \times 3}{3+3+3} = \frac{9}{9} = 1$$

$$R_2 = \frac{3 \times 3}{3+3+3} = \frac{9}{9} = 1$$

$$R_3 = \frac{3 \times 3}{3+3+3} = \frac{9}{9} = 1$$

→ By applying rule - 1 →
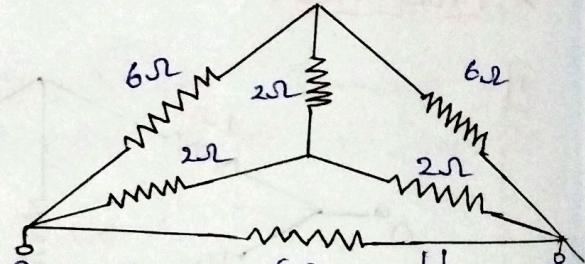
$$R_1 = 1 + 1 = 2 \Omega, \quad R_2 = 1 + 1 = 2 \Omega, \quad R_3 = 1 + 1 = 2 \Omega$$






→ By applying rule - 3 →

$$\Rightarrow R_{12} = \frac{4+4+4}{2} = 6$$


$$\Rightarrow R_{23} = \frac{4+4+4}{2} = 6$$
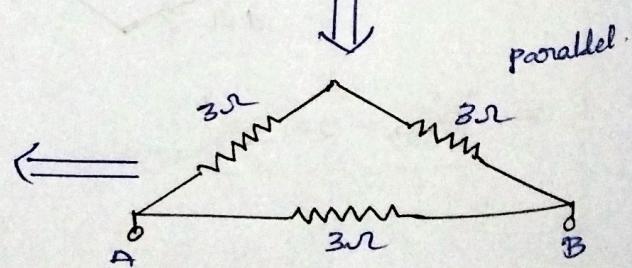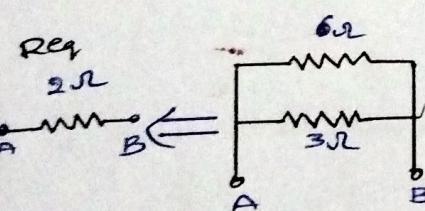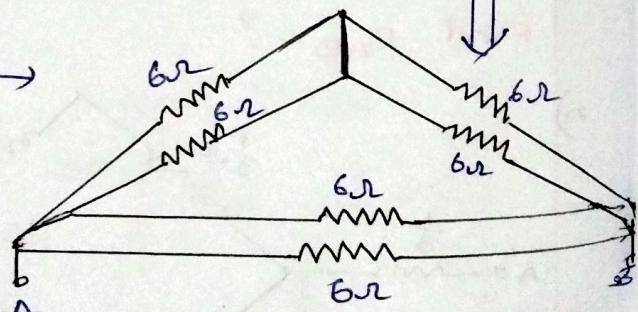
$$\Rightarrow R_{13} = \frac{4+4+4}{2} = 6$$





$$\therefore R_{eq} = \underline{\underline{2 \Omega}}$$


parallel.

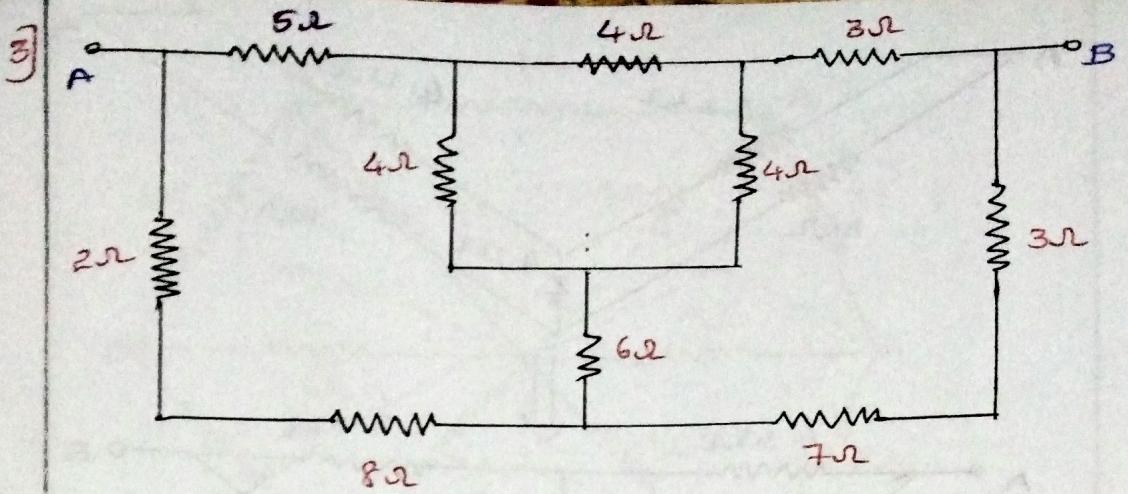

A) Redraw the circuit as


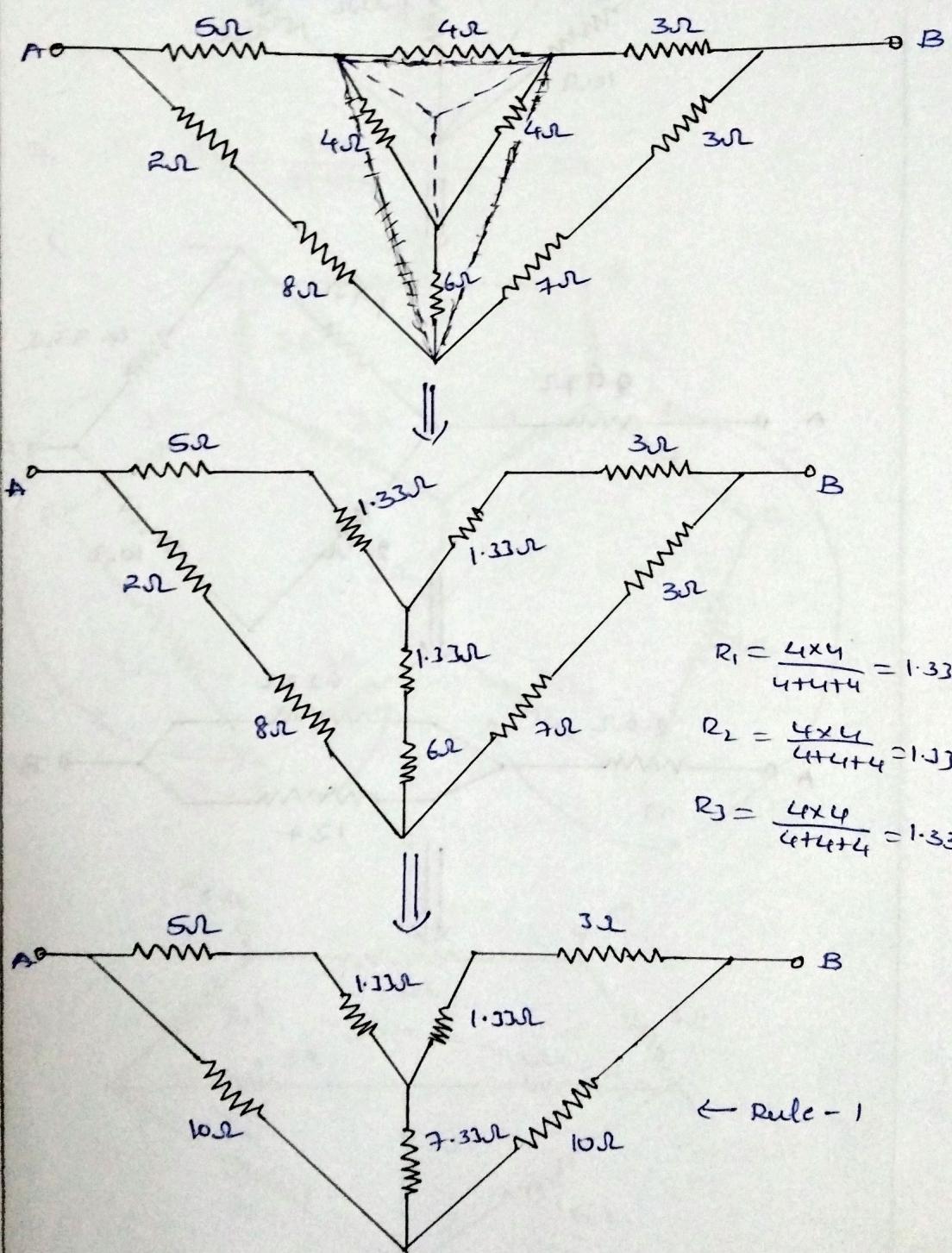



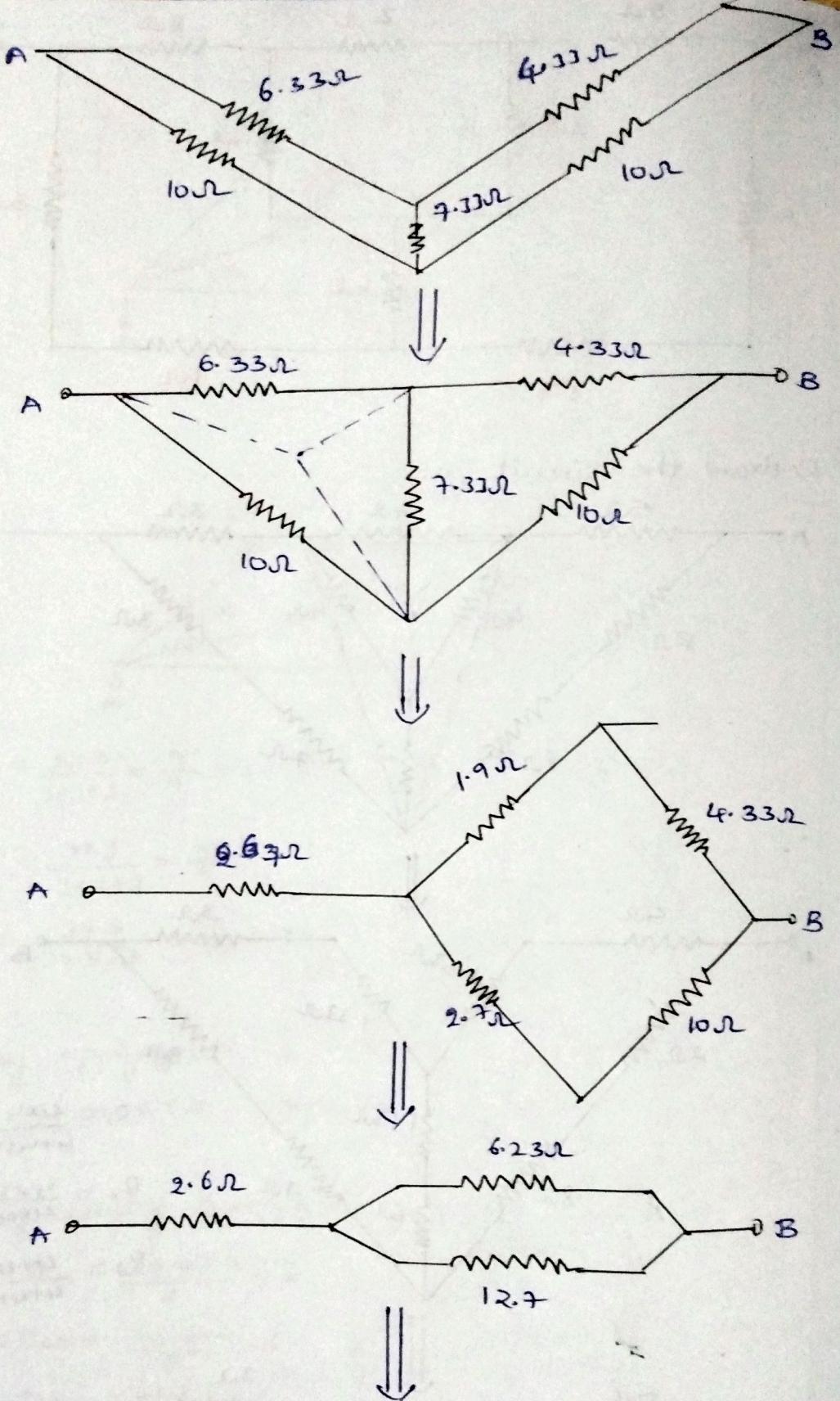


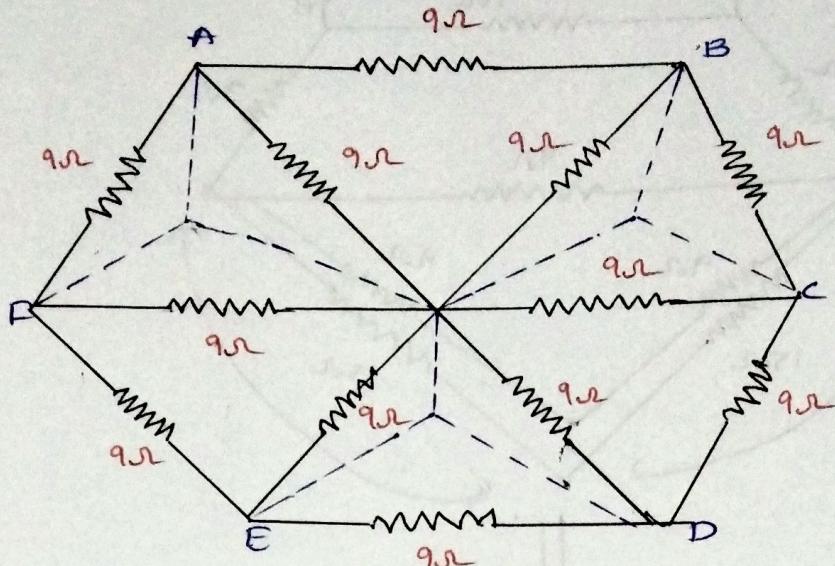

Find  $R_{eq}$ ?

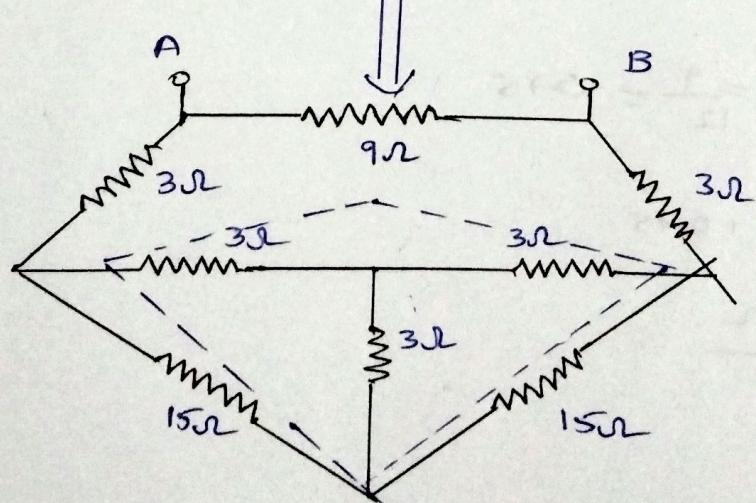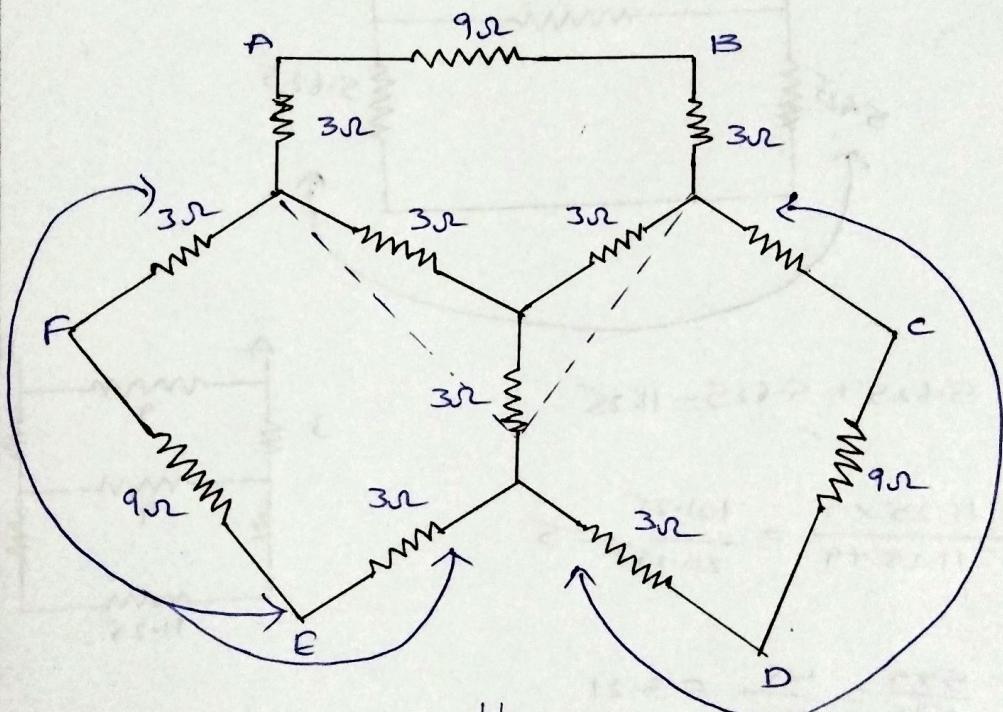
$$A) R_1 = R_2 = R_3 = \frac{9 \times 9}{9+9+9} = \frac{81}{27} = 3\Omega.$$



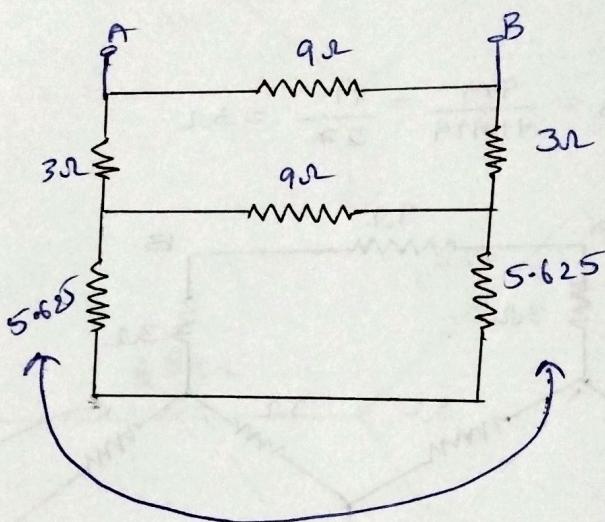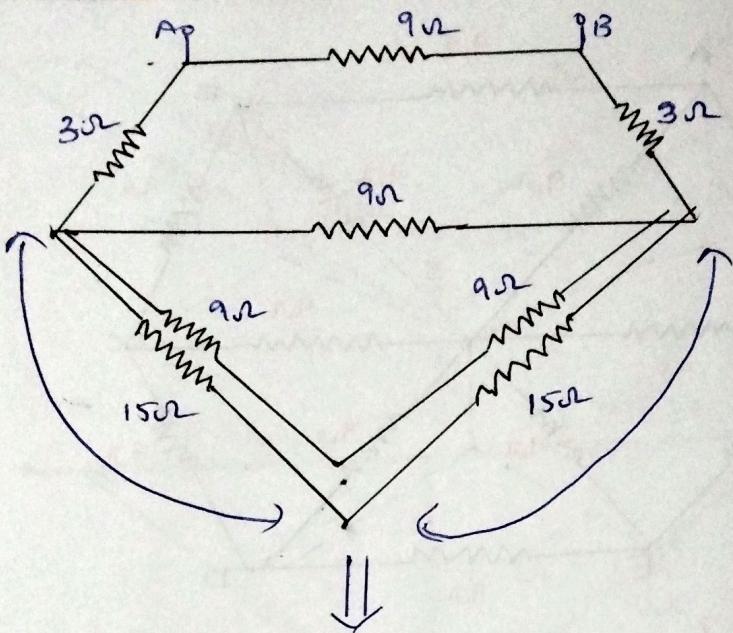

$$\Rightarrow 5.625 + 5.625 = 11.25$$
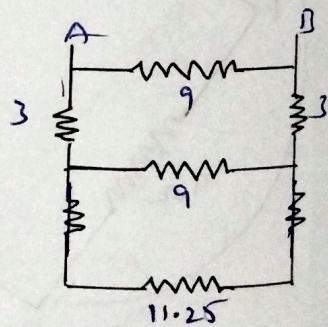
$$\Rightarrow \frac{11.25 \times 9}{11.25 + 9} = \frac{101.25}{20.25} = 5$$




$$+ \frac{5 \times 9}{5+9} = \frac{45}{14} = 3.21$$

$$\Rightarrow \frac{3 \times 3}{3+9} = \frac{9}{12} = 0.75$$

$$\Rightarrow 3.21 + 0.75$$

$$\Rightarrow \underline{4.2 \Omega}$$

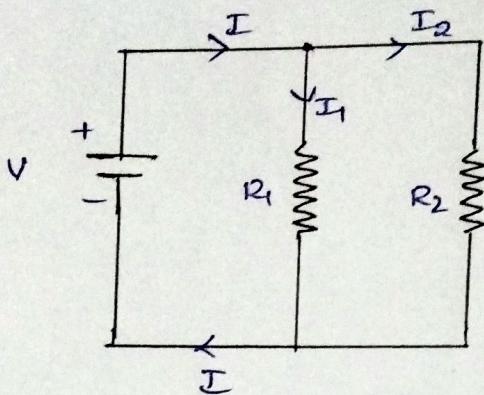\* current division Rule (or) Branch current :-




$$I = I_1 + I_2$$

$$\Rightarrow I_1 = \left( \frac{R_2}{R_1 + R_2} \right) \times I$$

$$\Rightarrow I_2 = \left( \frac{R_1}{R_1 + R_2} \right) \times I$$

\* Superposition Theorem :-

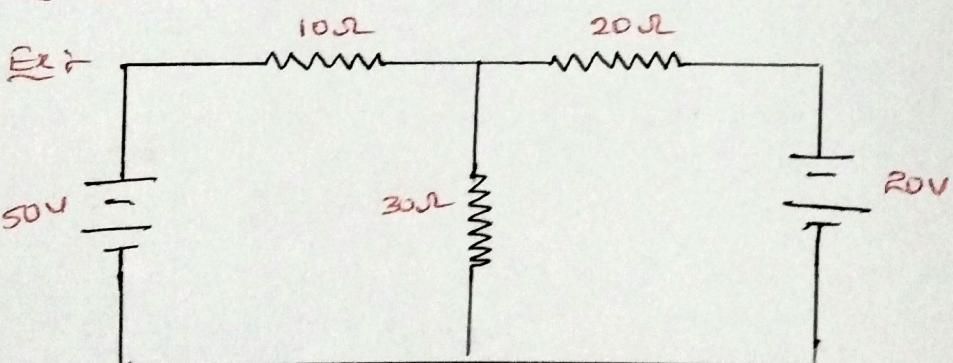


calculate  $I_{30\Omega} = ?$


'2 sources'  
'2+1 = 3 steps'

A) step 1 :-

For 50V source :-

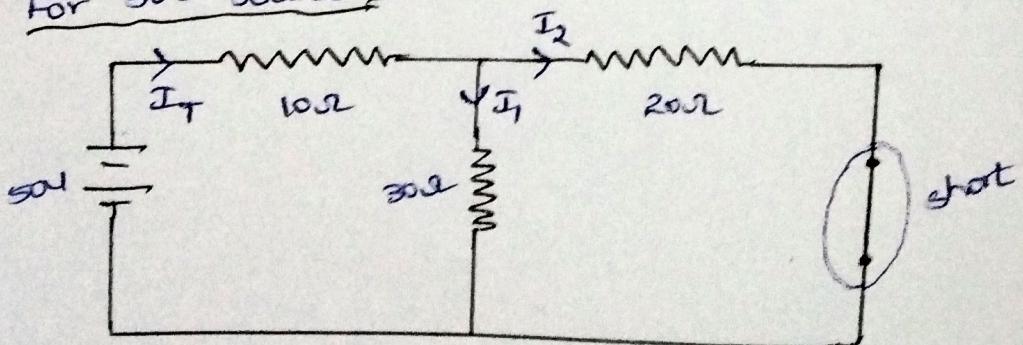

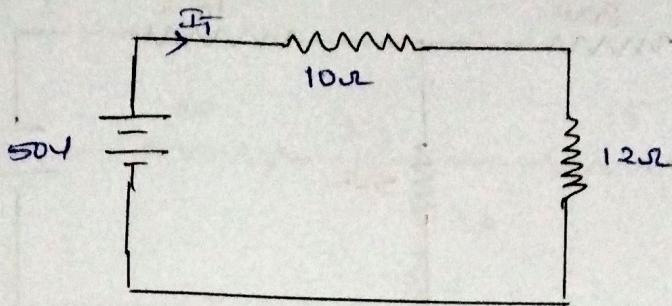$V \rightarrow$  short  
 $I \rightarrow$  open.



Because  $\frac{20 \times 30}{20+30} = \frac{600}{50} = 12\Omega$  [parallel].

Now, In series  $10 + 12 = 22\Omega$ .


$$\therefore I_T = \frac{50}{22} = 2.27 \text{ A} \quad [\because I = \frac{V}{R}]$$

$$\therefore I_{30} = 2.27 \times \left( \frac{20}{20+30} \right) = 0.908 \text{ A}$$

$$\therefore I_{30} = I_1 = 0.908 \text{ A} \downarrow$$

Step 2 :-

For 20V source

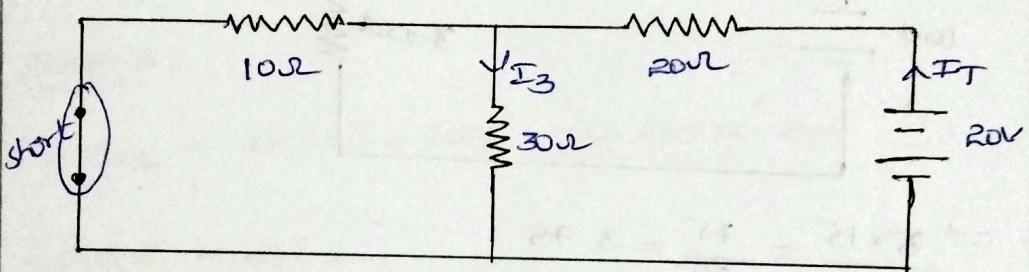

Parallel &  $\frac{10 \times 30}{10+30} = \frac{300}{40} = 7.5$

Series :-  $7.5 + 20 = 27.5$

$$\therefore I_T = \frac{V}{R} = \frac{20}{27.5} = 0.72 \text{ A}$$



$$\therefore I_3 = (0.72) \times \left( \frac{10}{10+30} \right) = 0.18 \text{ A} \downarrow$$

$$\therefore I_3 = 0.18 \text{ A} \downarrow$$

Step 3 :-

$$I_{30\Omega} = I + I_3 = 0.908 \text{ A} + 0.18 \text{ A} = 1.088 \text{ A} \downarrow$$

2

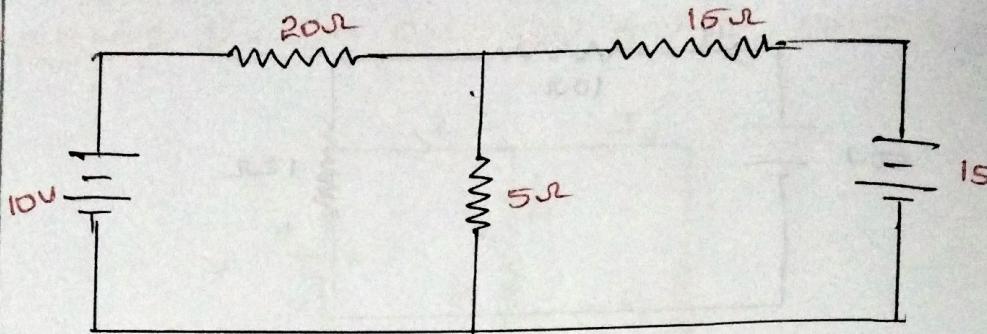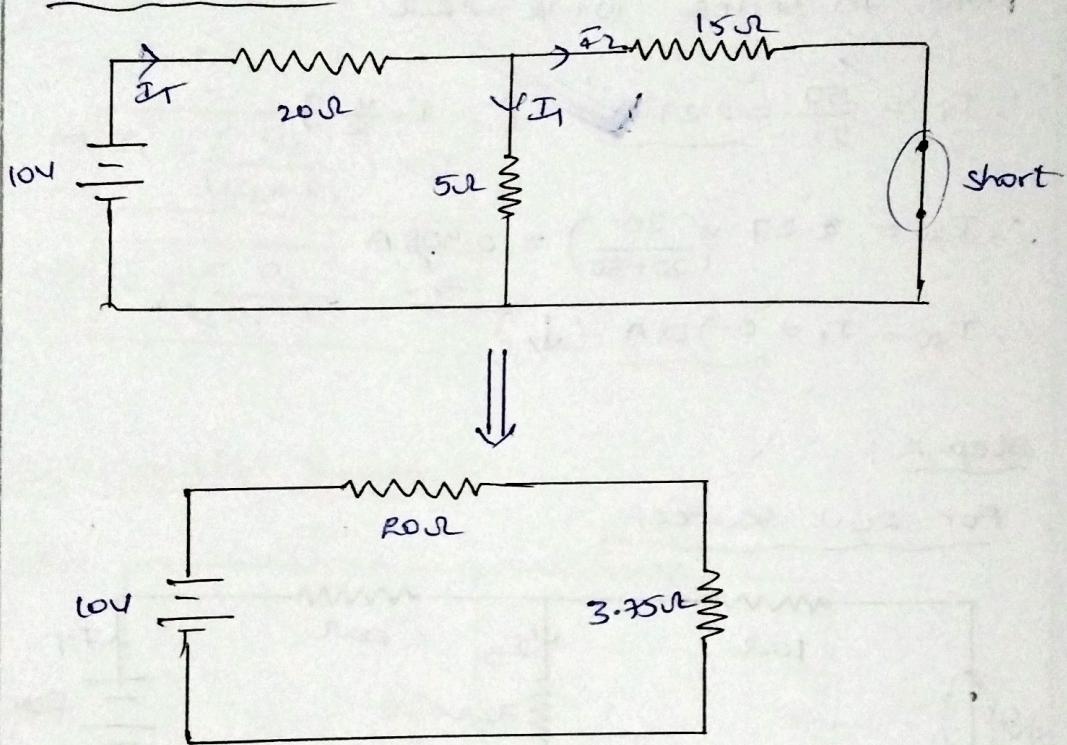A) Step 1:-For 10V source :-

$$\Rightarrow \frac{5 \times 15}{5+15} = \frac{75}{20} = 3.75$$


$$\text{series } r = 20 + 3.75 = 23.75$$

$$\therefore I = \frac{V}{r} = \frac{10}{23.75} = 0.421\text{A}$$

$$\therefore I_2 = 0.421 \times \left( \frac{5}{5+15} \right)$$

$$I_2 = 0.105\text{A} \quad (\rightarrow)$$

Step-2

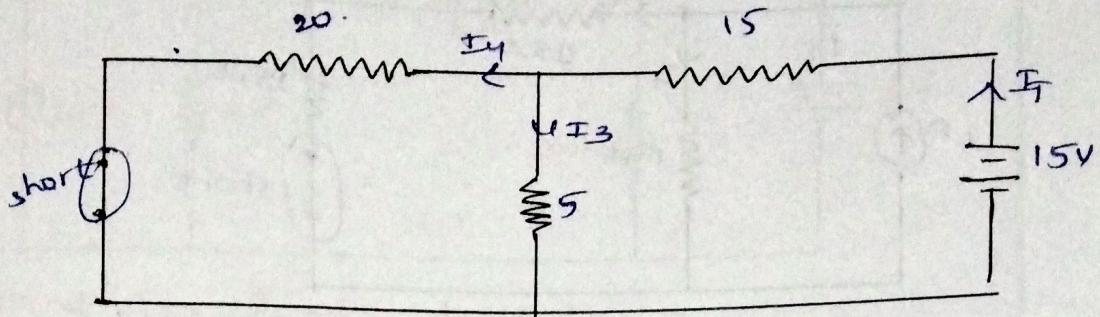

Parallel:

$$\Rightarrow \frac{20 \times 5}{20+5} = \frac{100}{25} = 4.$$

series:

$$\Rightarrow 15 + 4 = 19.$$


$$\therefore I_T = \frac{V}{R} = \frac{15}{19} = 0.789 \text{ A}$$

$$\therefore I_{15} = I_T = 0.789 \text{ A} \quad (\leftarrow)$$

Step-3:


$$\therefore I_{15} = 0.789 - 105 = \underline{\underline{0.685 \text{ A}}} \quad (\leftarrow)$$

second Model:

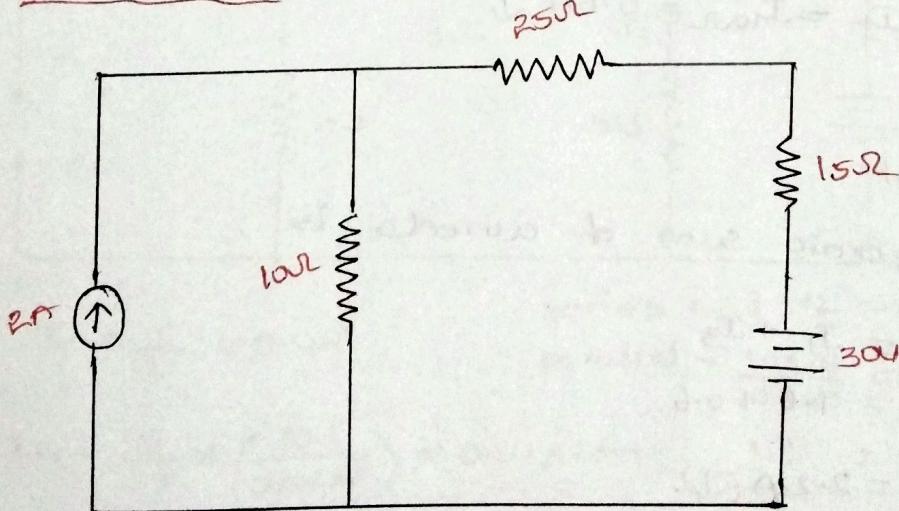

Find  $I_{10}$ ?

a) Step-1 (For 2A)

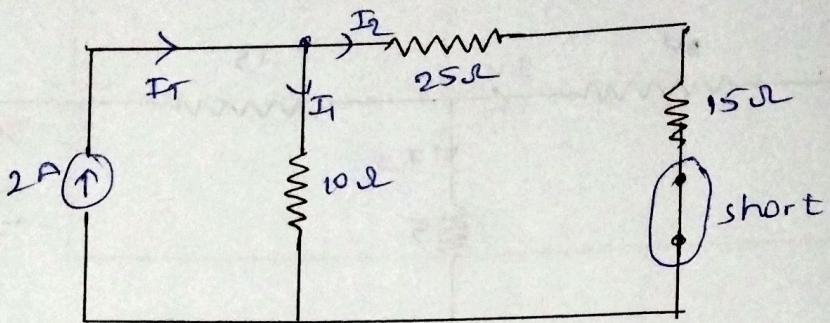


$$\text{series} \rightarrow 25 + 15 = 40.$$

$$I_T = 2 \text{ A.}$$

$$\therefore I_1 = 2 \times \left( \frac{40}{40+10} \right) = 1.6 \text{ A.} \downarrow$$

Step-2 (For 30V)

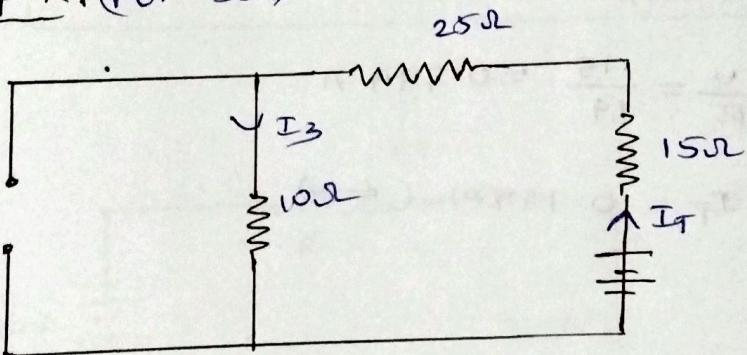

$$I_T = \frac{30}{15+25+10} = \frac{30}{50} = 0.6 \text{ A}$$

$$I_3 = I_T = I_{10\Omega} = 0.6 \text{ A} \downarrow.$$


Step-3

→ Algebraic sum of currents is

$$I_{10} = I_1 + I_3 \\ = 1.6 + 0.6$$


$$\therefore I_{10\Omega} = \underline{\underline{2.2 \text{ A}}} \downarrow.$$

Third model :-

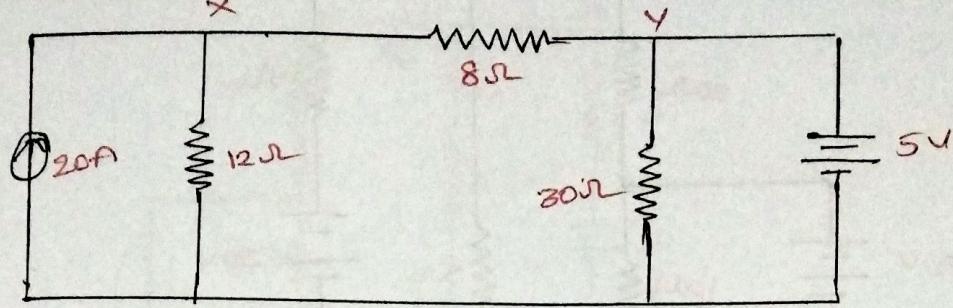

Find  $I_{8\Omega}$  ?, with direction?

A) Step-1 (For 20A)

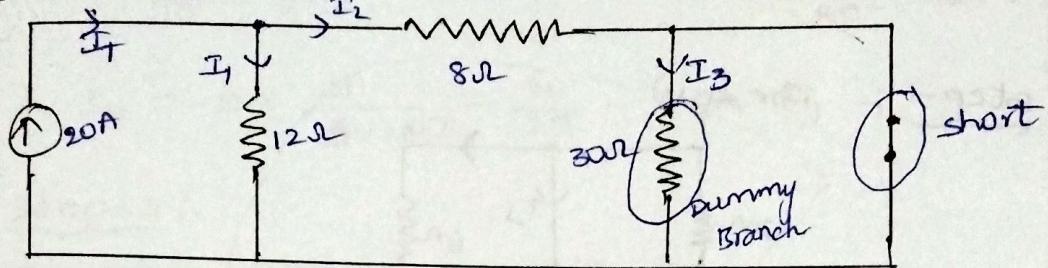


$$\rightarrow \text{parallel} : \frac{12 \times 8}{12+8} = \frac{96}{20} = 4.8 \text{ A} \quad (\text{No need}) \quad \frac{0 \times 30}{0+30} = 0.$$

$$I_T = 20 \text{ A}$$

$$\therefore I_2 = 20 \times \left( \frac{12}{12+8} \right) = 20 \times \frac{12}{20} = \underline{12 \text{ A}} \quad \rightarrow$$

Step-2 :

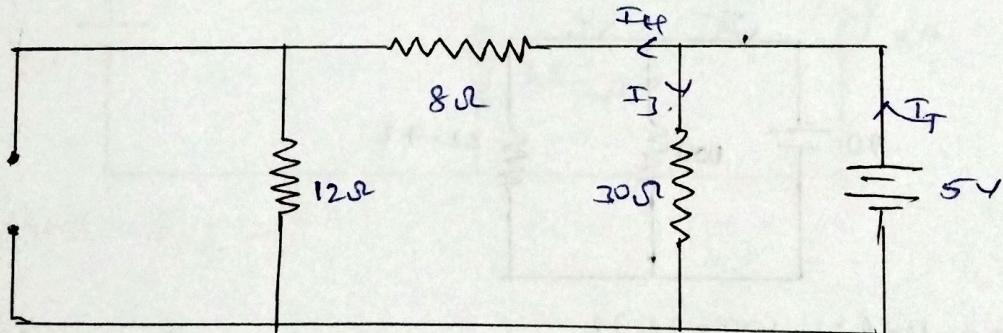

$$I_T = \frac{5}{12} = 0.41 \text{ A}$$


$$\text{series} = 8 + 12 = 20$$

$$\text{parallel} = \frac{30 \times 20}{30+20} = 12$$

$$I_4 = \frac{5}{12} \times \left( \frac{30}{30+20} \right) = \underline{0.24 \text{ A}} \leftarrow$$


Step-3
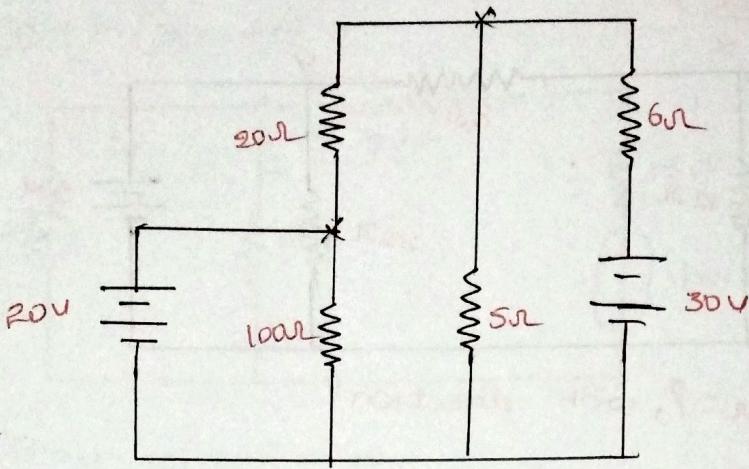
$$I_{8\Omega} = I_2 + I_4 = 12 - 0.24 = \underline{11.76 \text{ A}} \quad (\rightarrow) \quad \underline{x \rightarrow x}$$




Find  $I_{5\Omega} = ?$

A) step-1 i (For 20V)

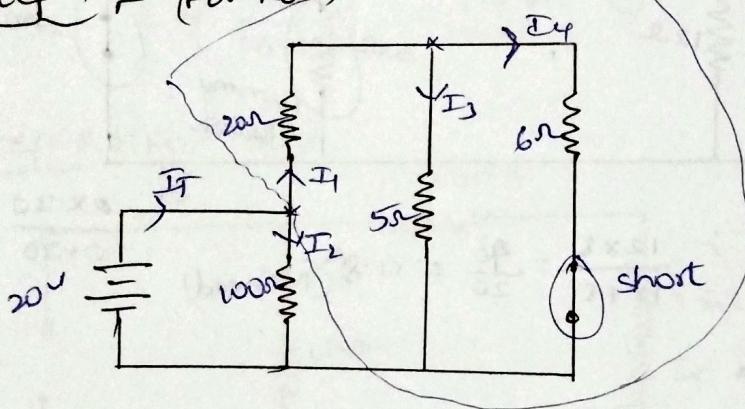

$$\text{Parallel } \left( \frac{5 \times 6}{5+6} = \frac{30}{11} = 2.72 \Omega \right)$$
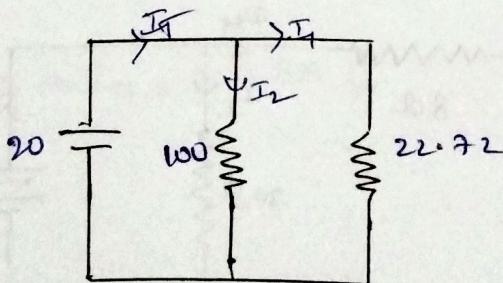
$$\text{series } 2.72 + 20 = 22.72 \Omega$$




$$\text{parallel } \frac{100 \times 22.72}{100 + 22.72} = 18.51.$$

$$\therefore I_T = \frac{U}{R} = \frac{20}{18.51} = 1.08 \text{ A}$$

$$I_1 = 1.08 \times \frac{100}{100 + 22.72} = 0.88 \text{ A}$$

$$\begin{aligned} \therefore I_{3\Omega} &= I_T \times \frac{6}{5+6} \\ &= 0.88 \times 0.54 \\ &= 0.48 \text{ A} \downarrow \end{aligned}$$

step-2 (For 30V)

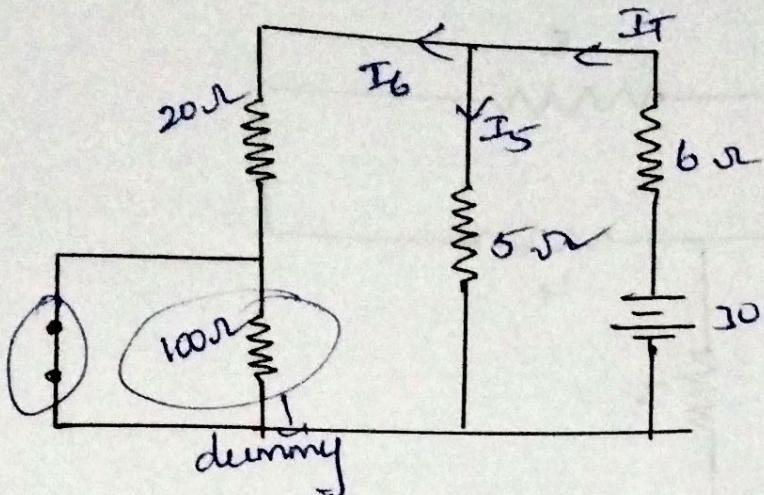

$$\text{parallel} = \frac{20 \times 5}{20 + 5} = 4$$

$$\text{series} = 4 + 6 = 10$$

$$IT = \frac{30}{10} = 3 \text{ A}$$


$$\therefore I_5 = 3 \times \frac{20}{5+20} = \frac{60}{25} = \underline{\underline{2.4 \text{ A}}} \downarrow$$

step-3 :-


Algebraic sum of currents is

$$\sum I = I_3 + I_5 = 0.48 + 2.4 = \underline{\underline{2.88 \text{ A}}} \downarrow$$


## \* Thevenin's Theorem :-

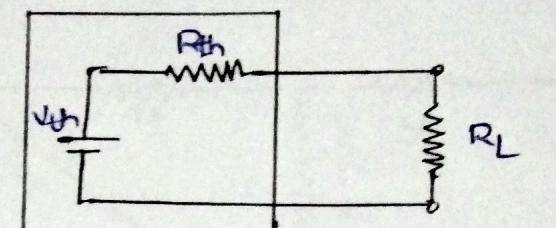


one voltage  
one Resistor } series

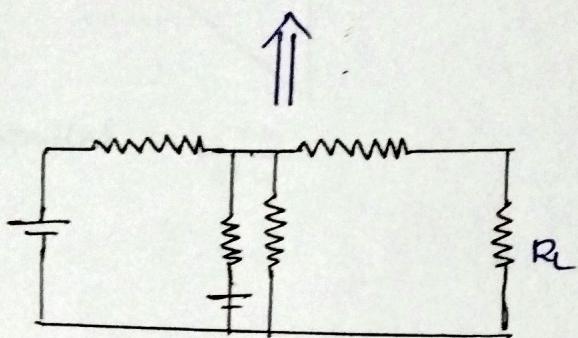

Example :-

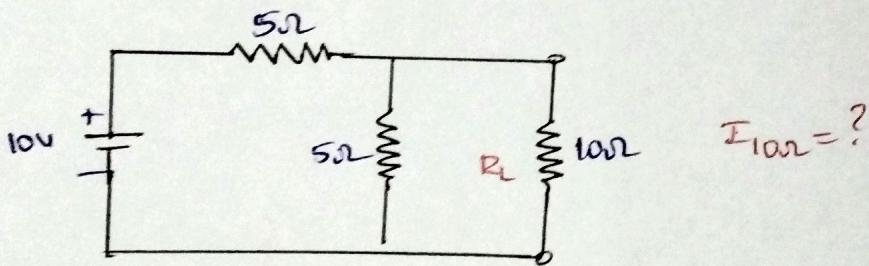

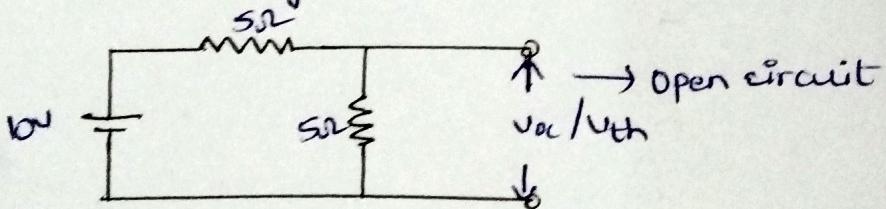Step-1 :- Identify & Remove Load source ( $R_L$ ).



Step-2 :- calculate voltage drop ( $V_{oc}$ ) at open circuit

5Ω & 5Ω are in series


$$\Rightarrow R = 10\Omega$$

$$\Rightarrow V = 10V$$

$$\therefore I = \frac{V}{R} = \frac{10}{10} = 1$$

$$\begin{aligned}\therefore V_{oc} / V_{th} &= IR \\ &= (1)(5) \quad [ \because R = 5\Omega ] \\ &= 5\end{aligned}$$


Step-3: calculate thevening resistance.

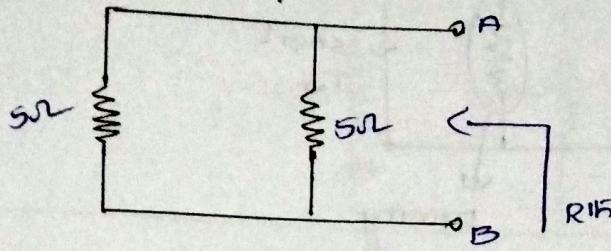

$$\therefore R_{AB} = \frac{5 \times 5}{5+5} = \frac{25}{10} = 2.5 \Omega$$

$$\therefore R_{TH} = \underline{2.5 \Omega}$$


Step-4: Equivalent circuit of Thevenin.

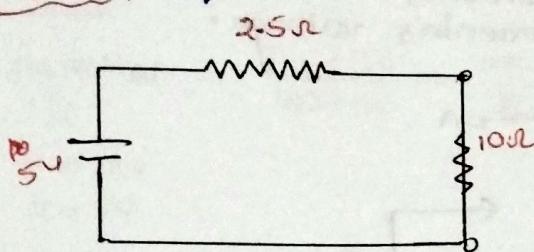

$$I_{10\Omega} = \frac{5}{2.5 + 10} = \frac{5}{12.5} = \underline{0.4 A}$$


====

\* Norton's Theorem:

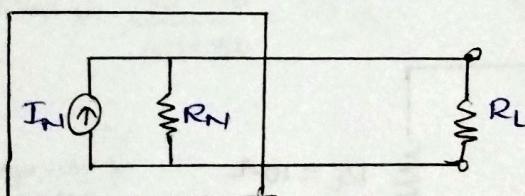


one current source }  
One Resistor } parallel

Example:

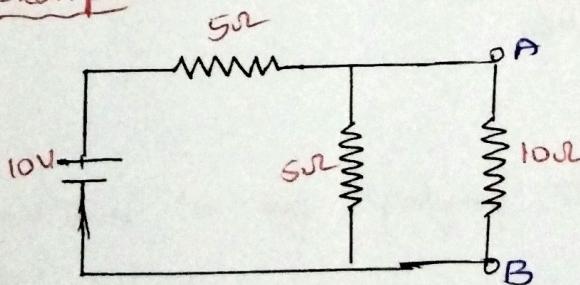

Step-1

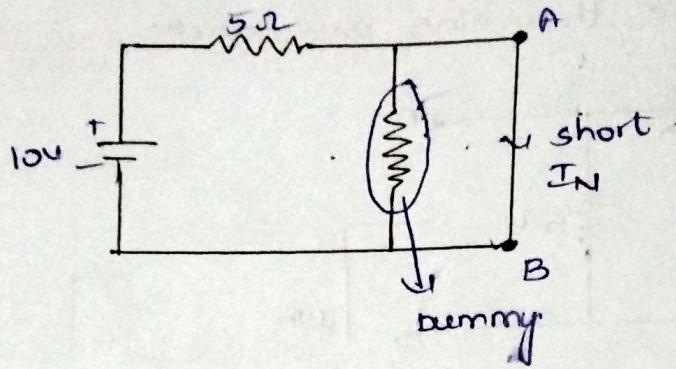
Identify & short the Load Resistor ( $R_L$ ).



Step-2 : calculate the current  $I_N$ .


$$\Rightarrow I_N = \frac{V}{R} = \frac{10}{5} = \underline{\underline{2A}}$$

Step-3 : calculate Thevenin's voltage.

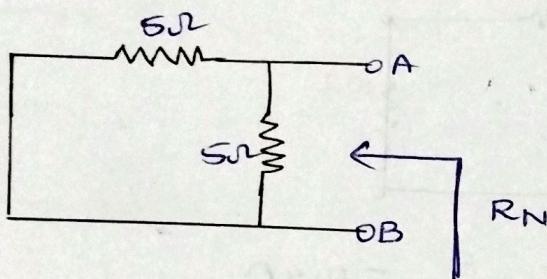

$$R_N = 2.5\Omega \quad [\because R_V = \frac{5 \times 5}{5+5}]$$

Step-4 : Equivalent circuit

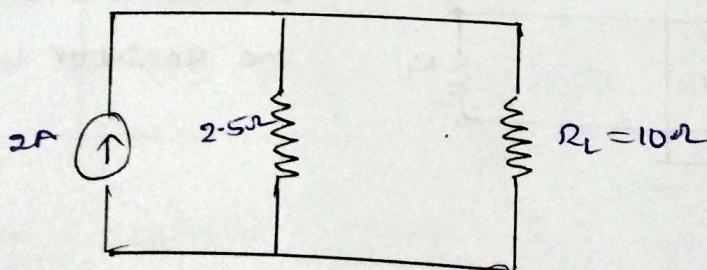


$$I_{10\Omega} = 2 \times \left( \frac{2.5}{2.5+10} \right)$$

$$I_{10\Omega} = \frac{5}{12.5}$$

$$\therefore I_{10\Omega} = \underline{\underline{0.4A}}$$
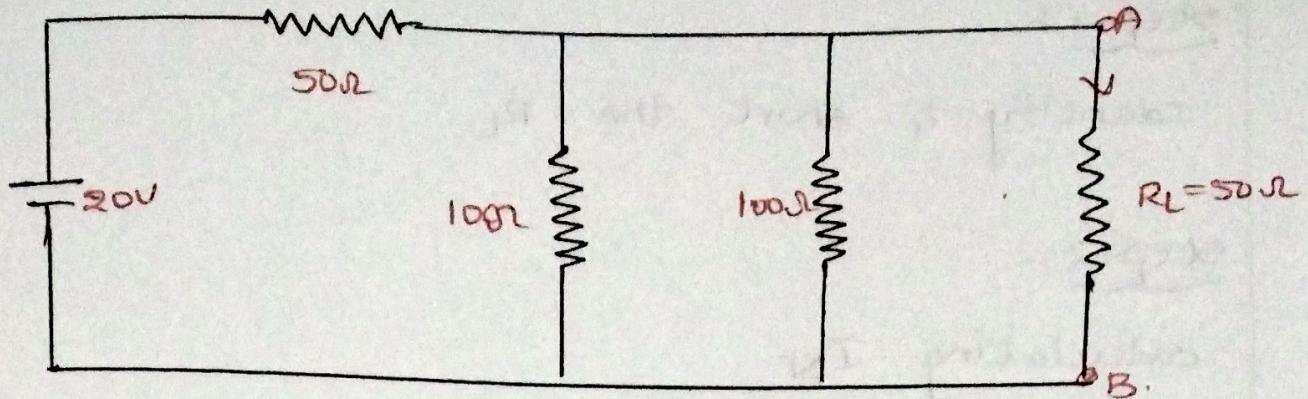
$$I_{\text{Thevenin's}} = I_{\text{Norton's}}$$



Find  $I_L = ?$

A) Step-1 :-

Identify & Remove  $R_L$ .

Step-2 :-

$$\text{parallel} = \frac{100 \times 100}{100+100} = \frac{50}{200} = 50 \Omega$$

$$V = 20$$


$$R = 50$$

$$\therefore I = \frac{20}{100} = 0.2 \text{ A} \quad I_{100\Omega} = (0.2) \times \left( \frac{100}{100+100} \right) = 0.1$$

$$\therefore V_R = IR = (0.1) \times 100 = \underline{\underline{10 \text{ V}}}$$


Step-3 :-
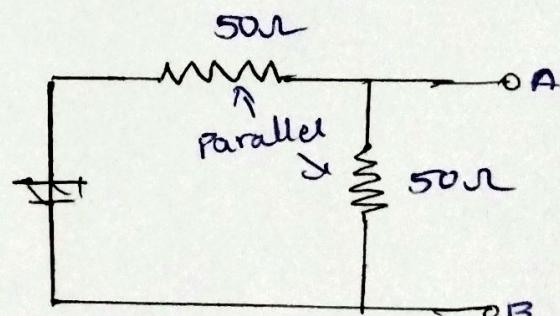
$$R_{th} = \frac{50 \times 50}{50+50} = \underline{\underline{25 \Omega}}$$



Step-4 :-


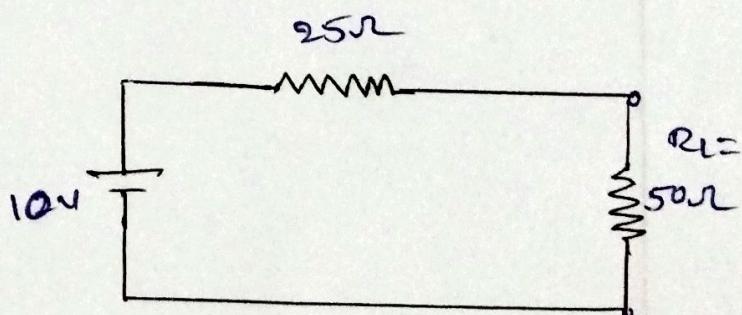
$$I_L = \frac{10}{50+25} = \frac{10}{75} = \underline{\underline{0.13 \text{ A}}}$$



## \* Maximum Power Transfer Theorem :-

→ In a given circuit, we can draw maximum power, when load resistance is equal to internal resistance of all the sources.

Ex:-

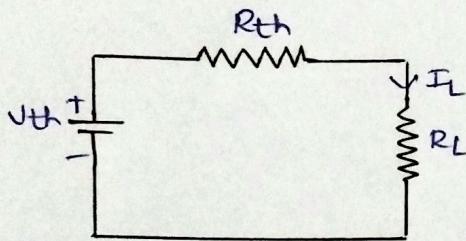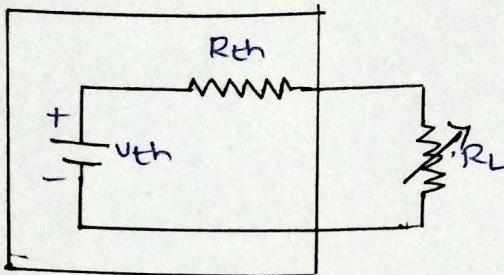

$$I_L = \frac{v_{th}}{R_{th} + R_L} \rightarrow ①$$

$$\text{power, } P = I_L^2 R_L \rightarrow ②$$

From ① & ②

$$\Rightarrow P = \frac{(v_{th})^2}{(R_{th} + R_L)^2} R_L \rightarrow ③$$

For maximum power,  $\frac{dP}{dR_L} = 0$ .

$$\Rightarrow (v_{th})^2 \left[ \frac{(R_L + R_{th})^2 (1) - R_L (2(R_L + R_{th})(1+0))}{((R_{th} + R_L)^2)^2} \right] = 0$$

$$\Rightarrow (R_L + R_{th})^2 - 2R_L(R_L + R_{th}) = 0$$

$$\Rightarrow (R_L + R_{th})^2 = 2R_L(R_L + R_{th}).$$

$$\Rightarrow R_L + R_{th} = 2R_L.$$

∴  $R_{th} = R_L$ . → When  $R_L = R_{th}$ , we can draw maximum power.