

Series R L C Circuit

Exp. No:

Date:

Aim: To study the behaviour of series R-L-C circuit.


Apparatus required:

S.No	Name of the equipment	Range/ Specification	Type	Quantity
1	Voltmeter	(0-150) V	MI	3
2	Voltmeter	(0-300) V	MI	1
3	Ammeter	(0-5) A	MI	1
4	Wattmeter	150V, 5A,UPF	EDW	1
5	Rheostat	100 Ω , 5A	Wire wound	1
6	Inductor	35mH	Core type	1
7	Capacitor	72 μ F, 440V	Electrolytic	1
8	1- Phase Auto Transformer	I/P:1- ϕ , 230V O/P: (0-270)V,10A	Core type	1
9	Connecting wires	1.5sq.mm	copper	Required

Procedure:

1. Connect the circuit as shown in the circuit diagram.
2. Adjust the rheostat for maximum resistance position and the auto transformer to the position of zero-output voltage and switch on the supply.
3. Adjust the voltage across the circuit to about 120 V by varying 1- ϕ auto transformer and note down the corresponding meter values i.e: V_s , I_L , W , V_R , V_L , V_C .

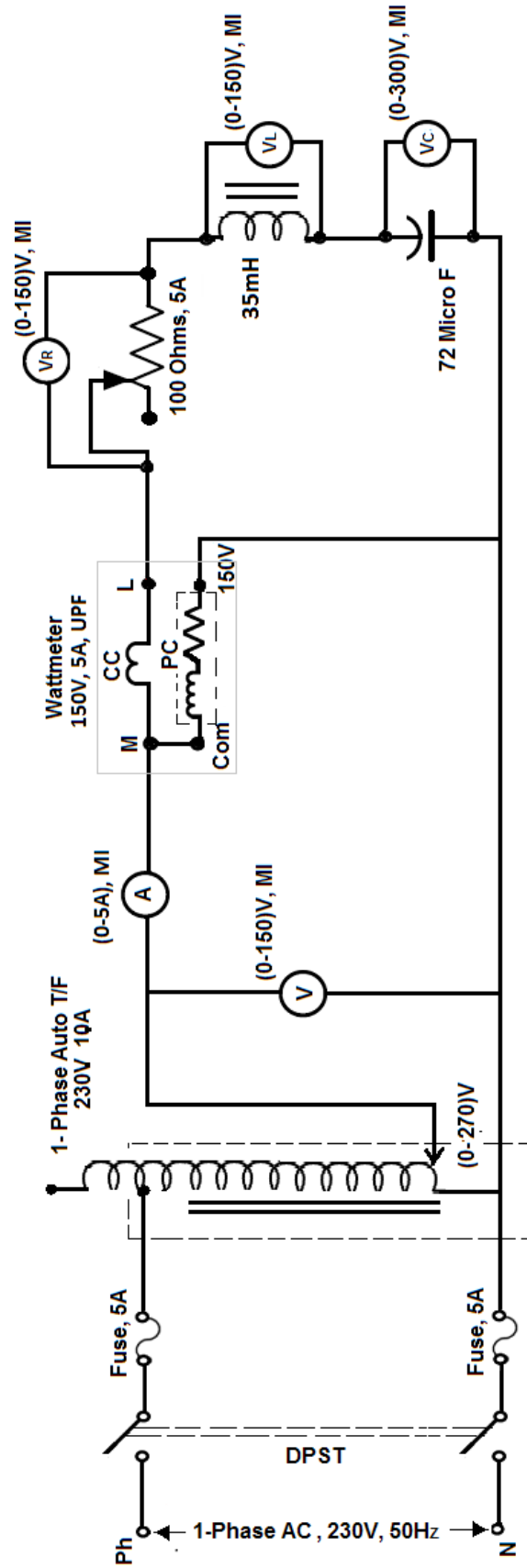4. Adjust the rheostat for several resistance value settings and note down the corresponding meter values.
5. Draw Phasor diagrams showing V_R , V_L , V_C , V_S , and ϕ for different sets of readings.
6. Compare the values of phase angle as obtained from the meter readings with the values obtained from the phasor diagrams.



Circuit diagram for R-L-C Series Circuit

Observation table:

S.No	V _s Volts	I _L Amps	W (Watt)	V _R (v)	V _L (v)	V _C (v)	V _s .I (VA)	Cos ϕ =W/ (V _s .I)	Phase angle ϕ	ϕ From Phasor diagram

Theoretical calculations:

Inductive Reactance, $X_L = 2 \pi f L$

Capacitive Reactance, $X_C = \frac{1}{2 \pi f C}$

Circuit Impedance, $Z = \sqrt{R^2 + (X_L - X_C)^2}$

Circuits Current, $I = \frac{V_s}{Z}$

Voltages across the Series RLC Circuit, V_R, V_L, V_C.

$$V_R = IR$$

$$V_L = I X_L$$

$$V_C = I X_C$$

Circuits Power factor and Phase Angle, θ .

$$\cos \theta = \frac{R}{Z}$$

Apparent Power in VA $S = V_S I$

Active Power in Watts $P = V_S I \cos \theta$

Resonant Frequency of the circuit, $f_0 = \frac{1}{2\pi\sqrt{LC}}$

Q- Factor, $Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}}$

Precautions:

1. All the connections should be tight.
2. Use proper ranges of the meters.
3. Take the readings without parallax error

Result: