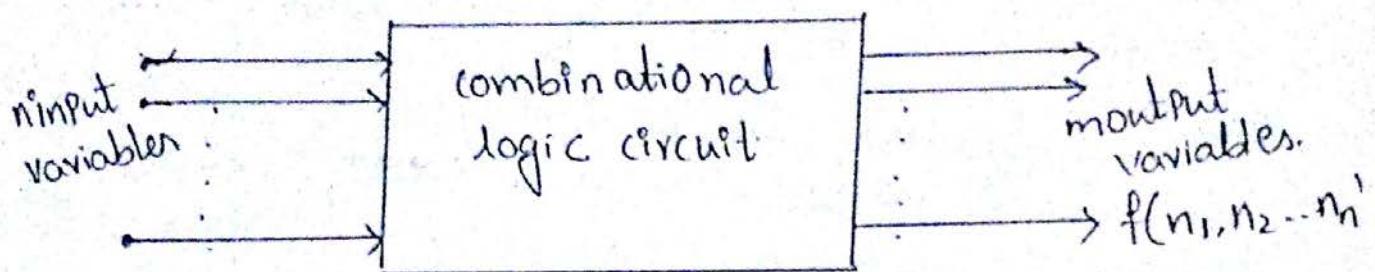


DLD

gate level minimization and combination circuits.

combinational circuits:

A combinational circuit consists of logic gates whose outputs at any time are determined directly from the present combination of input without regard to previous inputs and previous outputs, i.e. no need of memory.



A combinational circuit consists of input variables, logic gates & output variables. Logic gate accept signals from the inputs generate signals to the outputs. The input and output data are represented by binary signals (logic 1 or logic 0).

Minimization of functions or at Gate level:

Minimization of switching functions $f(x_1, x_2, \dots, x_n)$ is to find an expression $g(x_1, x_2, x_3, \dots, x_n)$ which is equivalent to f which minimizes cost criteria. There are various techniques to determine to determine minimum cost. The most common are:

- 1) Minimum number of appearance of literals (literal in a variable if appears in complemented and uncomplemented form) in the function.
- 2) Minimum no. of literals in sum of products or products of sum.

$$\begin{aligned}
 3-f(x,y,z) &= x'y'z + x'y'z' + xy'z' + x'yz + xyz + x'y \\
 &= x'y'z + xy'z + x'yz + xyz + x'y'z' - ① \\
 &\quad y'z(x+x') + yz(x+x') + xyz \\
 &= y'z + yz + xyz \\
 &= y'z + yz + xyz - ②
 \end{aligned}$$

Eq. ① is known as Redundant expression in Eq.
known as irredundant function at is equivalent to F.

Boolean functions may be simplified by algebraic method as in above processes. However this procedure of minimization is awkward because it lacks specific rules to predict each succeeding step in the manipulative process. If more number of variables are there it is a tedious process.

Map Method:

The map method provides a simple straight forward procedure for minimizing Boolean functions.

This method may be regarded either as a pictorial form of a truth table or as an extension of the Venn diagram. The map method first proposed by Veitch is slightly modified by Karnaugh is also known as the Veitch diagram or the Karnaugh map.

In fact map represents a visual diagram of all possible ways of function (may be expressed as minterms or maxterms).

Mapping of three variable kmap in SOP Expression

The minterm has '1' o/p value of the function and 0 is there take complement of the variable, 1 is there take uncomplement of the variables and in between variables take AND operation. Between the minterms take OR operation in order to represent.

SOP-format:

AB		C	
0	1	0	1
00	m_0	m_1	
01	m_2	m_3	
11	m_6	m_7	
10	m_4	m_5	

AB		C	
0	1	0	1
00	$\bar{A}\bar{B}C$	$\bar{A}B\bar{C}$	
01	$\bar{A}B\bar{C}$	$\bar{A}BC$	
11	$A\bar{B}\bar{C}$	ABC	
10	$A\bar{B}C$	$A\bar{B}\bar{C}$	

Mapping of three variables kmap in POS expression.

The maxterms are represented having 0 o/p value of the function. 0 is there unprimed variable w 1 is there primed variable in between take OR operation for variables w in between maxterms take AND operation in order to represent POS form.

AB		C	
0	1	0	1
00	$A+B+C$	$A+B\bar{C}$	
01	$A+\bar{B}+C$	$A+\bar{B}+\bar{C}$	
11	$\bar{A}+\bar{B}+C$	$\bar{A}+B+C$	
10	$\bar{A}+\bar{B}+\bar{C}$	$\bar{A}+B+\bar{C}$	

AB		C	
0	1	0	1
00	M_{10}	M_{11}	
01	M_2	M_3	
11	M_6	M_7	
10	M_4	M_5	

Four variable kmap:

Four variable kmap have four variables, so the number of possible combinations are $2^4 = 16$. So the kmap consists of (16 squares) 16 squares.

on column & Row

on column take 2 variables, so four combinations occurs, 00, 01, 11, 10. since kmap uses the Gray code.

	AB
CD	00 01 11 10
00	
01	
11	
10	

on Row take two variables, so four combinations can occur. 00, 01, 11, 10.

combine rows and columns form 4 variable kmap, having 16 number of squares. write the binary value of each square as shown in figure.

	AB
CD	00 01 11 10
00	0000 0100 1100 1000
01	0001 0101 1101 1001
11	0011 0111 1111 1011
10	0010 0110 1110 1010

	AB
CD	00 01 11 10
00	0 4 12 8
01	1 5 13 9
11	3 7 15 11
10	2 6 14 - 10

fig @

Replace the decimal equivalent values of binary values of each square.

Mapping of four variable kmap in SOP Expression.

The minterm has '1' op value of the function and '0' is there take complement of the variable, i.e. if there take uncomplement of the variable and in between variable take AND operation, between the minterms take OR operation.

		AB			
		CD			
		00	01	11	10
00		m_0	m_4	m_{12}	m_8
01		m_1	m_5	m_{13}	m_9
11		m_3	m_7	m_{15}	m_{11}
10		m_2	m_6	m_{14}	m_{10}

		AB			
		CD			
		00	01	11	10
00		$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$A\bar{B}C\bar{D}$	$A\bar{B}C\bar{D}$
01		$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}C\bar{D}$	$A\bar{B}C\bar{D}$	$A\bar{B}C\bar{D}$
11		$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}C\bar{D}$	$A\bar{B}C\bar{D}$	$A\bar{B}C\bar{D}$
10		$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}C\bar{D}$	$A\bar{B}C\bar{D}$	$A\bar{B}C\bar{D}$

MAPPING OF FOUR VARIABLES KMAP IN POS EXPRESSION.

The maxterms are represented has '0' o/p value of the function. 0 is the unprimed variable w, 1 is the there primed variable, in between take OR operation for variables, in between maxterm take 'AND' operation.

		AB			
		CD			
		00	01	11	10
00		M_{10}	M_4	M_{12}	M_8
01		M_1	M_5	M_{13}	M_9
11		M_3	M_7	M_{15}	M_{11}
10		M_2	M_6	M_{14}	M_{10}

		AB			
		CD			
		00	01	11	10
00		$A+B+C\bar{D}$	$A+\bar{B}+C+D$	$\bar{A}+\bar{B}+C+D$	$\bar{A}+B+C+D$
01		$A+B+\bar{C}+\bar{D}$	$A+\bar{B}+\bar{C}+\bar{D}$	$\bar{A}+\bar{B}+\bar{C}+\bar{D}$	$\bar{A}+\bar{B}+\bar{C}+\bar{D}$
11		$A+\bar{B}+\bar{C}+\bar{D}$	$A+\bar{B}+\bar{C}+\bar{D}$	$\bar{A}+\bar{B}+\bar{C}+\bar{D}$	$\bar{A}+\bar{B}+\bar{C}+\bar{D}$
10		$A+\bar{B}+\bar{C}+D$	$A+\bar{B}+\bar{C}+D$	$\bar{A}+\bar{B}+\bar{C}+D$	$A+\bar{B}+\bar{C}+D$

five variable k-map

	ABC \ DE	00	01	11	10			
000	0	00000	1	00001	3	00011	2	00010
001	4	00100	5	00101	7	00111	6	00110
011	12	01100	13	01101	15	01111	14	01110
010	8	01000	9	01001	11	01011	10	01010
110	24	11000	25	11001	27	11011	26	11010
111	28	11100	29	11101	31	11111	30	11110
101	20	10100	21	10101	23	10111	22	10110
100	16	10000	17	10001	19	10011	18	10010

11 row take three variables w on column take two variables.

01 row first write two variables

00

01

11

10

10

11

01

00

00

01

11

01

00

00

01

11

01

00

00

01

11

01

00

00

01

11

01

00


* K-map procedure for minimization.

$$\begin{aligned} P &= AB + A\bar{B} \\ &= A(B + \bar{B}) = A \end{aligned}$$


Two variable kmaps: Two variable kmap.

In two variable kmap, has two variable so the expression can have $2^2 = 4$ possible combinations.

So the map consists of four squares.

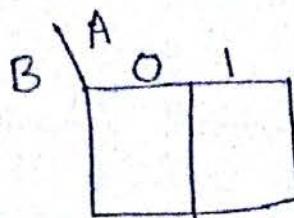

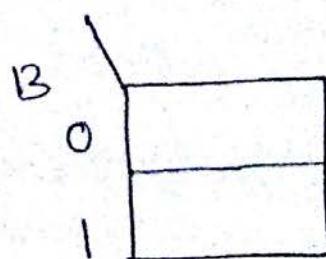→ On the column take the variable as A (one). It is only one variable can occur as either 0 or 1. 0 in column represent 0 & 1. Divide the cell has two parts on column.



→ On the Row take the B variable. It is only one variable can occur as either 0 or 1. so on Row represent 0 & 1. Divide the cell has two parts on the Row.

combine the rows in column of the kmap it forms the two variable kmap, having four squares as in fig(a). write the binary value of each square as shown in fig(a).

	A	B
	0	0
0	00	10
1	01	11

fig(a)

	B
0	0
1	2

fig(b)

Replace the decimal equivalence values of binary value of each square.

MAPPING OF TWO VARIABLE IN SOP EXPRESSION.

	A	B
	0	1
0	0	$\bar{A}\bar{B}$
1	0	$\bar{A}B$
0	1	$A\bar{B}$
1	1	AB

	B
0	m_0
1	m_1
2	m_2
3	m_3

The minterms are represented by '1' in SOP function
 0 — Primed or complemented
 1 — uncomplemented
 In between variables take AND operation.

These squares are called cells. Each square on the Kmap represents a unique minterm. SOP form = $m_0 + m_1 + m_2 + m_3$.

MAPPING OF TWO VARIABLES IN POS EXPRESSION.

	A	B
	0	1
0	0	$(A+B)$
1	0	$(A+\bar{B})$
0	1	$(\bar{A}+B)$
1	1	$(\bar{A}+\bar{B})$

The maxterms are represented by '0' in POS function.
 0 — unprimed or uncomplemented variable
 1 — complemented or primed variable.
 In between variables take OR operation.

	A	B
	0	1
0	0	M_0
1	0	M_1
0	1	M_2
1	1	M_3

POS FORM $M_0 \cdot M_1 \cdot M_2 \cdot M_3$.

Three variable kmap.

Three variable kmap have three variables so the number of possible combinations are $2^3 = 8$. So the kmap consists of 8 squares.

on column

AB \ C	0	1
00		
01		
11		
10		

on the column take one variable on the Row take two variables.

on the column one variable can occur as either '0' or '1'. Divide the cell has two parts on column as shown in fig,

on Row

AB \ C	0	1
00		
01		
11		
10		

on the Row take two variables so four combinations are there, 00, 01, 11, 10. The kmap is represented or uses the cyclic code or ~~unit distance~~ code. Cyclic code means two consecutive numbers differ in only one bit position. Cyclic codes are unit distance code.

combine rows and columns form 3 variable kmap having 8 number of squares. write the binary value of each square as shown in fig(a)

AB \ C	0	1
00	000	001
01	010	011
11	110	111
10	100	101

fig(a)

AB \ C	0	1
00	0	1
01	2	3
11	6	7
10	4	5

fig(b)

Replace the decimal equivalent value of binary valued of each square.

1. The O/P of a function is not able to predict one or don't care.
2. For certain input combinations, can't occur or invalid if then the O/P of the function are indicated as don't care.
3. Don't care terms are denoted by X, d or D.
4. Don't care value can be either '0' or '1' since it is unspecified value.

Minimization of switching functions:

For reducing the Boolean expressions in SOP or POS form on the K-map, look at the 1's (0's) present on the map. These represent the minterms (maxterms). Look for the minterms (maxterms) adjacent to each other, in order to combine them into larger squares.

Combining of adjacent squares in a K-map containing 1's or 0's for the purpose of simplification of a SOP or (POS) expression is called looping.

Some of the minterms (maxterms) may have many adjacencies always start with the minterm (maxterm) with the least number of adjacencies and try to form as large as a square possible and number of minterms are grouped or looping in 2^n .

The cells are said to be adjacent if they differ by only one cell.

adjacent cells: The cells are said to be adjacent if they differ by one bit.

Ex 001, 011 these two cells are adjacent since only one bit changes.

The Kmap uses the Gray code. So ^{those} every cells are side by side they are adjacent & corner cells are also adjacent to each other.

Grouping of cells:

→ Grouping of cells are done if they are adjacent to each other.

→ In grouping the number of cells should be 2^n . i.e $2^0, 2^1, 2^2, 2^3, 2^4, 2^5, \dots, 2^n$.

→ Always try to form large group i.e 2^n we have to check first, $2^{n-1}, \dots$ w 32 no. of cells check not possible try to form group for 16 not possible check for 8, \dots at last form as 1

- If 1 cell is there then the group is called as 'isolated'
- If 2 cells are grouped then the group is called as 'Pairs'
- If 4 cells are grouped then the group is called as 'quad'

- If 8 cells are grouped then the group is called as 'octets'

Finding Procedure for minimal form:

minimization by map procedure.

$$f = AB + A\bar{B}$$

$$= A(B + \bar{B}) = A$$

Here B variable is changed the value in a variable has a constant value. So eliminate the changed variable

and unchanged variable will be there in the o/p. ie check the number of minterms or maxterms.

minimal form of SOP.

The value of variable is changed then eliminate variable in minimal form of SOP.

The value of variable is unchanged then write the variable in minimal form as if '1' is there unprimed variable if '0' is there then primed variable. In between variables we 'And' operation are known as minterms & between minterms we OR operation.

minimal form of POS.

The value of variable is changed then eliminate variable in minimal form of SOP.

The value of variable is unchanged then write the variable in minimal form as if '1' is there primed variable & if '0' is there the unprimed variable. In between variables we OR operation are known as Maxterms & between maxterms we AND operation.

steps to find minimal form by using kmap.

1. check for maximum number of minterm or maxterm value depending on that choose noimber of variable kmap required.

2. Plot the kmap.

3. If minterms are given plot place value '1' ^{in k-map} corresponding value ~~given~~ of cell.

Maxterm are given then place value '0' ^{in k-map} corresponding value of cell.

Don't care are given the place 'd' 'x' 0 in kmap corresponding value of cell.

check for adjacent cells, try to form larger group and the number of cells should be 2^n . ($2^0, 2^1, \dots, 2^5, 2^4, 2^3, 2^2, 2^1, 2^0$)

5. Name groups as $S_1, S_2, S_3, \dots, S_n$. If group contains minterms or minimal maxterms.
6. Check positions of cells grouped in row wise or column wise, eliminate changed variable whose value is change. write the variable whose value is constant or not changed.
7. If minterms are used then write minimal form SOP.
8. By using procedure as '1' is there unprimed variable 'o' is there primed variable in between take 'AND' operation so we get minimal minterms w/ between minterms take OR operation forms minimal SOP form.

If maxterms are used in kmap write minimal form SOP By using procedure as '1' is ther primed variable, 'o' is there unprimed variable in between take 'OR' operation so we get minimal maxterms w/ between maxterms take AND operation forms minimal POS form.

Note

1. In Kmaps '1's & '0's are must to be covered in any one of the group.
2. Don't care are need not to be covered, if they are required to form larger group utilize them, ~~otherwise~~ ~~not~~ cover and form a group. otherwise donot cover ther them.
3. Always try to them cover larger more number of '1' or '0' w/ for try to form larger group.

Problems

without don't care condition.

$$① f = \bar{A}B + A\bar{B} + AB$$

The above expression is in the form of SOP.

$$f = \bar{A}B + A\bar{B} + AB$$

① minterm $\rightarrow \bar{A}B \Rightarrow 01 \Rightarrow 1$
 ② minterm $\rightarrow A\bar{B} \Rightarrow 10 \Rightarrow 2$
 ③ minterm $\rightarrow AB \Rightarrow 11 \Rightarrow 3$

$$f = \varepsilon(1,2)$$

Step-1 It requires two variable k-map.

step-2

A	B	
0	0	1
1	2	3

Step-3

A	B	O
O		I
I	I	I

place 1
in 4 2,3
place

step-~~up~~

The diagram shows a 2x2 matrix switch. The top row has two columns labeled '0' and '1'. The bottom row has two columns, each containing a switch symbol. The left column of the bottom row is labeled '0' and the right column is labeled '1'. An input line labeled 'A' enters from the top-left and connects to the top of the first column. An input line labeled 'B' enters from the top and connects to the top of the second column. The bottom-left switch is connected to an output line labeled S_1 . The bottom-right switch is connected to an output line labeled S_2 .

And S_4 group formed.

cells (1,3) are adjacent to each other. at groupname is S₂

Step 5

\ Pairs are formed $S_1 = (2, 3)$
 $S_2 = (1, 3)$.

cells $(2,3)$ are adjacent to each other.

(10,11) only one bit change
so they are adjacent to
each other.

6

check positions of cells grouped in row wise w column wise. eliminate variable whose value is changed. write the variable whose value is constant or not changed.

S_1 covered the positions (2, 3)

Step-7
Row wise

$A = 1$ constant (not changed) There are minterms A o A columnwise

$B = (0, 1) \rightarrow$ changed value no eliminate B variable
 $\begin{matrix} 0 \\ 1 \end{matrix}$

$S_1 = A$.

S_2 covered the positions (1, 3)

Row wise

$\begin{matrix} A \\ 0 \\ 1 \end{matrix}$ changed value eliminate

columnwise B no unchanged value, comes at 0/p.

$S_2 = B$

SOP form $S_1 + S_2 = A + B$.

minimal form $S_1 + S_2 = A + B$.

$$\textcircled{2} \quad F(x, y, z) = \Sigma(3, 4, 6, 7)$$

Step-1

Σ is given nothing expression is SOP form. The maximum number of minterm is 7. so 3 variable kmap is required.
 $\therefore 2^3 = 8$.

Step-2

Plot the k-map.

$x \backslash y^2$	00	01	11	10
0	0	1	3	2
1	4	5	7	6

Step-3 4 4 4 5

$x \backslash y^2$	00	01	11	10
0	00	01	11	10
1	11	11	11	11

Step-6 4 7 S_1 Pair $\rightarrow (4, 6)$ Row $x=1$ constant $\Rightarrow x$

ON column

y^2	00	01
0	0	0
1	0	0

 y unchanged eliminate w z is const. $z=0 \Rightarrow \bar{z} \Rightarrow$

$$S_1 = x \cdot \bar{z}$$

 S_2 Pair $\rightarrow (3, 7)$ Row
 ~~x~~ ~~y^2~~ $x, \neq 0$ y changed eliminate

ON column

 ~~y^2~~ y unchanged $\Rightarrow yz$.

$$S_2 = y \cdot z$$

Minimal SOP form is $S_1 + S_2 = x \cdot \bar{z} + yz$

- ③ $F = A'c + A'B + AB'C + Bc$. find the minimal sop form by using k-map.

The above expression is not a canonical form. The above expression has to change into canonical form.

Step-4 check for adjacent cells try to form larger group
 $\rightarrow (1, 3, 5, 7) \Rightarrow$ Quad.
 $\rightarrow (3, 2) \rightarrow$ Pair

Step-5 Name the group

		BC	
		00	01
A	0	1	1
	1	1	1

$$S_1 = (1, 3, 5, 7) \Rightarrow \text{Quad}$$

$$S_2 = (3, 2) \Rightarrow \text{Pair}$$

Step-6 w/f

S_1 \Rightarrow on Row A, $\{0\}$ changed eliminate

on column BC, $\{0\}$ \Rightarrow B unchanged w/c is constant $\Rightarrow C=1$.

$$S_1 = C$$

S_2 group (2, 3)

on Row A, $\{1\}$ unchanged $A=0 \Rightarrow \bar{A}$

on column BC, $\{1\}$ \Rightarrow C is changed w/B is constant
 $\{1\}$ \Rightarrow B=1 \Rightarrow B.

$$S_2 = \bar{A} \cdot B$$

minimal SOP in $S_1 + S_2 = C + \bar{A} \cdot B$.

$$④ F = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13)$$

Step-1 The maximum number is 13 so it requires four variable k-map.

The expression is said to be canonical form if it has all variables of a function. The function have three variables so that every minterm should have three variables.

$$A'C \cdot 1 + A'B \cdot 1 + \overbrace{ABC}^{\text{emissing}} + B'C \cdot 1$$

L.B missing L.A missing.

By Idempotency law $A+A'=1$.

$$\begin{aligned} & A'C(B+\bar{B}) + A'B(C+C) + AB'C + BC(A+A') \\ & \overbrace{A'B'C}^1 + \overbrace{A'B'C}^2 + \overbrace{A'BC}^3 + \overbrace{A'BC'}^4 + \overbrace{AB'C}^5 + \overbrace{ABC}^6 + \overbrace{ABC}^7 \end{aligned}$$

$1=7=3$ — write only once

$$\Rightarrow \overbrace{A'B'C}^1 + \overbrace{A'B'C}^2 + \overbrace{A'BC}^3 + \overbrace{AB'C}^4 + \overbrace{ABC}^5$$

1 minterm $A'B'C \Rightarrow 011 \Rightarrow 3$

primed - 0
unprimed - 1

2 , , $A'B'C \Rightarrow 001 \Rightarrow 1$

3 , , $AB'C' \Rightarrow 010 \Rightarrow 2$

4 , , $AB'C \Rightarrow 101 \Rightarrow 5$

5 , , $ABC \Rightarrow 111 \Rightarrow 7$

$$f = \Sigma(1, 2, 3, 5, 7).$$

Step-1 check maximum number $\rightarrow 7 \Rightarrow 3$ variables reqd.

Step-2 Plot 3-kmap.

		BC	
		00	01
A	0	0	1
	1	4	5
		11	2
		7	6

Step-3

		BC	
		00	01
A	0	00	01
	1	11	11
		11	11

	CD	00	01	11	10
00		0	1	3	2
01		4	5	7	6
11		12	13	15	14
10		8	9	11	10

	CD	00	01	11	10
00		1	1	1	1
01		1	1	1	1
11		1	1	1	1
10		1	1	1	1

Step-5

$$S_1 \Rightarrow (0, 1, 4, 5, 8, 9, 12, 13) \rightarrow \text{octet}$$

$$S_2 \Rightarrow (0, 2, 4, 6) \Rightarrow \text{quad}$$

Step-6.

$$S_1 = (0, 1, 4, 5, 8, 9, 12, 13)$$

on Row

AB	C D
00	0 0
01	0 1
11	1 0

A value w/ B value are changed eliminate.

on column

C D	A B
0 0	0 0
0 1	0 1

D unchanged w/ C is const. $C=0 \Rightarrow \bar{C}$

$$S_1 = \bar{C}$$

$$S_2 = (0, 2, 4, 6)$$

on Row

AB	C D
00	0 0
01	0 1

B is changed w/ A is const. $A=0 \Rightarrow \bar{A}$

on column

C D	A B
0 0	0 0
0 1	0 1

C is changed w/ D is constant. $D=0 \Rightarrow \bar{D}$

$$\Rightarrow \bar{A} \cdot \bar{D}$$

$$S_2 = \bar{A} \cdot \bar{D}$$

minimal SOP in $S_1 + S_2 = \bar{C} + \bar{A}\bar{D}$

$$F = A'B'C' + B'C'D' + A'BCD' + AB'C'$$

The above expression is not a canonical form convert S_1 , S_2 into standard or canonical form.

$$F = A'B'C'D' + \overset{\rightarrow \text{Amining}}{1 \cdot B'C'D'} + \overset{\rightarrow \text{Amining}}{A'BCD'} + \overset{\rightarrow \text{Amining}}{AB'C' \cdot 1} \quad \text{L Dismining.}$$

$$\Rightarrow \begin{aligned} &= A'B'C'(D+D) + (A+A')B'C'D' + A'BCD' + AB'C'(D+D') \\ &= \underbrace{A'B'C'D}_{1} + \underbrace{A'B'C'D'}_{2} + \underbrace{A'BCD'}_{3} + \underbrace{A'B'C'D'}_{4} + \underbrace{A'BCD'}_{5} + \underbrace{A'B'C'D}_{6} + \underbrace{AB'C'D}_{7} \end{aligned}$$

- ① minterm $A'B'C'D \Rightarrow 0001 \Rightarrow 1$
- ② ... $A'B'C'D' \Rightarrow 0000 \Rightarrow 0$
- ③ ... $A'B'C'D' \Rightarrow 1010 \Rightarrow 10$
- ④ ... $A'B'CD' \Rightarrow 0010 \Rightarrow 2$
- ⑤ ... $A'BCD' \Rightarrow 0110 \Rightarrow 6$
- ⑥ ... $A'B'C'D \Rightarrow 1001 \Rightarrow 9$
- ⑦ ... $A'B'C'D' \Rightarrow 1000 \Rightarrow 8$

$$F = \Sigma(0, 1, 2, 6, 8, 9, 10)$$

Step-1 2 4 9 3 14

		CD			
		00	01	11	10
AB	00	0 1	1 1	3 2	1 1
	01	5 4	7 6	15 16	1 1
11	12 13	13 14	15 16	16 17	1 1
10	11 12	11 13	11 15	10 16	1 1

P-6, 7

$$\begin{aligned} S_1 &= (0, 1, 8, 9) \Rightarrow \text{quad} \\ S_2 &= (0, 2, 8, 10) \Rightarrow \text{quad} \\ S_3 &= (2, 6) \Rightarrow \text{Pair.} \end{aligned}$$

 S_1 group (0, 1, 8, 9)on Row

$$\begin{array}{c} AB \\ 00 \\ 10 \end{array} \left. \begin{array}{l} A \text{ is changed} \\ B \text{ is const.} \end{array} \right\} B=0 \Rightarrow \bar{B}$$

$$S_1 = \bar{B} \cdot \bar{C}$$

on column

$$\begin{array}{c} CD \\ 00 \\ 01 \end{array} \left. \begin{array}{l} C \text{ is changed} \\ C=0 \Rightarrow \bar{C} \end{array} \right\} C \text{ is const.}$$

 S_2 group (0, 2, 8, 10)on Row

$$\begin{array}{c} AB \\ 00 \\ 10 \end{array} \left. \begin{array}{l} A \text{ is changed} \\ B \text{ is const.} \\ B=0 \Rightarrow \bar{B} \end{array} \right\}$$

$$S_2 = \bar{B} \cdot \bar{D}$$

on column

$$\begin{array}{c} CD \\ 00 \\ 10 \end{array} \left. \begin{array}{l} C \text{ is changed} \\ D \text{ is constant} \\ D=0 \Rightarrow \bar{D} \end{array} \right\}$$

$S_3 \Rightarrow$ minimal SOP form is $S_1 + S_2 + S_3 = \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}\bar{C}\cdot\bar{D}$

 S_3 group (2, 6)on Row

$$\begin{array}{c} AB \\ 00 \\ 01 \end{array} \left. \begin{array}{l} B \text{ is changed} \\ A \text{ is const.} \\ A=0 \Rightarrow \bar{A} \end{array} \right\}$$

$$S_3 = \bar{A} \cdot C \cdot \bar{D}$$

on column

$$\begin{array}{c} CD \\ 00 \\ 10 \end{array} \left. \begin{array}{l} \text{const} \\ C=1, D=0 \Rightarrow \bar{CD} \end{array} \right\}$$

$$\text{minimal SOP } S_1 + S_2 + S_3 = \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}C \cdot \bar{D} = F$$

$$f = (0, 1, 2, 3, 4, 5, 8, 9, 10, 11, 12, 13)$$

Step-1, 2, 3, 4

AB \ CD	00	01	11	10	$\rightarrow S_2$
00	1 1	3 1	2 1		
01	4 1	5 1	6 1		
11	12 1	13 1	15 1	14 1	
10	11 1	11 1	10 1		

Step-5, 6, 7

$$S_1 = (0, 1, 4, 5, 8, 9, 12, 13) = \bar{C}$$

$$S_2 = (0, 1, 2, 3, 8, 9, 10, 11) \Rightarrow \bar{B}$$

$$S_1 = \bar{C}$$

$$S_2 = \bar{B}$$

$$\text{minimal SOP in } S_1 + S_2 = \bar{B} + \bar{C} = f$$

$\rightarrow f(A, B, C, D, E) = (0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$

Step-1, 2, 3, 4

ABC \ DE	00	01	11	10	S_1
0 00	0 1	1	3	2	
0 01	4 1	5	7	6 1	
0 11	12	13 1	15	14	
0 10	8	9 1	11	10	
1 10	24	25 1	27	26	
1 11	28	29 1	31 1	30	S_2
1 01	20	21 1	23 1	22	
1 00	16	17	19	18	

$$S_1 = (0, 2, 4, 6)$$

$$S_1 = \bar{A} \bar{B} E$$

$$S_2 = (9, 13, 25, 29)$$

$$S_2 = B \cdot \bar{D} E$$

$$S_3 = (21, 23, 29, 31)$$

$$S_3 = A C E$$

$$\text{minimal SOP in } S_1 + S_2 + S_3$$

$$A' B' E' + B D' E + A C E = f$$

n. don't cover:

$$f(w, x, y, z) = \Sigma(1, 3, 10) + \Sigma_d(0, 2, 8, 12)$$

step-1, 2, 3, 4

		CD		00		01		11		10		
		AB		00	01	11	10	11	10	10	11	
		00		d	1	1	1	1	d			S_1
		01		4	5	7	6					
		11		d	13	15	14					
		10		8	d	9	11	10	1			S_2

step, 5, 6, 7

$$S_1(0, 1, 2, 3)$$

$$S_1 = \bar{A}B$$

$$S_2(0, 2, 8, 10)$$

$$S_2 = \bar{B}\bar{D}$$

minimal SOP is $S_1 + S_2$

$$\bar{A}\bar{B} + \bar{B}\bar{D}$$

Note: Don't cover are need not to be covered. If they are required to form larger group utilize them to form a group. otherwise don't cover them.

i.e why 12 minterm don't care is left as it is ungrouped it.

→ But in kmaps '1's '0' are must to be covered in any one of the group.

$$\Rightarrow f(x, y, z) = \Sigma(2, 3, 4, 6, 7) + \Sigma_d(x, y, z).$$

solution
 Σ_d

$$x \cdot 1 \cdot 1 + y \cdot 1 \cdot 1 + 2 \cdot 1 \cdot 1 \rightarrow y_{\min}$$

$\swarrow 2^{\text{missing}}$ $\swarrow 2^{\text{missing}}$ $\swarrow y_{\min}$

$\swarrow y_{\min}$ $\swarrow x_{\min}$ $\swarrow x_{\min}$

$$x(y+z)(z+\bar{z}) + (x+\bar{x})y(z+\bar{z}) + 2(x+\bar{x})(y+\bar{y})$$

$$(xy+x\bar{y})(z+\bar{z}) + (xy+\bar{x}y)(z+\bar{z}) + 2x+2\bar{x}(y+\bar{y})$$

$$= xyz + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z} + \bar{x}yz + \bar{x}y\bar{z} + \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z}$$

$$+ xyz + x\bar{y}z + \bar{x}yz + \bar{x}\bar{y}z.$$

$$= 111 + 110 + 101 + 100 + 111 + 110 + 011 + 010$$

$$+ 111 + 101 + 011 + 001$$

$$= 7 + 6 + 5 + 4 + 7 + 6 + 3 + 2 + 7 + 6 + 3 + 1$$

$\Sigma d = \{1, 2, 3, 4, 5, 6, 7\}$ but the minterms are $\{2, 3, 4, 6, 7\}$ no eliminate the minterms $\{1, 5\}$ group don't cover.

$$\Sigma m(2, 3, 4, 6, 7) + \Sigma d(1, 5) = f$$

y_2

		00	01	11	10		
		0	1	0	1	2	S_1
		1	1	0	1	1	$S_1 = 1$
		0	1	0	1	2	

Minimize the following Boolean function.

$$Y(A, B, C, D) = \Sigma m(1, 3, 5, 8, 9, 11, 15) + \Sigma d(2, 13).$$

Step-1, 2, 3

The function requires four variable kmap.

Plot 4-kmap

y_2

		00	01	11	10	
		0	1	3	2	\emptyset
		1	4	5	6	S_1
		12	11	15	14	
		8	1	1	10	S_2
		1	1	1	1	S_3
		1	1	1	1	S_4

Step-4, 5

$S_1(1, 5, 9, 13)$ forms quad

$S_2(9, 11, 13, 15)$ forms quad

$S_3(1, 3, 9, 11)$ forms quad

$S_4(8, 9)$ forms pair.

S₁ group (1, 5, 9, 13)

Row $\begin{matrix} AB \\ 00 \\ 01 \\ 11 \\ 10 \end{matrix}$ } changed eliminate $A \oplus B$

column $\begin{matrix} CD \\ 01 \\ 10 \end{matrix}$ } const $\Rightarrow \bar{C}D$.

$$S_1 = \bar{C}D$$

S₂ On Row: $\begin{matrix} AB \\ 11 \\ 10 \end{matrix}$ } A is const $A = 1 \Rightarrow A$ on column $\begin{matrix} CD \\ 00 \\ 01 \end{matrix}$ } C = const $C = 0 \Rightarrow \bar{C}$

$$S_2 = A \cdot \bar{C}$$

S₃ (1, 3, 9, 11)

on Row $\begin{matrix} AB \\ 00 \\ 10 \end{matrix}$ } B = const $B = 0 \Rightarrow \bar{B}$

on column $\begin{matrix} CD \\ 01 \\ 11 \end{matrix}$ } D is const $D = 1 \Rightarrow D$

$$S_3 = \bar{B} \cdot D$$

S₄ (8, 9)

on Row $\begin{matrix} AB \\ 10 \end{matrix}$ } $A \cdot \bar{B}$

on column $\begin{matrix} CD \\ 00 \\ 01 \end{matrix}$ } $\Rightarrow C = \text{const} \Rightarrow C$

$$S_4 = A \bar{B} \cdot C$$

minimal form of SOP is $S_1 + S_2 + S_3 + S_4 = \bar{C}D + A\bar{C} + \bar{B}D + A\bar{B}C$

Minimal Form for POS

$$f(A, B, C, D) = \overline{\pi}(1, 2, 3, 8, 9, 10, 11, 14) \cdot \overline{\oplus d}(7, 15).$$

Solution:

step 1: Max no. is 15 to represent we require four variable kmap.

Step-2 Plot 4k-map.

		AB	CD		
		00	01	11	10
00	00	0	1	3	2
	01	4	5	7	6
11	10	12	13	15	14
	11	8	9	11	10

Step-3

Given symbol in π it represents these are don't care
are represented by value '0'

Step-4 4.5

AB \ CD	00	01	11	10	S2
00	0	10	0	0	0
01	4	5	d	6	
11	12	13	c	14	$\rightarrow S_4$
10	5	0	0	0	$\rightarrow S_3$

Step-5

S_1 forms $(8, 9, 10, 11) \rightarrow$ quad

S_2 $(2, 3, 10, 11) \rightarrow$ quad

S_3 $(9, 11, 1, 3) \rightarrow$ quad

S_4 $(10, 11, 14, 15) \rightarrow$ quad.

Step-6

The given terms are maxterms No ~~if~~ variables have value of '1' represents Primed variable if variable value '0' represents unprimed variable, between variable take OR operation w/ between maxterm or groups we 'And' operation.

 S_1

Row

AB y unchanged $A=1 B=0 \Rightarrow (\bar{A}+B)$

column CD 00, 01, 11, 10 \rightarrow changed eliminate.

$$S_1 = \bar{A}+B$$

group (2, 3, 10) 11)

on Row

$\bar{A}B$	\bar{B}	A is changed w/ B is const
00	0	
10	1	$B=0 \Rightarrow B$

$S_2 = B + \bar{C}$

on column

$\bar{C}\bar{D}$	\bar{C}	C is const w/ D is changed
11	1	
10	0	

$C=1 \Rightarrow \bar{C}$

S_3 on Row (9, 11, 1, 3)

$\bar{A}B$	\bar{B}	A is changed w/
00	0	
10	1	B is const w/ $B=0 \Rightarrow \bar{B} \Rightarrow B$

$S_3 = (\bar{B} + \bar{D})$

S_4 (10, 11, 14, 15)

on Row

$\bar{A}B$	\bar{B}	B is changed w/
11	1	
10	0	A is const $\Rightarrow A=1 \Rightarrow \bar{A}$

on column

$\bar{C}\bar{D}$	\bar{C}	C is const w/ D is changed.
11	1	
10	0	

$C=1 \Rightarrow \bar{C}$

$S_4 = \bar{A} + \bar{C}$

minimal POS form is $S_1 \cdot S_2 \cdot S_3 \cdot S_4 = (\bar{A}+B)(B+\bar{C})(\bar{B}+\bar{D})(\bar{A}+\bar{C})$

Note: do not cover need not to be covered \wedge do not care (left) not considered.

$\rightarrow F(A, B, C) = (A' + B' + C') (A' + B') + (A' + C')$
 $= (A' + B' + C') (A' + B') (A' + C')$

The above function is not a standard POS function. convert above function to standard POS. Standard POS function is a function that every maxterm should have all (three) variables of the function.

$$F = (A' + B' + C') (A' + B') (A' + C') \xrightarrow{\text{B minima}} \\ = (A' + B' + C') \cdot (A' + B' + 0) (A' + 0 + C') \xrightarrow{\text{C is minima}}$$

$A \cdot A' = 0$ — by Idempotency law.

$$= (A' + B' + C) (A' + B' + C \cdot C') (A' + B \cdot B' + C')$$

$$= (A' + B' + C') (A' + B' + C) (A' + B' + C') (A' + B + C') (A' + B' + C')$$

$$= (A' + B' + C') (A' + B' + C) (A' + B + C') (A' + B' + C')$$

(1)

(2)

(3)

(4)

maxterm.

$$\text{① } A' + B' + C' = 111 \Rightarrow 7$$

$$\text{② } A' + B' + C = 110 \Rightarrow 6$$

$$\text{③ } A' + B + C' = 101 \Rightarrow 5$$

$$\text{④ } \cancel{A' + B + C} = \cancel{100}$$

$A' = 1$
complemented
uncom = 0

$$F = \pi(5, 6, 7)$$

3-Kmap

		BC				
		00	01	11	10	
A		0	0	1	3	2
		1	4	5	7	6

$\rightarrow S_1$

$\rightarrow S_2$

$$S_1(6, 7) \Rightarrow (\bar{A} + \bar{B})$$

$$S_2(5, 7) \Rightarrow (\bar{A} + \bar{C})$$

minimal POS form is $(\bar{A} + \bar{B})(\bar{A} + \bar{C})$.

Find the minimal form of SOP for following function.
 $\pi(5, 6, 7)$.

SOP function & POS function are complement to each other. In the question asked find the minimal SOP form so first find minterms.

numbers (decimal numbers which are not in minterm form) are known as maxterms.

other than minterm numbers are known as maxterm numbers.

$$\pi(5, 6, 7)$$

$$\Sigma(0, 1, 2, 3, 4) \Rightarrow SOP \rightarrow f = (0, 1, 2, 3, 4).$$

A	BC	00	01	11	10
0		1	1	1	1
1		1	1	1	1
		u	s	t	u

$\downarrow S_2$

S_1 = minterm group:

$$S_1 = \bar{A} (0, 1, 2, 3) | S_1 = \bar{A}$$

$$S_2 = (0, u) \Rightarrow \bar{B}\bar{C} | S_2 = \bar{B}\bar{C}$$

$$\text{minimal SOP } S_1 + S_2 = \bar{A} + \bar{B}\bar{C} = f$$

obtain minimal forms by using kmap
as sum of Product and

b) Product of sum expressions for the given function below

$$F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10).$$

a) $F = \Sigma(0, 1, 2, 5, 8, 9, 10)$ sum of minterm form.

b) $\pi(3, 4, 6, 7, 11, 12, 13, 14, 15).$

AB	CD	00	01	11	10
00		1	1	1	1
01		1	1	1	1
11		12	13	15	14
10		8	9	11	10
		1	1	1	1

$\downarrow S_1$

$$S_1(0, 1, 8, 9)$$

$$S_1 = \bar{B} \cdot \bar{C}$$

$$S_2(0, 2, 8, 10)$$

$$S_2 = \bar{B}D$$

$$S_3(1, 5)$$

$$S_3 = \bar{A} \bar{C} D$$

$$F = S_1 + S_2 + S_3 = \bar{B}\bar{C} + \bar{B}D + \bar{A}\bar{C}D.$$

$$\textcircled{6} \quad \pi(3, 4, 6, 7, 11, 12, 13, 14, 15)$$

		CD				
		00	01	11	10	
AB	00	0	1	3	2	S_2
	01	4	5	7	6	S_1
AB	11	12	13	15	14	S_3
	10	8	9	11	10	

$$S_1 (12, 13, 14, 15) \quad (\bar{A} + \bar{B})$$

$$S_2 (3, 7, 11, 15) \quad (\bar{C} + \bar{D})$$

$$S_3 (4, 6, 12, 14) \quad \bar{B} + D$$

$$\text{minimal POS is } (\bar{A} + \bar{B})(\bar{C} + \bar{D})(\bar{B} + D)$$

Find minimal form of POS.

$$Y(A, B, C, D) = \Sigma(1, 3, 5, 8, 9, 11, 15) + \Sigma d(2, 13)$$

solution:

Don't care will be same in both POS w ROP form.
other than minterms are maxterms.

$$\pi(0, 2, 4, 6, 7, 10, 12, 13) + d(2, 13)$$

$$\pi(0, 4, 6, 7, 10, 12, 14) + d(2, 13)$$

		CD				
		00	01	11	10	
AB	00	0	1	3	2	S_1
	01	4	5	7	6	S_2
AB	11	12	13	15	14	S_3
	10	8	9	11	10	

$$S_1 (2, 6, 10, 14)$$

$$S_1 = \bar{C} + D = \bar{C} + D$$

$$S_2 (6, 14, 14, 12)$$

$$S_2 = \bar{B} + \bar{D} = \bar{B} + D$$

$$S_3 (0, 4, 2, 6)$$

$$S_3 = A + D$$

$$\text{minimal POS } S_1 \cdot S_2 \cdot S_3 = (\bar{C} + D) \cdot (\bar{B} + D) \cdot (A + D)$$


Conversion of basic gates to NAND gate: NAND

NOT gate

$$f = x' \rightarrow \text{it is a single variable}$$

NAND
 $f = \overline{x}y$
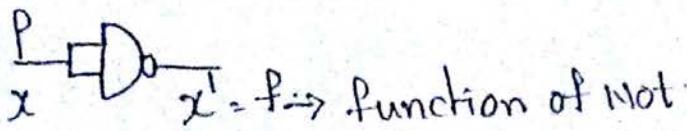
$$f = \overline{x}y \rightarrow \text{nand function } f = \overline{x \cdot x} = x'$$




AND gate AND function has to be implemented by nand gate

$$f = x \cdot y \rightarrow \text{and gate function.}$$

NAND $f = \overline{x} \cdot y$

Take double time complement $f = x \cdot y$ in order to get same function value ($\because x=0$ assume $\bar{x}=1 \Rightarrow \bar{\bar{x}}=0$)
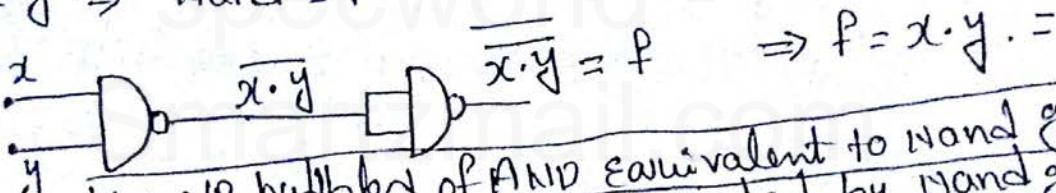
$$f = \overline{\overline{x} \cdot y} \Rightarrow \text{NAND} = f.$$



OR gate OR function has to be implemented by nand gate

$$f = x + y \rightarrow \text{or gate function}$$

NAND gate $f = \overline{x} \cdot y$

Take double time complement $f = x + y$ in order to get same function value.


$$f = \overline{\overline{x+y}} = \overline{x' \cdot y'} \text{ assume } x' = A \quad y' = B \quad f = \overline{A \cdot B} \rightarrow \text{nand function}$$

$$f = \overline{\overline{x' \cdot y'}} \Rightarrow \text{nand function functionality.}$$

$$f = \overline{x' \cdot y'}$$

No iIP bubbled of OR gate is equivalent to nand gate function.

$$f = \overline{x \cdot y}$$

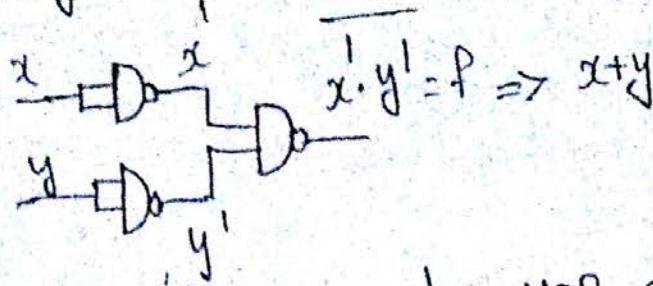

conversion of Basic gates NOR gates.

NOT

$$f = x'$$

$$f = \overline{x+x} = \bar{x} \quad x+x=x.$$

NOT



NOR

$$f = \overline{x+y}$$

NOR symbol




AND gate

$$f = x \cdot y$$

Take double time complement for the AND function.

$$f = \overline{\overline{x} \cdot \overline{y}} = \overline{x'+y'} \Rightarrow A = x' \quad B = y' \Rightarrow \overline{A+B} \Rightarrow \text{NOR}$$

functionality.

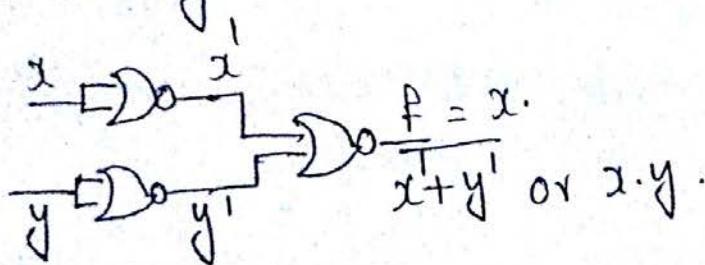


OR gate

$$f = x+y$$

Take double complement for the OR function.
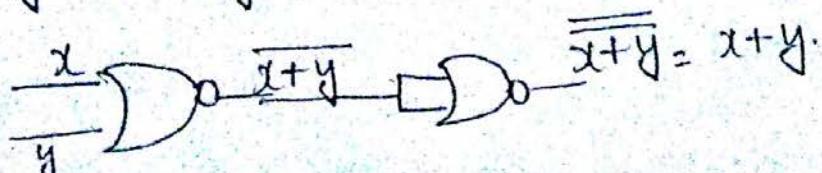
$$f = \overline{\overline{x+y}} = \overline{\overline{x+y}} = A \Rightarrow \overline{\overline{A}} = f$$



Equivalent representation of Basic gates in universal gates.






AND-OR-NOT are basic gates

NAND-NOR are universal gates - Any function can be implemented by using these gates.


EXOR-EXNOR are derived gates

↳ These functions can be implemented by using basic gates.




MAIN

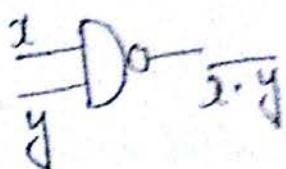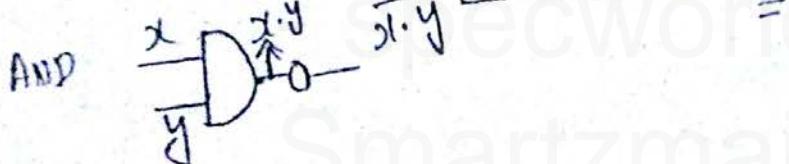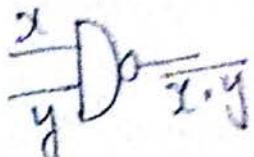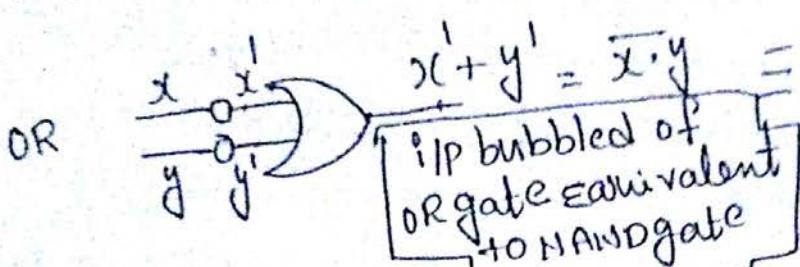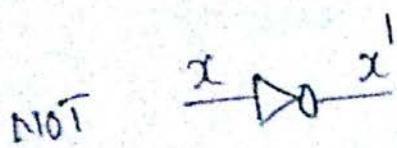

NOR

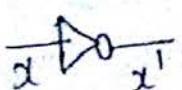
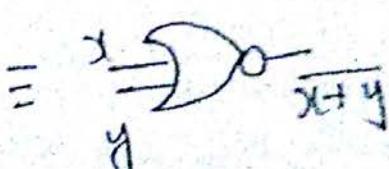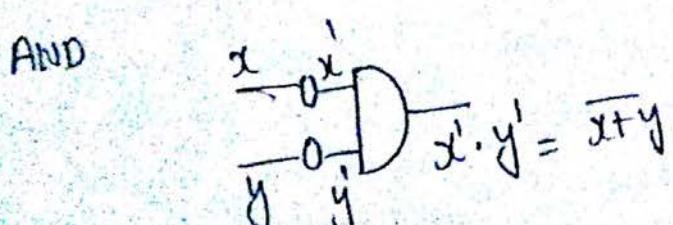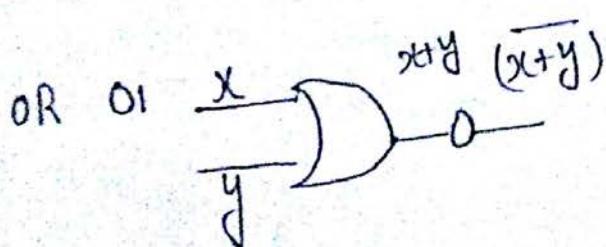
$$f = x + y \\ = \bar{x} + \bar{y} = \bar{x} \cdot \bar{y}$$



Note

1. I/P bubbled OR gate is equivalent to NAND gate.
 2. O/P bubbled AND gate is equivalent to NOR gate.
 3. I/P bubbled OR gate is equivalent to NOR gate.
 4. I/P bubbled AND gate is equivalent to NOR gate.
- logic step

NAND - NOR Implementation OR
converting AND-OR-Invert logic to NAND/NOR logic.

Steps:


1. Draw the circuit in AND-OR-Invert logic
2. If NAND hardware is chosen, add a bubble at the output of each AND gate and at the inputs to all the OR gates.
3. If NOR hardware is chosen, add a bubble at the O/P of each OR gate and at the inputs to all the AND gates.
4. Add or subtract an inverter on each line that received a bubble in step 2 & 3 so that the polarity of signals on those lines remain unchanged from that of the original diagram.
5. Replace the I/P bubbled OR by NAND & Replace the I/P bubbled AND by NOR.
6. Eliminate double inversions or NOT or bubbles.

Note:


1. If the function is in SOP form then it is easy to implement by NAND logic
2. If the function is in POS form then the function can be easily implemented by NOR logic.

$f = A \bar{B} + \bar{A} B$. Implement the function by using NAND logic.


Step-1 AOI logic

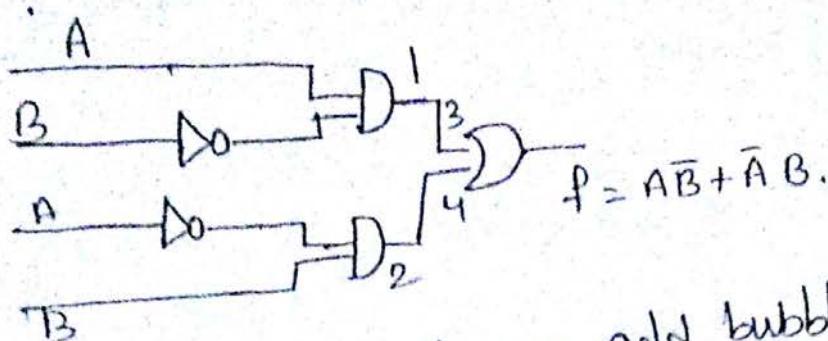

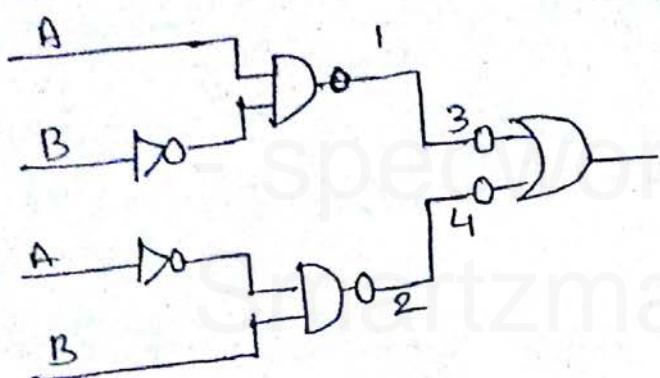Step-2 NAND logic chosen add bubbles at O/P of AND
 ,,, bubbles at I/P of OR gate.



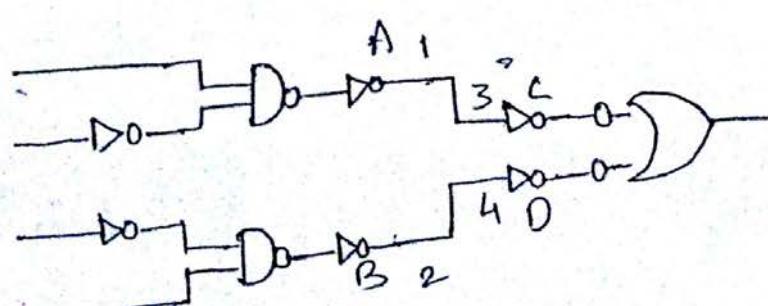Step-3 Add or subtract an inversion on each line that received bubble. so that polarity remains unchanged






at 1, 2, added bubbles
 to eliminate A₄
 B₅ NOT gates are added.

at 3, 4 added bubbles
 to eliminate OR get equal
 functionality C₆ D
 NOT gates are added.

Step-4

eliminate double inversions 1-3 \Rightarrow 1-NOT w/ 3-NOT
 eliminate double inversions 2 \Rightarrow 2-NOT w/ 4-NOT

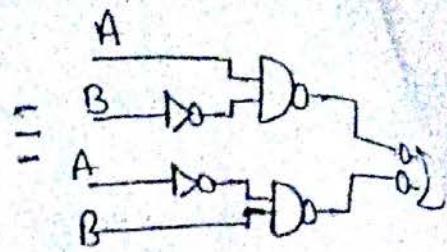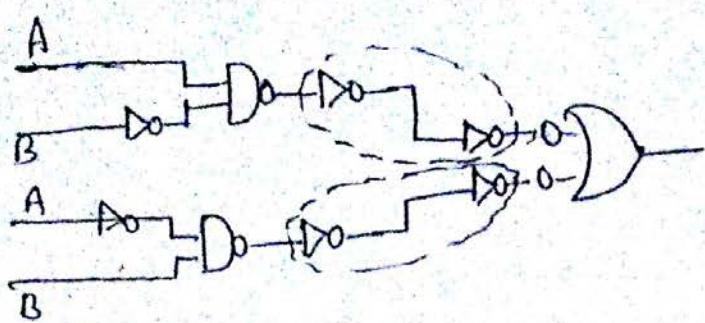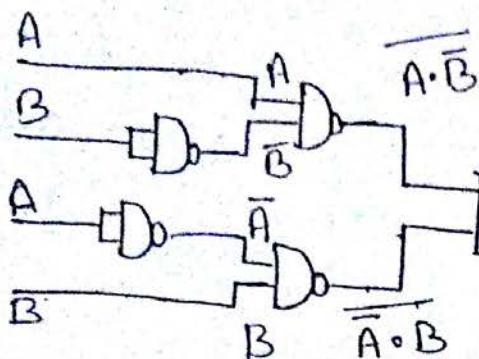Step-5

$$f = (\overline{A \cdot \bar{B}}) \cdot (\overline{\bar{A} \cdot B})$$

Verification.


$$(\overline{A+B}) \cdot (\overline{A+\bar{B}})$$

$$(\overline{\bar{A} \cdot \bar{B}}) + (\overline{\bar{A} \cdot B})$$

$$A \cdot \bar{B} + \bar{A} \cdot B$$


$f = (A + \bar{B}) \cdot (A + \bar{B})$ Implement the above function by NOR gates.

The above function is in POS form so it can be easily implemented by NOR logic.

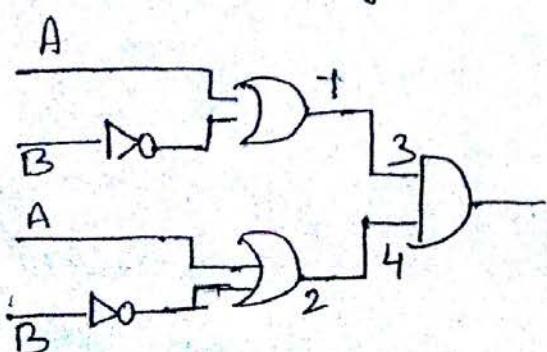
Step-1 AOI logic

Step-2 NOR logic is chosen add bubbles at o/p of OR gate and add bubbles at i/p of AND gate.

at 1, 2, 3, 4 positions add bubbles.

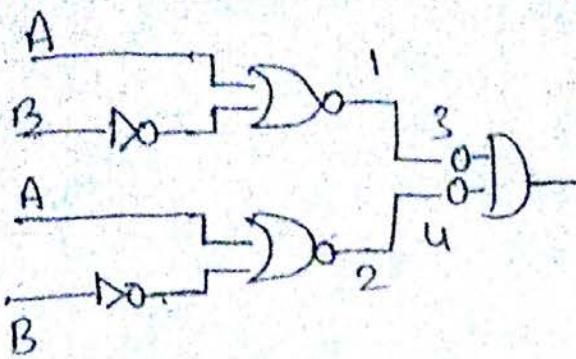Step-3

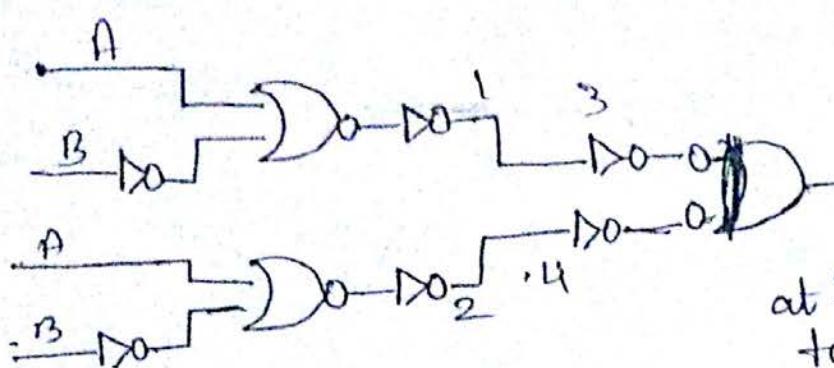Add or subtract an inversion on each line that received bubble. Note that polarities remain unchanged.







at 1, 2, added bubbles to get equal functionality add NOT gate.

at 3, 4 added bubbles to eliminate or get equal functionality add NOT gate

Step-4

eliminate double inversions (1,3) 1-NOT w 3-NOT
eliminate double inversions (2,4) 2-NOT w 4-NOT

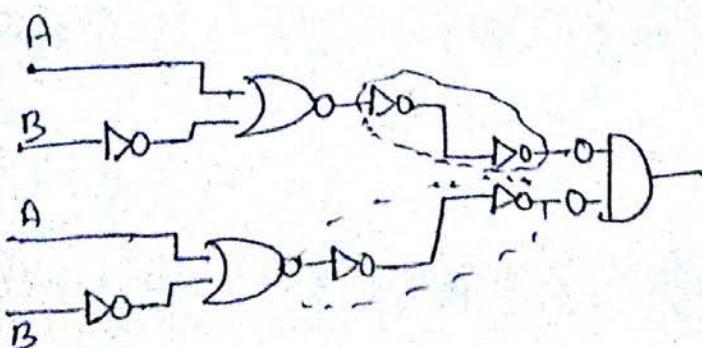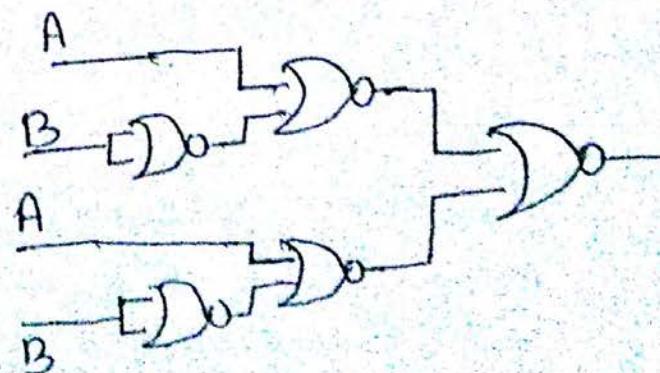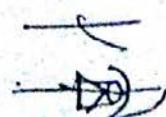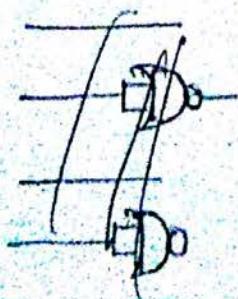Step-5

Minimize the Boolean equation
 $F(A, B, C, D) = \Sigma m(7, 9, 10, 11, 12, 13, 14, 15)$ using L1102
 Also realize the simplified expression using
 a) AND-OR b) OR-AND c) NAND-NAND
 d) NOR-NOR.

Solution

For AND-OR & NAND-NAND: Realization.

And-OR is represented for SOP : For SOP NAND realization is easy. So for AND-OR & NAND-NAND logic can be implemented by for SOP form.

$$F = \Sigma m(7, 9, 10, 11, 12, 13, 14, 15)$$

Step-1 42, 3

		CD	00	01	11	10
		AB	00	01	11	10
00	00	0	1	3	2	
01	01	4	5	7 S1	6	
11	11	12 (1)	13	5	14 S1	1
10	10	8	9	11	10	1
					S3	

Step-4

$$S_1(12, 13, 14, 15) \Rightarrow AB$$


$$S_2(10, 11, 14, 15) \Rightarrow AC$$

$$S_3(9, 11, 13, 15) \Rightarrow AD$$

$$S_4(7, 15) \Rightarrow BCD$$


minimal SOP is $AB + AC + BCD$.

ND-OR logic


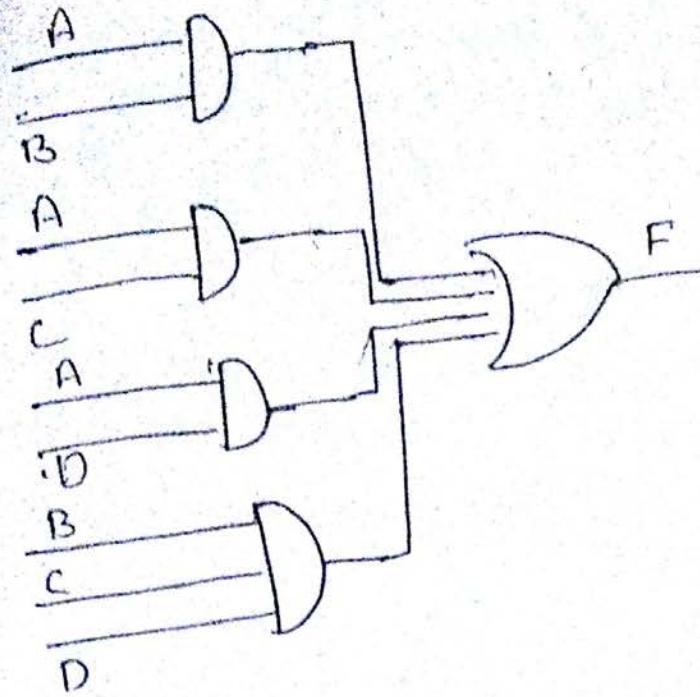


NAND-NAND

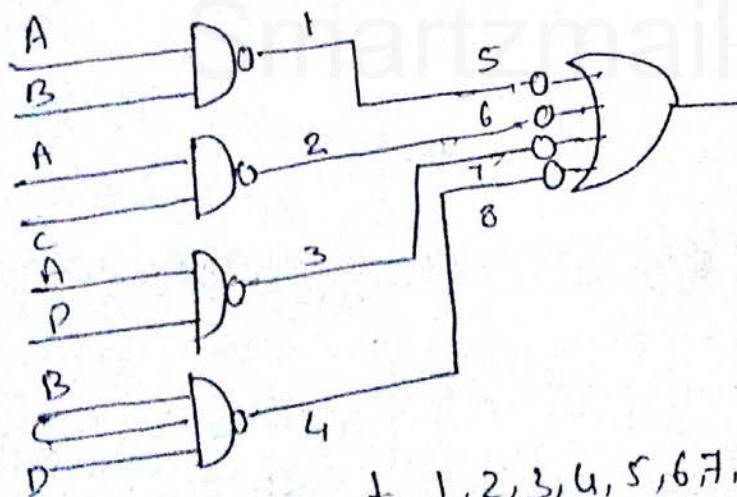add bubbles of o/p of And gate w add bubbles o/p of OR gate.



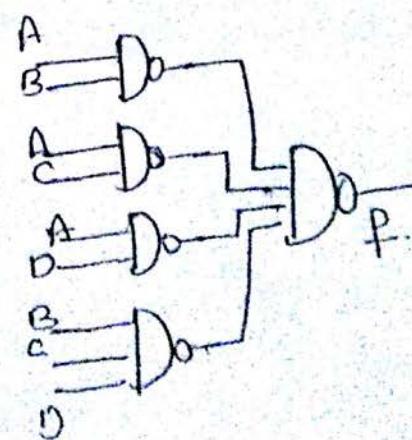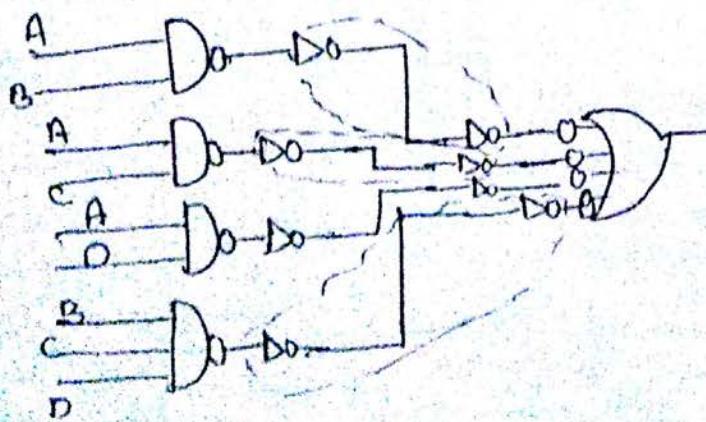add inversions at 1, 2, 3, 4, 5, 6, 7, 8.



if it is not adjacent to any other 1's.


Two adjacent 1's form a Prime Implicant provided that they are not within a group of four adjacent squares.

Four adjacent 1's form Prime Implicant if they are not within a group of eight adjacent squares. Also....

The essential Prime implicant are found by looking at each square marked with a 1 by checking the number of Prime Implicants that cover it. The prime implicant is essential if it is the only Prime Implicants that covers minterms.

Find Prime Implicants & essential Prime Implicants by kmap for following function.

$$\Sigma(3, 4, 5, 7, 9, 13, 14, 15)$$

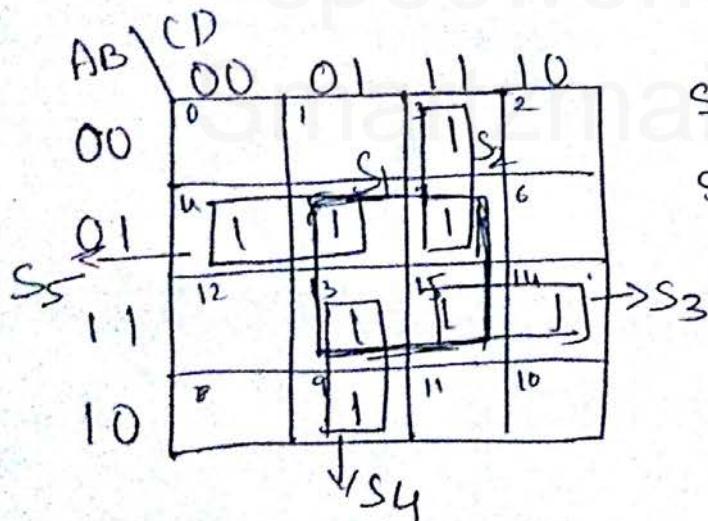

$$S_1(5, 7, 13, 15) = BD$$

$$S_2(3, 7) = \bar{A}CD$$

$$S_3(14, 15) = A\bar{B}C$$

$$S_4(9, 13) = \bar{A}\bar{C}D$$

$$S_5(4, 5) = \bar{A}\bar{B}\bar{C}$$

Prime Implicants $S_1 = BD, S_2 = \bar{A}CD, S_3 = A\bar{B}C$

$$S_4 = \bar{A}\bar{C}D, S_5 = \bar{A}\bar{B}\bar{C}$$

Essential Prime Implicants

$$S_2 = \bar{A}CD, S_3 = A\bar{B}C$$

$$S_4 = \bar{A}\bar{C}D, S_5 = \bar{A}\bar{B}\bar{C}$$

Note: For two level implementation:

Represent the following function all two level possible implementations.

$$F(A, B, C, D) = \Sigma m(0, 1, 2, 3, 4, 8, 9, 12)$$


Solution By using SOP format the function we get $1 in 14$ implemented by basic AND-OR logic

For the given function find minimal form of SOP.

AB	CD	00	01	11	10
00	1	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$$\begin{aligned} S_1(0, 1, 2, 3) &= \bar{A}\bar{B} \\ S_2(0, 4, 8, 12) &= \bar{C}\bar{D} \\ S_3(0, 1, 8, 9) &= \bar{B}\bar{C} \\ \text{minimal SOP} &= \bar{A}\bar{B} + \bar{C}\bar{D} + \bar{B}\bar{C} = F \end{aligned}$$

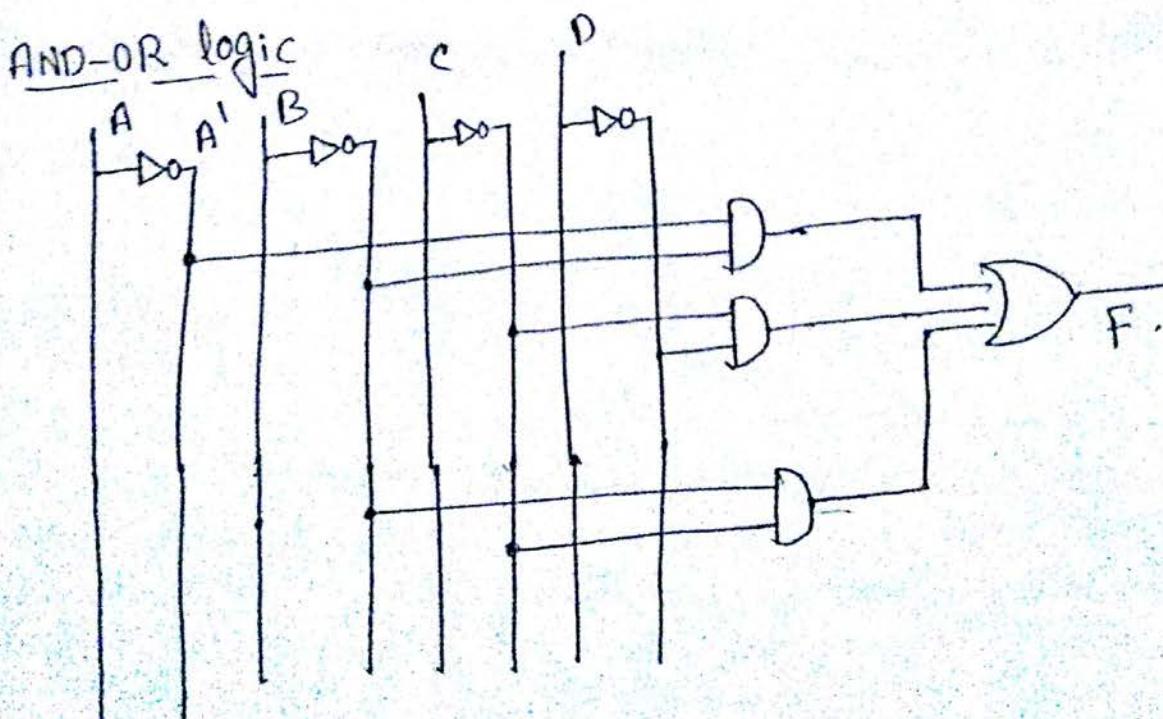Implement above equation by only AND-OR logic



$$F = \bar{A}\bar{B} + \bar{C}\bar{D} + \bar{B}\bar{C}$$

$\bar{F} = F \Rightarrow$ By demorgan law.

operations AND \rightarrow OR
OR \rightarrow AND
var? Primed - unPrimed
able unPrimed - Primed


$$F = \bar{A}\bar{B} + \bar{C}\bar{D} + \bar{B}\bar{C}$$

Take double complementation to get same function.


$$\begin{aligned}\bar{F} &= \overline{\bar{A}\bar{B} + \bar{C}\bar{D} + \bar{B}\bar{C}} \\ &= (\bar{\bar{A}}\bar{\bar{B}}) \cdot (\bar{\bar{C}}\bar{\bar{D}}) \cdot (\bar{\bar{B}}\bar{\bar{C}}) = (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) \cdot (\bar{B} + \bar{C}) \\ \bar{F} &= (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) \cdot (\bar{B} + \bar{C}) = F. \quad - \textcircled{2}\end{aligned}$$

Eqn. $\textcircled{2}$ in b/n variables have OR operator w/ b/n no. terms have AND followed a complement. So above function can be implemented by OR-NAND.

OR-NAND

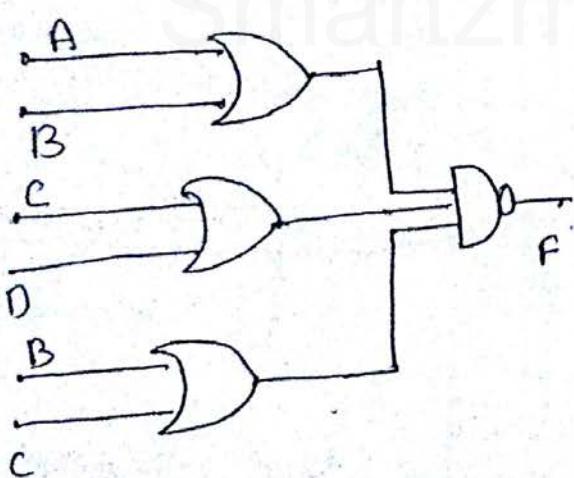


OR-NOT-OR

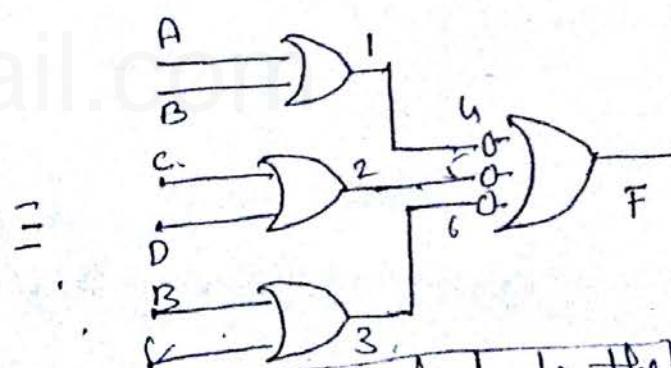

∴ NAND equivalent to the
i/p bubbled of OR gate.

The bubble of 4th position transfer to 1 position w/ bubble of 5th position transfer to 2nd position, bubble of 6th position transfer to 3 position.

OR-NOT-OR
NOR-OR

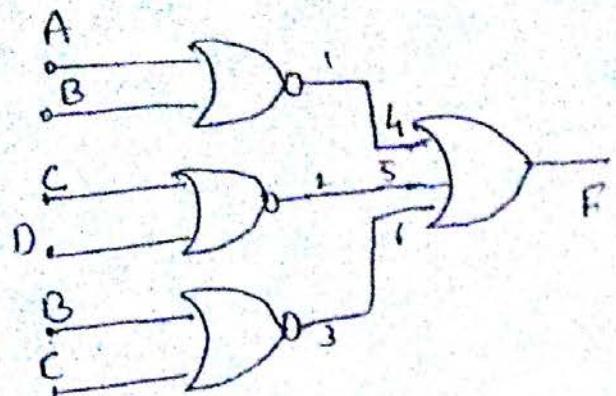'NOR - OR'

Pos Next implementation designing done for P08.

By using POS format the function can be designed by basic OR-AND logic.

$$\Sigma \text{ (given minterms)} = \Sigma(0, 1, 2, 3, 4, 8, 9, 12)$$

$$\Pi \text{ (remaining terms)} = \Pi(5, 6, 7, 10, 11, 13, 14, 15)$$

$$F = \Pi(5, 6, 7, 10, 11, 13, 14, 15)$$

AB\CD	00	01	11	10
00	0	1	3	2
01	4	0	0	0
11	12	13	0	0
10	8	9	0	0

$$S_1(10, 11, 14, 15) = \bar{A} + \bar{C}$$

$$S_2(6, 7, 11, 15) = \bar{B} + \bar{C}$$

$$S_3(5, 7, 13, 15) = \bar{B} + \bar{D}$$

minimal POS in S_1, S_2, S_3
 $(\bar{A} + \bar{C}) (\bar{B} + \bar{C}) (\bar{B} + \bar{D})$

OR-AND logic