

# Multiplexers



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



## MULTIPLEXERS (Data Selectors)

A multiplexers (MUX) is a device that allows digital information from several sources to be routed onto a single line for transmission over that line to a common destination.

The basic multiplexers has several data input lines and a single output line. It also has data-select inputs, which permit digital data on any one of the inputs to be switched to the output line.



IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



## MUX-continued...

A modern stereo system may have **a switch that selects music from one of four sources**: a cassette tape, CD, a radio tuner , or an auxiliary input such as audio from a VCR or DVD. The switch selects one of the electronic signals from one of these four sources and sends it to the power amplifier and speakers.

In simple terms, this is what a multiplexer (MUX) does; it selects one of several input signals and passes it on to the output.




IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



## Functional diagram of MUX

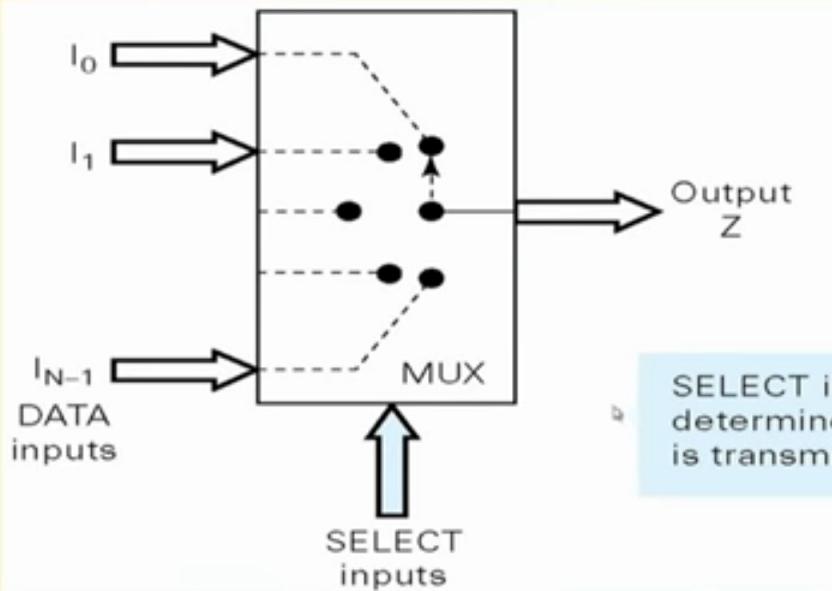

SELECT input code  
determines which input  
is transmitted to output Z.




IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



# Two-input multiplexer

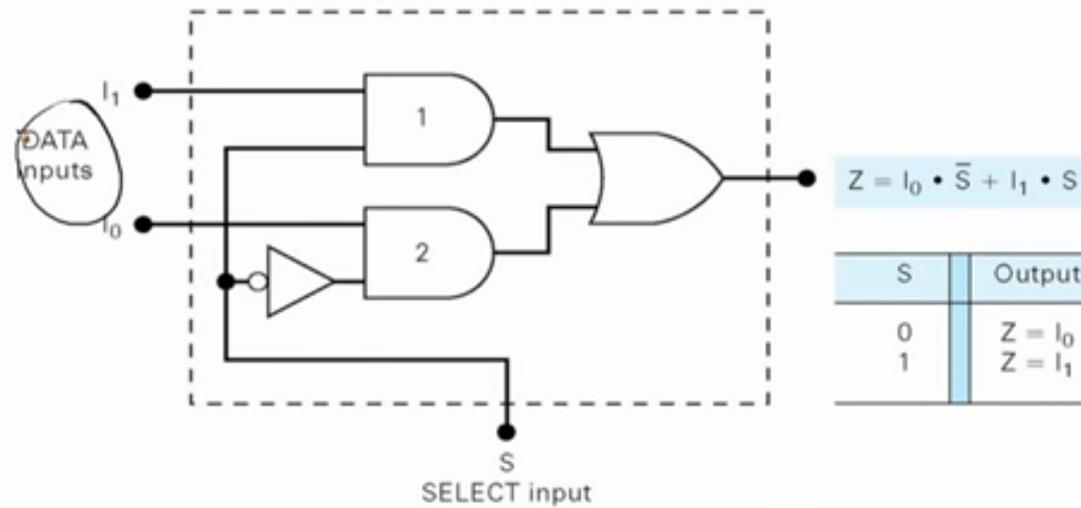


IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



## Four-input multiplexer

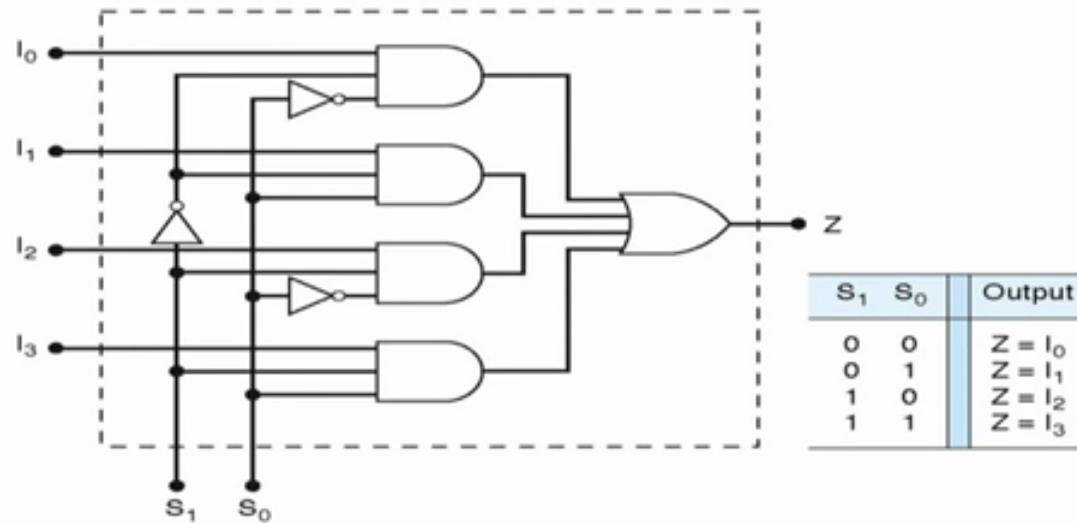


IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



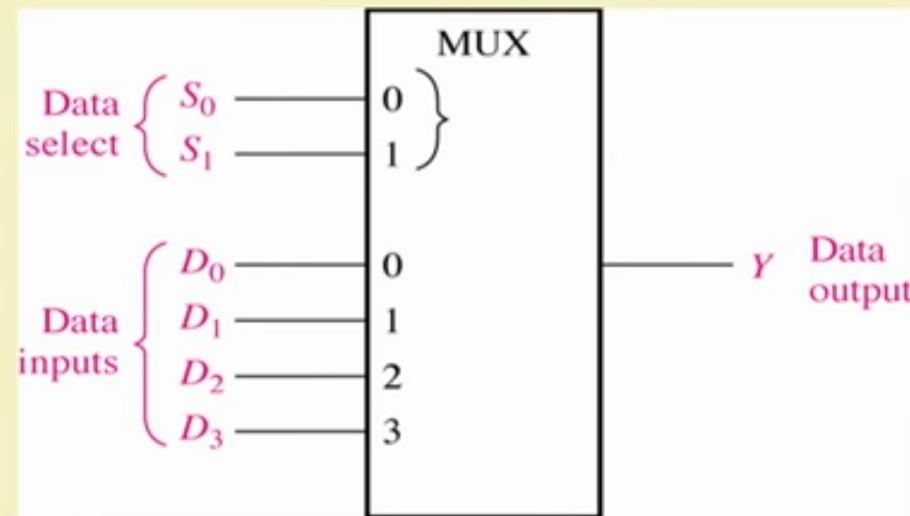Logic symbol for a 1-of-4 data selector/multiplexer.



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



## Logic symbol for a 1-of-4 data selector/multiplexer.

FUNCTION TABLE

		INPUTS				STROBE $\bar{G}$	OUTPUT Y
SELECT		C0	C1	C2	C3		
S1	S0	X	X	X	X	H	Z
-	-	L	X	X	X	L	L
L	L	H	X	X	X	L	H
L	H	X	L	X	X	L	L
L	H	X	H	X	X	L	H
H	L	X	X	L	X	L	L
H	L	X	X	H	X	L	H
H	H	X	X	X	L	L	L
H	H	X	X	X	H	L	H

Select inputs A and B are common to both sections.




IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES


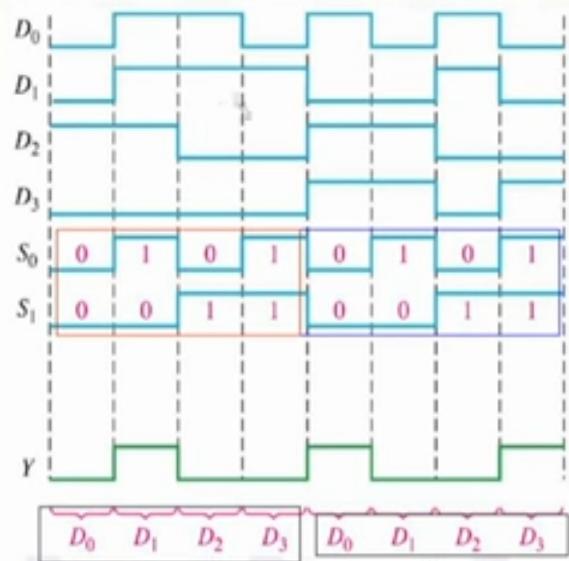
## Output Waveforms in relation with the Data-Input and Data-Select waveforms - 4-input MUX



The binary state of the data-select inputs during each interval determines which data input is selected. Here the data-select inputs go through a repetitive binary sequence **00,01,10,11,00,** and so on. The resulting output waveform is shown.




IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES




# 8-input multiplexer

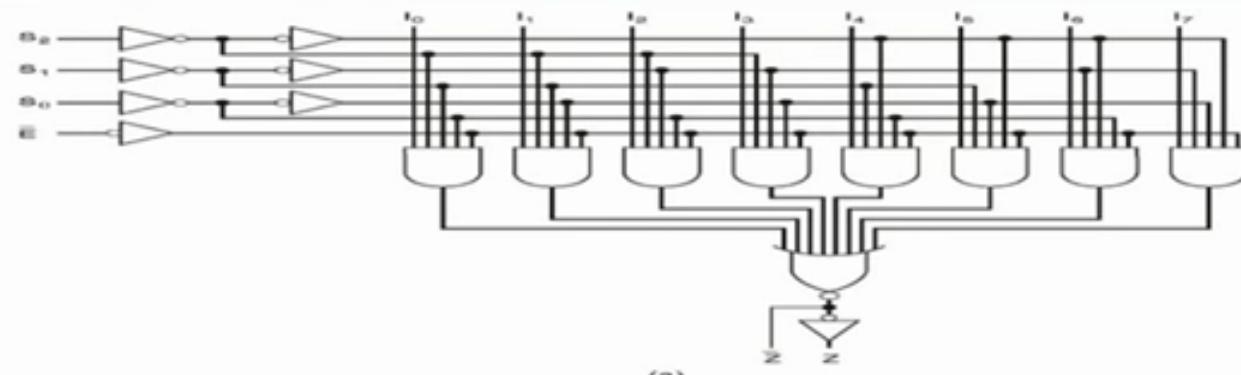

(a)

Inputs			Outputs	
$E$	$s_2$	$s_1$	$s_0$	$Z$
H	X	X	X	H L
L	L	L	L	I <sub>0</sub>
L	L	L	0	I <sub>1</sub>
L	L	L	1	I <sub>2</sub>
L	L	L	1	I <sub>3</sub>
L	L	L	1	I <sub>4</sub>
L	L	L	1	I <sub>5</sub>
L	L	L	1	I <sub>6</sub>
L	L	L	1	I <sub>7</sub>

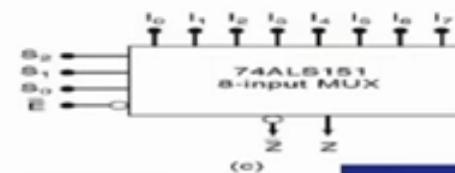

(c)



IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



## MSI Quad Two–input Multiplexer

- The **74LS157** contain of quad two–input multiplexers,  $I_{0a} I_{0b} I_{0c} I_{0d}$  and  $I_{1a} I_{1b} I_{1c} I_{1d}$ .
- The logic symbol and truth table is shown in Figure.
- Notice that each of the four multiplexer shares a common data select line and a common *Enable*.
- Each multiplexer has only one data select input because there are only two groups of inputs to be selected.




IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



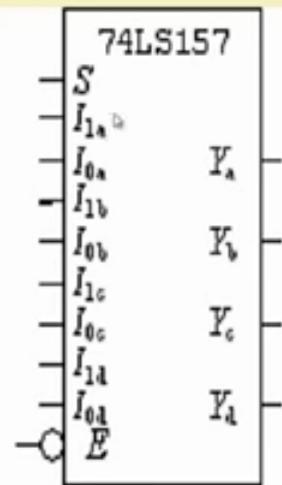

Inputs		Outputs			
$\bar{E}$	$S$	$Y_a$	$Y_b$	$Y_c$	$Y_d$
H	X	L	L	L	L
L	L	$I_{0a}$	$I_{0b}$	$I_{0c}$	$I_{0d}$
L	H	$I_{1a}$	$I_{1b}$	$I_{1c}$	$I_{1d}$

*Logic symbol and truth table for 74LS157 multiplexer.*




IIT KHARAGPUR



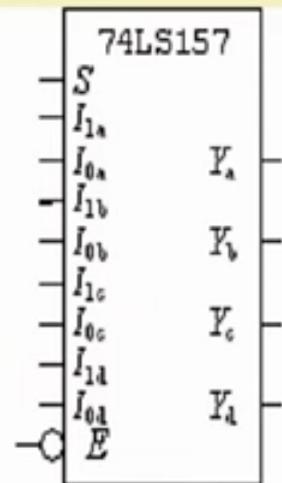NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES





Inputs		Outputs			
$\bar{E}$	$S$	$Y_a$	$Y_b$	$Y_c$	$Y_d$
H	X	L	L	L	L
L	L	$I_{0a}$	$I_{0b}$	$I_{0c}$	$I_{0d}$
L	H	$I_{1a}$	$I_{1b}$	$I_{1c}$	$I_{1d}$

*Logic symbol and truth table for 74LS157 multiplexer.*



IIT KHARAGPUR



NPTEL  
ONLINE  
CERTIFICATION COURSES



## MSI Quad Two-input Multiplexer

- $\overline{E}$  Input is *LOW* – allows the selected input data to pass through to the output.
- $\overline{E}$  Input is *HIGH* – will disable the multiplexers, all of the outputs will be *LOW*.
- When  $\overline{E} = 0$  and  $S = 1$ , the  $Y$  outputs will follow the set of  $I_1$  inputs, that is  $Y_a = I_{1a}$ ,  $Y_b = I_{1b}$ ,  $Y_c = I_{1c}$ , and  $Y_d = I_{1d}$ .



IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



## LOGIC FUNCTION GENERATION USING MUX

Exercise 1:

Implement the logic circuit function specified in the table given below by using 74LS151 8-input data selector/multiplexer.

Input			Output	
A2	A1	A0	Y	
0	0	0	0	0
0	0	1	1	1
0	1	0	0	2
0	1	1	1	3
1	0	0	0	4
1	0	1	1	5
1	1	0	1	6
1	1	1	0	7




IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



Solution :

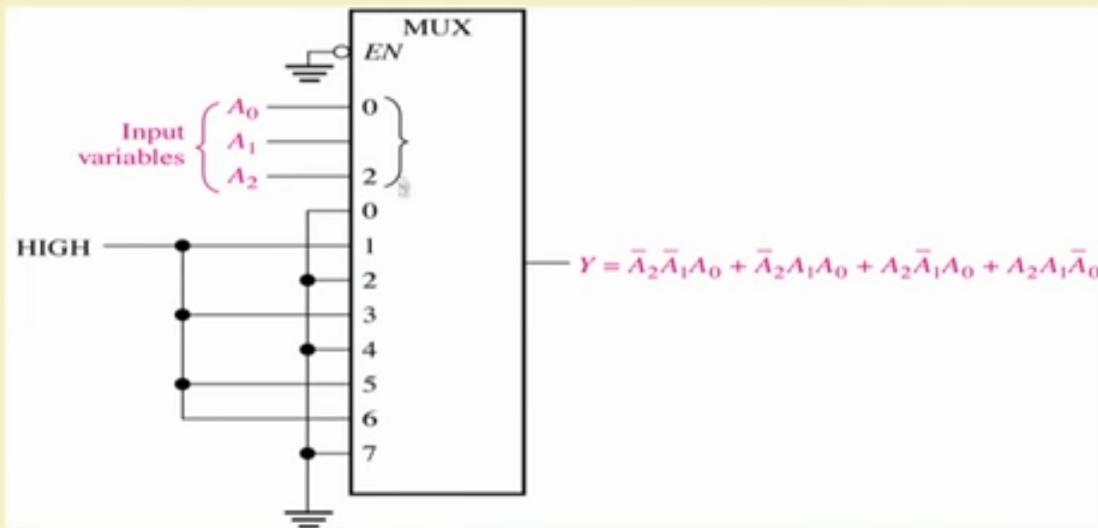

IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



## LOGIC FUNCTION GENERATION USING MUX-Method

- An efficient method for implementing a Boolean function of  $n$  variables with a MUX that has  $n-1$  selection inputs and  $2^{n-1}$  data inputs is given below:
  - List the Boolean function in a truth table
  - Apply the first  $n-1$  variables in the table to the selection inputs of the MUX.
  - For each combination of the selection variables, evaluate the output as a function of the last variable. This function can be 0,1, the variable, or the complement of the variable. Apply these values to the data inputs in the proper order.



IIT KHARAGPUR




NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



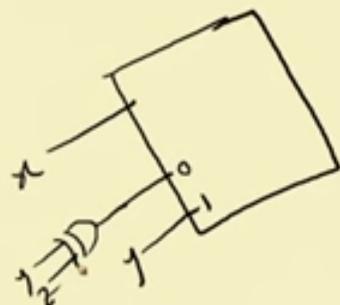
## LOGIC FUNCTION GENERATION USING MUX-Example 2

Implement the Boolean function  $F = x'y'z + x'yz' + xyz' + xyz$  using a suitable MUX



x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$F = z \oplus z'$

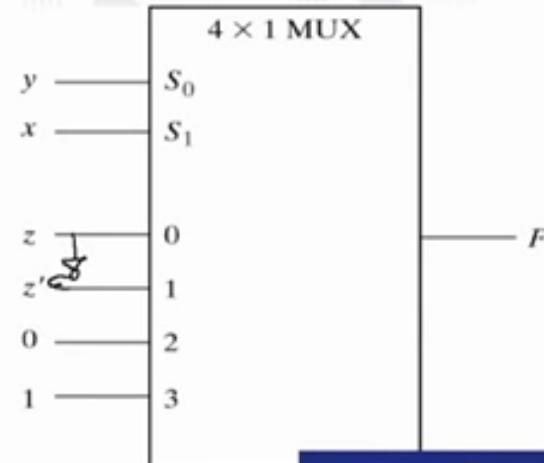

IIT KHARAGPUR




NPTEL ONLINE  
CERTIFICATION COURSES



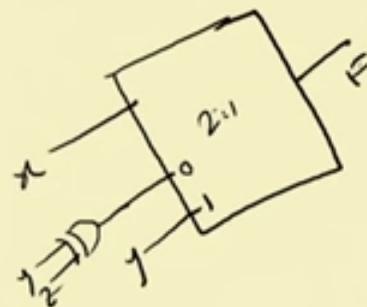
## LOGIC FUNCTION GENERATION USING MUX-Example 2

Implement the Boolean function  $F = x'y'z + x'yz' + xyz' + xyz$  using a suitable MUX



A Karnaugh map for three variables x, y, and z. The columns represent y (0, 1) and the rows represent z (0, 1). The minterms are grouped as follows:

x\z	00	01	10	11
0	0	1	1	0
1	0	0	0	1
$F = z$	0	1	2	3

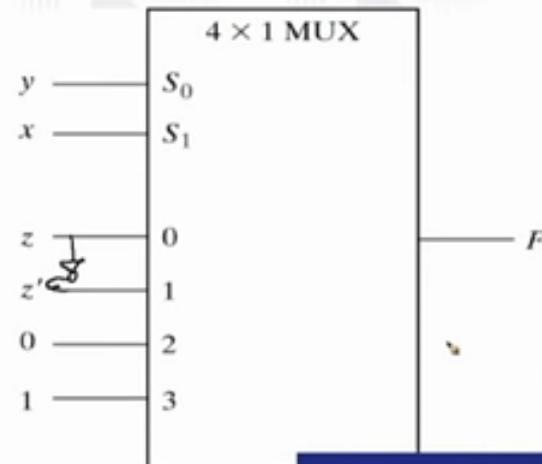

IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



## LOGIC FUNCTION GENERATION USING MUX-Example 2

- The two variables  $x$  and  $y$  are applied to the selection lines in that order;  $x$  is connected to the  $S_1$  input and  $y$  to the  $S_0$  input.
- The values for the data input lines are determined from the truth table of the function
  - For ex., when  $xy=00$ , output  $F$  is equal to  $z$  because  $F=0$  when  $z=0$  and  $F=1$  when  $z=1$ . This requires that variable  $z$  is applied to the data input 0



IIT KHARAGPUR




NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES


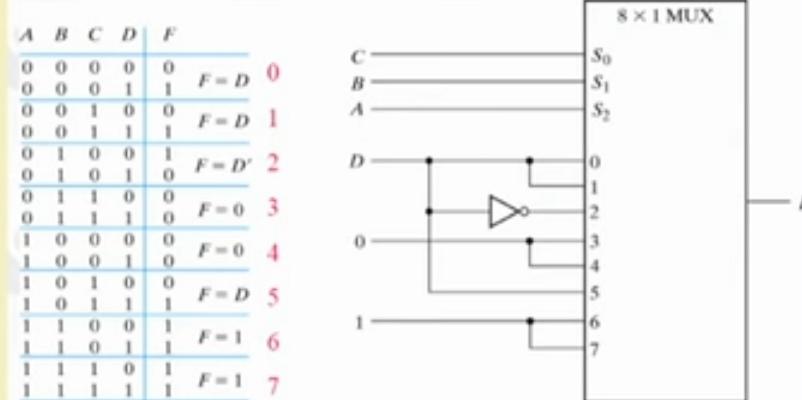
## LOGIC FUNCTION GENERATION USING MUX-Example 3

Implement the Boolean function  $F = A'B'C'D + A'B'CD + A'BC'D' + AB'CD + ABC'D' + ABC'D + ABCD' + ABCD$  using a suitable MUX



IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



Shannon Decomposition

$$f(x_1, y, z) = (\bar{x}y + \bar{x}\bar{z}) +$$

$$x_1 f(x_1, x_2, \dots, x_n, \bar{x}_1, \bar{x}_2, \dots, \bar{x}_n)$$

$$f(x_1, x_2, \dots, x_n) = \bar{x}_1 f(x_1, x_2, \dots, x_n, x_1=0) +$$

$$\bar{x}_2 f(x_1, x_2, \dots, x_n, x_2=1) + \dots +$$


$$f(x_1, x_2, \dots, x_n, x_n=0)$$

$$f(x_1, z) = f(x_1=0, z) +$$

$$+ f(x_1=1, z)$$

$$= \bar{x}_1 \cdot 2 + x_1 \cdot 1$$

$$= \bar{x}_1 \cdot 2$$

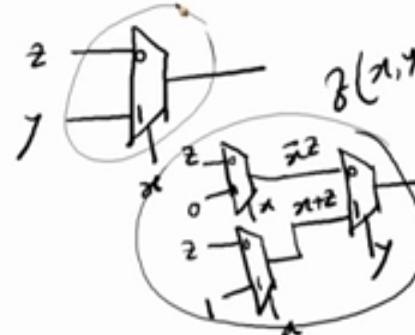

$$f(x_1, y, z) = \bar{y} \cdot \bar{x}_1 f(x_1, y=0, z) +$$

$$+ y \cdot \bar{x}_1 f(x_1, y=1, z)$$

$$= \bar{y} \cdot \bar{x}_1 + y \cdot (\bar{x}_1 + \bar{x}_2)$$

$$= \bar{y} \cdot (\bar{x}_1) + y \cdot (x_1 + z)$$

$$= \bar{y} \cdot (\bar{x}_1) + y \cdot (x_1 + z)$$



Universal logic element

$$\begin{aligned} f &= \overline{s}x + sy \\ &= \overline{a} \cdot 0 + ab \\ &= ab \end{aligned}$$

$$\begin{aligned} f &= \overline{a} \cdot ab \\ &= ab \end{aligned}$$

$$\begin{aligned} f &= \overline{a} \cdot \overline{x} \cdot b \\ &= \overline{a} \cdot \overline{ab} \\ &= 0 \end{aligned}$$


$$\begin{aligned} f &= \overline{s} \cdot 1 + s \cdot 0 \\ &= \overline{s} \end{aligned}$$

$$\begin{aligned} f &= \overline{s}x + sy \\ &= \overline{s}x + s \\ &= a \cdot \overline{ab} \\ &= \overline{ab} + a = a + b \end{aligned}$$



# General demultiplexer

Functional diagram:-

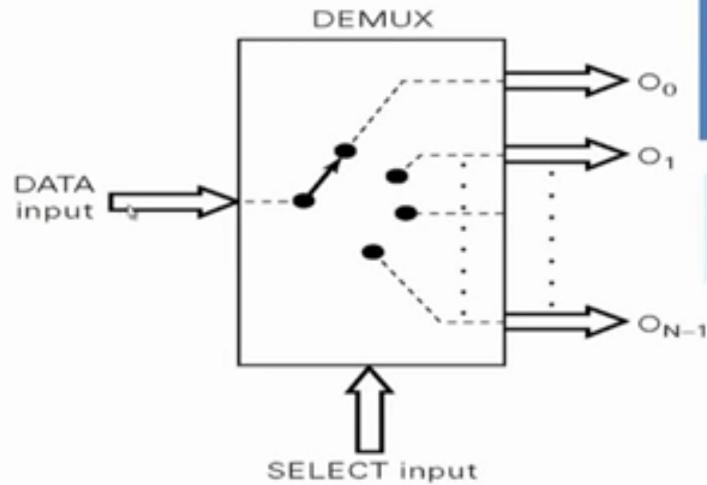

The large arrow indicates one or more lines.  
The select i/p code determines to which output the DATA input will be transmitted

DATA input is transmitted to only one of the outputs as determined by select input code

In other words, the demultiplexer takes one data input source and selectively distributes it to 1 of N output channels just like multiposition switch




IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



## A 1-line-to-4-line demultiplexer.

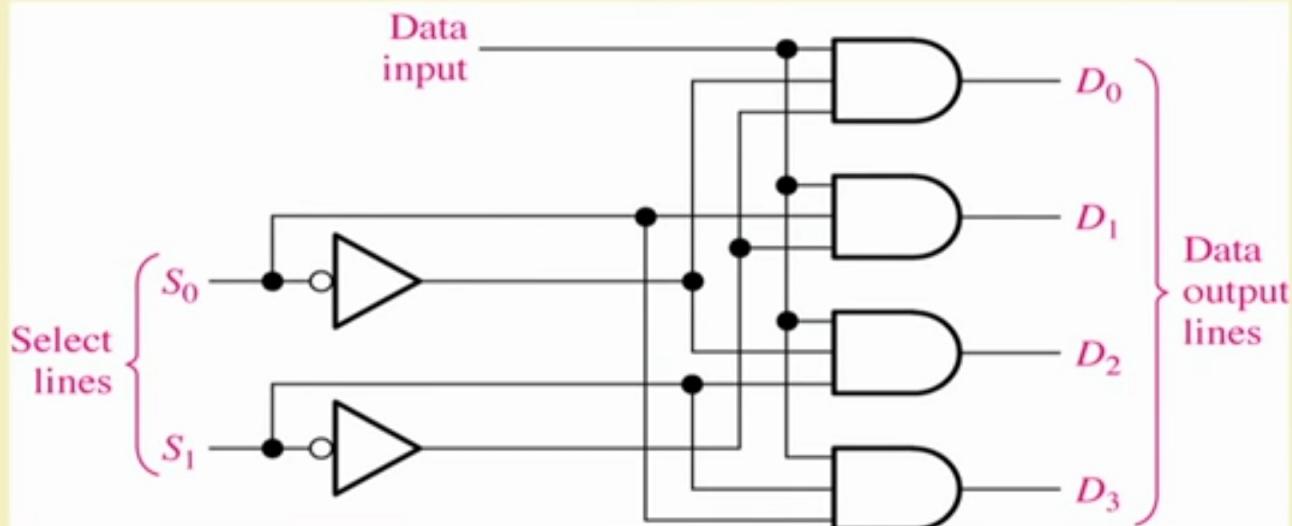


IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES



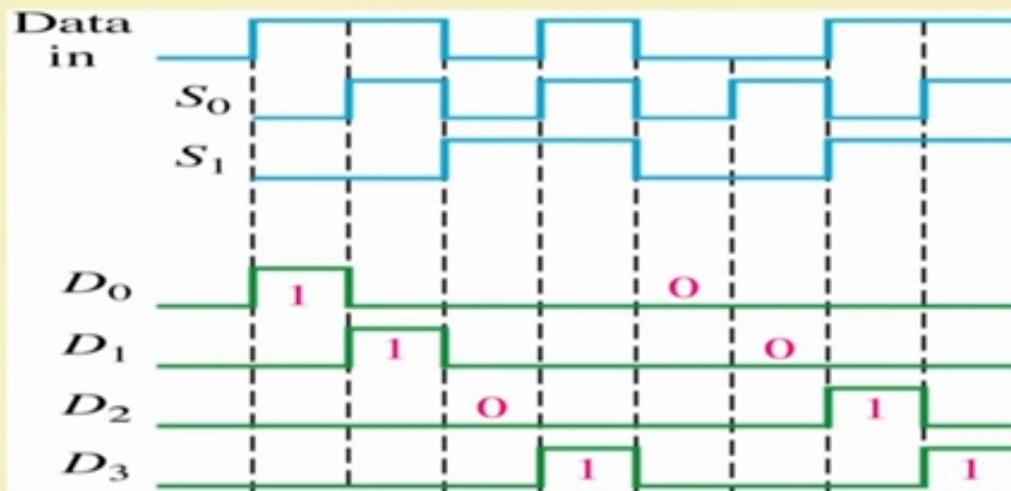The serial data input waveform (Data in) and data select inputs ( $S_0$  and  $S_1$ ) and the corresponding data output waveforms ( $D_0$  through  $D_3$ ) are shown below




IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES

## 1-line- to-8 line demultiplexer

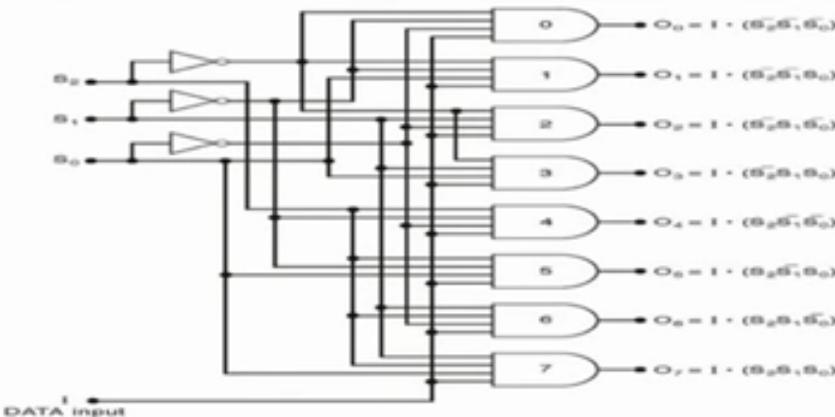

SELECT code			OUTPUTS							
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	O <sub>7</sub>	O <sub>6</sub>	O <sub>5</sub>	O <sub>4</sub>	O <sub>3</sub>	O <sub>2</sub>	O <sub>1</sub>	O <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	I
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	1	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	I	0	0	0	0	0	0	0

Note: I is the data input



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



# Buffers

- Buffer:
  - Doesn't change the input.
  - Only amplifies.



IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES



## Three-State Buffers

- Buffer output has 3 states: 0, 1, Z
- Z stands for High-Impedance  $\cong$  Open circuit



EN	in	out
0	X	Z
1	0	0
1	1	1

EN = 0  $\rightarrow$  out = Z (open circuit)

EN = 1  $\rightarrow$  out = in (regular buffer)







IIT KHARAGPUR



NPTEL ONLINE  
CERTIFICATION COURSES


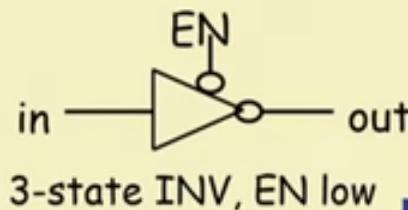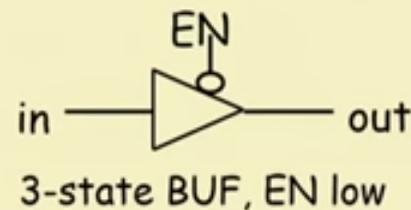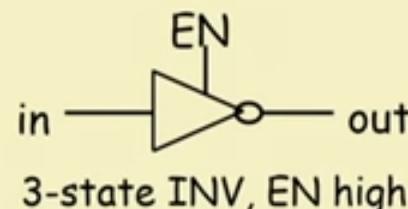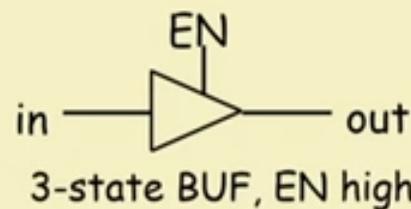
## Three-state buffer(BUF)/inverter(INV) symbols



IIT KHARAGPUR



NPTEL  
NPTEL ONLINE  
CERTIFICATION COURSES

