

12-12-2023

2. A.C CIRCUITS


* A.c circuit:-

→ A circuit in which 'currents' & 'voltages' vary sinusoidally i.e vary with time is called Alternating current or A.c circuit.

→ All A.c circuits are made up of combination of 'R', 'L', 'C'.

→ The circuit elements R, L, C are called "circuit parameters".

* Sinusoidal signal:-

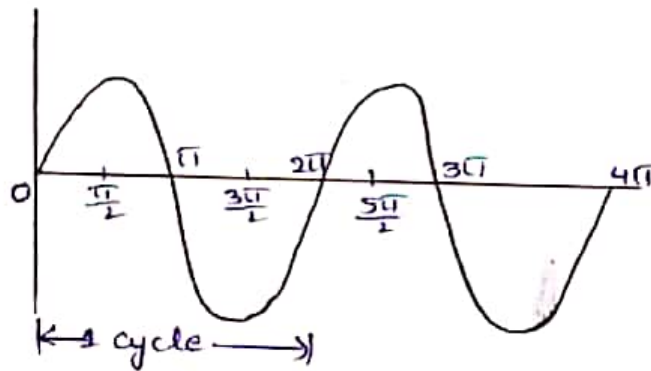

* Frequency:- No. of cycles per second.

$$f = \frac{1}{T}$$

$$\omega = 2\pi f = \frac{2\pi}{T}$$

* Time period:-

→ The time taken by an alternating quantity in seconds to trace one complete cycle is called "Time period", (T).

* Peak factor:- (or) crest (or) Amplitude factor:-

$$\text{Peak factor} = \frac{\text{Maximum value}}{\text{RMS value}}$$

* Form factor:-

$$\text{Form factor} = \frac{\text{RMS value}}{\text{Average value}}$$

* RMS value:-

For sinusoidal signal, $V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$ & $I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$.


* Average value:-

For sinusoidal signal, $V_{\text{avg}} = \frac{2V_m}{\pi}$, $I_{\text{avg}} = \frac{2I_m}{\pi}$.

Circuit Element	Sym bol	Resistance or Reactance	Phase of current	Phase constant	Amplitude Relation.
Resistor	R	R	In phase with V_R	0°	$V_R = I_R R$
capacitor	C	$X_C = \frac{1}{\omega C}$	Leads V_R by 90°	90°	$V_C = I_C X_C$
Inductor	L	$X_L = \omega L$	Lags V_R by 90°	90°	$V_L = I_L X_L$

Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

* A.C through Pure Resistor:

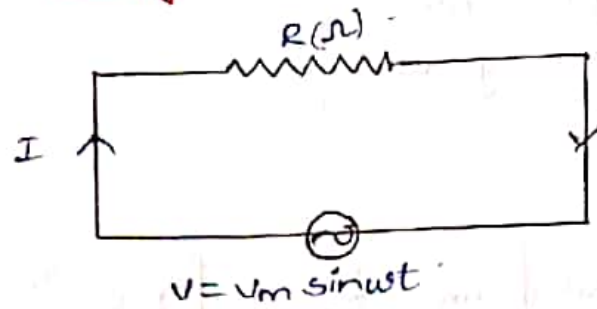

$$v = v_m \sin \omega t$$

Here $v = v_m \sin \omega t \longrightarrow \textcircled{1}$

We know $I = \frac{V}{R}$

$$\Rightarrow I = \frac{v_m \sin \omega t}{R} = \frac{v_m}{R} \sin \omega t = I_m \sin \omega t$$

$$\therefore \boxed{I = I_m \sin \omega t} \longrightarrow \textcircled{2} \quad \left[\because I_m = \frac{v_m}{R} \right]$$



From $\textcircled{1}$ & $\textcircled{2}$

There is 'no phase difference'

i.e. v & I are 'inphase'.

$$v = v_m \angle 0^\circ \text{ volts}$$
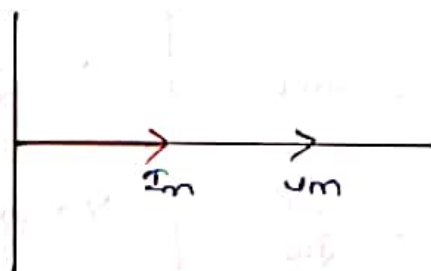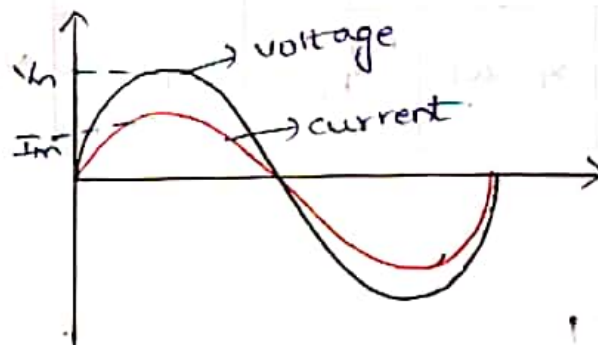
$$I = I_m \angle 0^\circ \text{ Amperes}$$



Phaser diagram.

Power, $P = VI$

$$\Rightarrow P = V_m \sin \omega t \cdot I_m \sin \omega t$$

$$\Rightarrow P = V_m I_m \sin^2 \omega t$$

$$\Rightarrow P = V_m I_m \left(\frac{1 - \cos 2\omega t}{2} \right)$$

$$\Rightarrow P = \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$


$$\Rightarrow P = \frac{V_m I_m}{2} - 0 \quad [\because \text{In a complete cycle}]$$

$$\Rightarrow P = \frac{V_m I_m}{2}$$

$$\Rightarrow P = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$\therefore \boxed{P = V_{rms} \cdot I_{rms}}$$

* AC through Pure Inductor :-

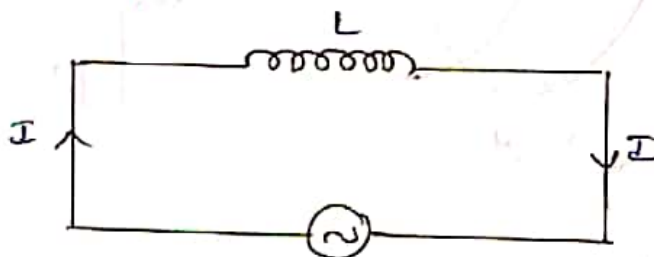

$$V_i = V_m \sin \omega t$$

Here, $V = V_m \sin \omega t \longrightarrow \textcircled{1}$

We know, $V = L \frac{dI}{dt}$

$$\Rightarrow \frac{V}{L} dt = dI$$

$$\Rightarrow I = \int \frac{V}{L} dt$$

$$\Rightarrow I = \frac{1}{L} \int V dt$$

$$\Rightarrow I = \frac{1}{L} \int V_m \sin \omega t dt$$

$$\Rightarrow I = \frac{V_m}{L} \left(\frac{-\cos \omega t}{\omega} \right) = \frac{V_m}{\omega L} (-\cos \omega t)$$

$$\Rightarrow I = \frac{V_m}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$\therefore I = I_m \sin \left(\omega t - \frac{\pi}{2} \right) \longrightarrow \textcircled{2}$$

$$[\because I_m = \frac{V_m}{\omega L}]$$

$$I = I_m \sin(\omega t - \frac{\pi}{2})$$

$$\text{Here, } I_m = \frac{V_m}{\omega L}$$



$$X_L = \omega L = 2\pi fL$$

$$\underline{I_m = \frac{V_m}{X_L}} \quad \because X_L \text{ is Inductive Reactance}$$

$$\rightarrow \text{Now, } \left. \begin{aligned} I &= I_m \sin(\omega t - \frac{\pi}{2}) \\ V &= V_m \sin \omega t \end{aligned} \right\} \text{① \& \text{②}}$$

$$\text{And } V = V_m \angle 0^\circ$$

$$I = I_m \angle -90^\circ$$

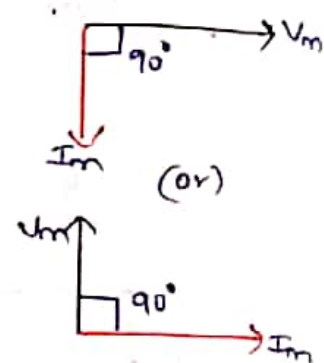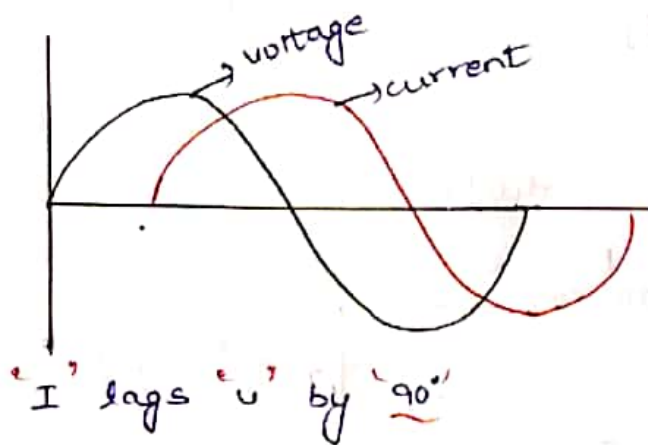

Power :

$$\text{We know, } P = VI$$

$$\Rightarrow P = V_m \sin \omega t (I_m \sin(\omega t - \frac{\pi}{2}))$$

$$\Rightarrow P = -V_m I_m \sin \omega t \cos \omega t$$

$$\Rightarrow P = -\frac{V_m I_m}{2} (2 \sin \omega t \cos \omega t)$$

$$\Rightarrow P = -\frac{V_m I_m}{2} (\sin 2\omega t)$$

$$\therefore \boxed{P = 0}$$

\therefore Power dissipation in pure Inductor is 0

* conclusions :-

① 'I' lags 'V' by 90° .

② 'Power dissipation' in pure Inductor is zero.


③ $X_L = j\omega L = j 2\pi fL$.

'Inductor' opposes 'A.C.'

④ If frequency, ' $f=0$ ', short circuit. [$X_L=0$]

If frequency, ' $f=\infty$ ', open circuit [very high]. [$X_L=\infty$].

* A.C through pure capacitor :-

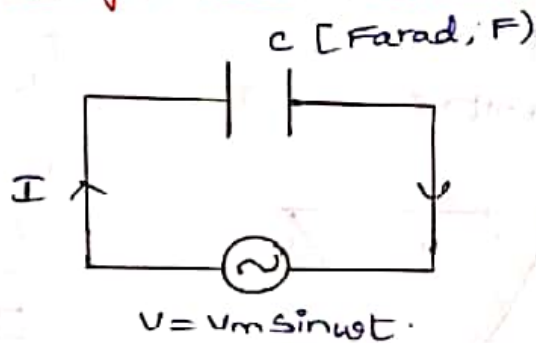

Here, $V = V_m \sin \omega t$ \longrightarrow ①

We know, $I = C \frac{dV}{dt}$.

$$\Rightarrow I = C \cdot \frac{d}{dt} [V_m \sin \omega t].$$

$$\Rightarrow I = C V_m [\cos \omega t (\omega)].$$

$$\Rightarrow I = C V_m \omega [\cos \omega t].$$

$$\Rightarrow I = \omega C V_m \left[\sin \left(\omega t + \frac{\pi}{2} \right) \right].$$

$$\therefore \boxed{I = I_m \sin \left(\omega t + \frac{\pi}{2} \right)} \longrightarrow \textcircled{2} \quad [\because I_m = \omega C V_m].$$

By comparing with Ohm's Law.

$$I = \frac{V_m}{\frac{1}{\omega C}} \sin \left(\omega t + \frac{\pi}{2} \right).$$

$$I_m = \frac{V_m}{\frac{1}{\omega C}} = \frac{V_m}{X_C}.$$

$$\text{Here, } X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}.$$

* conclusions :-

① 'I' leads 'v' by '90°'

② 'v' lags 'I' by '90°'

③ Power dissipation in pure capacitor is zero.

④ $x_c = \frac{1}{j\omega c}$, $x_c = \frac{1}{j2\pi f c} = \frac{-j}{2\pi f c}$



Capacitor blocks D.C. [$\because f = 0 \text{ Hz}$].

⑤ If $f=0$, circuit is open ' $x_c = \infty$ ' Ideal.

$f = \infty$, 'very high' \Rightarrow short circuit $x_c = 0$.

* Here $v = v_m \sin \omega t$

$$I = I_m \sin(\omega t + 90^\circ)$$

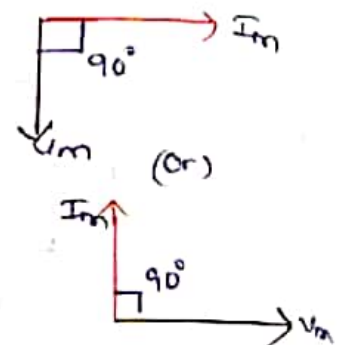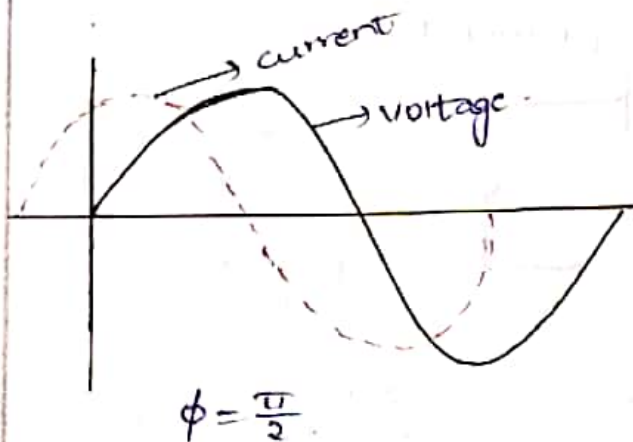

Power dissipation :-

We know, $P = vI$

$$\Rightarrow P = v_m \sin \omega t \cdot I_m \sin(\omega t + \frac{\pi}{2})$$

$$\Rightarrow P = v_m I_m \sin \omega t (\sin \omega t + \frac{\pi}{2})$$


$$\Rightarrow P = v_m I_m \sin \omega t \cos \omega t$$

$$\Rightarrow P = \frac{v_m I_m}{2} (2 \sin \omega t \cos \omega t)$$

$$\Rightarrow P = \frac{v_m I_m}{2} \sin 2\omega t$$

$$\therefore \underline{P = 0}$$

* Series RL circuit:-

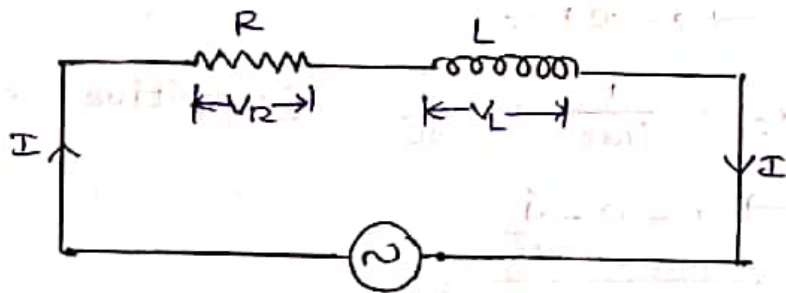

$$V = V_m \sin \omega t$$

$$I = I_m \sin(\omega t - \frac{\pi}{2})$$

→ According to KVL, $V = V_R + V_L$

We have, $I = \frac{V}{Z}$



$$\Rightarrow Z = R + X_L$$

$$\Rightarrow Z = R + j\omega L$$

$$\therefore |Z| = \sqrt{R^2 + X_L^2}$$

$$\therefore \phi = \tan^{-1}\left(\frac{X_L}{R}\right)$$


If $R=0$, $\phi = 90^\circ$

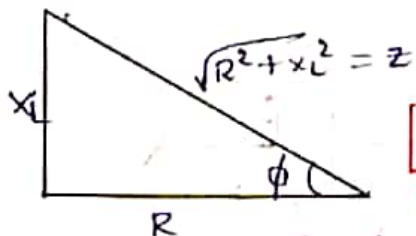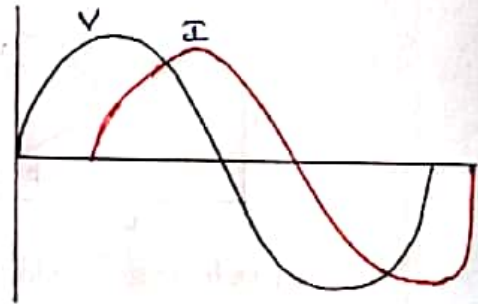

$$\cos \phi = \frac{R}{Z}$$


Power factor

Impedance Triangle

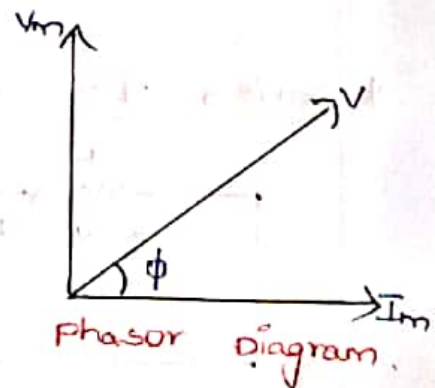

Phasor Diagram

* Series RC circuit:-

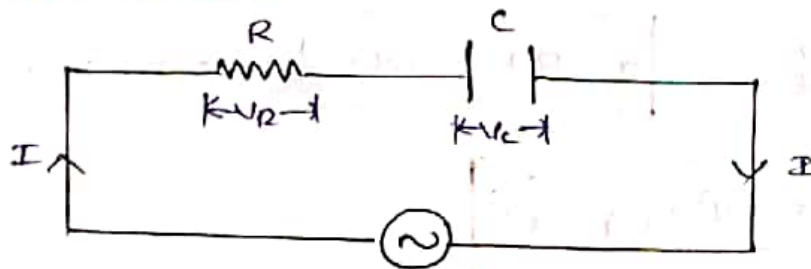

$$V = V_m \sin \omega t$$

$$I = I_m \sin(\omega t + \frac{\pi}{2})$$

$$V = V_R + V_C$$

$$I = \frac{V}{Z} \Rightarrow Z = R + X_C$$

We have, $I = \frac{V}{Z}$


$$\Rightarrow Z = R + X_C$$

Here, $X_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$ [capacitive Reactance]

$$\Rightarrow Z = R - \frac{j}{\omega C}$$

$$\Rightarrow |Z| = \sqrt{R^2 + X_C^2}$$

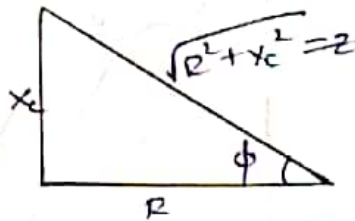
$$\therefore \phi = \tan^{-1}\left(\frac{Y}{X}\right) = \tan^{-1}\left(\frac{-1}{R\omega C}\right)$$



Impedance Triangle


$$\cos \phi = \frac{R}{Z}$$

Power factor

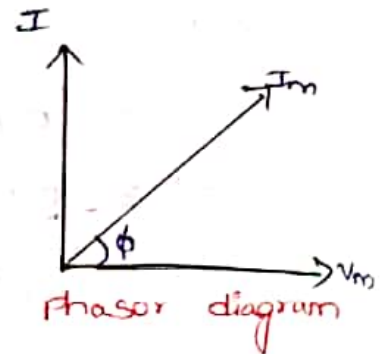

Phasor diagram

* Series RLC circuit :-

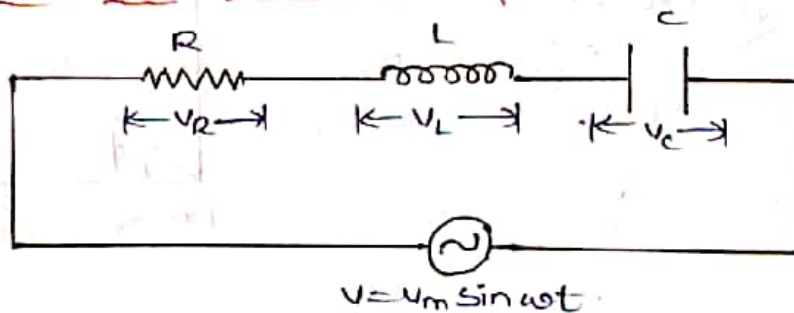

$$V = V_m \sin \omega t$$

$$\text{Here, } V = V_R + V_L + V_C$$

$$I = \frac{V}{Z}$$


$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) = R + j(X_L - X_C)$$

$$\therefore |Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\therefore \phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$


case-i :

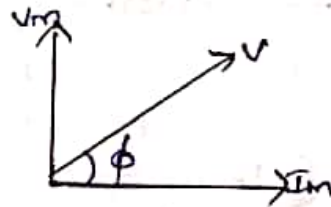→ If $x_L > x_C$ → Inductive RLC circuit.



case-ii :

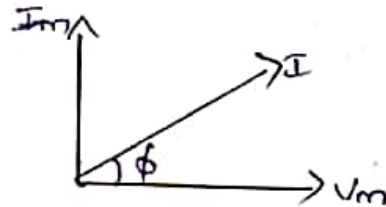→ If $x_L < x_C$ → Capacitive RLC circuit.



$$Z = \sqrt{R^2 + (x_C - x_L)^2}$$

$$\phi = \tan^{-1} \left(\frac{x_C - x_L}{R} \right)$$

case-iii :


→ If $x_L = x_C$ → Resonance condition.

$$Z = R$$

$$\phi = 0^\circ$$

→ At Resonance condition, circuit offers 'maximum current' and 'Impedance is minimum'.

→ This is Pure Resistive RLC circuit.

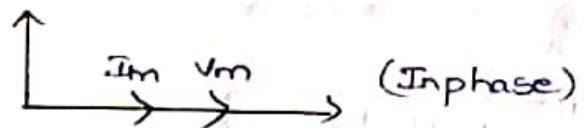

Resonance Frequency :

$$x_L = x_C$$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega^2 = \frac{1}{LC}$$


$$\Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow 2\pi f = \frac{1}{\sqrt{LC}}$$

$\therefore f = \frac{1}{2\pi\sqrt{LC}}$ is Resonance Frequency.

* Problems:

①

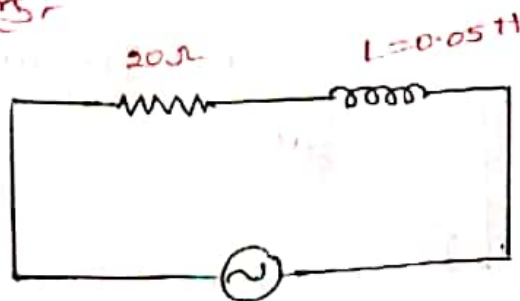

$$V = 100V$$

$$f = 50 \text{ Hz}$$

Find current (I) and power (P)?

A) We have, $I = \frac{V}{Z}$

$$Z = \sqrt{R^2 + X_L^2}$$

$$X_L = \omega L = 2\pi f (L)$$

$$= 2 \times 3.14 \times 50 \times 0.05$$

$$X_L = 15.7$$

$$\Rightarrow Z = \sqrt{R^2 + X_L^2} = \sqrt{20^2 + (15.7)^2} = 25.426$$

$$\therefore I = \frac{V}{Z} = \frac{100}{25.426} = 3.932 \text{ A}$$

$$\text{Now, } \phi = \tan^{-1}\left(\frac{X_L}{R}\right) = \tan^{-1}\left(\frac{15.7}{20}\right) = 38.14^\circ$$

$$\therefore I = 3.932 \angle -38.14^\circ \text{ A}$$

Power $p = |V| |I| \cos \phi$


$$\Rightarrow p = |100| |3.932| \cos(38.14)$$

$$\Rightarrow p = (393.2) \cos(38.14)$$

$$\Rightarrow p = (393.2) \times (0.786)$$

$$\therefore p = 309.253 \text{ W}$$

(R)

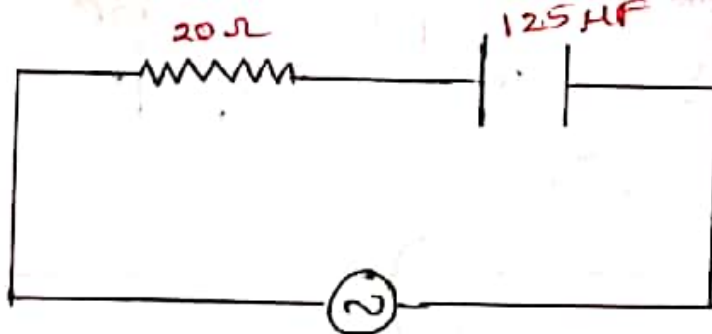

200V, 50Hz

Find current (I) and power (P)?

A) we have, $I = \frac{V}{Z}$

$$\Rightarrow Z = \sqrt{R^2 + (X_C)^2}$$

$$\Rightarrow X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi \times 50 \times 125 \times 10^{-6}}$$

$$X_C = 25.478$$

$$\Rightarrow Z = \sqrt{20^2 + (25.478)^2} = 32.3$$

$$\therefore I = \frac{V}{Z} = \frac{200}{32.3} = 6.19 \text{ A}$$

$$\therefore \phi = \tan^{-1}\left(\frac{X_C}{R}\right) = \tan^{-1}\left(\frac{25.478}{20}\right) = 51.34$$

$$\therefore \text{Power, } P = |V| |I| \cos \phi$$


$$\Rightarrow P = (200)(6.2) \cos(51.34)$$

$$\Rightarrow P = 1240 \times 0.624$$

$$\Rightarrow P = 773.76$$

$$\therefore \text{Power} = \underline{773.76 \text{ Watts}}$$

③

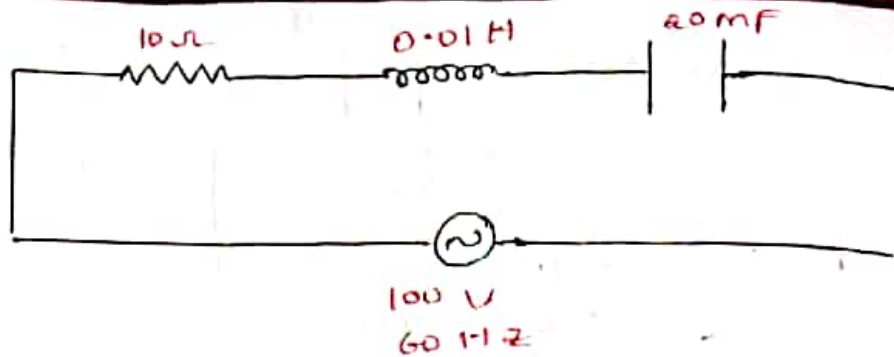

Find current (I)?

A) We have, $I = \frac{V}{Z}$

$$\Rightarrow Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\Rightarrow X_L = \omega L = 2\pi f L = 2 \times 3.14 \times 60 \times 0.01 = 3.768$$


$$\Rightarrow X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 60 \times 20 \times 10^{-3}} = 0.13269$$

$$\therefore Z = \sqrt{10^2 + (3.768 - 0.13269)^2} = 129.30 = 10.640$$

$$\therefore \left[I = \frac{V}{Z} = \frac{100}{129.30} = 0.77 \text{ A} \right]$$

$$\therefore I = \frac{V}{Z} = \frac{100}{10.640} = 9.39 \text{ A}$$

④

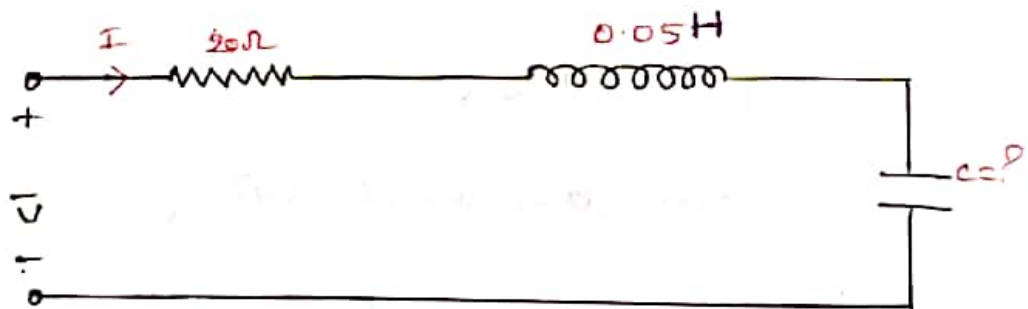

Given $I = 5 \angle 0^\circ \text{ A}$, $V = 100 + j200 \text{ V}$

$\omega = 1200 \text{ rad/s}$

Find 'C'?

A) Given, $R = 20 \Omega$

$L = 0.05 \text{ H}$

$X_L = j\omega L$

$\therefore X_L = j(1200 \times 0.05) \Omega$

$\therefore X_L = j60 \Omega$

$$X_C = \frac{-j}{\omega C} = \frac{-j}{1200C}$$

$$\therefore \text{Total Impedance, } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= 20 + (j60 - \frac{j}{1200C})$$

$$\therefore V = IZ$$

$$\Rightarrow 100 + j200 = 5 \angle 0^\circ [20 + j60 - \frac{j}{1200C}]$$


$$\Rightarrow 100 + j200 = 5 \angle 0^\circ [20 + j60 - \frac{j}{1200C}]$$

$$\Rightarrow 100 + j200 = 100 + 300j - \frac{5j}{1200C}$$

$$\Rightarrow 200j = 300j - \frac{j}{240C} \quad \text{[comparing imaginary part]}$$

$$\Rightarrow 200 = 300 - \frac{1}{240C}$$

$$\Rightarrow C = 41.6 \mu F$$

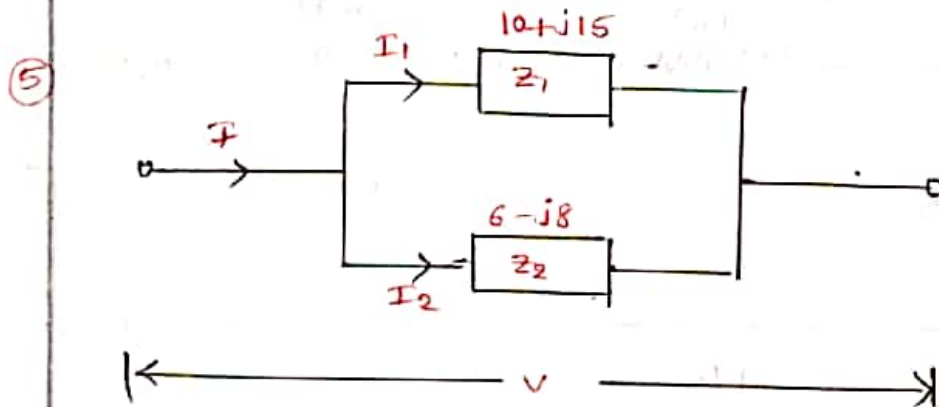

given $I = 15 \angle 0^\circ$, Find I_1, I_2 & V ?

A) According to current division rule

$$\Rightarrow I_1 = I \times \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow I_1 = I \times \frac{Z_2}{Z_1 + Z_2} = 15 \angle 0^\circ \left[\frac{6 - j8}{(10 + j15) + (6 - j8)} \right]$$

$$= 15 \angle 0^\circ \left[\frac{6 - j8}{16 + 7j} \right]$$

$$= 15 \angle 0^\circ \left[\frac{6 - j8}{16 + 7j} \right]$$

$$= 15 \left[\frac{6 - j8}{16 + 7j} \right] = \frac{120}{61} - \frac{510j}{61} = 8.58 \angle -76.7^\circ A$$

$$I_2 = I \times \frac{Z_1}{Z_1 + Z_2}$$

$$= 15 \angle 0^\circ \left[\frac{10 + j15}{(10 + j15) + (6 - j8)} \right]$$

$$= 15 \angle 0^\circ \left[\frac{10 + j15}{16 + j7} \right]$$



$$= 15 \angle 0^\circ \left[\frac{10 + j15}{16 + j7} \right] = \frac{345}{61} + \frac{510}{61}j = 15.49 \angle 32.7^\circ \text{ A}$$

$$\therefore V = I Z_1 \quad [\because V = I R_1]$$

$$= (8.58 \angle -76.7^\circ) (10 + j15)$$

$$= 144.98 - 53.89j$$

$$V = 154.67 \angle -20.39^\circ$$

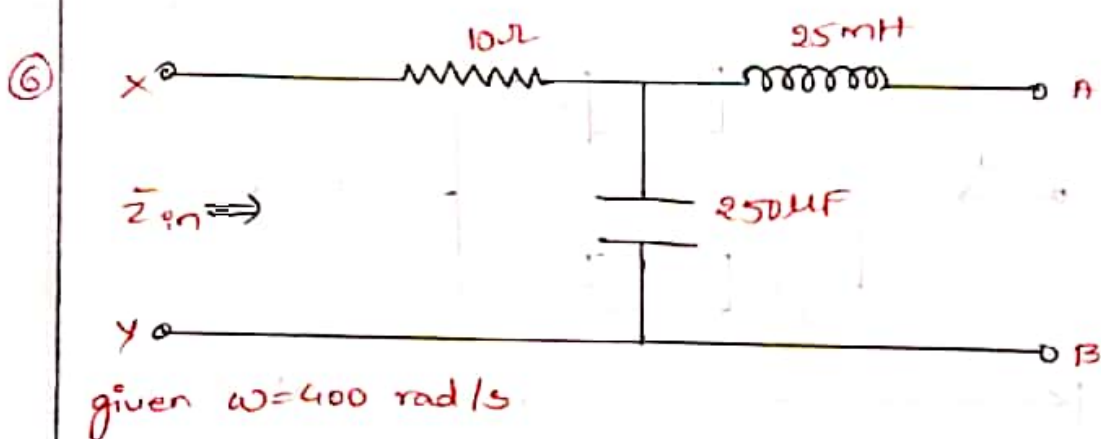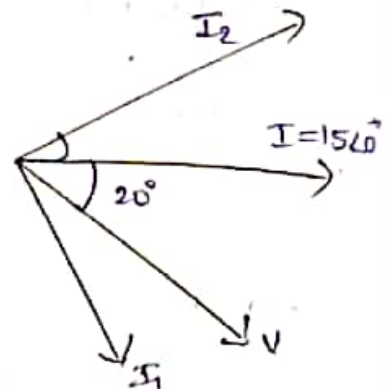

(a) When 'AB' opened find z_{in} ?

(b) When 'AB' short find z_{in} ?

(c) When 'AB' replaced by 10Ω find z_{in} ?

a) $X_L = j\omega L = j(400 \times 25 \times 10^{-3}) = j10 \Omega$

$$X_C = \frac{-j}{\omega C} = \frac{-j}{400 \times 250 \times 10^{-6}}$$

$$= \frac{-1000000j}{400 \times 250} = \frac{-1000000j}{100000} = -j10 \Omega$$

② When AB is opened. [25 mH is dummy].

$$Z_{in} = 10 + X_C$$

$$= 10 - j10 \Omega$$

$$\therefore Z_{in} = \underline{14.14 \angle -45^\circ \Omega}$$

③ When AB shorted,

series: $10 \Omega + (25 \parallel 250)$.

$$\text{parallel: } \frac{25 \times 250}{25 + 250} = \frac{X_L \times X_C}{X_L + X_C}$$

$$= \frac{j10 \times -j10}{j10 - j10} = \frac{j10 \times -j10}{0} = \infty$$

$$\therefore \text{series} = 10 \Omega + \infty j = 10 + \infty j$$

④ Series +
 $10 + (25 \text{ mH}) = 10 + X_L$
 $= 10 + 10j$

\neq

parallel + $(10 + 10j) \parallel (X_C)$

$$= \frac{(10 + 10j) \times (-j10)}{(10 + 10j) - j10}$$

$$= 10 - 10j$$

Series +

$$= 10 - 10j + 10 \Omega$$

$$= 20 - 10j$$


$$= \underline{22.36 \angle -26.6^\circ \text{ A}}$$

When AB replaced by 10Ω .

* <u>Element</u>	<u>Real part (P)</u>	<u>Imaginary Reactive part (Q)</u>
R	$P = I_{rms} V_{rms}$	—
L	$P = 0$	$Q_L = \frac{V_L}{X_L}$
C	$P = 0$	$Q_C = \frac{V_C}{X_C}$

* Complex Power:

$$S = P + jQ$$

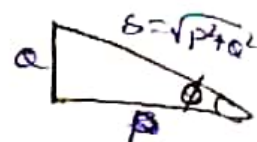

* → This is also called 'Power triangle'

→ ' $\cos \phi$ ' is 'power factor'

$$\rightarrow I_{avg} = 0$$


$$\rightarrow I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$P = I_{rms} V_{rms} \cos \phi$$

$$Q = I_{rms} V_{rms} \sin \phi$$


$$S = I_{rms} V_{rms}$$

* Problem [super position Theorem]

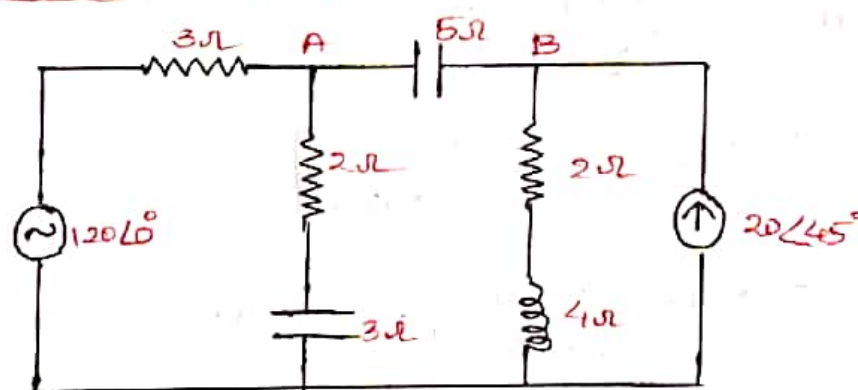

Find current passing through capacitor, $I_{CAB} = ?$

A) Step-1

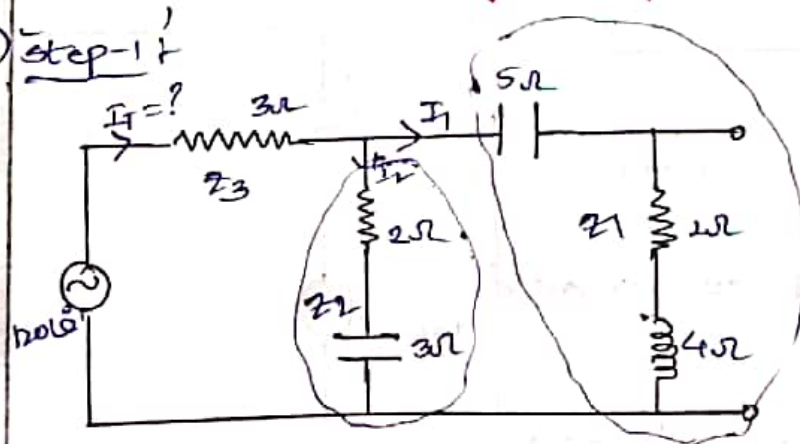

$$z_1 = 2 + j4 - j5 = (2 - j1) \Omega$$

$$z_2 = (2 - 3j) \Omega$$

$$\therefore z_T = z_3 + (z_2 \parallel z_1)$$

$$z_T = 3 + \left[\frac{(2-j) \times (2-3j)}{(2-j) + (2-3j)} \right] = 4.25 - 0.875j \Omega$$

$$\text{Now, } I_T = \frac{V}{z_T}$$

$$\Rightarrow I_T = \frac{120 \angle 0^\circ}{4.25 - 0.875j} = 27.84 + j5.90$$

$$\therefore I_T = \underline{28.46 \angle 11.96^\circ}$$


Now,

$$I_1 = I_T \left(\frac{z_2}{z_2 + z_1} \right)$$

$$I_1 = 28.46 \angle 11.96^\circ \left[\frac{(2-3j)}{(2-j1) + (2-3j)} \right]$$

$$\therefore I_1 = \underline{18.1375 + j0.2075 \text{ A}} \quad [A \rightarrow B]$$

Step-2

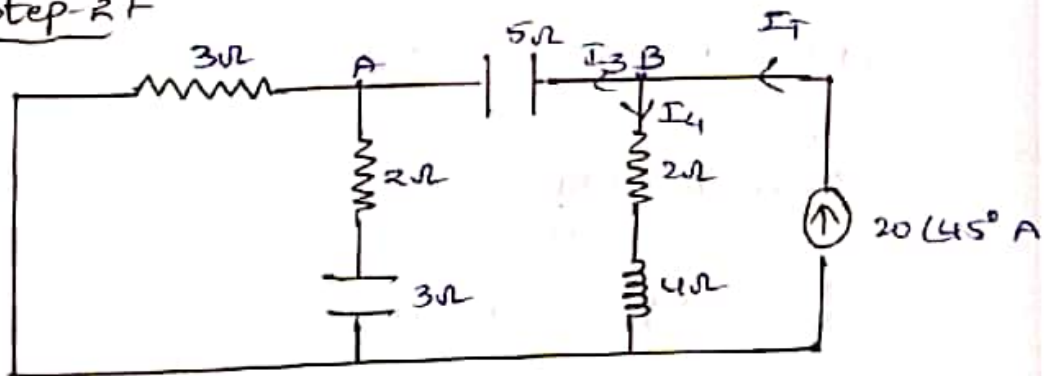

$$3\Omega \parallel (2\Omega + 3\Omega)$$

$$\Rightarrow 3\Omega \parallel (2-3j)$$

$$\Rightarrow \frac{3 \times (2-3j)}{3+2-3j} = \frac{(6-9j)}{5-j1} = 1.855 \angle -25.14^\circ = z_R$$

$$\therefore I_3 = I_T \left(\frac{z_R}{5+z_R} \right) = 7.064 + j16.92 \text{ A} \quad [B \rightarrow A]$$


$$\therefore I_{\text{Resultant}} = I_1 - I_3 =$$

* star connected 3 phase Network :


$$V_1 = V_m \sin \omega t$$

$$V_2 = V_m \sin(\omega t + 120^\circ)$$

$$V_3 = V_m \sin(\omega t + 240^\circ)$$

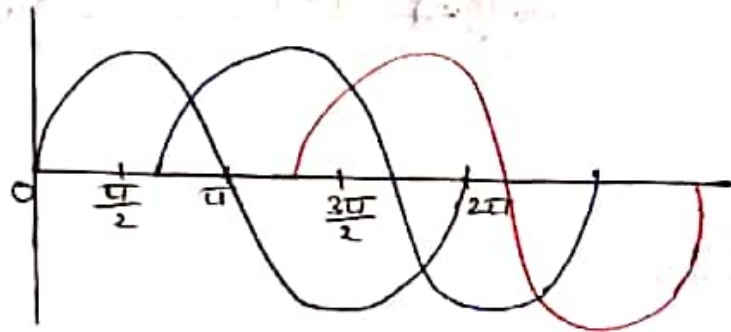

Balanced :

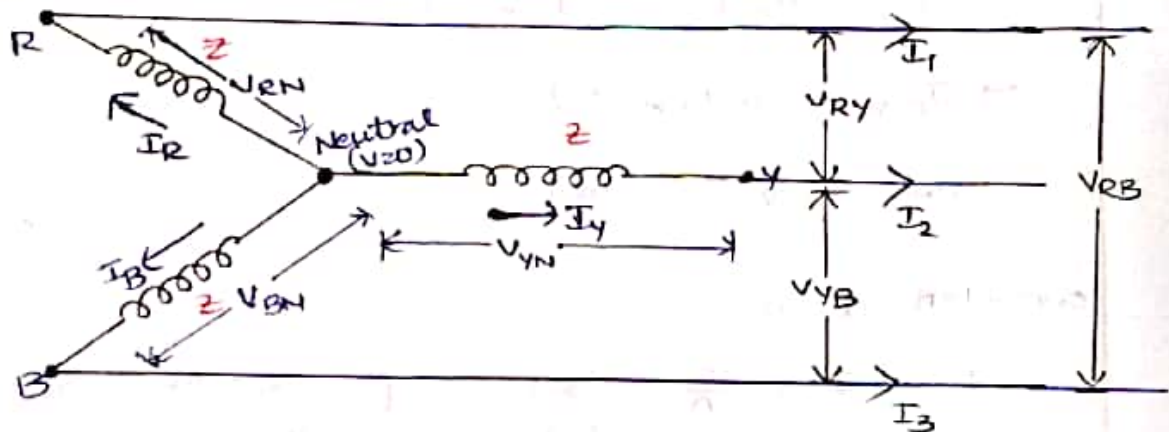

Here, 'phase currents' : I_R, I_Y, I_B

'Line currents' : I_1, I_2, I_3

→ In Balanced mode,

$$I_R = I_Y = I_B = I_{\text{phase}}$$

$$I_1 = I_2 = I_3 = I_{\text{Line}}$$

$$\therefore I_{\text{phase}} = I_{\text{Line}}$$

→ Here, In Balanced mode, $V_{RN} = V_{YN} = V_{BN} = V_{\text{phase}}$.


$$V_{RY} = V_{YB} = V_{RB} = V_{\text{Line}}$$

$$\text{But } V_{ph} \neq V_L$$

If N is connected to ground,

$$V_R = V_Y = V_B = V_{ph}$$

* Derivation for $V_{ph} \neq V_L$:-

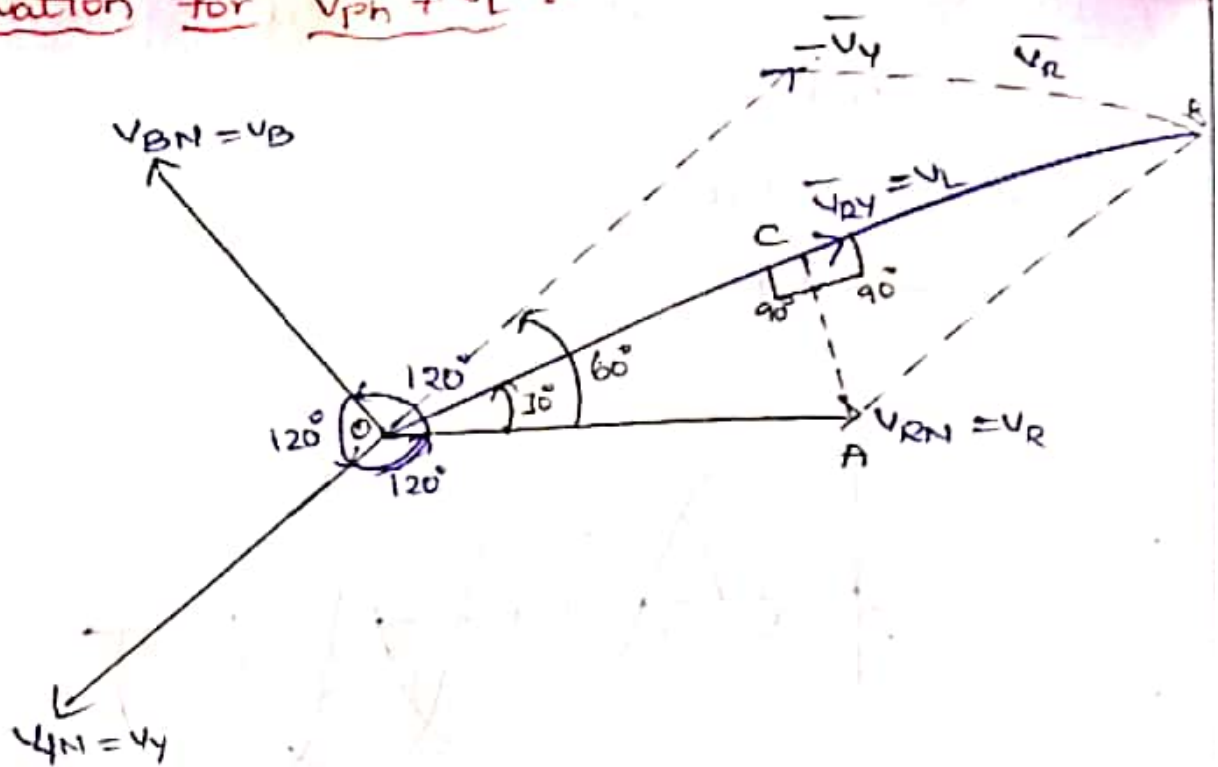

Now, $V_{RY} = V_R - V_Y$

$$\Rightarrow \vec{V}_{RY} = \vec{V}_R + (-\vec{V}_Y) \longrightarrow (1)$$

$$\Rightarrow \vec{V}_{RB} = \vec{V}_R + (-\vec{V}_B) \longrightarrow (2)$$

$$\Rightarrow \vec{V}_{YB} = \vec{V}_Y + (-\vec{V}_B) \longrightarrow (3)$$

consider, $\triangle OCA$

$$\Rightarrow \cos 30^\circ = \frac{OC}{OA} = \frac{\left(\frac{V_L}{2}\right)}{V_{ph}}$$

$$\left[\begin{array}{l} \because V_R = V_{phase} \text{ } \vec{E}_1 \\ V_L = V_{RY} \end{array} \right]$$

$$\Rightarrow \frac{\sqrt{3}}{2} = \frac{\left(\frac{V_L}{2}\right)}{V_{ph}}$$

$$\Rightarrow \frac{\sqrt{3}}{2} = \frac{1}{2} \left(\frac{V_L}{V_{ph}} \right)$$


$$\Rightarrow \sqrt{3} = \frac{V_L}{V_{ph}}$$

$$\therefore \boxed{V_L = \sqrt{3} V_{ph}}$$

$$(\text{or}) \boxed{V_{ph} = \frac{V_L}{\sqrt{3}}}$$

Now, $\vec{v}_{RB} = \vec{v}_R - \vec{v}_B$

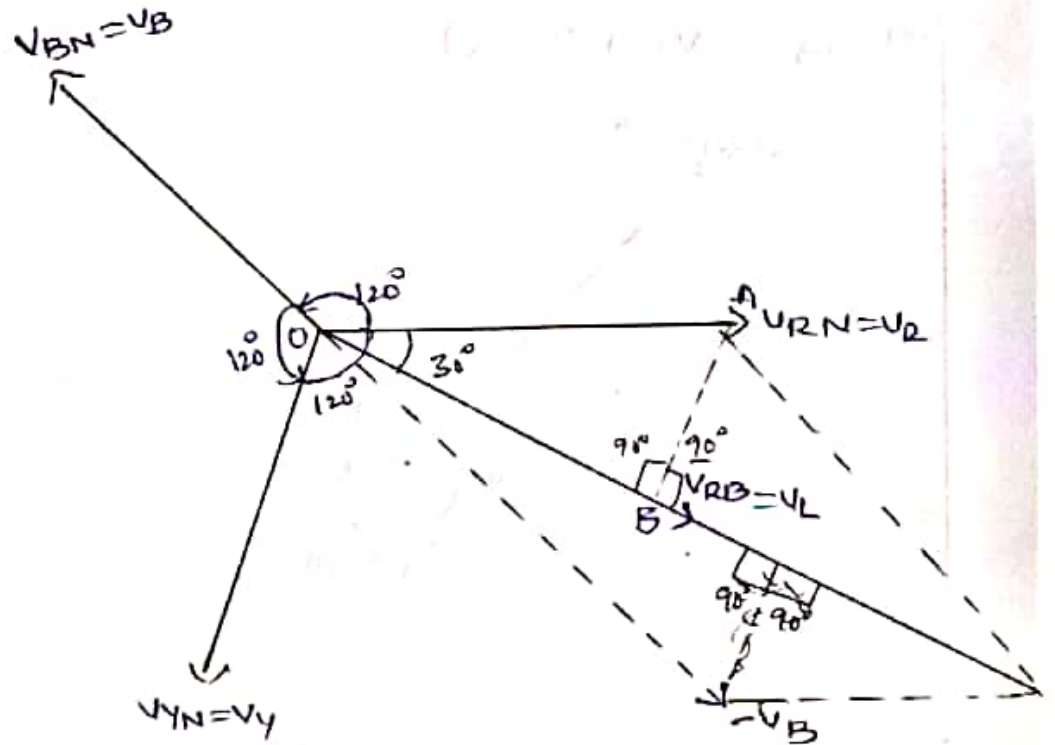$\Rightarrow \vec{v}_{RB} = \vec{v}_R + (-\vec{v}_B)$



Consider, $\triangle OAB$

$\Rightarrow \cos \theta = \frac{\text{Adj}}{\text{Hyp}}$

$\Rightarrow \cos 30^\circ = \frac{OB}{OA}$

$\Rightarrow \cos 30^\circ = \frac{\frac{v_{RB}}{2}}{v_R}$

$[\because \frac{v_{RB}}{2} = \frac{v_L}{2}]$

$[\because v_R = v_{ph}]$

$\Rightarrow \frac{\sqrt{3}}{2} = \frac{\frac{v_L}{2}}{v_{ph}}$

$\Rightarrow \frac{\sqrt{3}}{2} = \frac{1}{2} \frac{v_L}{v_{ph}}$

$\Rightarrow \sqrt{3} = \frac{v_L}{v_{ph}}$

$\therefore \boxed{v_L = \sqrt{3} v_{ph}}$


or

$\boxed{v_{ph} = \frac{v_L}{\sqrt{3}}}$

Now, equation-3

$$\Rightarrow \vec{v}_{yB} = \vec{v}_y - \vec{v}_B$$
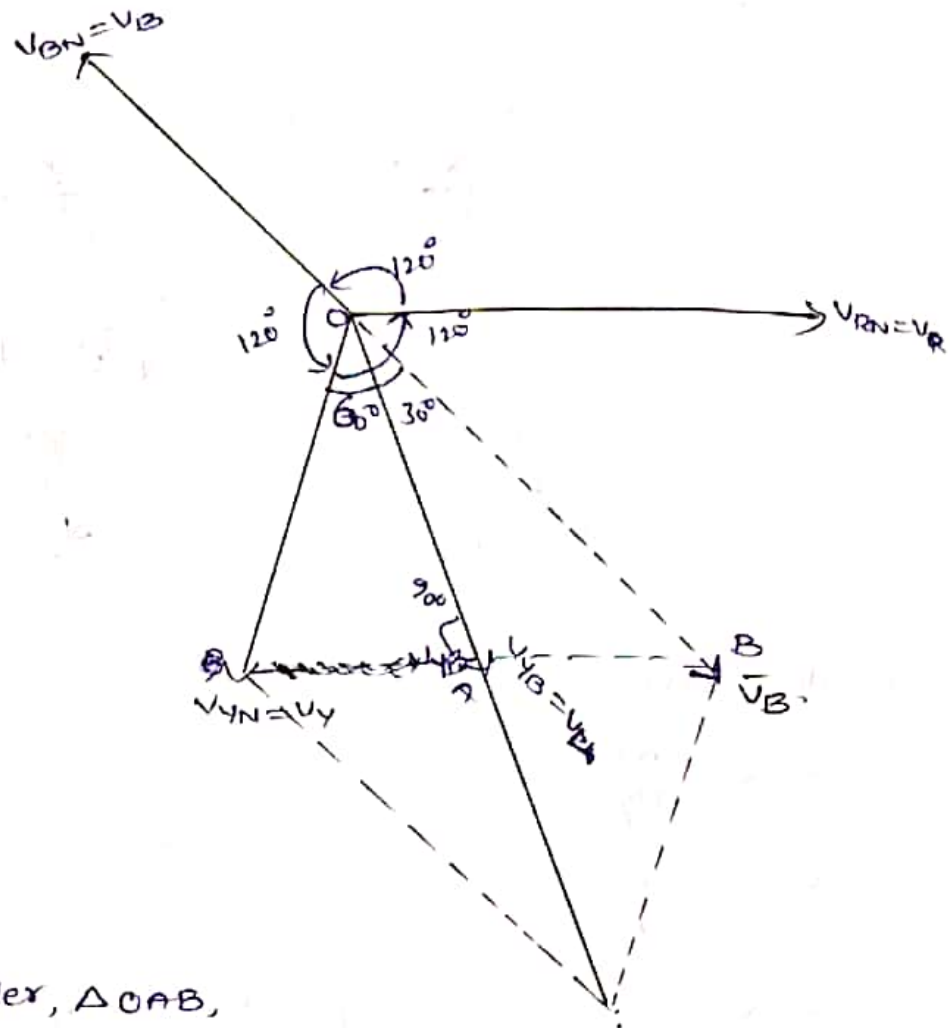
$$\Rightarrow \vec{v}_{yB} = \vec{v}_y + (-\vec{v}_B)$$



consider, $\triangle OAB$,

$$\Rightarrow \cos 30^\circ = \frac{OA}{OB}$$


$$\Rightarrow \frac{\sqrt{3}}{2} = \frac{\frac{v_y}{2}}{v_B}$$

$$\Rightarrow \frac{\sqrt{3}}{2} = \frac{1}{2} \frac{v_L}{v_{ph}} \quad \left[\because \frac{v_y}{2} = v_L \right]$$

$$\Rightarrow \sqrt{3} = \frac{v_L}{v_{ph}}$$

$$\therefore \boxed{v_L = \sqrt{3} v_{ph}} \quad (\text{or}) \quad \boxed{v_{ph} = \frac{v_L}{\sqrt{3}}}$$

* Delta connected 3phase Networks:-

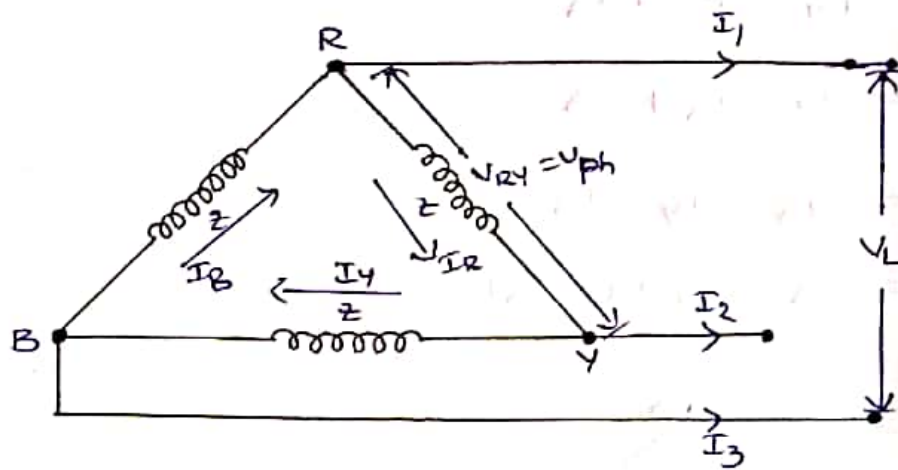

→ In delta connected network, Line current is not equal to phase current

Here, I_R, I_Y, I_B are phase currents

I_1, I_2, I_3 are Line currents.

$$\therefore \boxed{I_{ph} \neq I_L}$$

→ Here, $\boxed{V_{ph} = V_L}$

→ Apply KCL at R:

$$I_B = I_1 + I_R$$

$$I_1 = I_B - I_R$$

$$I_1 = I_B + (-I_R)$$


consider $\triangle OBC$

$$\Rightarrow \cos 30^\circ = \frac{OB}{OC}$$

$$\Rightarrow \cos 30^\circ = \frac{\frac{I_L}{2}}{I_{ph}} \quad \left[\begin{array}{l} OB = I_1 = \frac{I_L}{2} \\ OC = I_B = I_{ph} \end{array} \right]$$

$$\Rightarrow \frac{\sqrt{3}}{2} = \frac{1}{2} \left(\frac{I_L}{I_{ph}} \right)$$
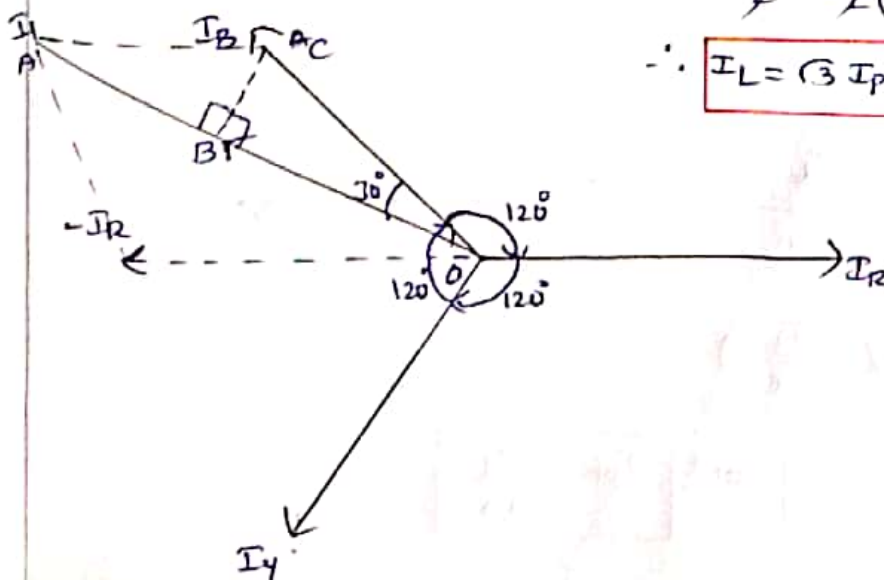
$$\therefore \boxed{I_L = \sqrt{3} I_{ph}} \quad (\text{or}) \quad \boxed{I_{ph} = \frac{I_L}{\sqrt{3}}}$$




Applying KCL at B:-

$$I_4 = I_3 + I_B$$

$$\Rightarrow I_4 = I_3 + I_B$$

$$\Rightarrow I_3 = I_4 - I_B$$

$$\Rightarrow I_3 = I_4 + (-I_B)$$

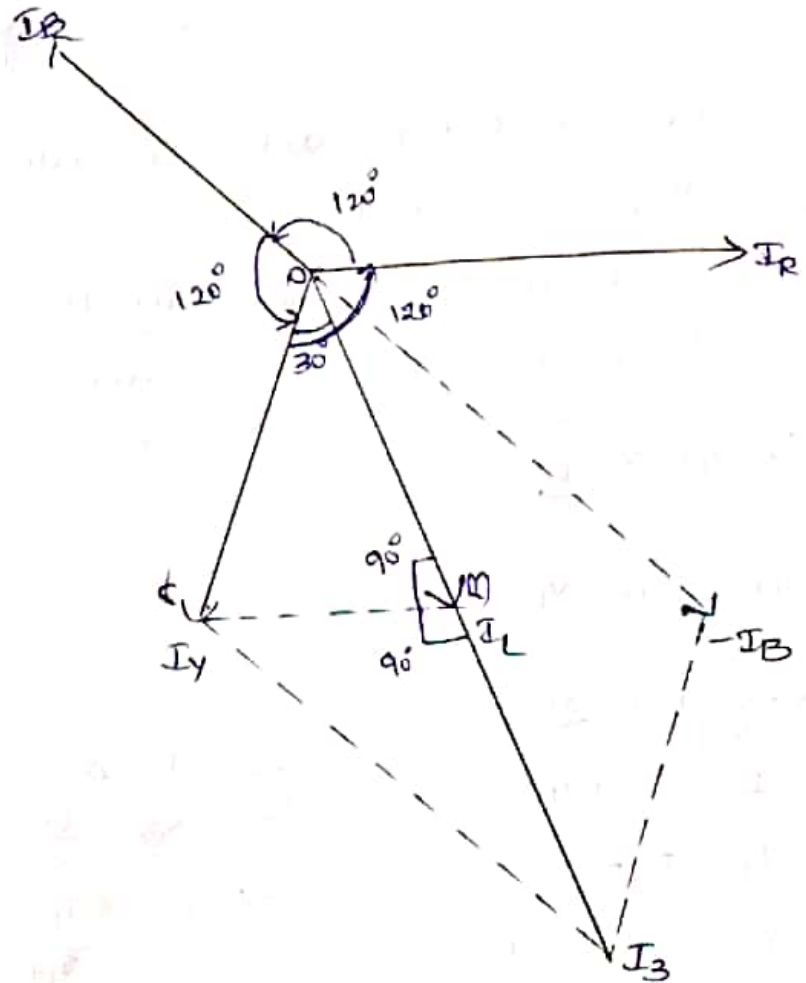

consider ΔOAB .

$$\Rightarrow \cos 30^\circ = \frac{OB}{OA}$$

$$\Rightarrow \frac{\sqrt{3}}{2} = \frac{\frac{I_L}{2}}{I_{ph}}$$

$$[\because I_4 = I_{ph} \text{ \& \& } I_3 = \frac{I_L}{2}]$$

$$\Rightarrow \frac{\sqrt{3}}{2} = \frac{1}{2} \left(\frac{I_L}{I_{ph}} \right)$$


$$\Rightarrow \boxed{I_L = \sqrt{3} I_{ph}} \text{ (or) } \boxed{I_{ph} = \frac{I_L}{\sqrt{3}}}$$

Applying KCL at y i

$$I_R = I_2 + I_y$$

$$\Rightarrow I_2 = I_R - I_y$$
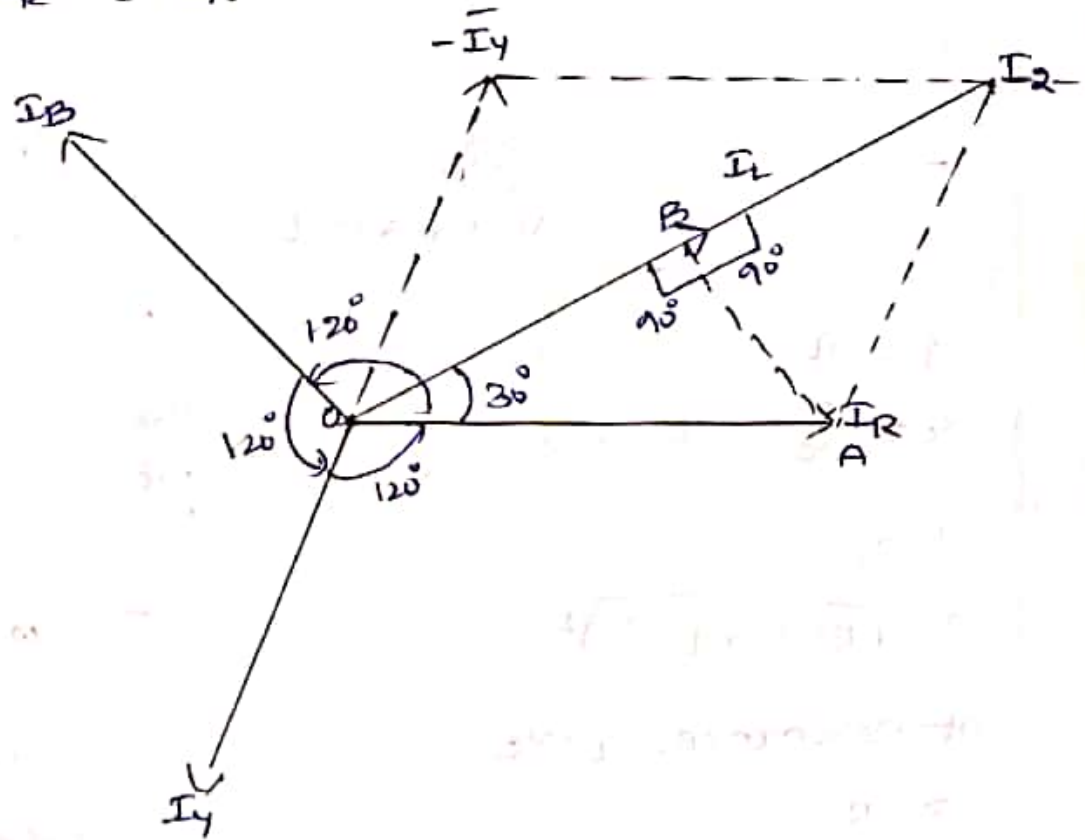
$$\Rightarrow I_2 = \bar{I}_R + (-\bar{I}_y)$$



Consider ΔOAB ,


$$\Rightarrow \cos 30^\circ = \frac{OB}{OA}$$

$$\Rightarrow \frac{\sqrt{3}}{2} = \frac{I_L}{I_R}$$

$$\Rightarrow \frac{\sqrt{3}}{2} = \frac{1}{2} \left[\frac{I_L}{I_{ph}} \right] \quad [\because I_R = I_{ph}]$$

$$\Rightarrow \sqrt{3} = \frac{I_L}{I_{ph}}$$

$$\therefore \underline{I_L = \sqrt{3} I_{ph}} \quad (\text{or}) \quad \underline{I_{ph} = \frac{I_L}{\sqrt{3}}}$$

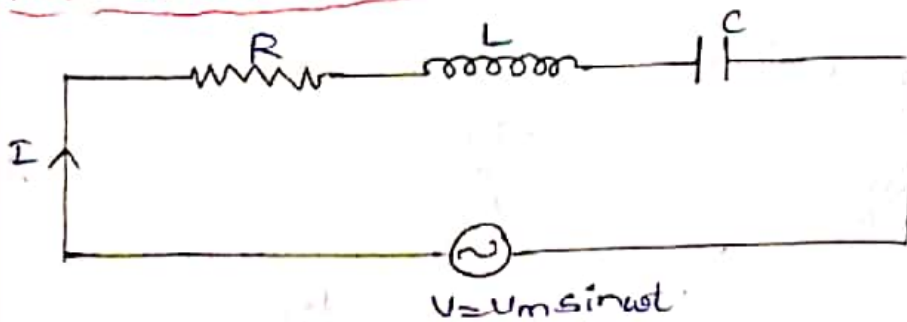* RLC - Series circuit :-

$$X_L = \omega L : \text{If } \omega = 0, X_L = 0, X_C = \infty$$

$$X_C = \frac{1}{\omega C} : \text{If } \omega = \infty, X_C = 0, X_L = \infty$$

At $X_L = X_C$


$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

At Resonance, $X_L = X_C$

$$Z = R$$


purely resistive.

$$I_{\max} = \frac{V}{R}$$

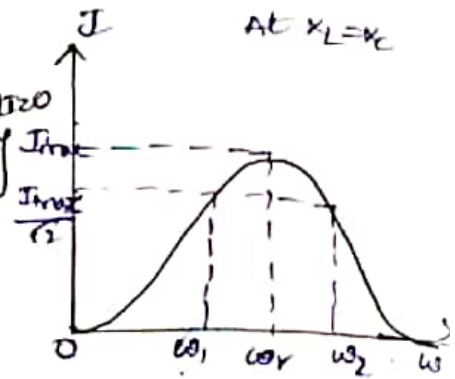

ω_1 = lower cut off frequency

ω_2 = higher cut off frequency

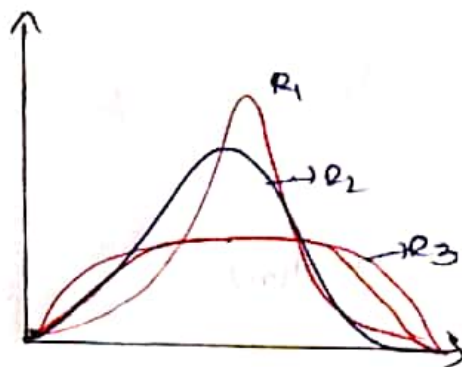

$$R_1 < R_2 < R_3$$

① Quality factor (Q) :-

$$Q = 2\pi \frac{\text{Energy stored}}{\text{Energy dissipated}}$$

② Bandwidth (BW) :-

→ The difference between half power frequencies is called Bandwidth.

$$BW = \omega_2 - \omega_1 \quad [\text{in the above graph}]$$

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$I_1 = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{I_{\max}}{\sqrt{2}} = \frac{\frac{V}{R}}{\sqrt{2}} = \frac{V}{\sqrt{2}R} \quad \left[\because I_{\max} = \frac{V}{R} \right]$$

$$\Rightarrow I_1^2 = \frac{V^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \frac{V^2}{2R^2}$$

$$= R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 = 2R^2$$

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = 2R^2 - R^2$$

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = R^2$$

$$\therefore \boxed{\omega L - \frac{1}{\omega C} = \pm R}$$

$$\text{Similarly, } \boxed{\omega_2 L - \frac{1}{\omega_2 C} = \pm R}$$

$$\text{Now, } \omega_1 < \omega_r < \omega_2$$

$$\Rightarrow \omega_1 L - \frac{1}{\omega_1 C} = -R$$

$$\Rightarrow \omega_1^2 LC - 1 = -R\omega_1 C$$

$$\Rightarrow \omega_1^2 LC + R C \omega_1 = 1$$

$$\Rightarrow \omega_1^2 LC + R C \omega_1 - 1 = 0$$

$$\Rightarrow \frac{\omega_1^2 LC}{LC} + \frac{R C \omega_1}{LC} - \frac{1}{LC} = 0$$

$$\Rightarrow \omega_1^2 + \frac{R}{L} \omega_1 - \frac{1}{LC} = 0$$

$$\Rightarrow \omega_1 = \frac{-R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4(1)\left(-\frac{1}{LC}\right)}$$

$$= \frac{-R}{L} \pm \frac{\sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}}}{2(1)}$$

$$\omega_1 = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\text{Similarly, } \omega_2 = \frac{+R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\therefore \text{Bandwidth, } BW = \omega_2 - \omega_1 = \frac{2R}{2L} = \frac{R}{L} \quad \therefore BW = \omega_2 - \omega_1 = \frac{R}{L}$$

quality factor, $Q = \frac{\text{avg. } I^2 X_L}{I^2 R} = \frac{I^2 X_C}{I^2 R}$

$$\Rightarrow Q = \frac{X_L}{R} = \frac{X_C}{R}$$

$$\Rightarrow Q = \frac{\omega L}{R} = \frac{1}{\omega R C}, \quad \omega = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}} ; \quad \boxed{Q = \frac{1}{R} \sqrt{\frac{L}{C}}}$$

Also,

$$\boxed{Q = \frac{\omega_r}{\Delta \omega}} \Rightarrow \boxed{Q = \frac{\omega_r}{\omega_2 - \omega_1}}$$