

Unit-6

Bi – Polar Junction Transistors

Bi – Polar Junction Transistor


- ▶ **Define Transistor** : Transistor = Trans + Resistor ,Transfer of resistance from lower concentration to higher concentration or Vice versa
- ▶ BJT was invented by William Shockley ,John Bardeen and Barttaint in 1947 Dec 23
- ▶ A BJT is device of two back to back connected PN junction diodes having three terminals like Emitter (E), Base (B) & Collector (C)
- ▶ BJT is a 3 terminal , 3 layer, 2 junctions , bi-directional & current controlled device
- ▶ 3 terminals : Base, Emitter, Collector
- ▶ 3 Layer : N P N or P N P
- ▶ 2 Junctions : E-B junction (J_E), C-B Junction (J_C)
- ▶ Bi-directional : Current flow due to both majority & minority charge carriers

Continued.....

- ▶ **Transistor terminal description :**
- ▶ **Emitter:** It has moderate size, heavily doped terminal, its main function is to supply a number of majority carriers or charge carriers either electrons or holes. Emitter emits the charge carriers, it occupies moderate area
- ▶ **Base:** middle terminal is base terminal ,this is thin and lightly doped terminal
- ▶ Its main function is to pass the majority charge carriers from the emitter to collector
- ▶ It acts like a mediator in between emitter & collector
- ▶ It occupies less area
- ▶ **Collector:** it is moderately doped, it occupies more area compared to emitter and base, size of collector terminal is large, its function is to collect the charge carriers from base and emitter
- ▶ BJT is a Asymmetrical device


Continued.....

► Types of Transistors :

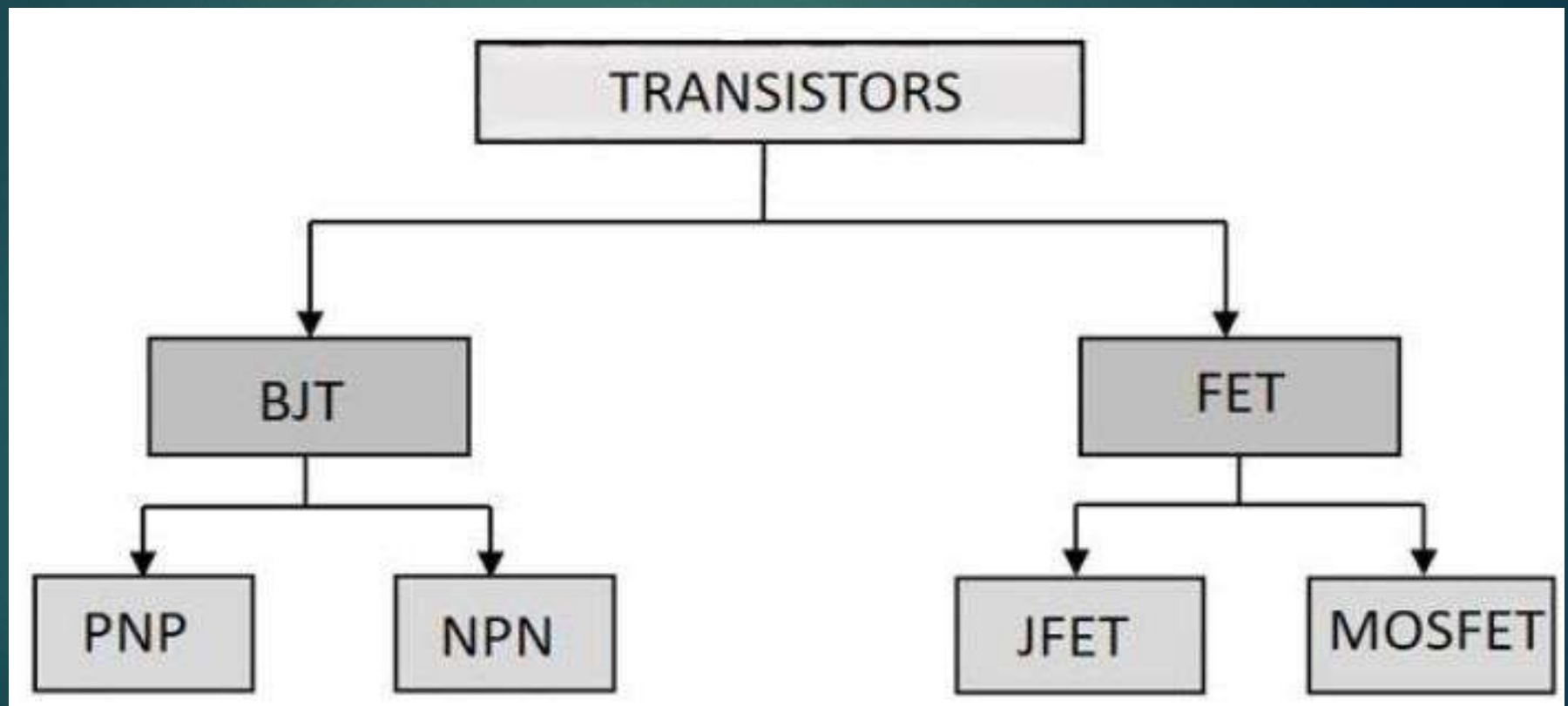


Continued.....

► Symbols of NPN & PNP Transistors :

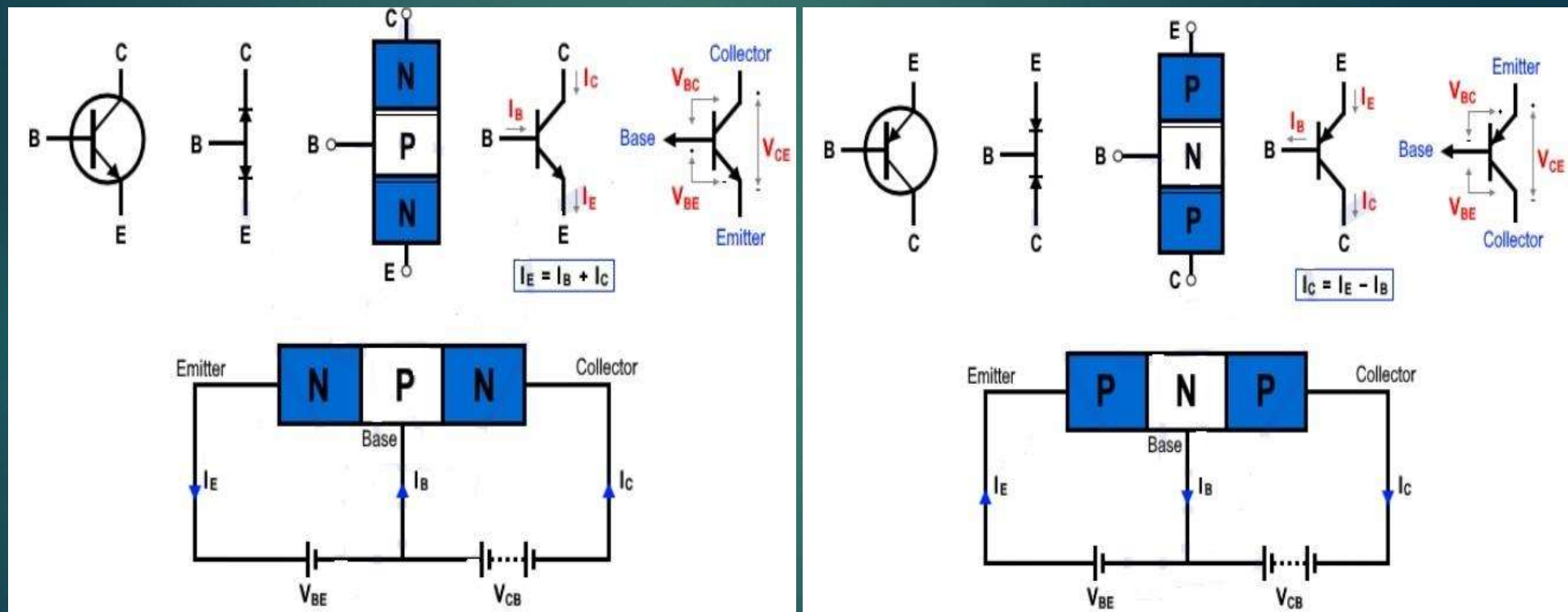

Continued.....

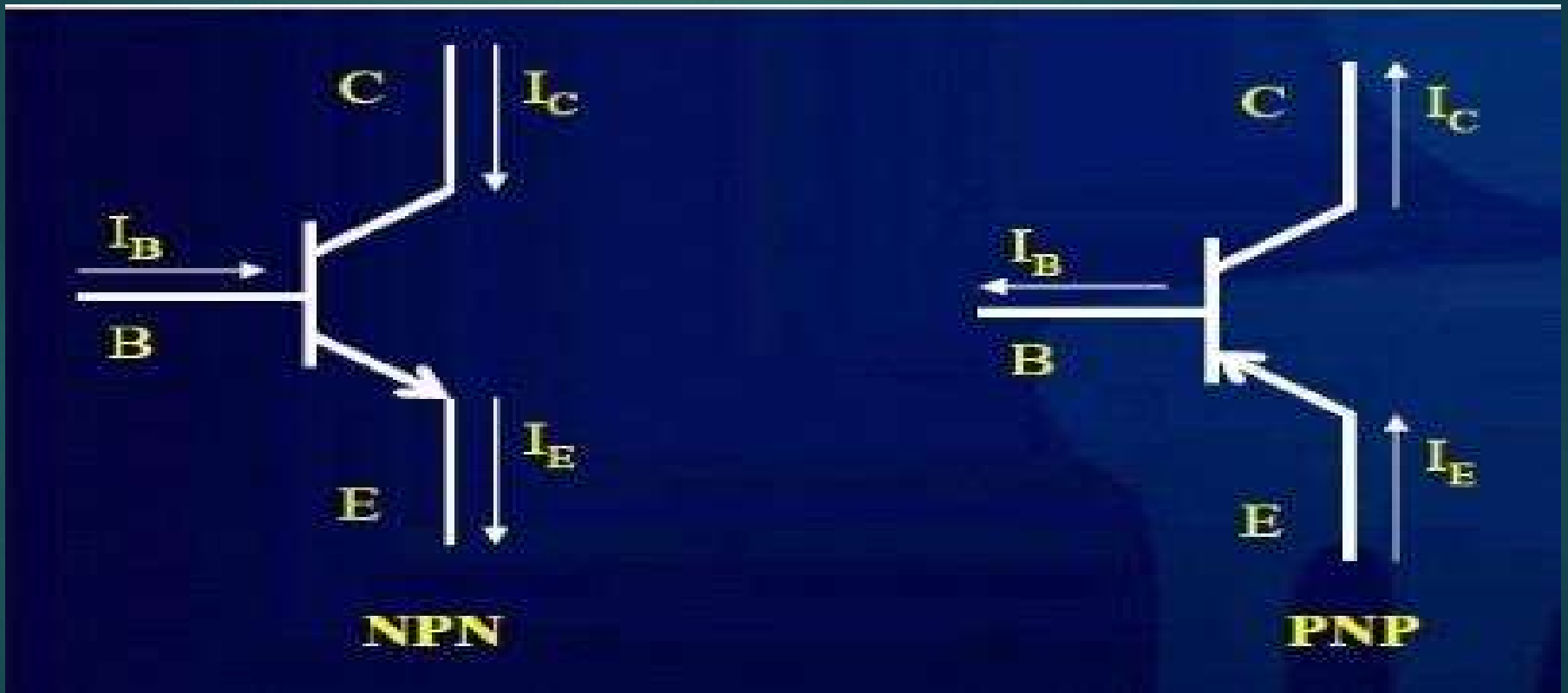
- Current Directions in both NPN & PNP Transistors :



From circuit : $I_E = I_C + I_B$

Continued.....

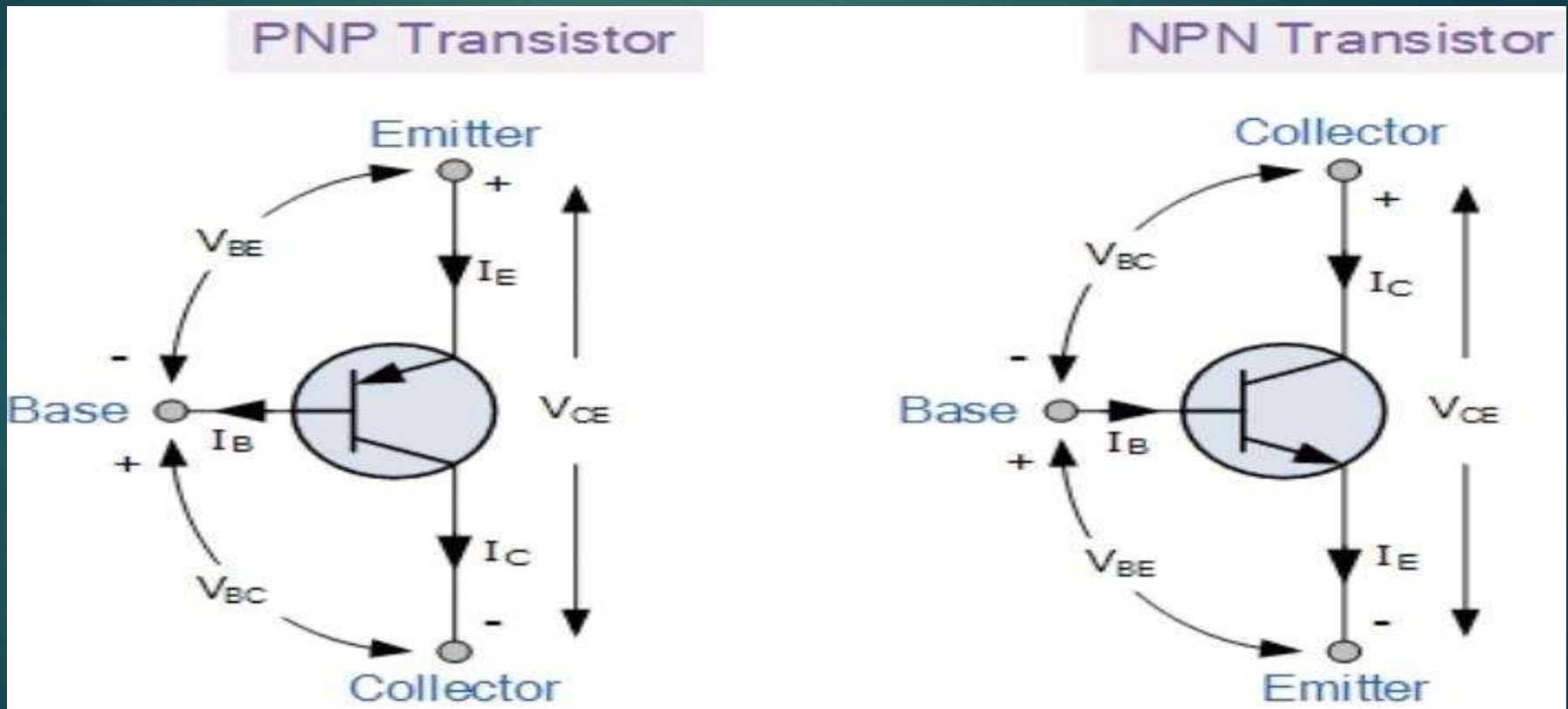- Voltage representation of PNP & NPN Transistor :



100

-


Continued.....

- ▶ **Transistor Parameters :**
- ▶ **Transistor current :** current flowing across the collector (I_E , I_B , I_C)
- ▶ **Alpha (α):**It is the ratio of the DC collector current to the DC emitter current ,it is always equal to 1 or slightly less than 1
$$\alpha = I_C / I_E$$
 where α is “**current amplification factor**” of Common Base configuration
- ▶ **Beta (β):**It is the ratio of the DC collector current to the DC base current ,it is always equal to 1 or slightly less than 1
$$\beta = I_C / I_B$$
 where β is “**current amplification factor**” of Common Emitter configuration
- ▶ **Gamma (γ):**It is the ratio of the DC emitter current to the DC base current
$$\gamma = I_E / I_B$$
 where γ is “**current amplification factor**” of Common Collector configuration
- ▶ **Current rating:** Maximum current a transistor can pass through its collector and emitter $I_{C_{max}}$

Continued.....


- ▶ **Transistor Operating Regions** : Transistor can be operating in four (4) regions depending on J_E and J_C junctions

<u>Operating region</u>	<u>E - B Junction (J_E)</u>	<u>C - B Junction (J_C)</u>	<u>Application</u>
Active region	J_E forward biased	J_C reverse biased	Amplifier
Saturation region	J_E forward biased	J_C forward biased	ON switch or logic 1
Cut off region	J_E reverse biased	J_C reverse biased	OFF switch or logic 0
Inverse active region	J_E reverse biased	J_C forward biased	Attenuator

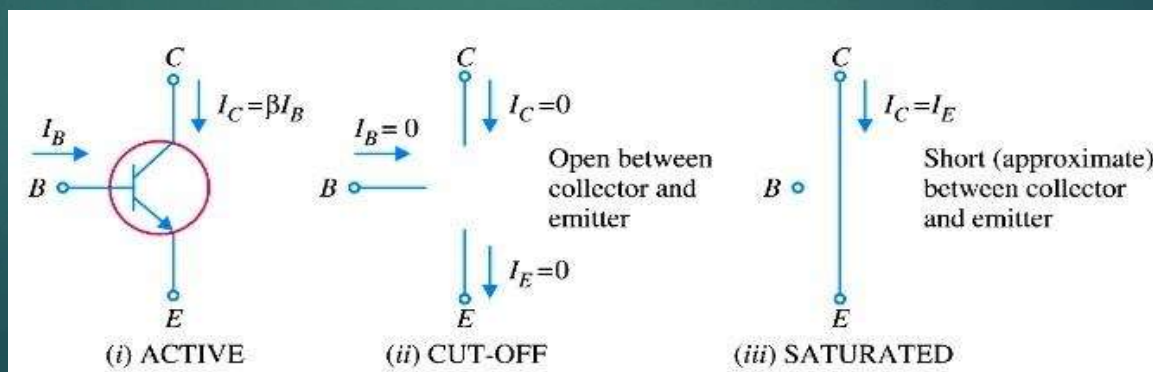


Transistor Regions Circuits

► Operating region circuits :

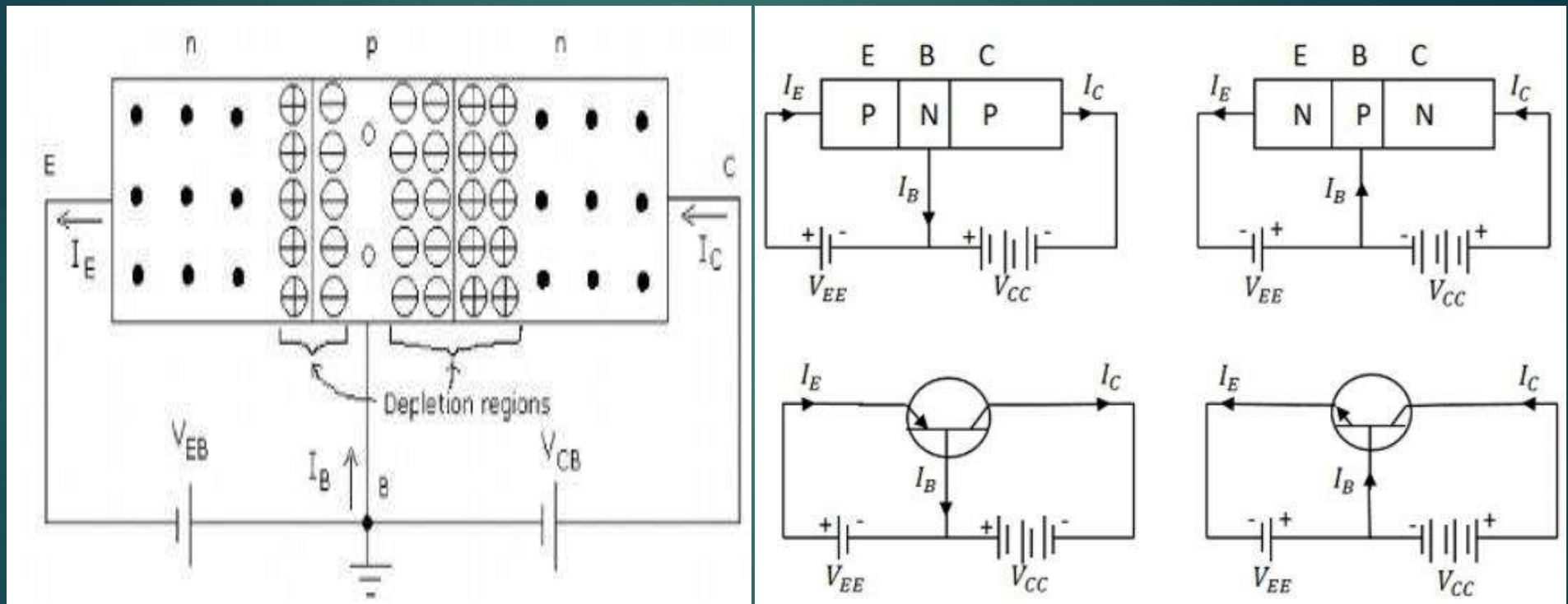


Continued.....

► Common Emitter NPN Transistor :

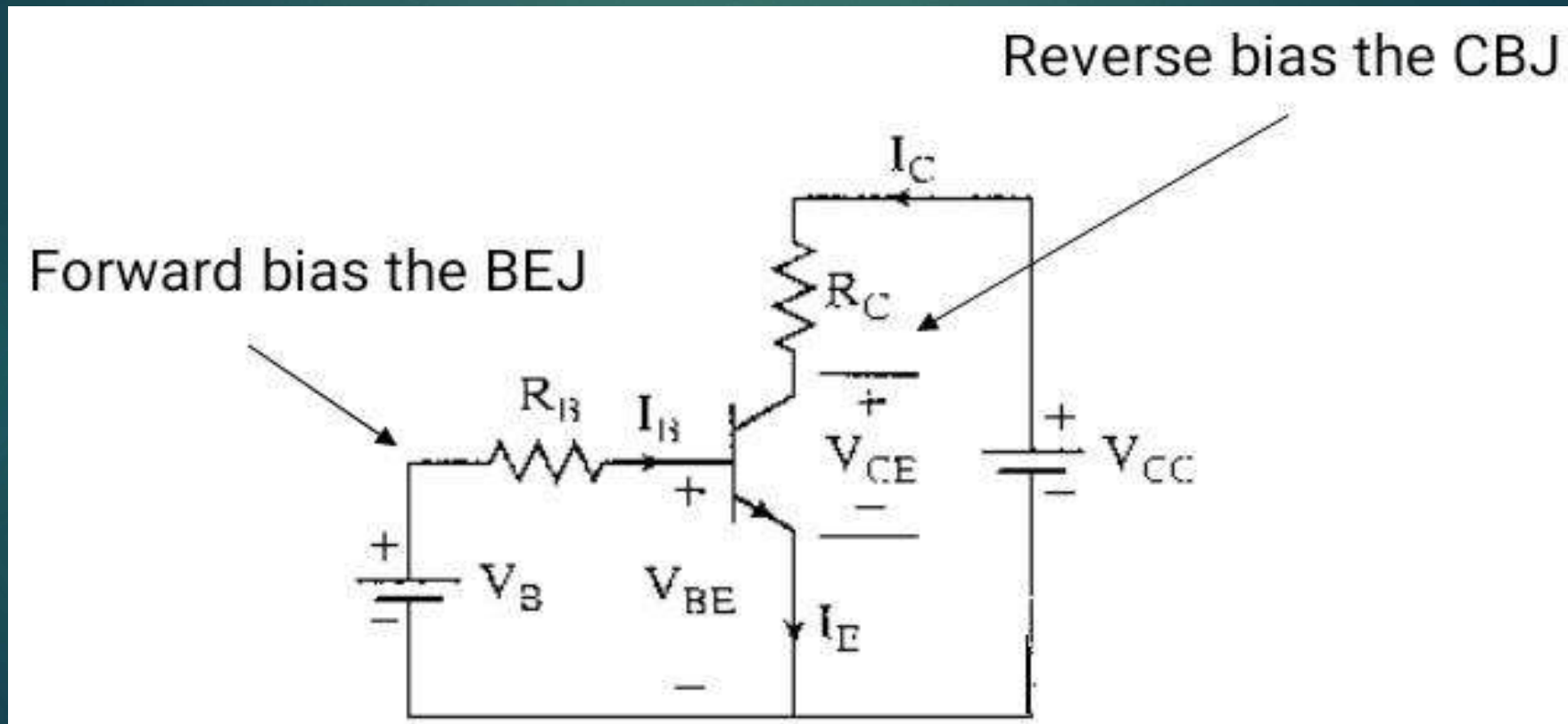

Operation of NPN Transistor

► NPN Transistor Construction:

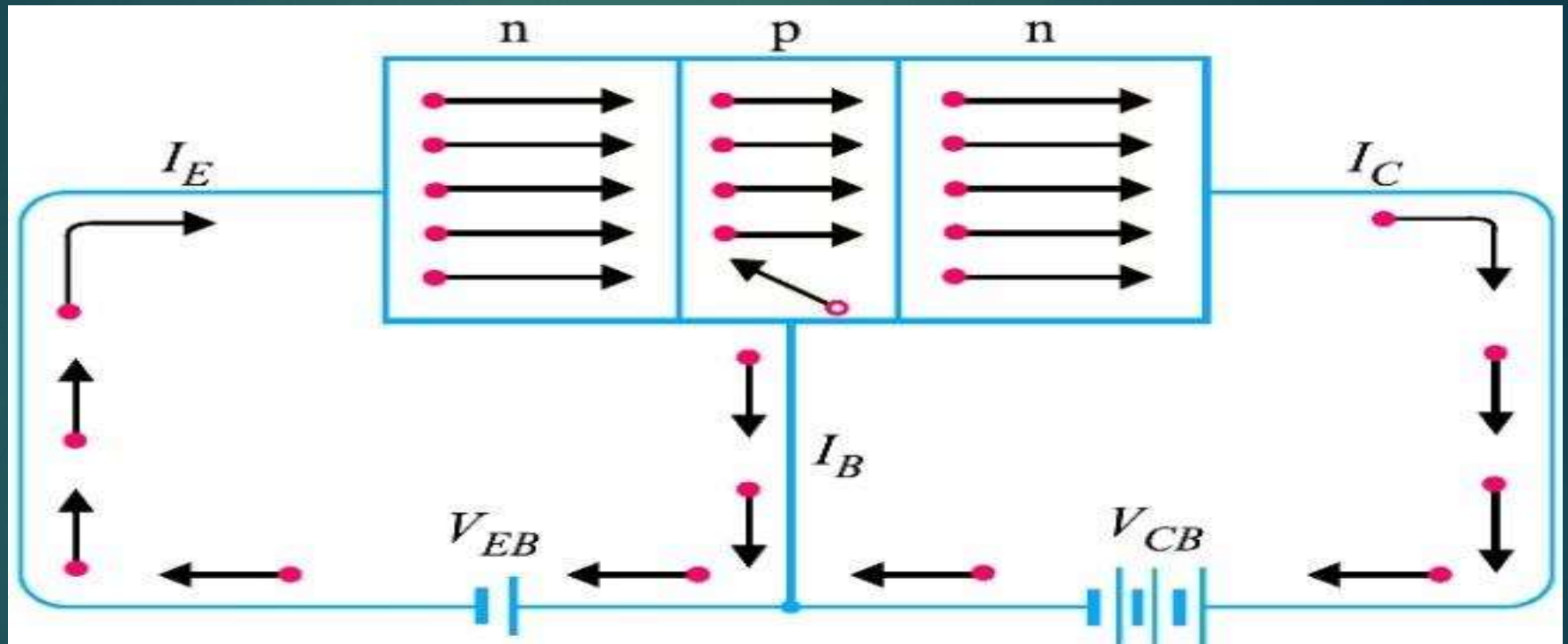

$$I_E = I_C + I_B$$

Continued.....

- ▶ **Working Operation of NPN Transistor:**
- ▶ The above figure shows the NPN transistor with forward bias to emitter-base junction (J_E) reverse bias to collector base junction (J_C)
- ▶ The forward bias causes the electrons in the N-type emitter to flow towards the base, this constitutes the emitter current I_E .
- ▶ As these electrons flows through the P-type base, they tend to combine with holes, as the base is lightly doped and very thin
- ▶ Therefore only a few electrons (less than 5%) combine with holes to constitute the base current I_B .
- ▶ The remaining 95% of the electrons cross over into the collector region to constitute collector current I_C .
- ▶ In this way almost entire emitter current flows in the collector circuit

Continued.....


- ▶ It is clear that emitter current is the sum of the base current and collector current

$$I_E = I_B + I_C$$

- ▶ In actual practice a very little current (micro amperes) would flow in the collector circuit
- ▶ This is called collector cut off current and is due to minority carriers
- ▶ The electrons which combine with holes become valence electrons. Then as valence electrons they flow down through holes and into the external base lead, this constitutes base current I_B
- ▶ The reasons that most of the electrons from emitter continue their journey through the base to collector to form collector current (i) **base is lightly doped and very thin**, therefore there are few holes which find enough time to combine with electrons
- ▶ Emitter is highly doped and collector is moderate doped, high reverse bias

Continued.....

► NPN Transistor Circuit :

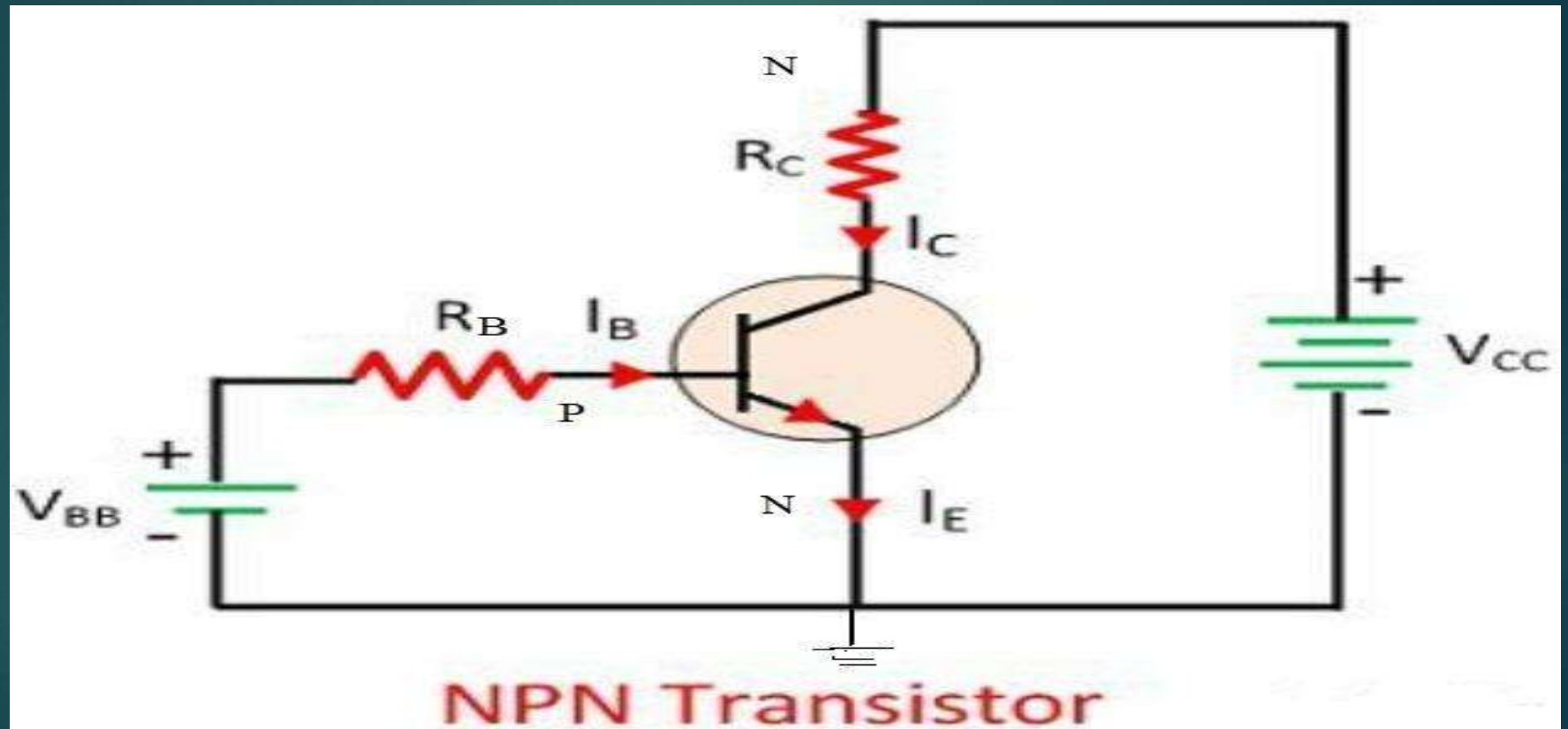

Continued.....

- Relationship between alpha & beta in NPN transistor :

α and β Relationship in a NPN Transistor

$$\text{DC Current Gain} = \frac{\text{Output Current}}{\text{Input Current}} = \frac{I_C}{I_B}$$

$$I_E = I_B + I_C \dots\dots (\text{KCL}) \quad \text{and} \quad \frac{I_C}{I_E} = \alpha$$

$$\text{Thus: } I_B = I_E - I_C$$

$$I_B = I_E - \alpha I_E$$

$$I_B = I_E (1 - \alpha)$$

$$\therefore \beta = \frac{I_C}{I_B} = \frac{I_C}{I_E (1 - \alpha)} = \frac{\alpha}{1 - \alpha}$$

$$\alpha = \frac{\beta}{\beta + 1} \quad \text{or} \quad \alpha = \beta(1 - \alpha)$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad \text{or} \quad \beta = \alpha(1 + \beta)$$


$$\text{If } \alpha = 0.99 \quad \beta = \frac{0.99}{0.01} = 99$$

Continued.....

- ▶ Importance of Transistor action :
- ▶ The input circuit emitter base junction has low resistance because of forward bias ,where as output circuit collector base junction has high resistance due to reverse bias
- ▶ The input emitter current almost entirely flows in the collector circuit, therefore a transistor transfers the input signal current from low resistance circuit to high resistance circuit
- ▶ This is the key factor responsible for the **amplifying** capability of the transistor

Operation of PNP Transistor

► PNP Transistor Construction :

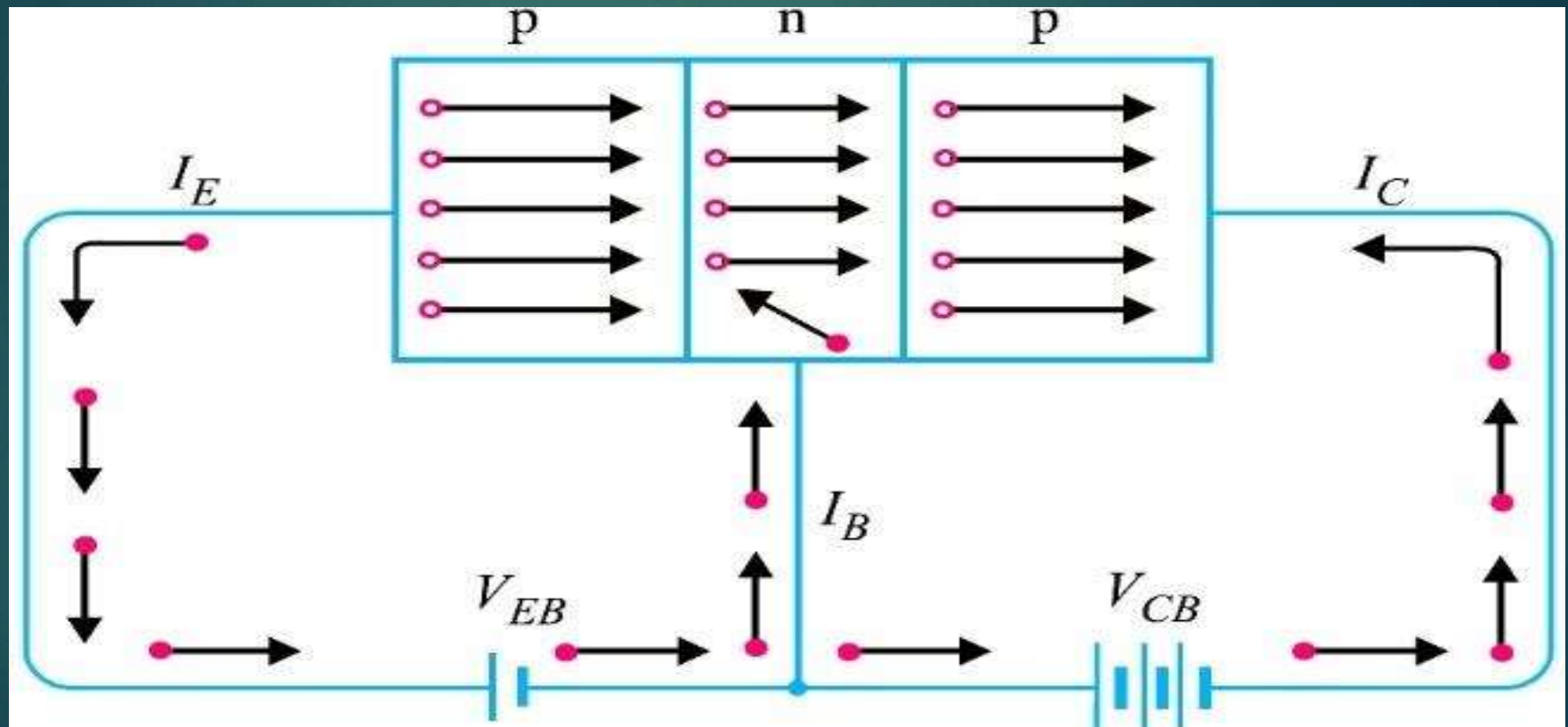

Continued.....

- ▶ **Working operation of PNP Transistor:**
- ▶ The above figure shows the basic connection of PNP transistor
- ▶ The forward bias causes the holes in the P-type emitter to flow towards the base ,this constitutes the emitter current I_E .
- ▶ As these holes cross into N-type base ,they tend to combine with electrons ,as the base is lightly doped and very thin ,therefore only few holes (less than 5%) combine with electrons ,the remaining more than 95% cross into the collector region to constitute collector current I_C .
- ▶ In this way almost entire emitter current flows in the collector circuit
- ▶ It may be noted that current conduction within PNP transistor is by holes
- ▶ However in the external connecting wires, the current is still by electrons

Transistor Configurations


- ▶ **Types of Transistor Configurations** : Depending up on the terminals of transistors ,there are three types of configurations
- ▶ (i) **Common Base Configuration** (common terminal is base .i.e base terminal is grounded)
Input parameters : I_E , V_{EB} (keep constant output voltage V_{CB})
Output parameters : I_C , V_{CB} (keep constant input current I_E)
- ▶ (ii) **Common Emitter Configuration** (common terminal is emitter .i.e E is grounded)
Input parameters : I_B , V_{BE} (keep constant output voltage V_{CE})
Output parameters : I_C , V_{CE} (keep constant input current I_B)
- ▶ (iii) **Common Collector Configuration** (common terminal is collector .i.e C is grounded)
Input parameters : I_B , V_{BC} (keep constant output voltage V_{EC})
Output parameters : I_E , V_{EC} (keep constant input current I_E)

Continued.....

► Transistor configurations :


Common Emitter configuration

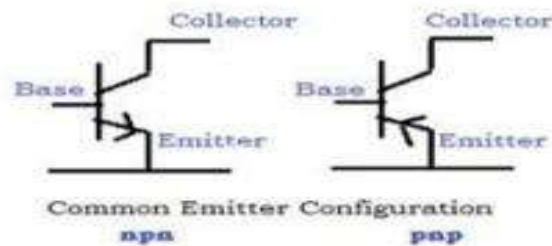- The emitter of the transistor is common to both the input and the output as shown in figure.




Common Base configuration

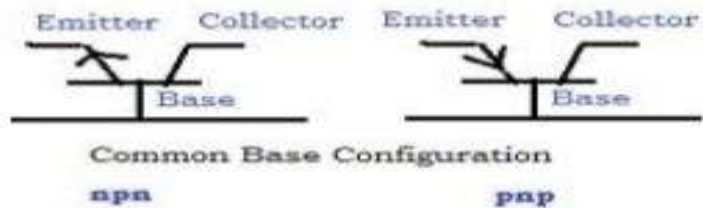- The base of the transistor is common to both the input and the output as shown in figure.




Common Collector Configuration

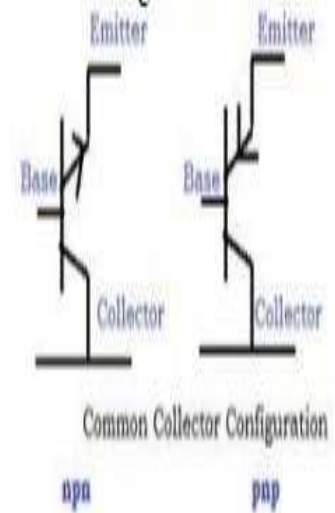

Continued.....

Common Emitter characteristics

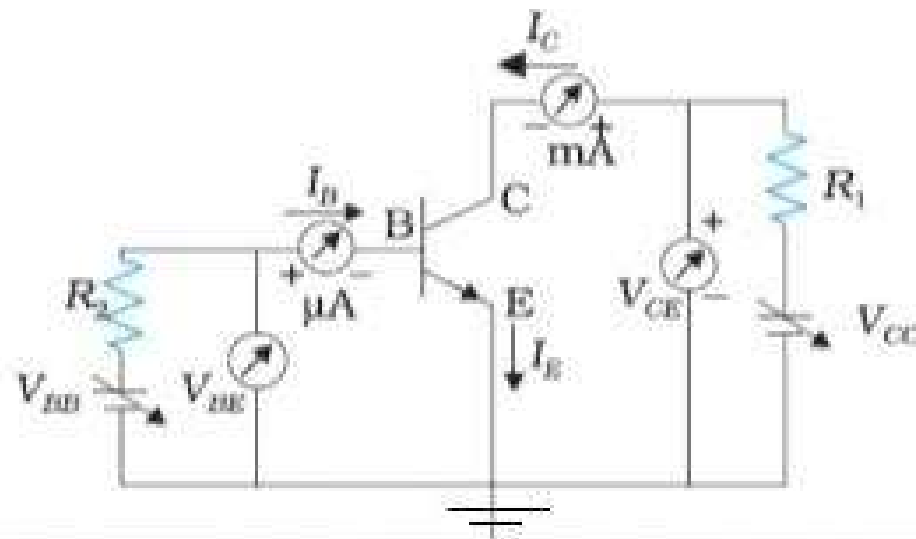When the transistor is used in Common Emitter configuration, the input is measured between the base and the emitter; the output is measured between the collector and the emitter.




Continued.....

► Common Emitter Input Characteristics :

Common Emitter characteristics

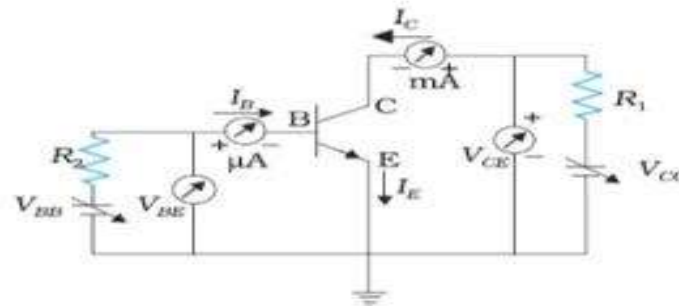
When the transistor is used in Common Emitter configuration, the input is measured between the base and the emitter; the output is measured between the collector and the emitter.



Input characteristics

- The variation of base current I_B with base-emitter voltage V_{BE} is called input characteristics.
- While studying the dependence of I_B on V_{BE} , the collector-emitter voltage V_{CE} is kept fixed.
- The current is small as long as V_{BE} is less than the barrier voltage.
- When V_{BE} is greater than the barrier voltage, the curves look similar to that of a forward biased diode.
- Input dynamic resistance of transistor – Input dynamic resistance of transistor (R_i) is defined as the ratio of change in base-emitter voltage δV_{BE} to the resulting change in the base current δI_B at constant collector-emitter voltage V_{CE} .
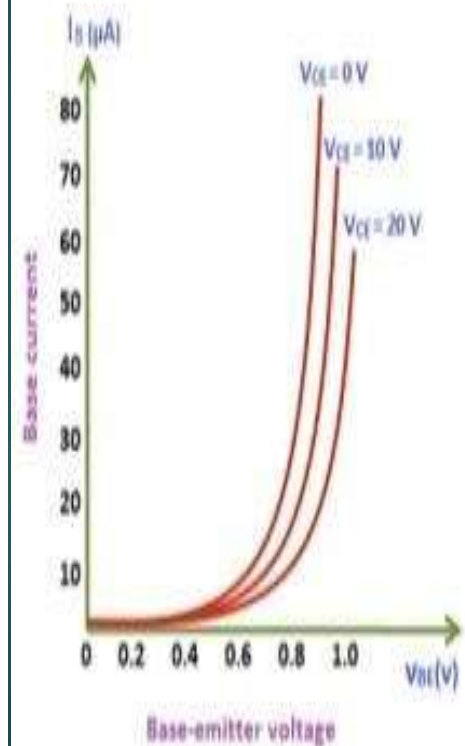
$$R_i = \left(\frac{\delta V_{BE}}{\delta I_B} \right) \text{ when } V_{CE} \text{ is constant}$$




Continued.....

► Output Characteristics of CE Configuration :

Output characteristics


- The variation of collector current I_C with collector-emitter voltage V_{CE} is called output characteristics.
- While studying the dependence of I_C on V_{CE} , the base current I_B is kept constant.
- From the graph, we see that as long as the collector-emitter junction is reverse biased, we get I_C almost independent of V_{CE} .
- We also find that for the given value of V_{CE} , I_C is large for large value of I_B .
- Output dynamic resistance of transistor – Output dynamic resistance of transistor (R_o) is defined as the ratio of change in collector-emitter voltage δV_{CE} to the resulting change in the collector current δI_C at constant base current I_B .
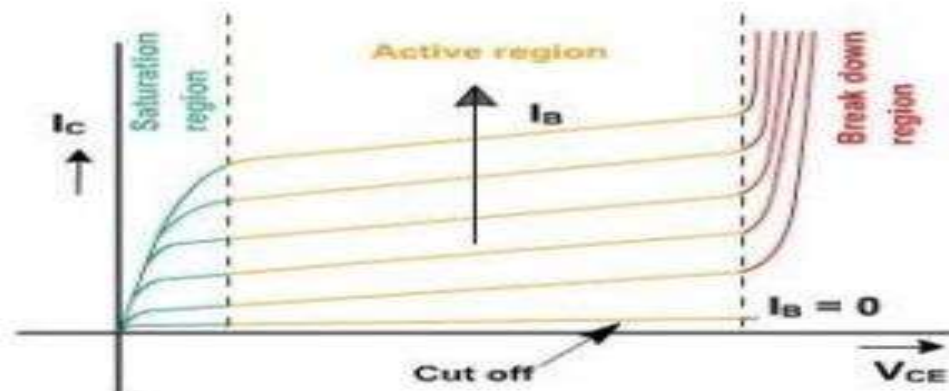
$$R_o = \left(\frac{\delta V_{CE}}{\delta I_C} \right) \quad \text{when } I_B \text{ is constant}$$



Continued.....

► Output Characteristics :

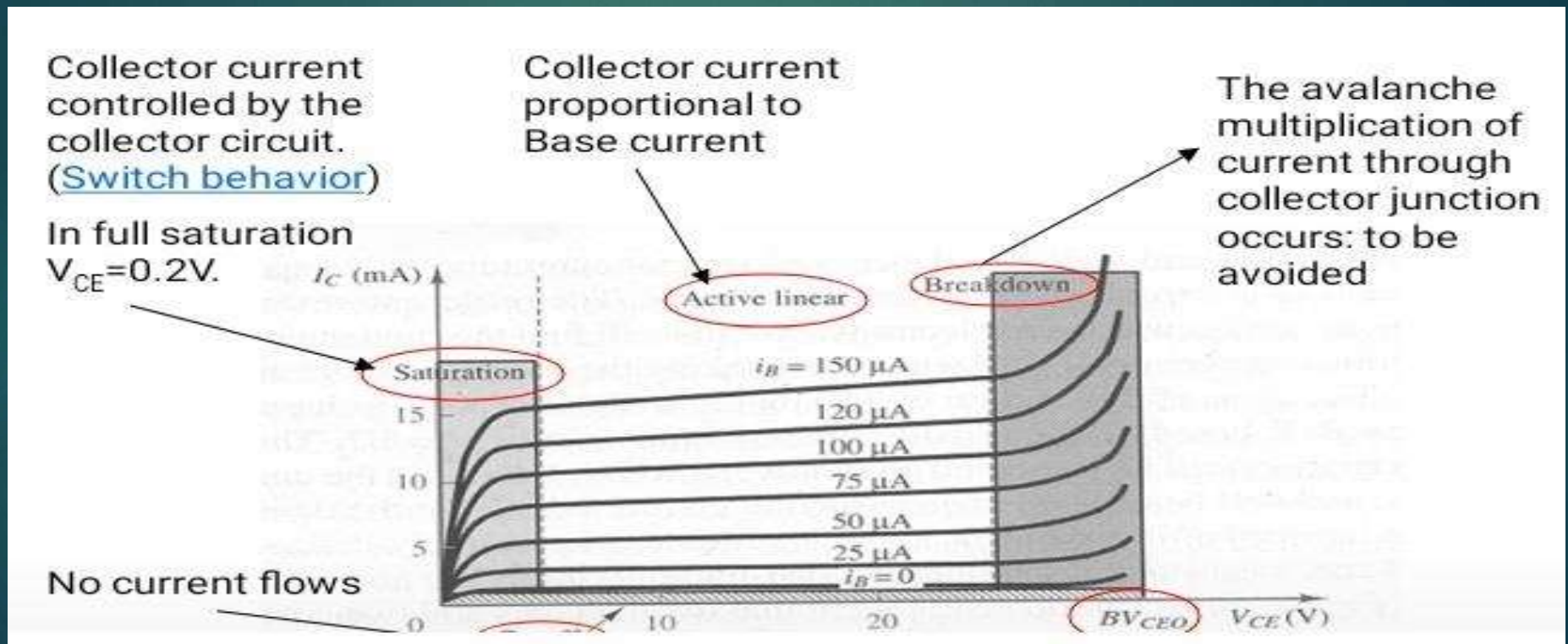

Continued.....

- ▶ Common Emitter Amplification Factor :
- ▶ It is the ratio of change in collector current to change in base current ,when collector voltage V_{CE} kept constant, $\beta = \Delta I_C / \Delta I_B$ at constant V_{CE}
- ▶ Expression for collector current:

In the Common Emitter configuration, I_B is the input current and I_C is the output current.

We know

$$I_E = I_B + I_C$$

And

$$I_C = \alpha I_E + I_{CBO}$$

$$= \alpha(I_B + I_C) + I_{CBO}$$

$$I_C(1 - \alpha) = \alpha I_B + I_{CBO}$$

$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO}$$

If base circuit is open, i.e. if $I_B = 0$,

The collector emitter current with base open is I_{CEO}

$$I_{CEO} = \frac{1}{1 - \alpha} I_{CBO}$$

Substituting the value of this in the previous equation, we get


$$I_C = \frac{\alpha}{1 - \alpha} I_B + I_{CEO}$$

$$I_C = \beta I_B + I_{CEO}$$

Continued.....

► Common Base Characteristics :

a) Input Characteristics

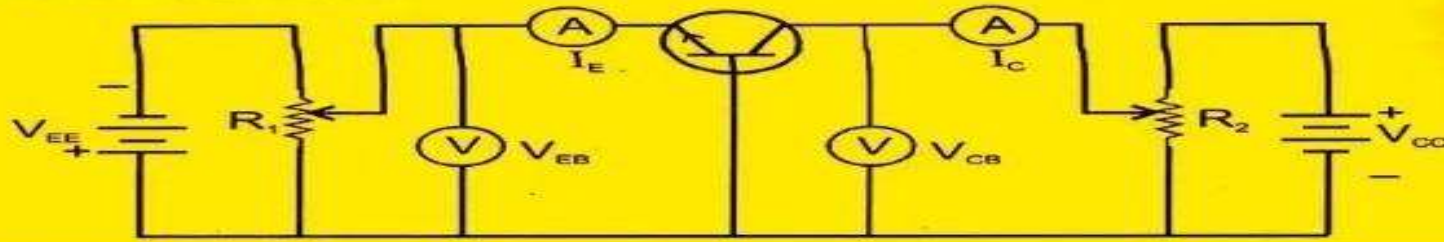

This characteristic may be used to find the input resistance of the transistor. Its value is given by the reciprocal of its slope.

$$R_{in} = \frac{\Delta V_{EB}}{\Delta I_E} \text{ when } V_{CB} \text{ constant}$$

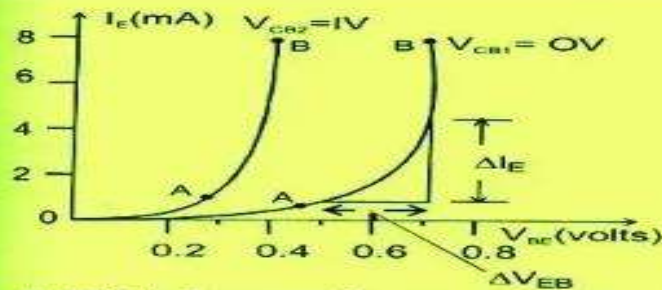


Figure 5.47(b): Input characteristics

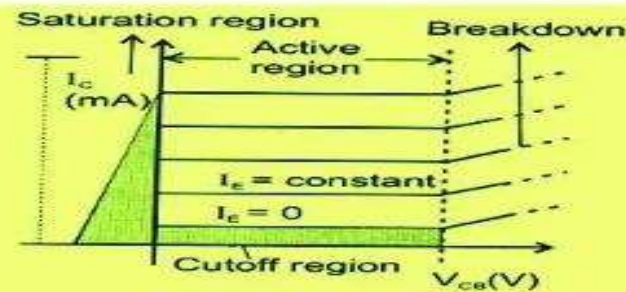


Figure 5.47(c): Output characteristics

Continued.....

- ▶ **Common Base Amplification Factor :**
- ▶ It is the ratio of change in collector current to change in emitter current ,when collector voltage V_{CB} kept constant, $\alpha = \Delta I_C / \Delta I_E$ at constant V_{CB}
- ▶ **Expression for collector current:**
- ▶ The Emitter current that reaches the collector terminal is αI_E
- ▶ Total collector current $I_C = \alpha I_E + I_{leakage}$ (due reverse bias junction)
- ▶ If the emitter base voltage is zero $V_{EB} = 0$ even then ,there flows a small leakage current which can be termed as I_{CB0} collector base current with emitter terminal is open

Continued.....

► Collector current :

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_C + I_B$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$I_C(1 - \alpha) = \alpha I_B + I_{CBO}$$

$$I_C = \left(\frac{\alpha}{1 - \alpha}\right) I_B + \left(\frac{I_{CBO}}{1 - \alpha}\right)$$

$$I_C = \left(\frac{\alpha}{1 - \alpha}\right) I_B + \left(\frac{1}{1 - \alpha}\right) I_{CBO}$$

Continued.....


► Common Collector Configuration :

It means that collector terminal is common to input and output. In this case, input signal is applied between base and collector and output signal is taken out from emitter-collector circuit. Obviously, conventionally speaking, here I_B is the input current and I_E is the output current as shown in figure 5.49(a). The current gain of the circuit is defined as the ratio of output current (I_E) to input current I_B . It is designated as γ .


$$\gamma = I_E / I_B$$

Characteristics of CC Configuration

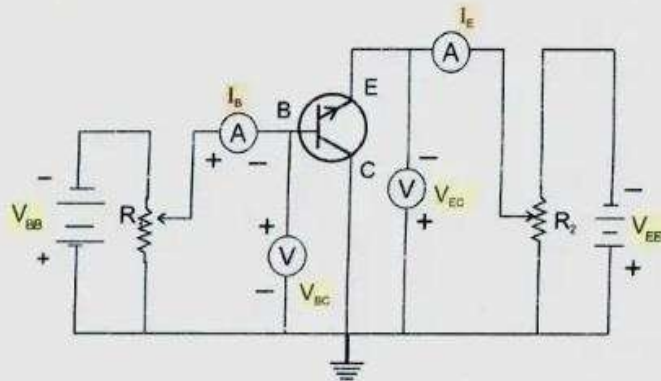
The circuit arrangement for common collector configuration is shown in figure 5.49(a).



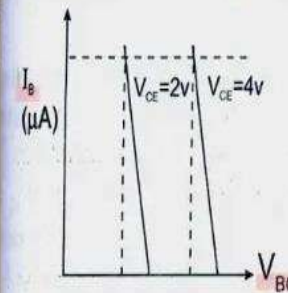The CC output characteristics are plotted, I_E vs V_{CE} for several fixed values of I_B . We know that the CE output characteristics are plotted I_C vs V_{CE} . Since I_C is approximately equal to I_E thus, common collector characteristics are identical to CE configuration.



Input Characteristics

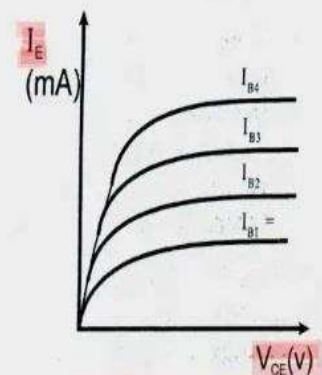

Output Characteristics

Figure 5.49(b): VI Characteristics of CC configuration

The common collector input characteristics are different from CB and CE configuration. The difference is due to the fact that the input voltage is largely determined by the level of CE voltage.

Continued.....

- ▶ Common Collector Amplification Factor :
- ▶ It is the ratio of change in emitter current to change in base current ,when collector voltage V_{CE} kept constant, $\gamma = \Delta I_E / \Delta I_B$ at constant V_{EC}
- ▶ Expression for collector current:

Expression for collector current

We know

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_B + I_C = I_B + (\alpha I_E + I_{CBO})$$

$$I_E(1 - \alpha) = I_B + I_{CBO}$$

$$I_E = \frac{I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha}$$

$$I_C \cong I_E = (\beta + 1)I_B + (\beta + 1)I_{CBO}$$


Continued.....

Comparison of three configurations

Characteristics	CB	CE	CC
Input Impedance	low (about 100Ω)	low (about $750k\Omega$)	high (about $750k\Omega$)
Output Impedance	Very high (about $1M\Omega$)	High (about $45k\Omega$)	Low (about 50Ω)
Voltage Gain	about 150 (Medium)	about 500 (Medium)	Less than 1
Current Gain	less than unity	High	High
Application	for high frequency application	for audio frequency application	for impedance matching

Transistor as an Amplifier

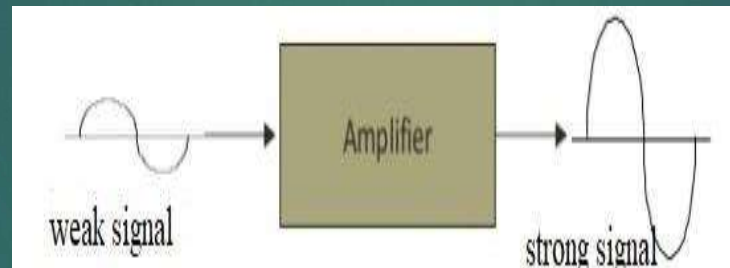
- ▶ **What is an Amplifier** :It is an electronic circuit ,it increases the strength of weak signal without changing its corresponding shape and frequency
- ▶ The function of amplifier is to provide an output which is greater than input



- ▶ **Types of Amplifiers:**
- ▶ **Voltage amplifier**: intended provide to voltage gain , $A_V = V_{out} / V_{in}$
- ▶ **Current amplifier**: intended to give current gain , $A_I = I_{out} / I_{in}$
- ▶ **Power amplifier**: both current and voltage can be amplifier
- ▶ **Inverting amplifier**: Gives an amplified output out of phase from input


Continued.....

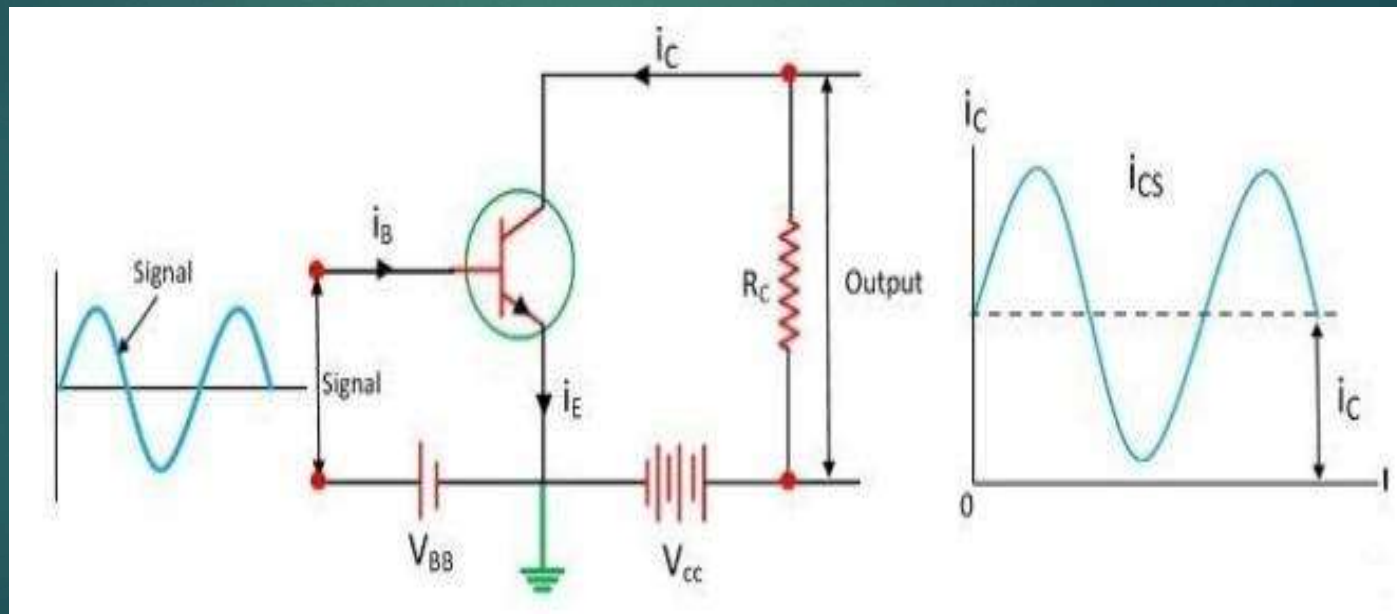- ▶ **Amplification** :The ability of a circuit to receive a small change of input voltage or current and produce a large change in the output voltage or current
- ▶ Amplification is depends on the change in the transistors resistance caused by an input signal




Continued.....

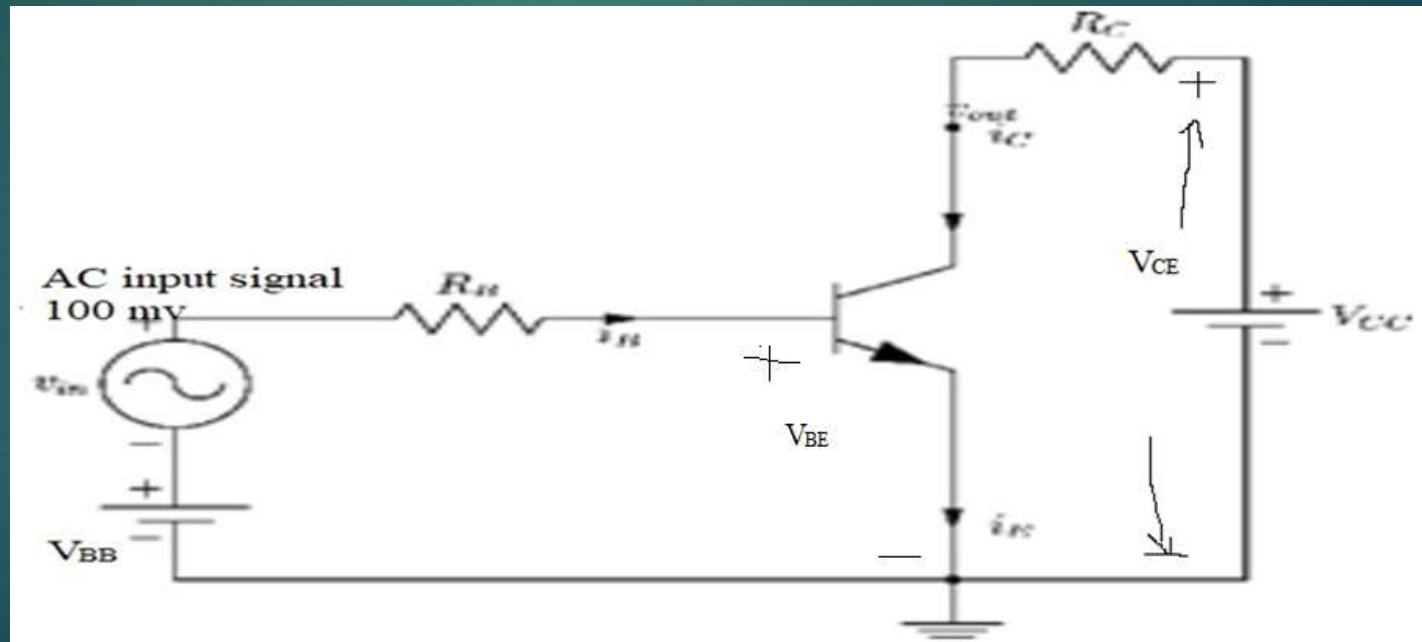- ▶ **Amplification** : The ability of a circuit to receive a small change of input voltage or current and produce a large change in the output voltage or current
- ▶ Amplification is depends on the change in the transistors resistance caused by an input signal



Continued.....

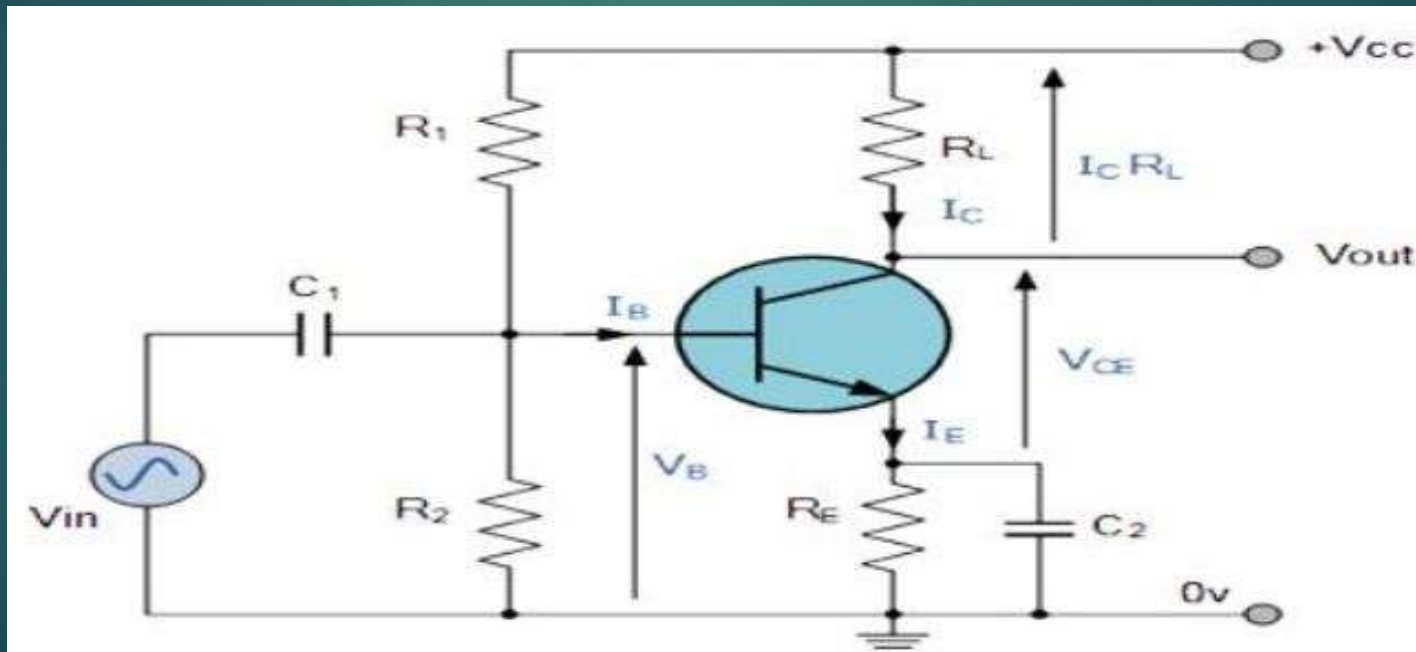- ▶ **Amplification** :The ability of a circuit to receive a small change of input voltage or current and produce a large change in the output voltage or current
- ▶ Amplification is depends on the change in the transistors resistance caused by an input signal



Continued.....

- ▶ **Analysis** :if you considered V_o or V_{CE} and V_{in} as small changes in output and input voltages respectively ,then V_o / V_{in} is called as small signal voltage gain A_v of the amplifier
- ▶ Apply KVL for the output loop : $-V_{CC} + I_C R_C + V_{CE} = 0$

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_C = (V_{CC} - V_{CE}) / R_C$$

For AC analysis DC supply is Zero ,So collector current

$$I_C = (0 - V_{CE}) / R_C$$

$$I_C = - V_{CE} / R_C$$

Finally output voltage is expressed as $V_{CE} = - I_C R_C \rightarrow (i)$

Continued.....

► **Analysis** : Apply KVL for input loop : $-V_{BB} - V_{in} + I_B R_B + V_{BE} = 0$

$$V_{in} = -V_{BB} + I_B R_B + V_{BE}$$

For AC analysis DC supply is zero ,So input voltage is

$$V_{in} = 0 + I_B R_B + 0$$

$$V_{in} = I_B R_B \rightarrow (ii)$$

$$I_B = V_{in} / R_B$$

Voltage gain $A_V = V_{CE} / V_{in} = -I_C R_C / I_B R_B$

$$A_V = -\beta R_C / R_B$$

Continued.....

- ▶ **Amplification** :The ability of a circuit to receive a small change of input voltage or current and produce a large change in the output voltage or current
- ▶ Amplification is depends on the change in the transistors resistance caused by an input signal