

State Space Models For Electrical Networks

- Concept of state
- State equations
- Equivalent source method
- State space model and evaluation of state transition matrix
- Application to electrical networks

- Transfer function of a systems is used for analysis and design control systems. It is also called as classical approach or technique.
- This is a useful representation if the system is
 - Linear and time invariant
 - Having a single input and single output (SISO)
 - Having zero initial conditions only.

- But transfer function representation is not useful for,
 - Systems with initial conditions
 - Nonlinear systems
 - Time varying systems and
 - Multiple input multiple output (MIMO) systems
 - It does not throw any light on the variation of internal variables (Sometimes this information is necessary because, some internal variables may go out of bounds, even though the output remains within the desired limits).

To overcome all these disadvantages of transfer function representation, the state space representation of the system was evolved. This is a modern approach.

- This representation forms the basis for the development of control systems.
- This representation contains the information about some of the variables along with the output variable and is useful for analysis and design using digital computer.

- It is suitable for representing
 - Linear and nonlinear systems.
 - Time invariant and time varying systems.
 - SISO and MIMO systems.
- State variable analysis is a way of analyzing the dynamic circuits in order to obtain its transfer function.
- Matrix notations and Laplace transformations are extensively used in state variable analysis.

Concept of State:

STATE:

The concept of state is related to minimum set of variables. variables are called as state variables.

Now we can define the **state and state variables**


The minimum number of variables required to be known at time t_0 along with the input for $t \geq t_0$, to completely determine the behavior of the system for $t > t_0$, are known as the state variables of the system. The state of the system at any time 't' is given by the values of these variables at time 't'.

- **State vector:** If n variables represent behavior of a given system, then n State variables can be considered as n components of a vector x . Such vector is called as state vector.
- **State space:** The n dimensional space whose co-ordinates consist of x_1 axis, x_2 axis,....., x_n axis is called as state space.
- **State equations:** It is the set of n simultaneous first order differential equation with n variables.
- **Output equation:** It is the linear combination of state variables and inputs.


If the dynamic behavior of a system can be described by an n th order differential equation, we require n initial conditions of the system and hence, a minimum of n state variables are required known at $t = t_0$ completely determine the behavior of the system a given input.

It is a standard practice to denote these **n state variables** by $x_1(t)$, $x_2(t)$ $x_n(t)$ and **m inputs** by $u_1(t)$, $u_2(t)$ $u_m(t)$ and **p outputs** $y_1(t)$, $y_2(t)$ $y_p(t)$.


System block diagram

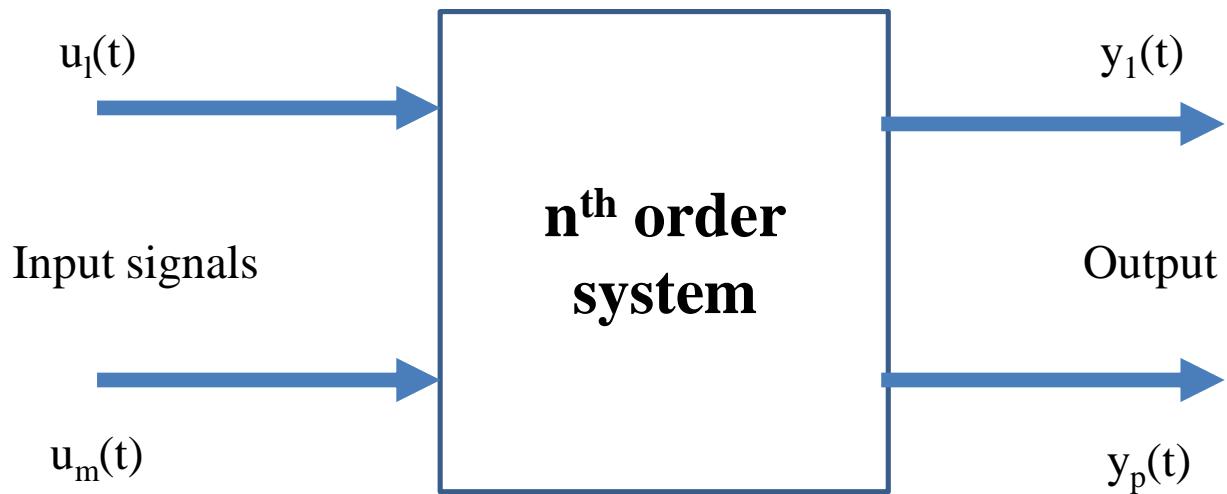

State space representation

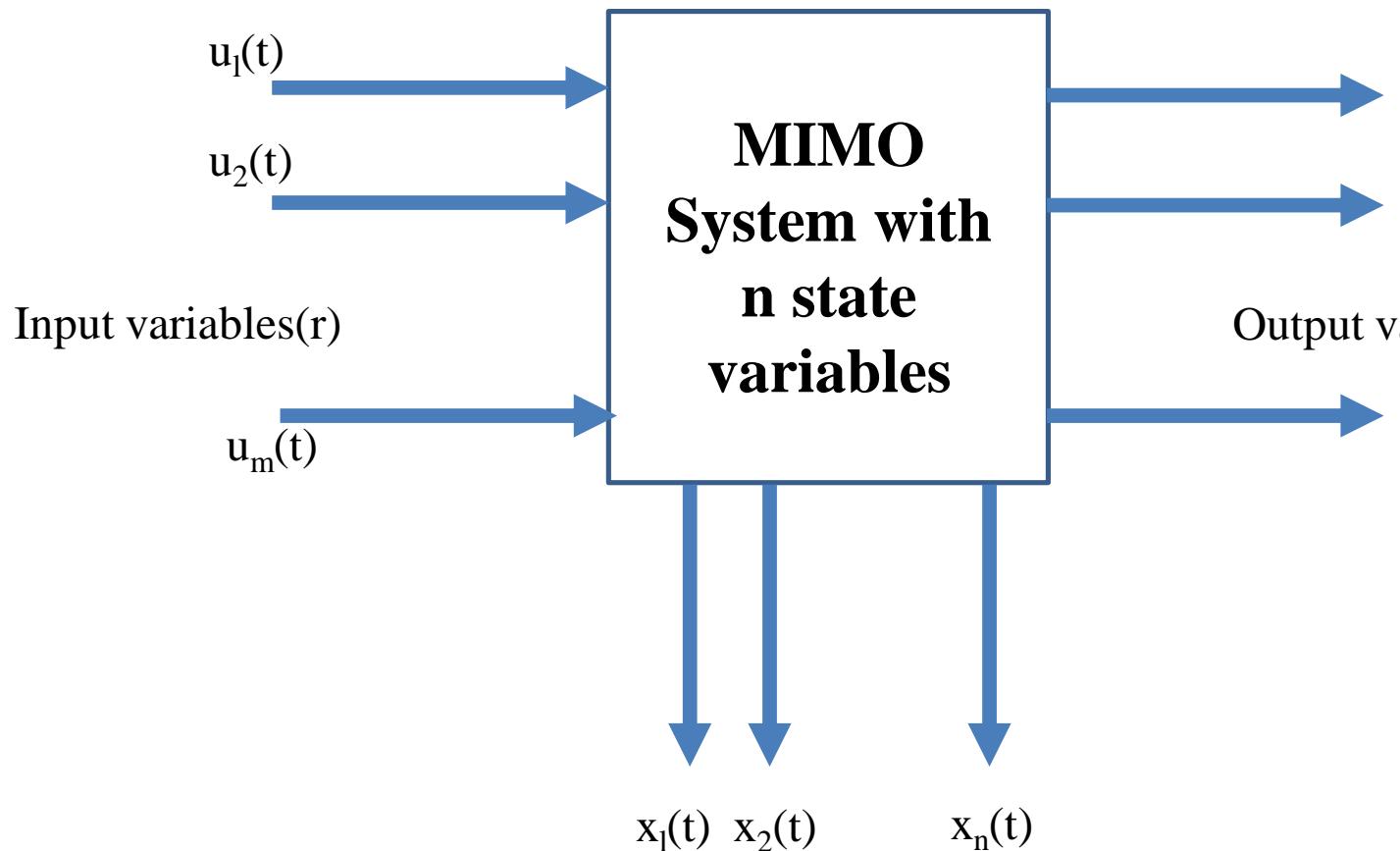

State variable technique

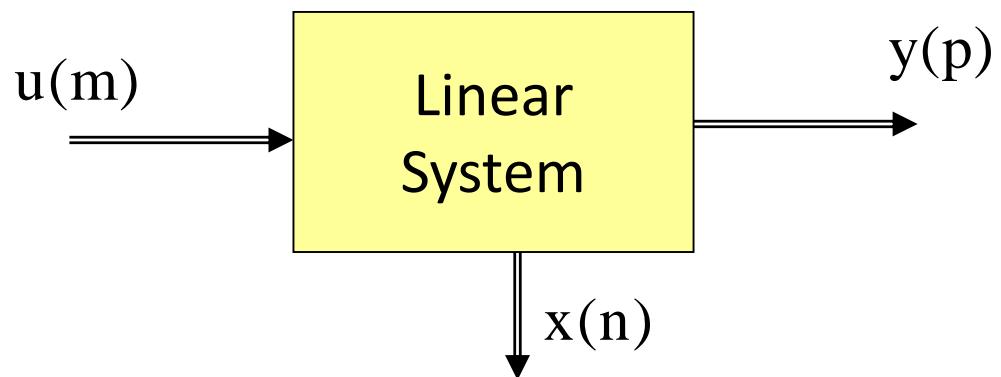

$$u(t) = \begin{bmatrix} u_1(t) \\ u_2(t) \\ \vdots \\ u_i(t) \\ \vdots \\ u_m(t) \end{bmatrix}$$

Input vector

$$x(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \\ \vdots \\ x_i(t) \\ \vdots \\ x_n(t) \end{bmatrix}$$

State vector

$$y(t) = \begin{bmatrix} y_1(t) \\ y_2(t) \\ \vdots \\ y_i(t) \\ \vdots \\ y_p(t) \end{bmatrix}$$

Output vector

The state representation can be arranged in the form of n first order differential equations, as shown in the next slide.

For linear systems, the derivatives of state variables can be expressed as combinations of the state variables and inputs.

$$\dot{x}_1 = a_{11} x_1 + a_{12} x_2 + \dots + a_{1n} x_n + b_{11} u_1 + b_{12} u_2 + \dots + b_{1m} u_m$$

$$\dot{x}_2 = a_{21} x_1 + a_{22} x_2 + \dots + a_{2n} x_n + b_{21} u_1 + b_{22} u_2 + \dots + b_{2m} u_m$$

⋮

$$\dot{x}_n = a_{n1} x_1 + a_{n2} x_2 + \dots + a_{nn} x_n + b_{n1} u_1 + b_{n2} u_2 + \dots + b_{nm} u_m$$

where a_{ij} and b_{ij} are constants.

Eqns. (1) can be written in a matrix form as,

$$\dot{X}(t) = A X(t) + B U(t) \quad \dots \dots \dots (2)$$

where $X(t)$ is a $n \times 1$ state vector

A is a $n \times n$ constant system matrix

B is a $n \times m$ constant input matrix

$U(t)$ is a $m \times 1$ input vector.

$$A = \begin{bmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & & \vdots \\ a_{n1} & a_{n2} & \dots & a_{nn} \end{bmatrix}; \quad B = \begin{bmatrix} b_{11} & b_{12} & \dots & b_{1m} \\ b_{21} & b_{22} & \dots & b_{2m} \\ \vdots & \vdots & & \vdots \\ b_{n1} & b_{n2} & \dots & b_{nm} \end{bmatrix}$$

Similarly, the outputs can also be expressed as linear combinations of state variables

$$\begin{aligned}y_1(t) &= c_{11} x_1 + c_{12} x_2 \dots + c_{1n} x_n + d_{11} u_1 + d_{12} u_2 + \dots + d_{1m} u_m \\&\vdots \\y_p(t) &= c_{p1} x_1 + c_{p2} x_2 \dots + c_{pn} x_n + d_{p1} u_1 + d_{p2} u_2 + \dots + d_{pm} u_m\end{aligned}$$

The above equation, eq(3), can be written as:

$$Y(t) = C X(t) + D U(t) \quad \dots \dots (4)$$

Where $Y(t)$ is a $p \times 1$ output vector

C is a $p \times n$ output matrix

D is a $p \times m$ transmission matrix

$$C = \begin{bmatrix} c_{11} & c_{12} & \dots & c_{1n} \\ \vdots & & & \vdots \\ c_{p1} & c_{p2} & \dots & c_{pn} \end{bmatrix}; \quad D = \begin{bmatrix} d_{11} & d_{12} \\ \vdots & \\ d_{p1} & d_{p2} \end{bmatrix}$$

The complete state model for linear systems is given by the two equations, eq (2) and eq (4), as,

$$\dot{x} = \frac{dx}{dt} = AX(t) + BU(t)$$


..... State equation

$$Y(t) = CX(t) + DU(t)$$


..... Output equation

Block diagram representation of state model of a linear multi-input-m systems

Representation of $\dot{x} = Ax + Bu$

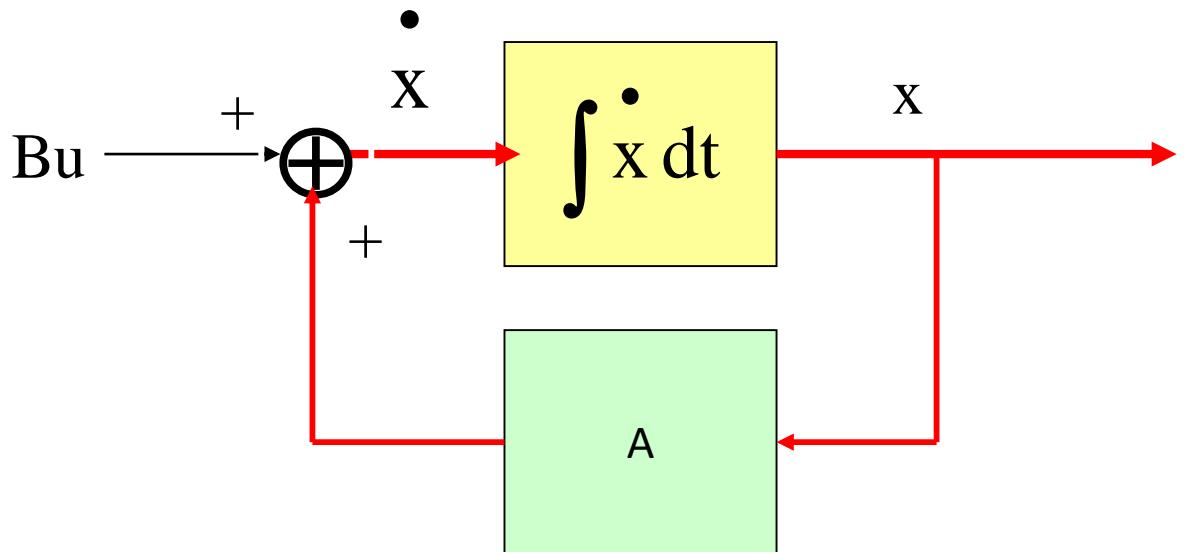

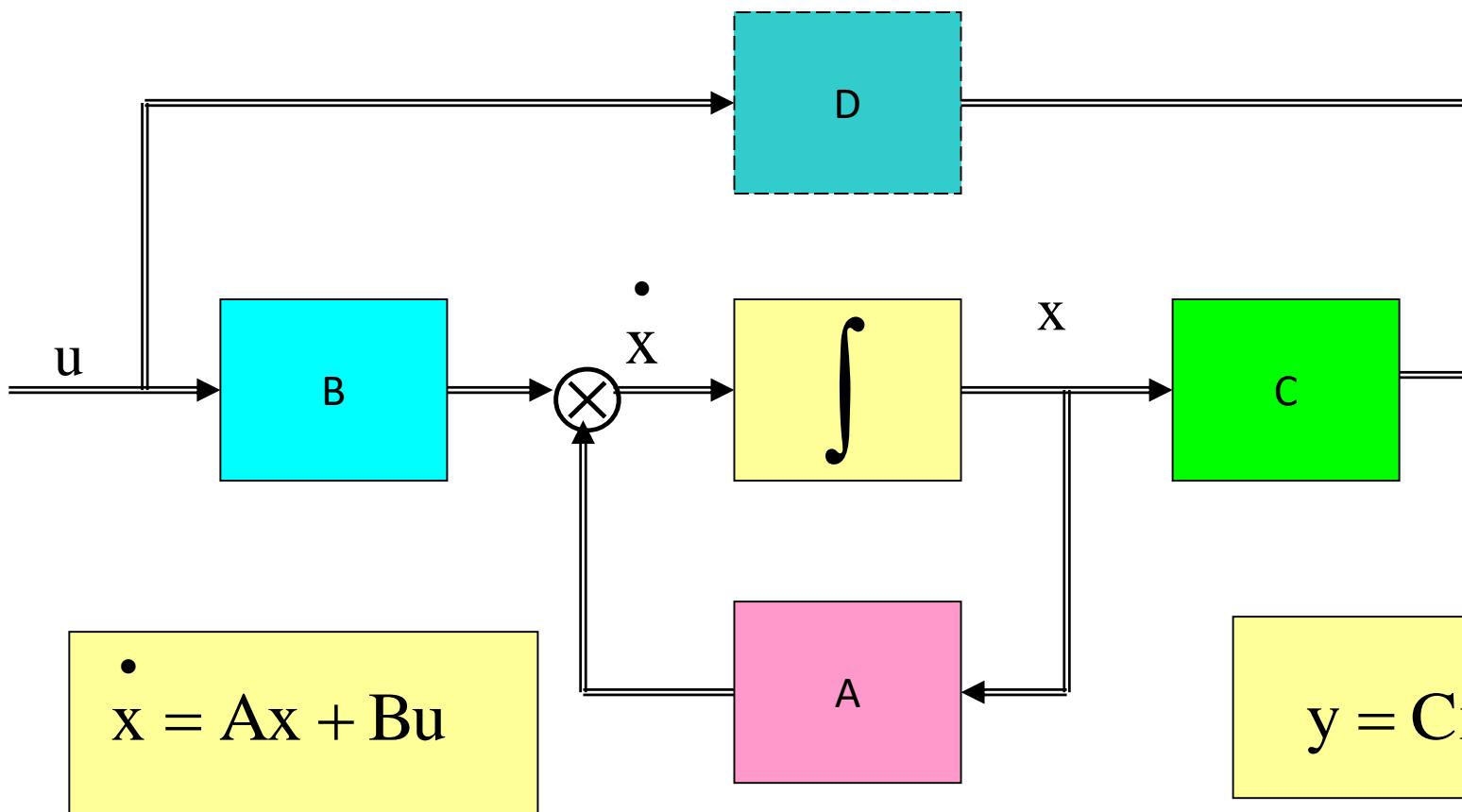Block diagram representation of the state model of an MIM



A = System Matrix $(n \times n)$
 B = Input Matrix $(n \times m)$
 x = State Vector $(n \times 1)$
 u = Input Vector $(m \times 1)$

C = Output Matrix $(p \times n)$
 D = Direct Transmission Matrix
 y = Output Vector $(p \times 1)$

The system is described by n first order differential equations in these states

$$\frac{dx_1}{dt} = \dot{x}_1 = f_1(x_1, x_2, \dots, x_n; u_1, u_2, \dots, u_m, t)$$

$$\frac{\vdots}{dx_n} = \dot{x}_n = f_n(x_1, x_2, \dots, x_n; u_1, u_2, \dots, u_m, t)$$

The functions f_1, f_2, \dots, f_n may be time varying or time invariant and linear or nonlinear

Using vector notation to represent the states, their derivatives, and inputs

$$X(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \\ \vdots \\ x_n(t) \end{bmatrix}; \dot{X}(t) = \begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \\ \vdots \\ \dot{x}_n(t) \end{bmatrix}; U(t) = \begin{bmatrix} u_1(t) \\ u_2(t) \\ \vdots \\ u_m(t) \end{bmatrix}$$

where $X(t)$ is known as state vector and $U(t)$ is known as input vector

State Transition Matrix:

Consider a homogeneous(unforced) state equation,

$$\dot{x}(t) = Ax(t)$$

The solution of this equation can be found out using Laplace tra

$$sX(s) - x(0) = AX(s)$$

$$(sI - A)X(s) = x(0)$$

$$X(s) = (sI - A)^{-1}x(0)$$

Inverse Laplace transform of $X(s)$ gives the required solution, i

$$\Rightarrow x(t) = e^{At} x(0)$$

Let $x(0) = x_0$

Therefore the solution is $x(t) = e^{At}x(0)$.

- This solution of homogeneous state equation shows that the initial state x_0 at $t=0$, is driven to a state $x(t)$ at time t .
- Since this transition in state is carried out by the matrix exponential e^{At} , e^{At} is known as the **state transition matrix (STM)** and is denoted by $\varphi(t)$.

$$\varphi(t) = e^{At}$$

Summary :

- State Transition matrix

$$\varphi(t) = e^{At}$$

$$\Phi(t) = L^{-1}[(sI - A)^{-1}]$$

Significance of STM:

- Since state transition matrix satisfies the homogeneous state equations, it represents the free response of the system.
- In other words, it governs the response that is excited by the initial conditions only.
- As the STM is dependent on A only, it is therefore, sometimes referred to as STM of A .
- As the name implies, the STM describes the change of state from initial time $t=0$ to any time t , when the inputs are zero.

Properties

$$\Phi(t) \stackrel{\Delta}{=} e^{At} = L^{-1}[(sI - A)^{-1}]$$

$$1. \quad \Phi(0) = I$$

$$2. \quad \Phi^{-1}(t) = \Phi(-t)$$

$$3. \quad x(0) = \Phi(-t)x(t)$$

$$4. \quad \Phi(t_2 - t_1)\Phi(t_1 - t_0) = \Phi(t_2 - t_0)$$


$$5. \quad \Phi(t)^k = \Phi(kt)$$

State space representation of electrical networks:

- The desired output information is usually the voltage and currents associated with various elements of the network.
- This information at any time 't' can be obtained if the initial voltage across the capacitor $e_C(t_0)$ and initial current through the inductor $i_L(t_0)$ are known in addition to the values of the input $e(t)$ applied for $t > t_0$.
- The voltage across the capacitor and current through inductor thus constitute a set of characterizing variables of the circuit. The values of these variables at any time 't' describe the state of the network at that time. These variables are therefore called as state variables of the circuit.

{ The initial state of the circuit is given by $e_C(t_0)$ & $i_L(t_0)$, and the state of the circuit at any time t is given by $e_C(t)$ and $i_L(t)$. }

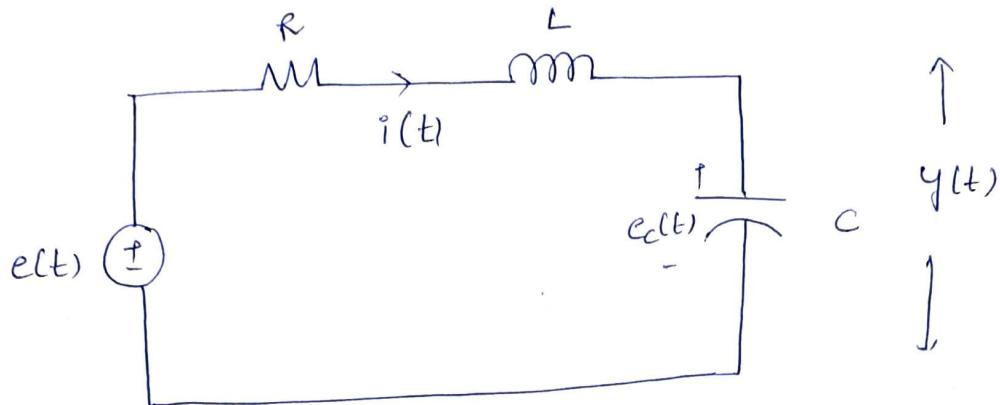Q1) Obtain the state space representation of the given series RLC circuit. The output is $y(t)$. The input is $e(t)$.



Sol) { State model equations are :

$$\textcircled{1} \quad \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = [A] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + [B] \begin{bmatrix} u_1 \\ u_2 \end{bmatrix}$$

Here, the state variables are, $e_c(t)$ and $\dot{i}_L(t)$ and input is $e(t)$.

(As $\dot{i}_L(t) = i(t)$)

$$\therefore \begin{bmatrix} \dot{e}_c(t) \\ \dot{i}_L(t) \end{bmatrix} = [A] \begin{bmatrix} e_c(t) \\ i_L(t) \end{bmatrix} + [B] \begin{bmatrix} e(t) \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} \dot{e}_c(t) \\ \dot{i}_L(t) \end{bmatrix} = \begin{bmatrix} A_1 & A_2 \\ A_3 & A_4 \end{bmatrix} \begin{bmatrix} e_c(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} B_1 \\ B_2 \end{bmatrix} \begin{bmatrix} e(t) \end{bmatrix}$$

$$\Rightarrow \dot{e}_c(t) = A_1 e_c(t) + A_2 \dot{i}_L(t) + B_1 e(t) \quad \rightarrow \textcircled{1}$$

$$\text{and } \dot{i}_L(t) = A_3 e_c(t) + A_4 \dot{i}_L(t) + B_2 e(t). \quad \rightarrow \textcircled{2}$$

(2)

$$y(t) = C x(t) + D u(t)$$

$$\begin{bmatrix} y_1(t) \\ y_2(t) \end{bmatrix} = \begin{bmatrix} C_1 & C_2 \\ C_3 & C_4 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} D_1 \\ D_2 \end{bmatrix} \begin{bmatrix} u_1(t) \\ u_2(t) \end{bmatrix}$$

Here only one output is present i.e., $y(t)$

and only one input, i.e., $u_1(t) = e(t)$

$$\therefore \begin{bmatrix} y_1(t) \\ y_2(t) \end{bmatrix} = \begin{bmatrix} C_1 & C_2 \\ C_3 & C_4 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} D_1 \\ D_2 \end{bmatrix} \begin{bmatrix} e(t) \end{bmatrix}$$

$$\Rightarrow y_1(t) = C_1 x_1(t) + C_2 x_2(t) + D_1 e(t) \rightarrow \textcircled{2}$$

$$\Rightarrow y_2(t) = C_3 x_1(t) + C_4 x_2(t) + D_2 e(t) \rightarrow \textcircled{3}$$

So, apply KVL or KCL on mesh (or) nodal or any other technique

and frame equations in the form of eq (1), (2) and (3).

}

from the circuit,

apply KVL in the loop,

$$e(t) = i_L(t) \cdot R + L \frac{di_L(t)}{dt} + e_C(t)$$

$$\Rightarrow e(t) = i(t) R + L \frac{di(t)}{dt} + e_C(t)$$

$$\Rightarrow e(t) = R \cdot i(t) + L \frac{di(t)}{dt} + e_C(t)$$

$$\Rightarrow \dot{i}(t) = \frac{e(t) - R i(t) - e_c(t)}{L}$$

$$\Rightarrow \dot{i}(t) = \frac{1}{L}(e_c(t)) - \frac{R}{L}(i(t)) + \frac{1}{L}e(t). \rightarrow (4)$$

$$\text{and, } e_c(t) = \frac{1}{C} \int i(t) dt$$

Apply differentiation ,

$$\frac{d e_c(t)}{dt} = \frac{1}{C} \dot{i}(t)$$

$$\Rightarrow \dot{e}_c(t) = \frac{1}{C} \dot{i}(t).$$

$$\dot{e}_c(t) = 0(e_c(t)) + \frac{1}{C}(i(t)) + 0(e(t)) \rightarrow (5)$$

Comparing of ① and ② with of ⑤ and ④ respectively ,

to write the state equation.

$$\begin{bmatrix} \dot{e}_c(t) \\ \dot{i}_L(t) \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} e_c(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} [e(t)]$$

from the circuit,

$$y(t) = e_c(t)$$

$$\Rightarrow y(t) = e_c(t) + 0(i_L(t)) + 0(e(t)) \rightarrow (6)$$

Comparing eq (3) and eq (6), to write the output equation,

$$[y(t)] = [1 \ 0] \begin{bmatrix} e_c(t) \\ i_L(t) \end{bmatrix} + [0] [e(t)]$$

$$y(t) = [1 \ 0] \begin{bmatrix} e_c(t) \\ i_L(t) \end{bmatrix} +$$


(*)

∴ The state model equations are,

$$\begin{bmatrix} \dot{e}_c(t) \\ \dot{i}_L(t) \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} e_c(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} e(t)$$

$$\text{and } y(t) = [1 \ 0] \begin{bmatrix} e_c(t) \\ i_L(t) \end{bmatrix}$$

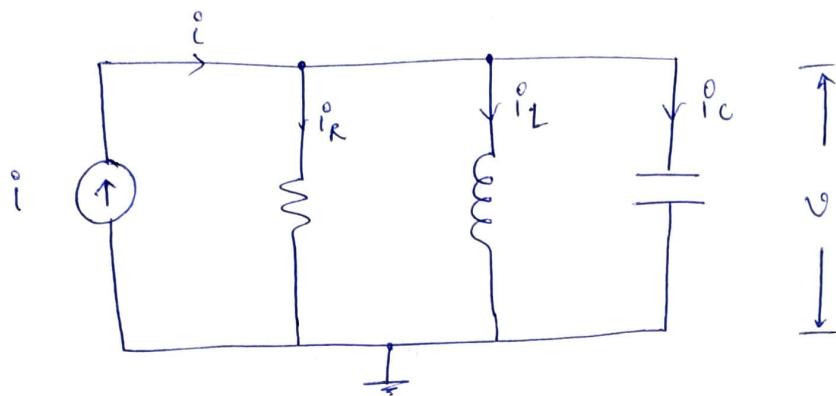Q2) Write the state variable formulation of the parallel RLC network shown below. The current through the inductor and voltage across the capacitor are the output variables.



Sol) Here the state variables are \dot{i}_L and v_C i.e v .

The output variables are also given as \dot{i}_L and v .

From state model equations,

$$\textcircled{1} \quad \begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} A_1 & A_2 \\ A_3 & A_4 \end{bmatrix} \begin{bmatrix} \dot{i}_L \\ v_C \end{bmatrix} + \begin{bmatrix} B_1 \\ B_2 \end{bmatrix} \begin{bmatrix} i \end{bmatrix}$$

$$\Rightarrow \dot{i}_L = A_1 \dot{i}_L + A_2 v_C + B_1 i \quad \rightarrow \textcircled{1}$$

$$\text{and } \dot{v}_C = A_3 \dot{i}_L + A_4 v_C + B_2 i \quad \rightarrow \textcircled{2}$$

$$\textcircled{2} \quad y \cdot y(t) = C x(t) + D u(t)$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} C_1 & C_2 \\ C_3 & C_4 \end{bmatrix} \begin{bmatrix} \dot{i}_L \\ v_C \end{bmatrix} + \begin{bmatrix} D_1 \\ D_2 \end{bmatrix} \begin{bmatrix} i \end{bmatrix}$$

$$\Rightarrow \overset{\circ}{i}_L = C_1 \overset{\circ}{i}_L + C_2 V_C + D_1 \overset{\circ}{i} \quad \rightarrow \textcircled{3}$$

$$\text{and } \overset{\circ}{V}_C = C_3 \overset{\circ}{i}_L + C_4 V_C + D_2 \overset{\circ}{i} \quad \rightarrow \textcircled{4}$$

}

Apply KCL at top node,

$$\overset{\circ}{i} = \overset{\circ}{i}_R + \overset{\circ}{i}_L + \overset{\circ}{i}_C$$

$$\Rightarrow \overset{\circ}{i} = \frac{V(t)}{R} + \overset{\circ}{i}_L + C \frac{dV_C(t)}{dt}$$

$$\Rightarrow \overset{\circ}{i} = \frac{V_C(t)}{R} + \overset{\circ}{i}_L + C \overset{\circ}{V}_C(t)$$

$$\Rightarrow \overset{\circ}{V}_C(t) = \frac{1}{C} \left(\overset{\circ}{i} - \overset{\circ}{i}_L - \frac{V_C}{R} \right)$$

$$\Rightarrow \overset{\circ}{V}_C(t) = -\frac{1}{C} (\overset{\circ}{i}_L) + \left(-\frac{1}{RC} \right) (V_C) + \frac{\overset{\circ}{i}}{C} \rightarrow \textcircled{5}$$

for inductor,

$$V_L(t) = L \frac{d\overset{\circ}{i}_L(t)}{dt}$$

$$\Rightarrow V_C(t) = L \frac{d\overset{\circ}{i}_L(t)}{dt}$$

$$\Rightarrow V_C(t) = L \overset{\circ}{i}_L(t)$$

$$\Rightarrow \overset{\circ}{i}_L(t) = \frac{1}{L} V_C(t)$$

$$\Rightarrow \overset{\circ}{i}_L = \textcircled{1} (\overset{\circ}{i}_L) + \left(\frac{1}{L} \right) V_C + \textcircled{0} (\overset{\circ}{i}). \rightarrow \textcircled{6}$$

Comparing eq ⑤ and ⑥ with ① and ②,

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{L} \\ -\frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{C} \end{bmatrix} i$$

and output is current through inductor and voltage across capacitor. so, it can be written as

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} i$$

$$\Rightarrow \begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$


∴ State model equations are,

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{L} \\ -\frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{C} \end{bmatrix} i$$

and $\begin{bmatrix} \dot{i}_L \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$

Q3) Obtain the state model for the below network. i is input

& output is i_5 and v_2 .

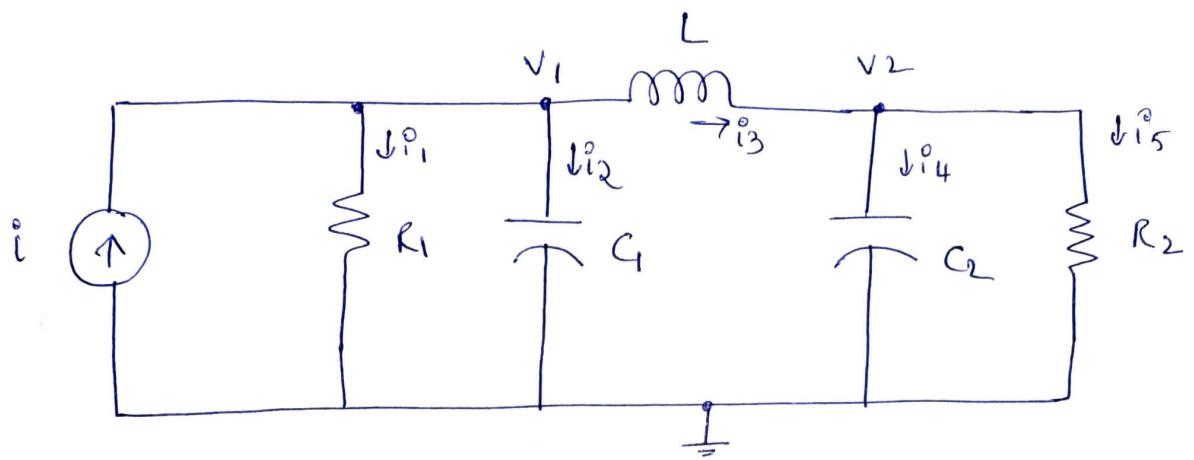

Q3) Ans:

$$\begin{bmatrix} \dot{v}_1 \\ \dot{v}_2 \\ \dot{i}_3 \end{bmatrix} = \begin{bmatrix} -1/R_1C_1 & 0 & -1/C_1 \\ 0 & -1/R_2C_2 & 1/C_2 \\ 1/L & -1/L & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ i_3 \end{bmatrix} + \begin{bmatrix} 1/C_1 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} \dot{i}_5 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 1/R_2 & 0 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ i_3 \end{bmatrix} +$$


Q4) Obtain the state model for the above problem, when,

$$R_1 = R_2 = 1\Omega, C_1 = C_2 = 1F \text{ and } L = 1H$$

$$40 \rightarrow \text{Ans: } \begin{bmatrix} \dot{v}_1 \\ \dot{v}_2 \\ \dot{v}_3 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} i$$

$$\begin{bmatrix} \dot{v}_5 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

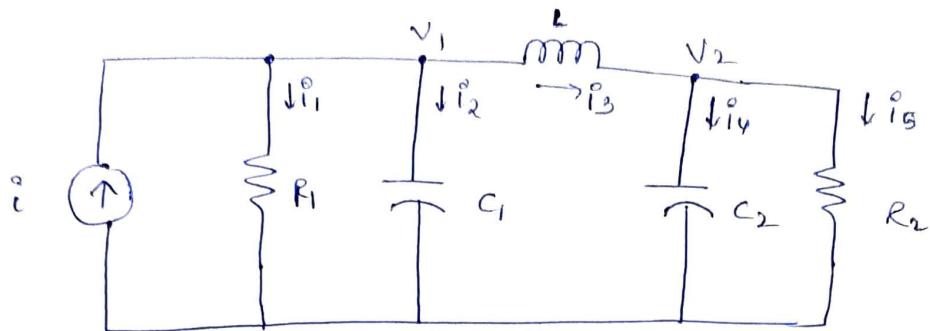Q3) Obtain the state model of the below network.



Input is \dot{i} & output is \dot{v}_2 and v_2

Sol) The behavior of the network at any time t can be determined if the initial current through inductor and initial voltages across the capacitors together with the input \dot{i} applied for $t > 0$ are known.

$\therefore \dot{v}_3, v_1, v_2$ are selected as state variable.

To obtain state equations, express the first derivatives of the state variables in terms of input variable & state variables.

Apply KCL at node 1,

$$\dot{i} = \dot{i}_1 + \dot{i}_2 + \dot{i}_3$$

$$\therefore \dot{i} = \frac{v_1}{R_1} + C_1 \frac{dv_1}{dt} + \cancel{i_3}$$

$$\therefore \dot{i} = \frac{v_1}{R_1} + C_1 \dot{v}_1 + \dot{i}_3 \Rightarrow \dot{v}_1 = \frac{1}{C_1} \left(-\frac{v_1}{R_1} + \dot{i}_3 + i \right) \rightarrow \textcircled{1}$$

Apply KCL at node 2,

$$\dot{i}_3 = \dot{i}_4 + \dot{i}_5$$

$$\Rightarrow \dot{i}_3 = C_2 \frac{dV_2}{dt} + \frac{V_2}{R_2}$$

$$\Rightarrow \dot{i}_3 = C_2 \dot{V}_2 + \frac{V_2}{R_2}$$

$$\Rightarrow \dot{V}_2 = \frac{1}{C_2} \left(-\frac{V_2}{R_2} + \dot{i}_3 \right) \rightarrow \textcircled{2}$$

Apply KVL in loop containing inductor,

$$L \frac{d\dot{i}_3}{dt} + V_2 - V_1 = 0$$

$$\Rightarrow \dot{i}_3 = \frac{1}{L} (V_1 - V_2) \rightarrow \textcircled{3}$$

Outputs are \dot{i}_5 and V_2

(To obtain, output equation, \dot{i}_5 and V_2)

$$\dot{i}_5 = \frac{V_2}{R_2} \rightarrow \textcircled{4}$$

must be written in terms of input & state variables)

i.e. \dot{i}_5 & \dot{V}_2 vs V_1, V_2

and V_2 is another output

∴ The complete state model can be written with the help of eq. ①, ②, ③ and ④, ⑤.

$$\begin{bmatrix} \dot{V}_1 \\ \dot{V}_2 \\ \dot{i}_3 \end{bmatrix} = \begin{bmatrix} -1/R_1 C_1 & 0 & -1/C_1 \\ 0 & -1/R_2 C_2 & 1/C_2 \\ 1/L & -1/L & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ i_3 \end{bmatrix} + \begin{bmatrix} 1/C_1 \\ 0 \\ 0 \end{bmatrix} i$$

$$q \begin{bmatrix} \dot{i}_5 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{R_2} & 0 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ \dot{i}_3 \end{bmatrix}$$

Q4) Obtain the state model for the above problem when,

$$R_1 = R_2 = 1 \Omega, C_1 = C_2 = 1 F \text{ and } L = 1 H$$


Sol)

$$\begin{bmatrix} \dot{v}_1 \\ \dot{v}_2 \\ \dot{i}_3 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 1 \\ 0 & -1 & 1 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ \dot{i}_3 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} i$$

and $\begin{bmatrix} \dot{i}_5 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ \dot{i}_3 \end{bmatrix}$

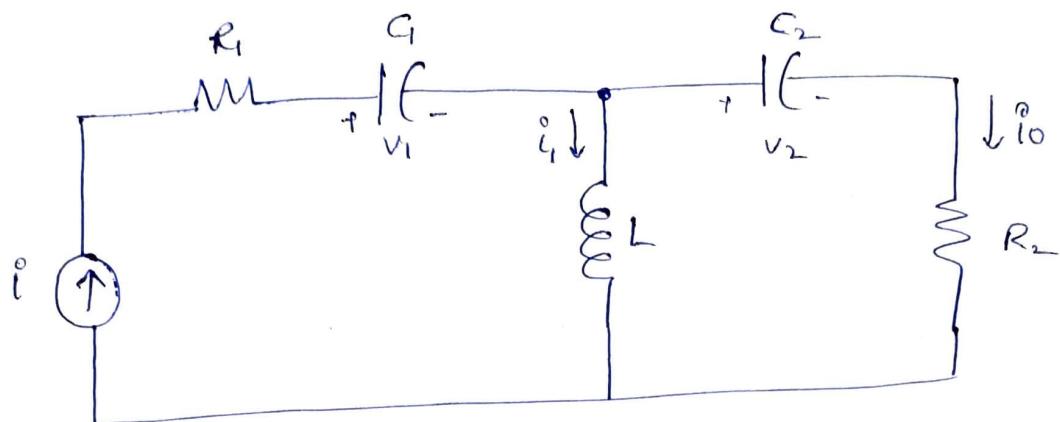Q5) Obtain the dynamic equations of the network shown below.

The current through R_2 is the output required.



Sol) State variables are v_1, v_2, i_1

Input is i

Output is i_0

∴ for state equation, the first derivatives of the state variables

i.e., \dot{v}_1, \dot{v}_2 and \dot{i}_1 must be expressed in terms of state variables

i.e. $x_1(t) = v_1, x_2(t) = v_2$ and $x_3(t) = i_1$ and input is $u(t)$

and output $y = i_0$ must be expressed in terms of the same

state variables and input

Apply KCL at node 1,

$$\dot{i} = \dot{i}_1 + \dot{i}_o$$

$$\dot{i} = \dot{i}_1 + C_2 \frac{d\dot{v}_2}{dt}$$

$$\dot{i} = \dot{i}_1 + C_2 \dot{v}_2$$

$$\Rightarrow \dot{v}_2 = \frac{1}{C_2} \left(-\dot{i}_1 + \dot{i} \right) \rightarrow \textcircled{1}$$

from capacitor C_1 ,

$$\text{if } \text{ & } \dot{i} = C_1 \frac{d\dot{v}_1}{dt}$$

$$\Rightarrow \dot{i} = C_1 \dot{v}_1$$

$$\Rightarrow \dot{v}_1 = \frac{1}{C_1} \dot{i} \rightarrow \textcircled{2}$$

Apply KVL in loop 2,

$$v_2 + \dot{i}_o R_2 = L \frac{d\dot{i}_1}{dt}$$

$$\Rightarrow v_2 + \left(C_2 \frac{d\dot{v}_2}{dt} \right) R_2 = L \dot{i}_1 \quad \left(\because \dot{i}_o = C_2 \frac{d\dot{v}_2}{dt} \right)$$

$$\Rightarrow v_2 + C_2 R_2 \dot{v}_2 = L \dot{i}_1$$

$$\Rightarrow v_2 + C_2 R_2 \left(\frac{1}{C_2} (-\dot{i}_1 + \dot{i}) \right) = L \dot{i}_1 \quad (\because \text{from } \textcircled{1})$$

$$\Rightarrow v_2 + R_2 (-\dot{i}_1 + \dot{i}) = L \dot{i}_1$$

$$\Rightarrow \dot{i}_1 = \frac{1}{L} \left(v_2 - R_2 \dot{i}_1 + R_2 \dot{i} \right) \rightarrow \textcircled{3}$$

from ①, ②, ③, state equation can be written as,

$$\begin{bmatrix} \dot{v}_1 \\ \dot{v}_2 \\ \dot{i} \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & -1/C_2 \\ 0 & 1/L & -R_2/L \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ i \end{bmatrix} + \begin{bmatrix} 1/C_1 \\ 1/C_2 \\ R_2/L \end{bmatrix} i.$$

$$\text{Output is } \dot{i}_o, \dot{i}_o = C_2 \frac{dv_2}{dt}$$

$$= C_2 \dot{v}_2$$

$$= C_2 \left(\frac{1}{C_2} (-\dot{i}_1 + i) \right)$$

$$\boxed{\dot{i}_o = \dot{i} - \dot{i}_1}$$


Or simply apply KCL at node.

$$\dot{i} = \dot{i}_1 + \dot{i}_o \Rightarrow \dot{i}_o = \dot{i} - \dot{i}_1$$

∴ output equation is

$$\dot{i} = [0 \ 0 \ -1] \begin{bmatrix} v_1 \\ v_2 \\ i_1 \end{bmatrix} + [1] i \quad //.$$

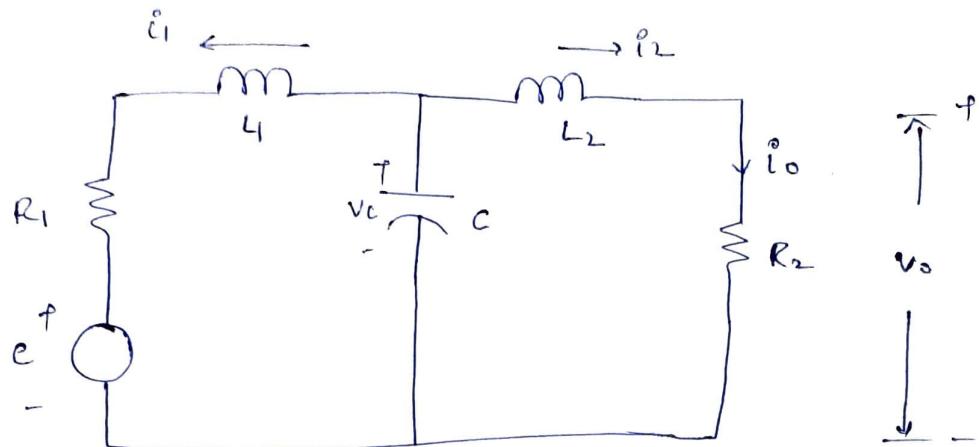Q6) Obtain the state space representation of RLC network shown.



$$\text{Ans: } \begin{bmatrix} \dot{i}_1 \\ \dot{i}_2 \\ \dot{v}_C \end{bmatrix} = \begin{bmatrix} -R_1/L_1 & 0 & 1/L_1 \\ 0 & -R_2/L_2 & 1/L_2 \\ -1/C & -1/C & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ v_C \end{bmatrix} + \begin{bmatrix} -1/L_1 \\ 0 \\ 0 \end{bmatrix} e$$

$$\begin{bmatrix} \dot{i}_0 \\ v_0 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 \\ 0 & R_2 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ v_C \end{bmatrix}$$

Numericals on state transition matrix:

Q1) Obtain the STM for the state model whose A matrix is given below,

$$(i) \quad A = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \quad \text{ii} \quad A = \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix} \quad \text{iii} \quad A = \begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix}$$

So1) $\phi(t)$ is the state transition matrix

$$\phi(t) = t^{-1} [(S\mathbb{I} - A)^{-1}] \quad \text{or} \quad \phi(t) = e^{At}$$

$$i, \quad A = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix}$$

$$S\mathbb{I} - A = S \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} 0 & 1 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} S-1 & -1 \\ 0 & S-1 \end{bmatrix}$$

$$(S\mathbb{I} - A)^{-1} = \frac{1}{(S-1)(S-1) - (-1)(0)} \begin{bmatrix} S-1 & 1 \\ 0 & S-1 \end{bmatrix}$$

$$\left\{ \therefore \text{If } M = \begin{bmatrix} a & b \\ c & d \end{bmatrix}, \quad M^{-1} = \frac{1}{(ad-bc)} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix} \right\}$$

$$= \frac{1}{(S-1)^2} \begin{bmatrix} S-1 & 1 \\ 0 & S-1 \end{bmatrix}$$

$$= \begin{bmatrix} \frac{s-1}{(s-1)^2} & \frac{1}{(s-1)^2} \\ 0 & \frac{s-1}{(s-1)^2} \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{s-1} & \frac{1}{(s-1)^2} \\ 0 & \frac{1}{(s-1)} \end{bmatrix}$$

$$\therefore \phi(t) = \begin{bmatrix} e^t & te^t \\ 0 & e^t \end{bmatrix}$$

$$\text{ii) } A = \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix}$$

$$\begin{aligned}\phi(t) &= L^{-1} \left[(5I - A)^{-1} \right] \\ &= L^{-1} \left\{ \left[\begin{pmatrix} s & 0 \\ 0 & s \end{pmatrix} - \begin{pmatrix} 0 & 1 \\ -1 & -2 \end{pmatrix} \right]^{-1} \right\} \\ &= L^{-1} \left\{ \begin{pmatrix} s & -1 \\ 1 & s+2 \end{pmatrix}^{-1} \right\}.\end{aligned}$$

$$= L^{-1} \left\{ \frac{1}{s(s+2) - (-1)(1)} \begin{bmatrix} s+2 & 1 \\ -1 & s \end{bmatrix} \right\}$$

$$= L^{-1} \left\{ \frac{1}{s^2 + 2s + 1} \begin{bmatrix} s+2 & 1 \\ -1 & s \end{bmatrix} \right\}$$

$$= L^{-1} \left\{ \frac{1}{(s+1)^2} \begin{bmatrix} s+2 & 1 \\ -1 & s \end{bmatrix} \right\}$$

$$= L^{-1} \begin{bmatrix} \frac{s+2}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{s}{(s+1)^2} \end{bmatrix}$$

$$= L^{-1} \begin{bmatrix} \frac{s+1}{(s+1)^2} + \frac{1}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{s+1}{(s+1)^2} - \frac{1}{(s+1)^2} \end{bmatrix}$$

$$= L^{-1} \begin{bmatrix} \frac{1}{(s+1)} + \frac{1}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{1}{(s+1)} - \frac{1}{(s+1)^2} \end{bmatrix}$$

$$= \begin{bmatrix} e^{-t} + t e^{-t} & t e^{-t} \\ -t e^{-t} & e^{-t} - t e^{-t} \end{bmatrix} = e^{-t} \begin{bmatrix} 1+t & t \\ -t & 1-t \end{bmatrix}$$

$$i(c) \quad A = \begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix}$$

$$\phi(t) = \tilde{L}[(S\mathbb{I} - A)^{-1}]$$

$$= \tilde{L} \left\{ \left[\begin{pmatrix} s & 0 \\ 0 & s \end{pmatrix} - \begin{pmatrix} 0 & 1 \\ -2 & -3 \end{pmatrix} \right]^{-1} \right\}$$

$$= \tilde{L} \left\{ \begin{bmatrix} s & -1 \\ -2 & s+3 \end{bmatrix}^{-1} \right\}$$

$$= \tilde{L} \left\{ \frac{1}{s(s+3) - (-1)(-2)} \begin{bmatrix} s+3 & 1 \\ -2 & s \end{bmatrix} \right\}$$

$$= \tilde{L} \left\{ \frac{1}{s^2 + 3s + 2} \begin{bmatrix} s+3 & 1 \\ -2 & s \end{bmatrix} \right\}$$

$$= \tilde{L} \left[\begin{array}{cc} \frac{s+3}{(s+1)(s+2)} & \frac{1}{(s+1)(s+2)} \\ \frac{-2}{(s+1)(s+2)} & \frac{s}{(s+1)(s+2)} \end{array} \right]$$

$$= \tilde{L} \left[\begin{array}{cc} \frac{2}{s+1} - \frac{1}{s+2} & \frac{1}{s+1} + \frac{-1}{s+2} \\ \frac{-2}{s+1} + \frac{+2}{s+2} & \frac{-1}{s+1} + \frac{2}{s+2} \end{array} \right]$$

$$\therefore \phi(t) = \begin{bmatrix} 2e^{-t} - e^{-2t} & e^{-t} - e^{-2t} \\ -2e^{-t} + 2e^{-2t} & -e^{-t} + 2e^{-2t} \end{bmatrix}$$

Q1) Obtain the time response (or) solution of the system described by,

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 1 \\ -1 \end{bmatrix} u$$

with initial conditions or initial state vector as,

$$\begin{bmatrix} x_1(0) \\ x_2(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

Sol) Solution of a homogeneous state equation is,

given by $x(t) = \phi(t) x(0)$

where, $x(0)$, = initial state vector

$$\begin{bmatrix} x_1(0) \\ x_2(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$\phi(t)$ is the state transition matrix,

$$\phi(t) = L \left[(S - A)^{-1} \right]$$

where, $A = \begin{bmatrix} 0 & 1 \\ -1 & -2 \end{bmatrix}$

$$\phi(t) = \mathcal{L}^{-1} \left[(sI - A)^{-1} \right]$$

$$= \mathcal{L}^{-1} \left\{ \left[\begin{pmatrix} s & 0 \\ 0 & s \end{pmatrix} - \begin{pmatrix} 0 & 1 \\ -1 & 0 \end{pmatrix} \right]^{-1} \right\}$$

$$= \mathcal{L}^{-1} \left\{ \left[\begin{pmatrix} s & -1 \\ 1 & s+2 \end{pmatrix} \right]^{-1} \right\}$$

$$= \mathcal{L}^{-1} \left\{ \frac{1}{s(s+2) - (-1)(1)} \begin{bmatrix} s+2 & 1 \\ -1 & s \end{bmatrix} \right\}$$

$$= \mathcal{L}^{-1} \left\{ \frac{1}{s^2 + 2s + 1} \begin{bmatrix} s+2 & 1 \\ -1 & s \end{bmatrix} \right\}$$

$$= \mathcal{L}^{-1} \begin{bmatrix} \frac{s+2}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{s}{(s+1)^2} \end{bmatrix}$$

$$= \mathcal{L}^{-1} \begin{bmatrix} \frac{s+1}{(s+1)^2} + \frac{1}{(s+1)^2} & \frac{1}{(s+1)^2} \\ \frac{-1}{(s+1)^2} & \frac{s+1}{(s+1)^2} - \frac{1}{(s+1)^2} \end{bmatrix}$$

$$= \begin{bmatrix} \bar{e}^t + t\bar{e}^t & t\bar{e}^t \\ -t\bar{e}^t & \bar{e}^t - t\bar{e}^t \end{bmatrix} = \bar{e}^t \begin{bmatrix} 1+t & t \\ -t & 1-t \end{bmatrix}$$

Now, the solution of homogeneous state equation is given by,

$$x(t) = \phi(t) x(0)$$

$$= e^{-t} \begin{bmatrix} 1+t & t \\ -t & 1-t \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$= e^{-t} \begin{bmatrix} t \\ 1-t \end{bmatrix} = \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix}$$

3Q) A linear time invariant system is characterized by the homogeneous state equation,

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

compute the solution of the homogeneous equation assuming

the initial state vector $x_0 = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$

Sq)

ϕ Solution, $x(t) = \phi(t) x(0)$

$$\begin{aligned} \phi(t) &= e^{\{(\frac{1}{2} - \frac{1}{2})t\}} \quad \text{, here } A = \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \\ &= e^{\{(\frac{1}{2} - \frac{1}{2})t\}} \left[\left\{ \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} - \begin{pmatrix} 1 & 0 \\ 1 & 1 \end{pmatrix} \right\}^{-1} \right] \end{aligned}$$

$$= \tilde{L}^{-1} \left\{ \begin{bmatrix} s-1 & 0 \\ -1 & s-1 \end{bmatrix}^{-1} \right\}$$

(Solution already done in R)

$$= \tilde{L}^{-1} \left\{ \frac{1}{(s-1)^2 - (0)(-1)} \begin{bmatrix} s-1 & 0 \\ +1 & (s-1) \end{bmatrix} \right\}$$

$$= \tilde{L}^{-1} \left\{ \frac{1}{(s-1)^2} \begin{bmatrix} s-1 & 0 \\ 1 & s-1 \end{bmatrix} \right\}$$

$$= \tilde{L}^{-1} \left\{ \begin{bmatrix} \frac{1}{s-1} & 0 \\ \frac{1}{(s-1)^2} & \frac{1}{(s-1)} \end{bmatrix} \right\}$$

$$= \begin{bmatrix} e^t & 0 \\ te^t & e^t \end{bmatrix}$$

$$\therefore x(t) = \phi(t) x(0)$$

$$= \begin{bmatrix} e^t & 0 \\ te^t & e^t \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$\therefore \boxed{x(t) = \begin{bmatrix} e^t \\ te^t \end{bmatrix}}$$