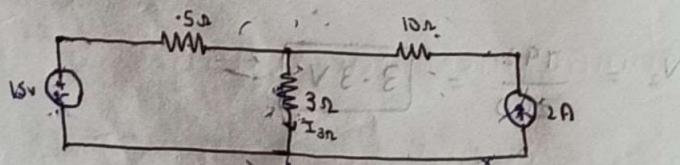


Unit-II { Theorems }

Superposition theorem: In any linear bilateral network consist with the no. of energy sources (i.e current or voltage) & no. of elements. It is possible to determine the response of any element by using superposition theorem directly

- * Response of any element is the algebraic sum of responses caused by individual sources acting alone. { only V & I responses... not power responses }
- * When individual sources acting alone, the energy sources must be replaced with their internal resistances.

Q Determine current through 3Ω resistor in given circuit.




Apply superposition theorem to above circuit.

Consider 15V source

current through 10Ω


is '0' as it is open.

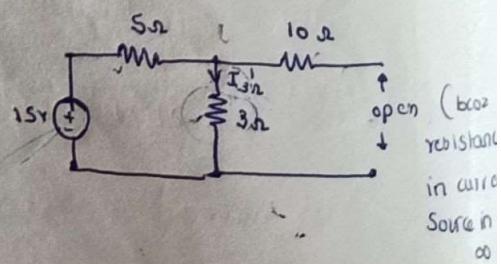

Let current through $\left(\frac{3\Omega}{10\Omega}\right)$ is $I_{3\Omega}$

$$I_{3n}^1 = \frac{V}{R_T} = \frac{15}{8} = \boxed{1.8A}$$

consider '2A' source

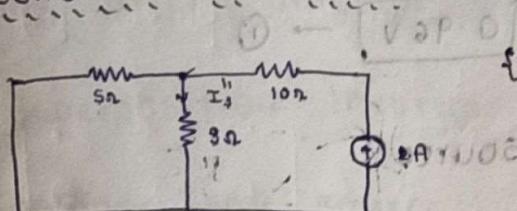

resistance of voltage circuit

Let current through 3Ω is $I_{3\Omega}$.

use current division rule to determine I_{32}^{11}

$$I''_{3n} = 2 \left(\frac{5}{5+3} \right) = 1.2 \text{ Amp}$$

According to superposition principle.

$$I_{3\Omega} = I_{3\Omega}^I + I_{3\Omega}^{II} \quad A_{\text{eff.0}} = \left(\frac{a}{0.8 + \epsilon} \right)^2 = s I$$


$$I_{3n} = 1.8A + 1.2A = 3A$$

2Q Find the voltage across 2Ω resistor in the

circuit shown in figure by using superposition

theorem. 1.2.109

A Consider 'lov' source

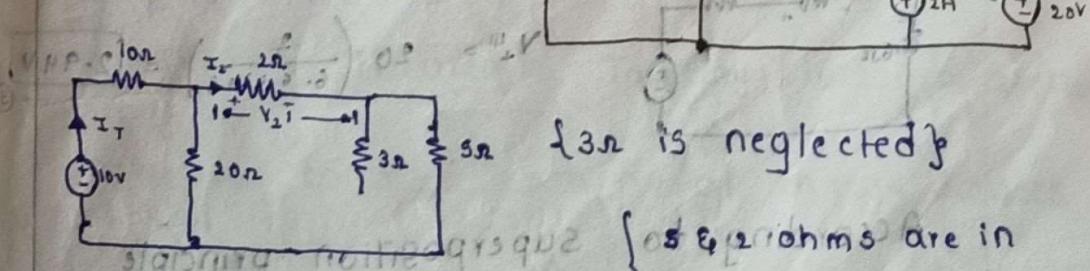

$$I_T = \frac{10}{10 + \left(\frac{20 \times 7}{20 + 7} \right) 20 \times 0} = 11.11 V$$


8 ohms & 2 ohms are in series & in parallel with 20 ohms in series with 10 ohms

$$\text{So, } I_2 = 0.65 \left(\frac{20}{20+7} \right) \quad \{ \text{current division rule} \}$$


$$I_2 = 0.48 \text{ Amp}$$

$$V_2' = I_2 \times 2\Omega \rightarrow \boxed{0.96 \text{ V}} \rightarrow ①$$

* Consider '2A' as source

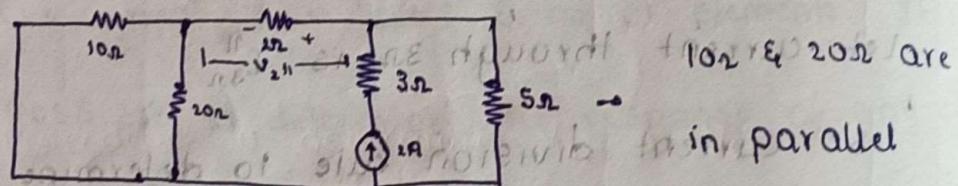


Effective resistance = 6.6Ω

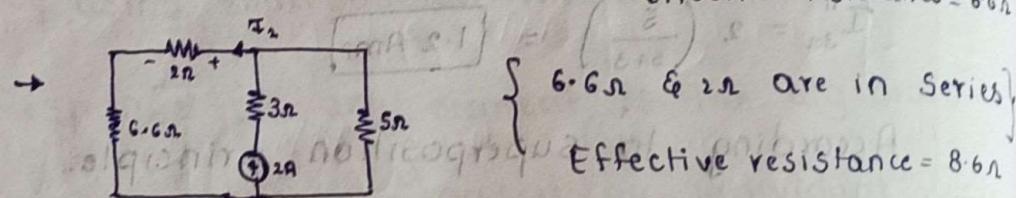


$$I_2 = 2 \left(\frac{5}{5+8.6} \right) = 0.73 \text{ A} \quad \{ 5 \text{ & } 8.6 \text{ are in parallel} \}$$

$$V_2'' = 0.73 \times 2 = \boxed{1.46 \text{ V}} \rightarrow ②$$

* Consider 20V Source

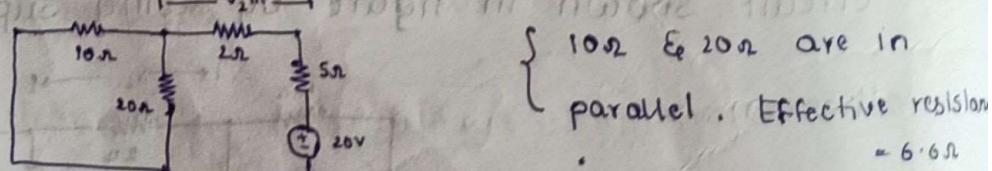

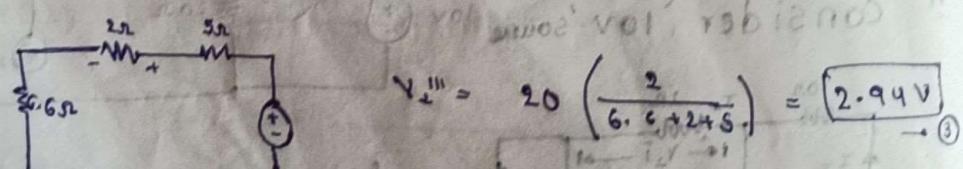10Ω & 20Ω are in parallel. Effective resistance = 6.6Ω



$$V_2''' = 20 \left(\frac{2}{6.6+20} \right) = \boxed{2.94 \text{ V}} \rightarrow ③$$

According to superposition principle

$$V_2 = V_2' + V_2'' - V_2''' = 0.96 + 1.46 - 2.94$$

$$= -3.4 \text{ V}$$

$$= 13.41 \text{ V}$$



$$A2 \times 1.341 = 7.1$$

= 3.4 V

3. Q. For the circuit shown in figure, Determine the current through 3Ω resistance by using

Superposition theorem.


A. Consider '50V' source

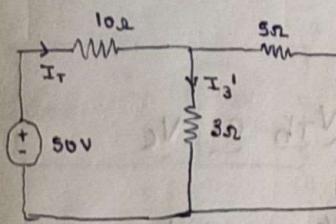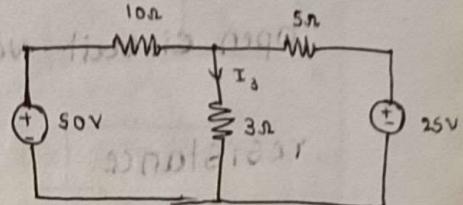

$$I_T = \frac{50}{10 + \left(\frac{5 \times 3}{5+3}\right)} = 4.21 \text{ A}$$

$$I_3' = 4.21 \left(\frac{3}{5+3}\right) = 2.63 \text{ A} \quad \rightarrow ①$$

Consider '25V' source

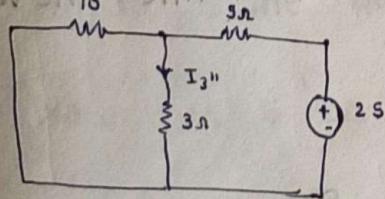

$$I_T = \frac{25}{10 + \left(\frac{10 \times 3}{10+3}\right)} = 3.42 \text{ A}$$

$$I_3'' = 3.42 \left(\frac{3}{10+3}\right) = 2.63 \text{ A} \quad \rightarrow ②$$

Now According to superposition principle.

$$I_3 = I_3' + I_3''$$

$$= 2.63 + 2.63$$

$$= 5.26 \text{ A}$$


* Thevenin's Theorem : In any linear bilateral

network consist with no. of energy sources.


(i.e current or voltage) & no. of elements. It

is possible to represent the given circuit with

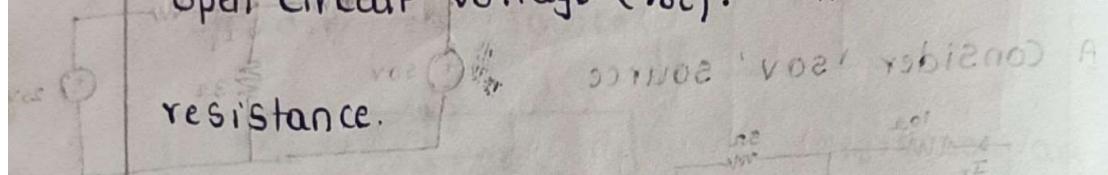the two terminals equivalent of V_{Th} in series with another two terminals equivalent of R_{Th} , where V_{Th} = Thevinin's voltage or open circuit voltage (V_{oc}). R_{Th} is Thevinin's resistance.



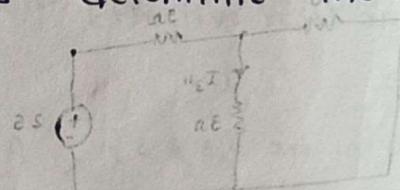- * Procedure to determine V_{Th} or V_c
 - 1) First identify the node resistor in given ckt
 - 2) Open the node and determine the voltage at open terminal.




- * Procedure to determine R_{Th}
 - 1) Identify the node resistance in given circuit and open it. & Replace all the energy sources with their internal resistances then look back the entire circuit through open circuit terminal.

- 2) Then calculate the equivalent resistance which is equal to Thevinin's resistance.



How to draw Thevenin's circuit

Q For the circuit shown below, 24Ω is node resistance. Determine node current by using thevenin's theorem.

A Here AB is the node.

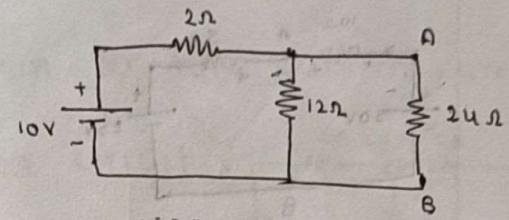

For V_{Th} or V_{oc} :

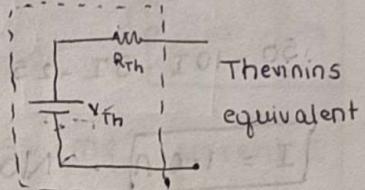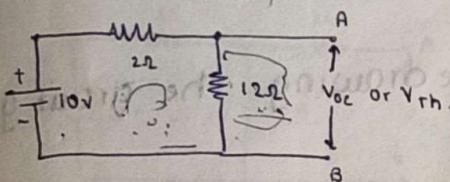


The voltage across AB & voltage across 12Ω is same bcoz they are in parallel.

* Now 2Ω & 12Ω are in series { AB is open }
 $= 14\Omega$

So, I (current) = $\frac{10}{14\Omega} = 0.71A$


$V_{oc} = V_{Th} = V_{AB} = 0.71 \times 12 = 8.5V$

For R_{Th} :

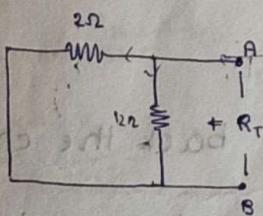


Here 2Ω & 12Ω are in parallel

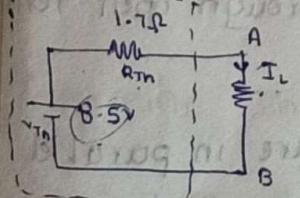Effective resistance = $\frac{2 \times 12}{2 + 12} = 1.72\Omega$




$I_L = \frac{8.5}{1.72 + 24}$

$I_L = 0.33A$

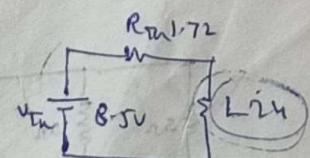


Q Determine the thevenin's equivalent circuit across AB, for the figure shown below.

AB is already open.

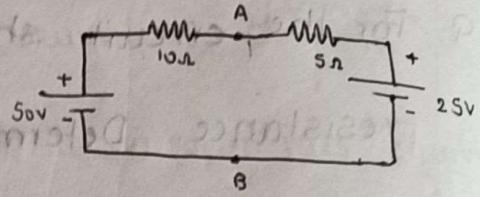


For V_{oc} or V_{th} :

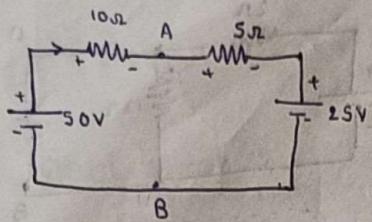

Assume current in circuit is I . Apply KVL

$$50 - 10I - 5I - 25 = 0$$

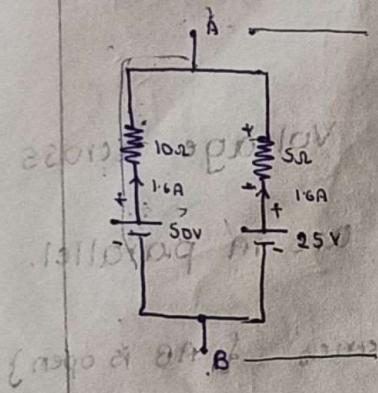$I = 1.6 \text{ A}$. Now Redrawing the circuit gives




Voltage across A & B is equal to voltage across 50V & 10Ω

& also equal to voltage across 25V & 5Ω


$$V_{oc} = 50 - 1.6 \times 10 = 33.33 \text{ V}$$

$$\text{or } V_{oc} = 50 - 25 - 5 \times 1.6 = 33.33 \text{ V}$$

For R_{th} :

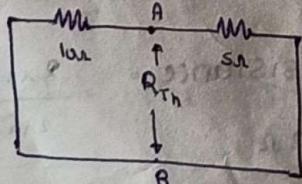

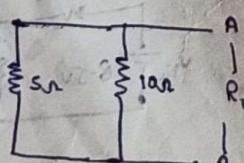
Now look back the entire circuit through open terminal



10Ω & 5Ω are in parallel

$$R_{th} = \frac{5 \times 10}{5 + 10} = 3.33 \Omega$$


Thevenin's equivalent.

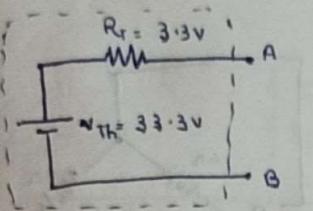

$$I = \frac{33.3 \text{ V}}{3.33 \Omega} = 10 \text{ Amp}$$

Q Use Thevinin's theorem to find out the current through 3Ω in given circuit.

* For V_{OC} or V_{Th} :

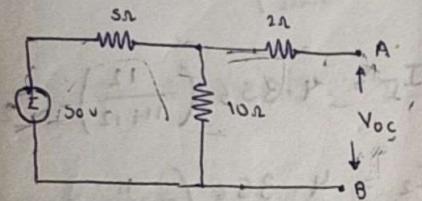


Assume current I

$$I = \frac{50}{10 + 5} = 3.33 \text{ A}$$

$$V_{OC} \text{ or } V_{Th} \text{ or } V_{AB} = 3.33 \times 10 = 33.33 \text{ V}$$

bcz voltage across V_{AB} & voltage across 10Ω is equal as they are in parallel.


For R_{Th} :

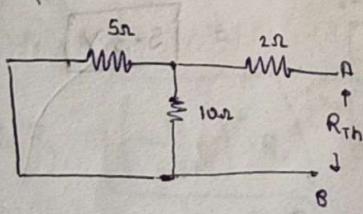

$$R_{Th} = 2 + \left(\frac{5 \times 10}{5 + 10} \right)$$

$$R_{Th} = 5.33 \Omega$$

Thevinin's equivalent:

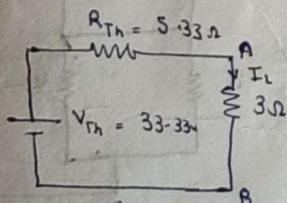

$$I_L = \frac{33.33}{5.33 + 3}$$


$$I_L = 4 \text{ amp}$$

Q Determine Thevinin's equivalent of given circuit



and also determine current through load resistor

A In the given circuit AB is the load

A For V_{oc} or V_{Th}

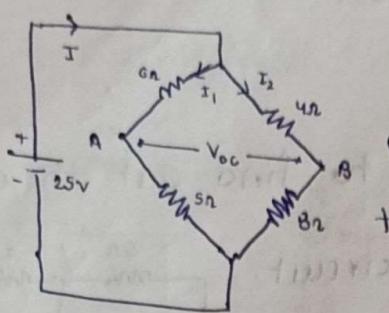

Now redraw the circuit.

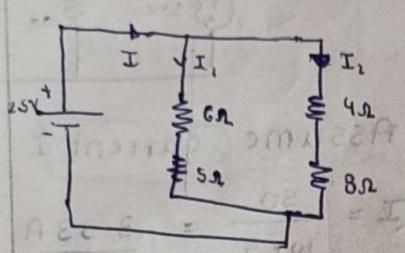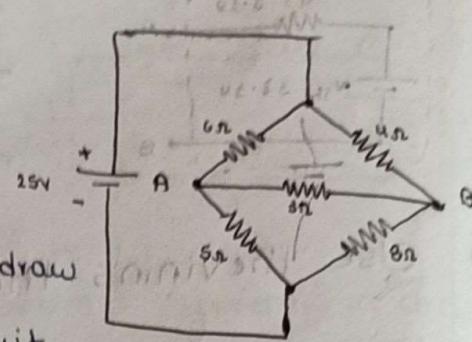


$$I = \frac{25}{(5 + 4)} = 4.356 \text{ Amp}$$

$$I_1 = 4.356 \left(\frac{12}{11+12} \right) = 2.272 \text{ Amp}$$

$$I_2 = 4.356 \left(\frac{11}{11+12} \right) = 2.083 \text{ Amp}$$

Redraw the circuit

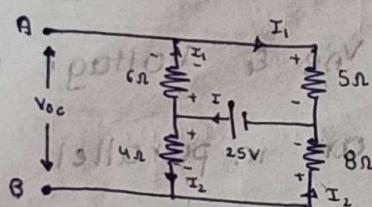


$$V_{oc} = V_{Th} = V_{AB} =$$


$$= 6 \times 2.27 - 4 \times 2.083$$

$$= 5.3 \text{ V}$$


For R_{Th}

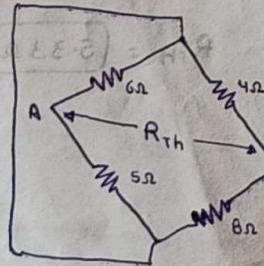

Redraw the circuit

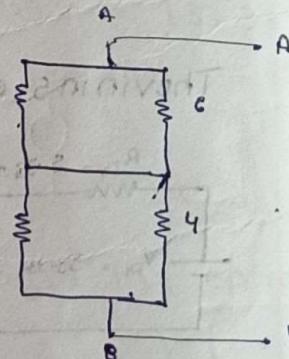


Now

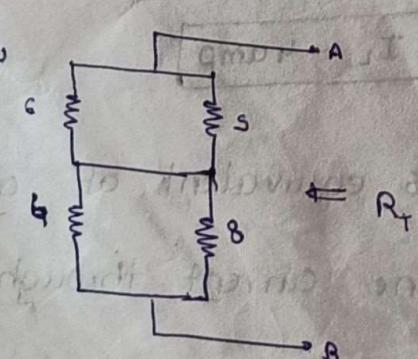

$$R_{Th} = \left(\frac{6 \times 8}{6+8} \right) + \left(\frac{8 \times 4}{8+4} \right)$$

$$R_{Th} = 5.39 \Omega$$

Thevenin's equivalent ..

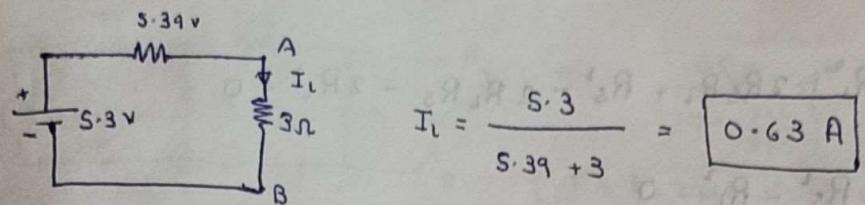

$$I_L = \frac{5.3}{5.39 + 3} = 0.63 \text{ A}$$

* maximum power transfer theorem:


In any linear bilateral network consist with the no. of energy sources (i.e. current or voltage), & no. of elements. It is possible to transfer the maximum power from source to the load, when the load resistance = source resistance.

* Variable resistance = Rheostat.

$$\text{Here } I = \left(\frac{V_s}{R_L + R_s} \right)$$

R_s looks like thevenin's equivalent.
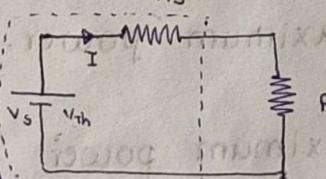
$$\text{Power at load} = I^2 R_L = \left(\frac{V_s}{R_L + R_s} \right)^2 \cdot R_L$$



Now differentiate w.r.t R_L & equate to zero.

$$\frac{dP}{dR_L} = 0 \rightarrow \frac{d}{dR_L} \left(\frac{V_s^2}{(R_L + R_s)^2} \right) R_L = 0$$

$$V_s^2 \frac{d}{dR_L} \left(\frac{R_L}{(R_L + R_s)^2} \right) = 0$$

$$R_t = \frac{V_{th}^2}{4R_s^2}$$

$$V_s^2 \left[\frac{(R_L + R_s)^2 - R_L^2(R_L + R_s)}{(R_L + R_s)^4} \right] = 0$$

$$(R_L + R_s)^2 - 2R_L(R_L + R_s) = 0$$

$$R_L^2 + 2R_S R_L + R_S^2 - 2R_L R_S - 2R_L^2 = 0$$

$$R_S^2 - R_L^2 = 0$$

$$R_S^2 = R_L^2$$

$$R_S = R_L$$

This means, when $R_S = R_L$, the

power is maximum. Condition is $R_S = R_L$

Now


$$P_{\max} = \frac{V_S^2}{4R_L}$$

$\{ R_L = R_S \text{ & from eq ①} \}$

$$\text{Or } P_{\max} = \frac{V_{Th}^2}{4R_L}$$

Q* To determine the value of R_L when the load draws maximum power. Also find the value of maximum power for the circuit shown below.

Condition of max power transfer

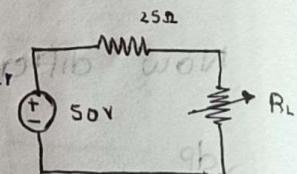



$$\text{is } R_L = R_S = 25\Omega$$

$$\text{Max Power} = \frac{V_S^2}{4R_L} \Rightarrow \frac{(50)^2}{4 \times 25} = \frac{2500}{100} = 25 \text{ Watts}$$

Q* Determine max power delivered to load in given circuit.

For V_{Th} :

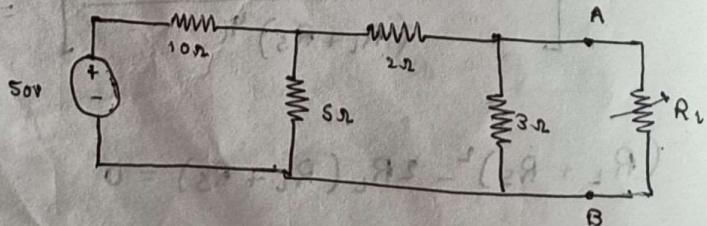

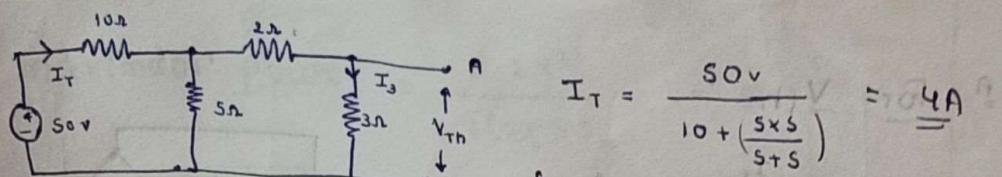


$$I_T = \frac{50V}{10 + \left(\frac{5 \times 5}{5+5}\right)} = 10A$$

{ 0.2 & 3Ω are in series & parallel

$$\text{Now } I_3 = 4 \left(\frac{5}{5+5} \right) = 2A \quad \text{with } 5\Omega \text{ & in series with } 10\Omega$$

$$V_{Th} = 2 \times 3 = 6V$$

For R_{Th} :

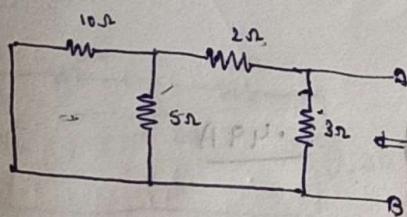


look back the entire circuit through open

$$R_{Th} = \left[\left(\frac{10 \times 5}{10+5} \right) + 2 \right] / 1 / 3\Omega$$

{ 10 & 5 are in parallel & in series with 2Ω & total in parallel with 3Ω }

$$R_{Th} = 1.919 \Omega$$

Arrange the circuit in thevenin's model.

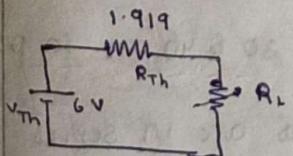

By max power transfer theorem,

for max power, $R_L = R_S = R_{Th}$


$$R_L = 1.919 \Omega$$

$$P_{max} = \frac{6^2}{4(1.919)}$$

$$= 4.68 \text{ watts}$$

- Q Determine the maximum power transferred to the load in given circuit.

For V_{Th}

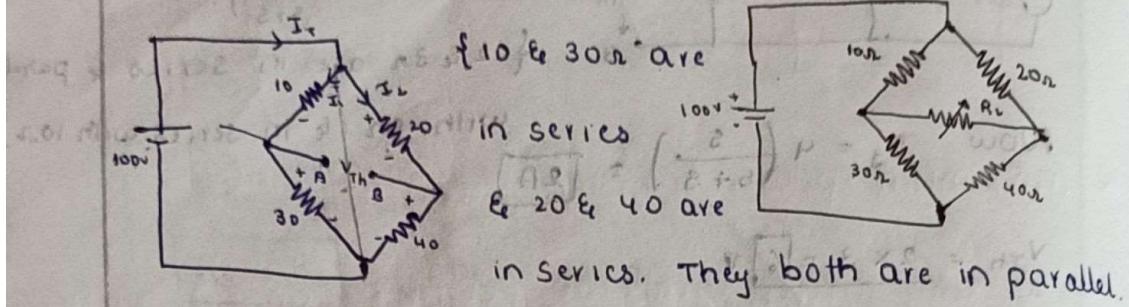

$$I_T = \frac{100}{\left(\frac{40 \times 60}{40+60}\right)} = 4.16 \text{ A}$$


$$I_{30} = (4.16) \left(\frac{60}{60+40} \right) = 2.49 \text{ A}$$

$$I_2 = (4.16) \left(\frac{40}{60+40} \right) = 1.66 \text{ A}$$

$$V_{Th} = 10 \times 2.49 - 20 \times 1.66$$

$$V_{Th} = 18.24 \text{ V}$$

For R_{Th} :

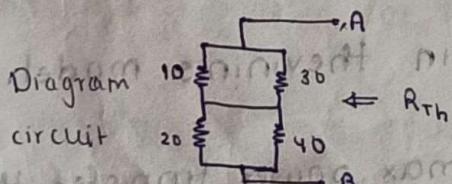

Now 10 & 20 are in parallel


also 30 & 40 are in parallel

Totals are in series.

$$R_{Th} = \left(\frac{10 \times 30}{10+30} \right) + \left(\frac{20 \times 40}{20+40} \right)$$

$$R_{Th} = 20.83 \Omega$$

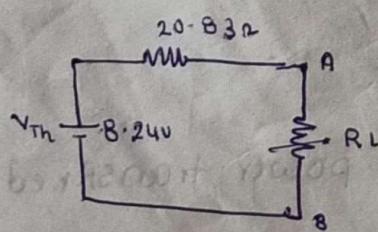Draw the circuit as thevenin's equivalent




Here $R_L = R_S = R_{Th}$

$$R_L = 20.83$$

$$\text{maximum power} = \frac{8 \cdot 24^2}{4(20 \cdot 83)}$$



$$P_{\max} = 0.81 \text{ W}$$

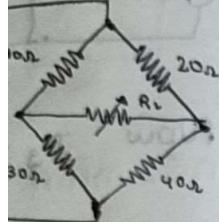

are in parallel.

Q Determine the maximum power transferred to the load in given circuit.


A For V_{Th} :

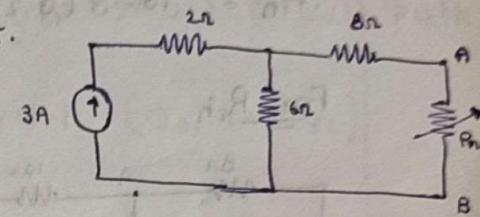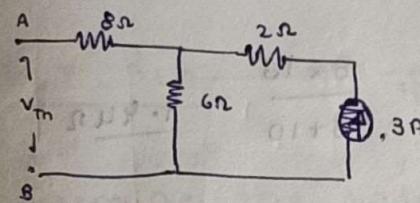

{ B_2 is neglected}


$$V_{Th} = 3(6) = 18 \text{ V} \quad \{ V_{Th} = \text{Voltage across } 6\Omega \}$$

For R_{Th}

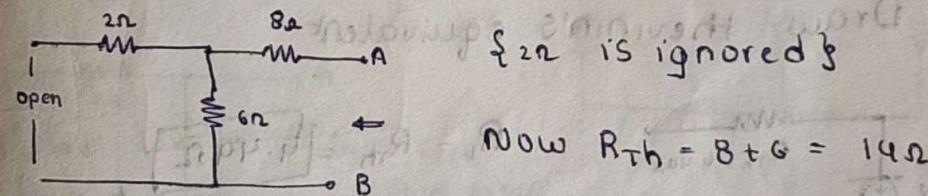

$$\text{Now } R_{Th} = 8 + 6 = 14 \Omega$$


Bring to thevenin's equivalent

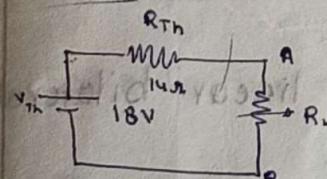


$$R_L = R_{Th} = 14 \Omega$$

$$P_{\max} = \frac{18^2}{4 \times 14} = 5.78 \text{ watts}$$

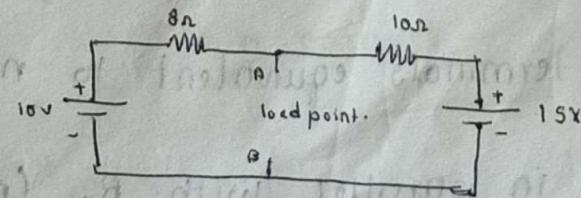Q Determine the value of load resistance in given circuit for the condition to transfer the maximum power.



A For V_{Th}

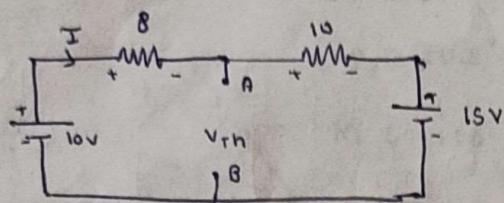

$$10 - 8I_1 - 10I - 15 = 0$$

$$I = -10.27 \text{ Amp.}$$


$$I = -0.27 \text{ A}$$

$$V_{Th} = 10 - 8(0.27) = 12.16 \text{ V}$$

$\{ V_{Th}$ = voltage across

10V & 8Ω }


For R_{Th}

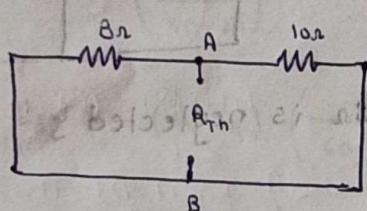

$$R_{Th} = \frac{8 \times 10}{8 + 10} = 4.44 \Omega$$

$$R_{Th} = \frac{8 \times 10}{8 + 10} = 4.44 \Omega$$

Draw thevenin's equivalent

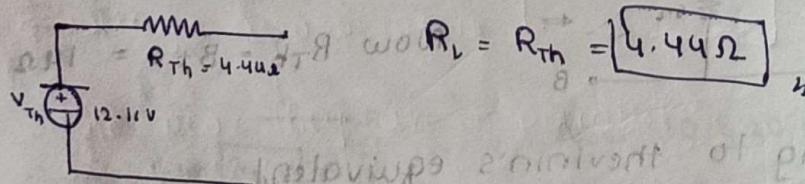

* Norton's Theorem: In any linear bilateral

network consist the no. of energy sources (:

current or voltage) & no. of elements. It is

possible to replace the given circuit with two

terminals equivalent to nortons current I_N &

in parallel with R_N (Nortons resistance)

Norton's Equivalent

- Procedure to find I_N



1) Identify the load given in the circuit and make it as short circuit.

2) Now the current through short circuit path is equal to Norton current (I_N or I_{SC})

- * $R_N = R_{Th}$. Same procedure to find R_{Th} & R_N .

Q Determine the value of load current in given circuit by using norton's theorem, wh

- * For I_N or I_{SC} :

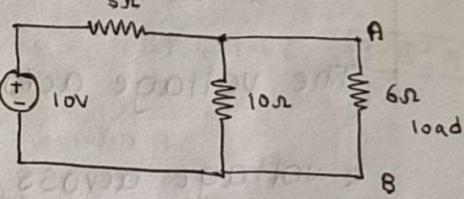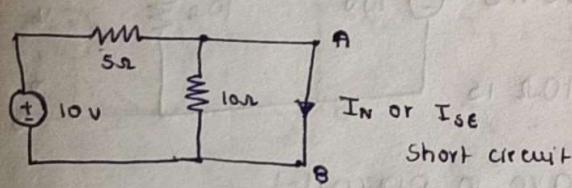


10Ω & short circuit (0Ω) are in parallel.

$$\text{So, effective resistance} = \frac{10 \times 0}{10 + 0} = 0\Omega$$

$$I_N \text{ or } I_{SC} = \frac{10}{5} = 2A$$


For R_N or R_{Th} :

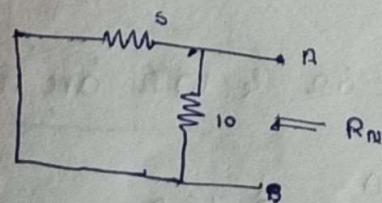

lookback, Now 10Ω & 5Ω are in parallel

$$R_{Th} = \frac{5 \times 10}{10 + 5} = 3.33\Omega$$


Convert into norton's equivalent

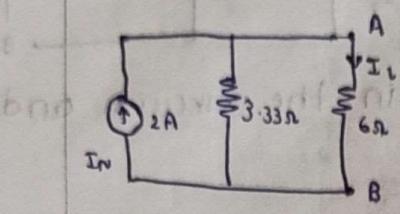

$$\text{Now } I_L = 2 \left(\frac{3.33}{3.33+6} \right)$$

$$I_L = 0.41 \text{ A}$$

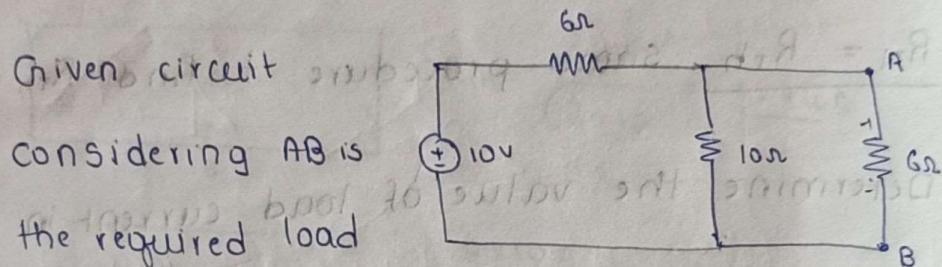Q) Determine the load current for same circuit using Thevenin's theorem



For V_{th} or V_{oc}

The voltage across AB

& voltage across 10Ω is


same bcoz they are in parallel

Now 6Ω & 10Ω are in series, $R_{eq} = 6 + 10 = 16\Omega$


$$V_{oc} = \text{Current} = \frac{10}{16} = 0.625 \text{ Amp}$$

$$V_{oc} = 10 \times 0.625 = 6.25 \text{ Volts}$$

For R_{th} :

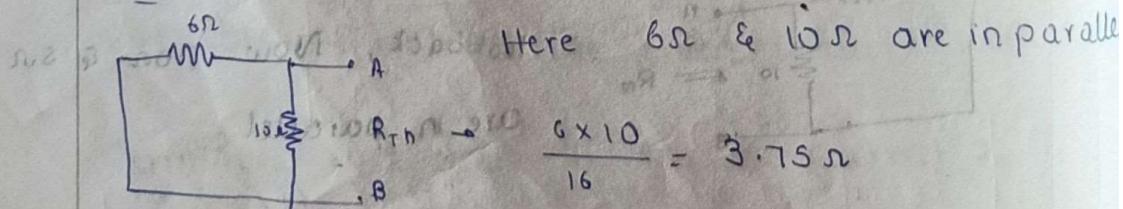

The load current is


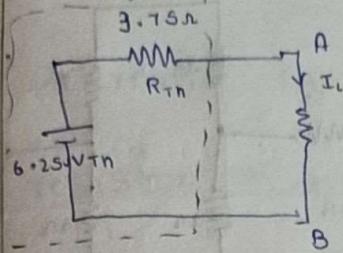


The load current = $\frac{6.25}{3.75 + 6.25}$
(load is 6 Ω)


$$I_L = \frac{6.25}{9.75} = 0.64 \text{ A}$$

Q Determine the Norton's equivalent for given circuit

A For I_{Th} or I_{sc} :

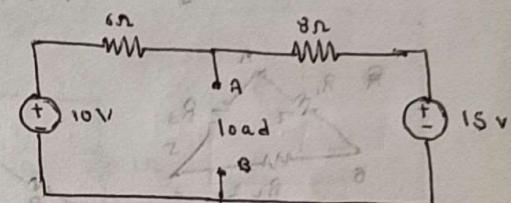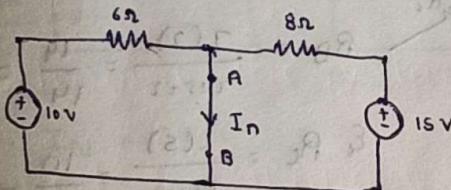

Now Redraw the circuit as follows

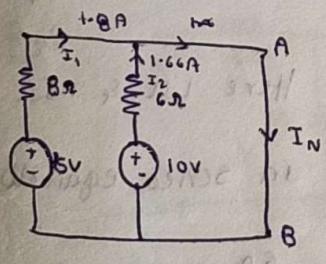


$$I_{Th} \text{ or } I_{sc} = 1.87 + 1.66 = 3.53 \text{ A}$$

$$I_1 = \frac{15}{8} = 1.87 \text{ A}$$

$$I_2 = \frac{10}{6} = 1.66 \text{ A}$$


For R_{Th}

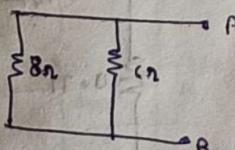

$$R_{Th} = \frac{8 \times 6}{8 + 6} = 3.42 \text{ A}$$

{ 8 Ω & 6 Ω are in parallel }



Now draw Norton's equivalent.

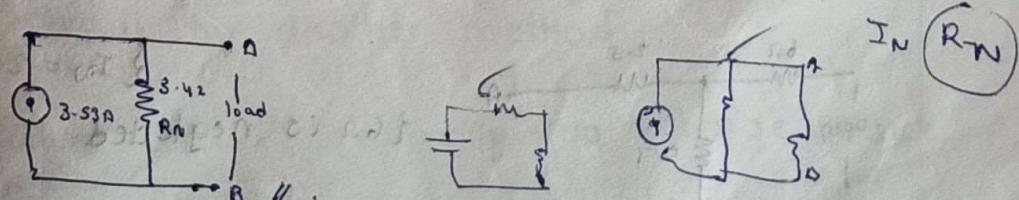

Q Determine the Norton's equivalent circuit for the circuit shown in figure.


Here 3 ω & 4 ω are in

Series, $E_g = 7\Omega$, Circuit

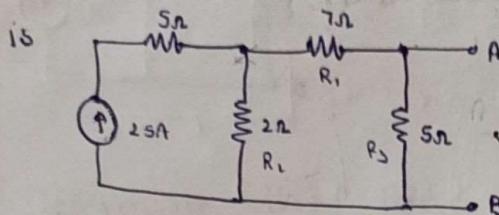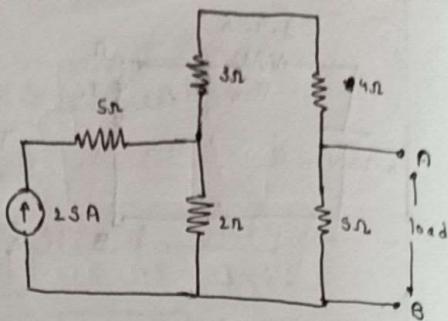


Let current flowing
through AB is I_n .

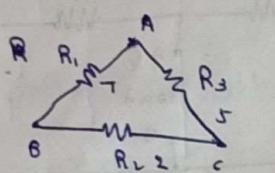converting 7Ω , 2Ω , 5Ω is star connection.



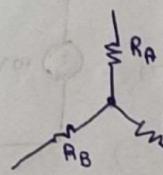
$$R_A = \frac{(7)(5)}{7+5+2} = \frac{35}{14} = 2.5\text{N}$$



$$= \frac{7(2)}{7+5+2} = \frac{14}{14} = 1\Omega$$

$$E_{P_C} = \frac{2(5)}{7+5+2} = \frac{10}{14} = 0.712$$

Redraw the circuit

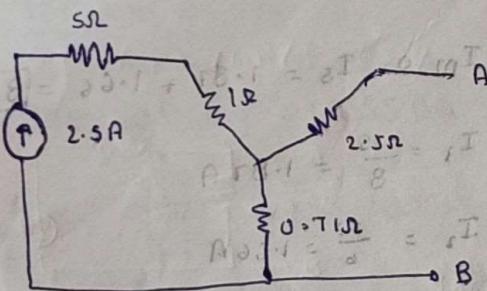


Here 1Ω & 5Ω are
in series equivalent =


so Redraw circuit

25% & 10% are in

parallel for \mathbb{R}^n

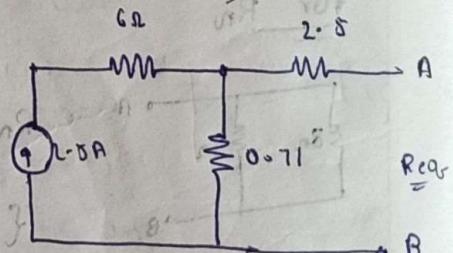

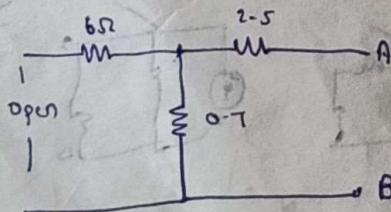Replace source with its internal resistance.




for is neglected


$$\{ I_N = 2.8 A \}$$

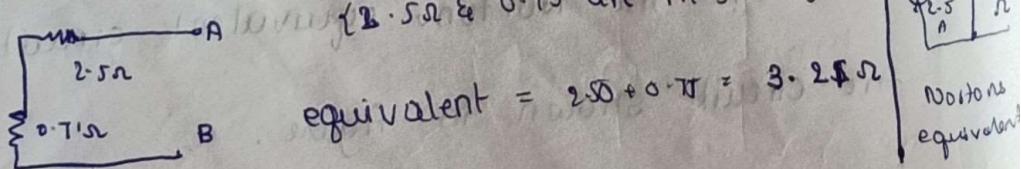(2.5Ω & 0.75 are in series)


$$\text{equivalent} = 250 + 0.75 = 3.25 \Omega$$



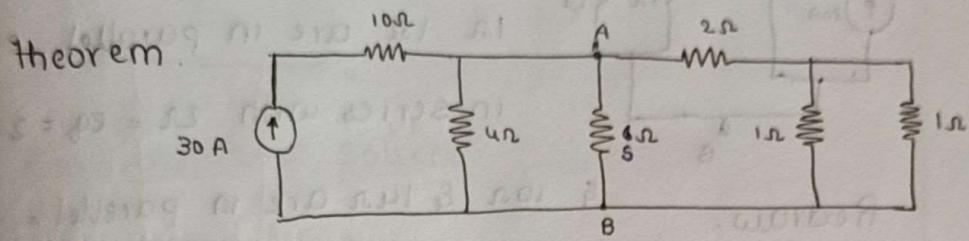
Q. Determine the current flowing through 2Ω resistor in a given circuit by using norton's theorem.



A. I_N or I_{sc}

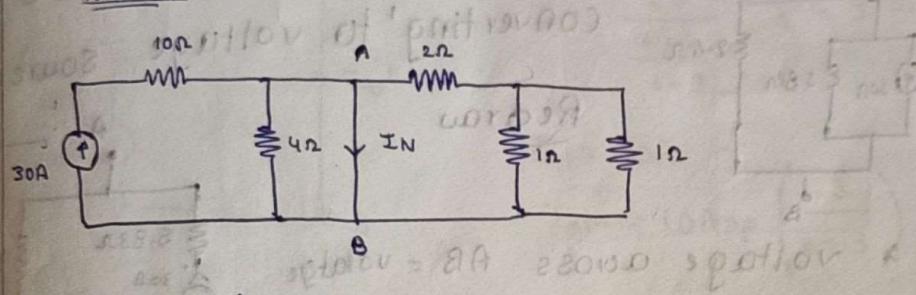


$$I_N = 30A$$

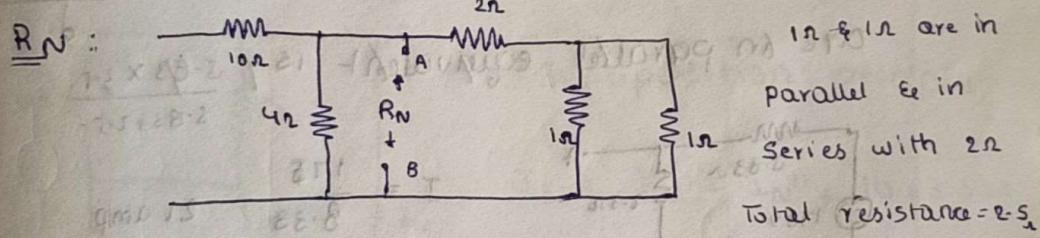

1Ω & 1Ω are in parallel & in series with 2Ω


Total resistance = 2.5Ω

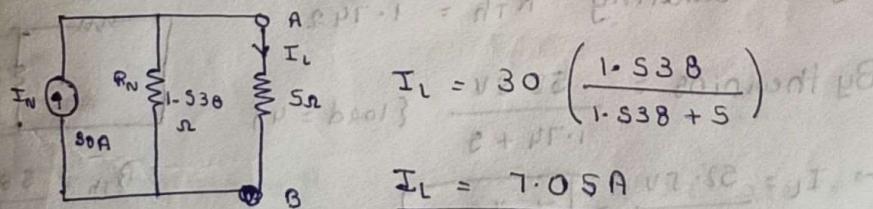
$$\therefore R_N = \frac{2.5 \times 4}{2.5 + 4} = 1.538\Omega$$



* Solve it by another method.

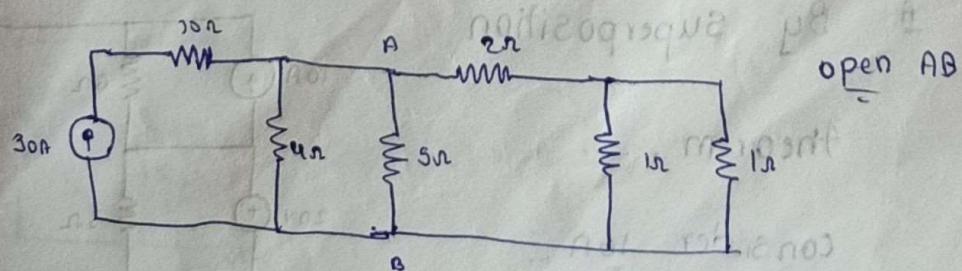Given circuit converting into voltage source



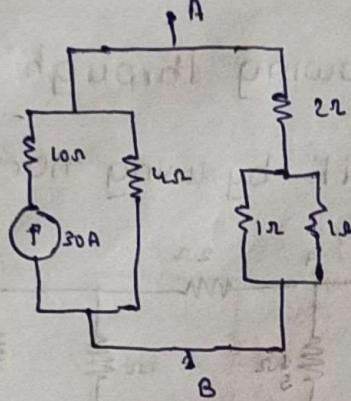


Redraw.

1Ω & 1Ω are in parallel, $\text{eq} = 0.5\Omega$

in series with 2Ω = $\text{eq} = 2.5\Omega$


5 10Ω & 14Ω are in parallel = $\frac{10 \times 14}{24} = 5.83\Omega$

Redraw.

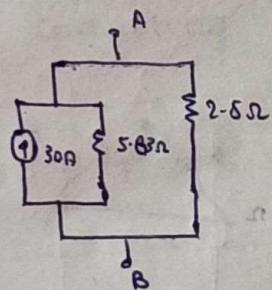

Converting to voltage source


Redraw

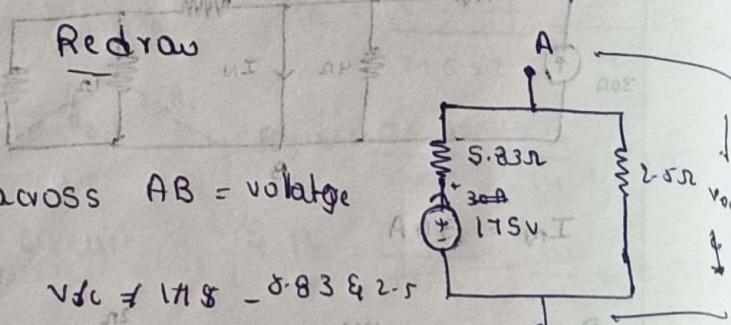

* voltage across AB = voltage

across 2.5Ω, $V_{OC} = 175 - 5.83 \times 2.5$

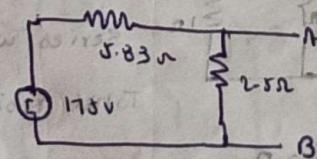direct in parallel equivalent is $\frac{5.83 \times 2.5}{5.83 + 2.5}$




$$I = \frac{175}{8.33} = 21 \text{ amp}$$

$$V_{OC} = 21 \times 2.5 \quad V_{OC} = 52.5 \text{ V}$$

By calculating $R_{Th} = 1.74\Omega$

$$\text{By thevenin} = \frac{52.5 \text{ V}}{1.74 + 5} \quad \{ \text{load} = 4 \}$$
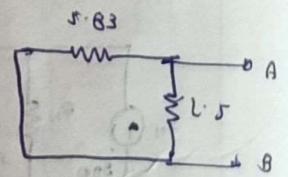
$$\Rightarrow I_L = \frac{52.5 \text{ V}}{6.74} = 7.7 \text{ amp}$$



$$R_{Th} = \frac{5.83 \times 2.5}{5.83 + 2.5} = 1.74\Omega$$


Q Replace the given network shown in figure


in a current source in parallel with resistance

A By superposition

theorem


consider 10A ..

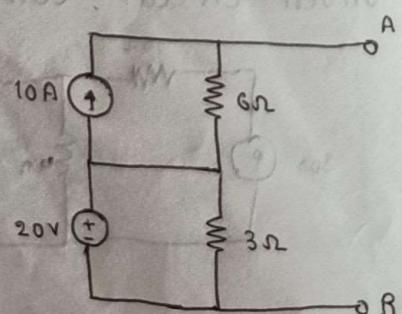

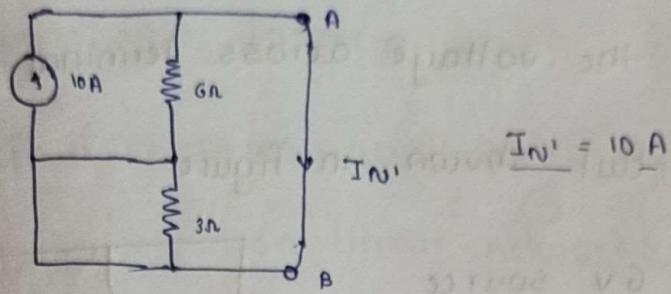

$$I_N^1 = 10 \text{ A}$$

Consider 20V Source

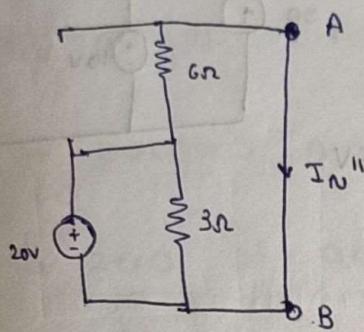


$$I = \frac{20}{6+3} \quad \{ \text{& } 3 \text{ are in parallel} \}$$

$$I = 10 \text{ A}$$

$$I_N^11 = 10 \text{ Amp} \left(\frac{3}{6+3} \right) = \frac{30}{9} = 3.33 \text{ A}$$


Now

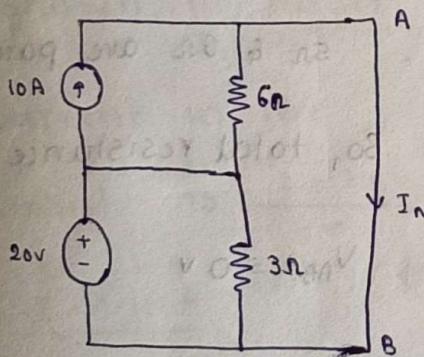

Superposition principle

$$I_N = I_N^1 + I_N^11 = 10 + 3.33 = 13.33 \text{ A}$$


For R_N

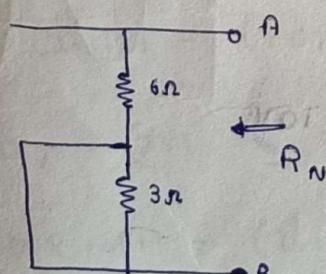

{ 3Ω & 0Ω are in parallel


total = 0Ω

$$\text{so } R_N = 6\Omega$$

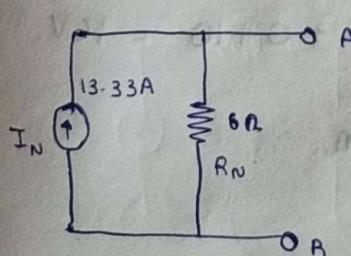


Q Determine the voltage across terminal A & B in the circuit shown in figure.


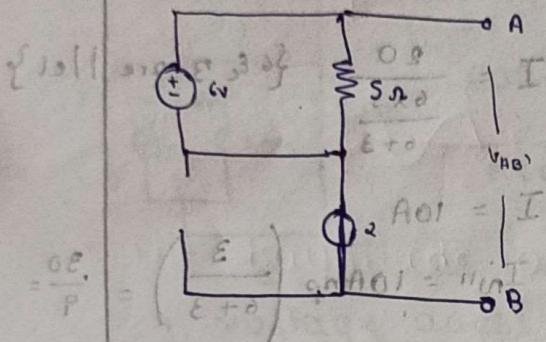
A Consider 6V source, by Superposition theorem.




$$V_{AB}' = 6V$$

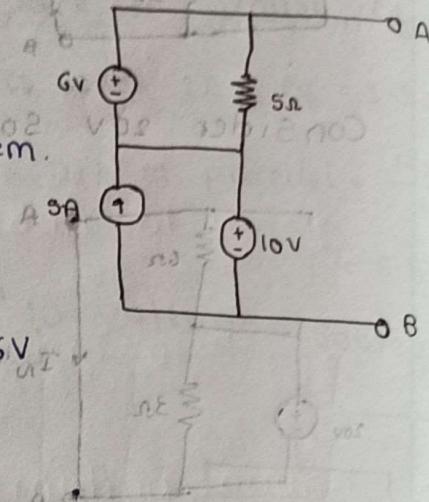

Consider 5Amp source,

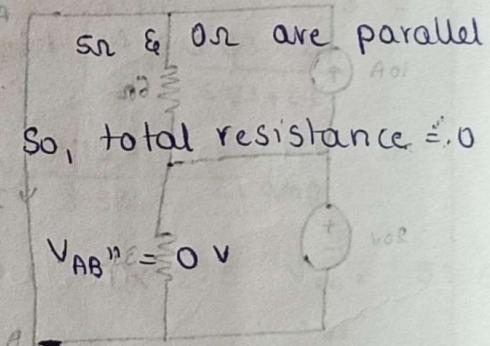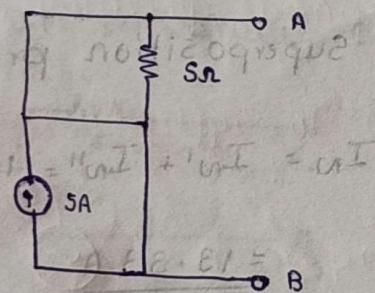

Consider 10V source,

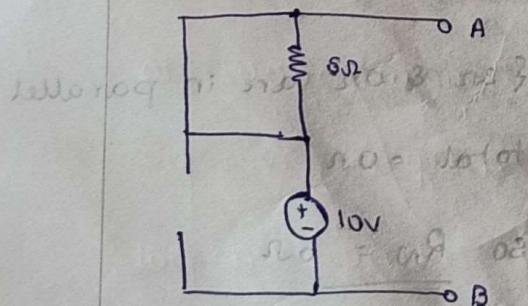

$$\text{So, voltage b/w } V_{AB} = 6 + 0 + 10 = 16V$$

By superposition system.

nal A & B

* Tellegen's Theorem

This theorem applicable to lumped elements, linear & non linear networks & also time variant & time invariant circuits.


* For a given circuit, the algebraic sum of powers in all branches in a circuit is zero at any instant

Q Verify the Tellegen's theorem for the circuit

shown in figure.

* Current in the
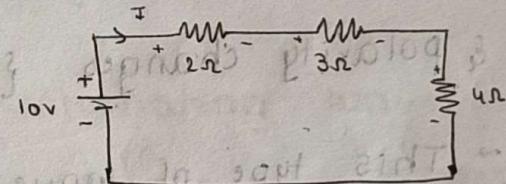
$$\text{circuit is } \frac{2 + 3 + 4}{10} = \frac{1}{I} \quad \Sigma V = 0$$



$$I = 1.111 \text{ A}$$

$$P = 0$$

By Tellegen's theorem,

$$10(1.111) - 1(1.111)^2(2) - 3(1.111)^2 - 4(1.111)^2 = 0, \quad (\text{Or})$$

$$10 \times 1.111 = (1.111)^2(2) + 3(1.111)^2 + 4(1.111)^2$$

16V